

Scattering parameters

Microwave Electronics

Giovanni Ghione, Marco Pirola

Politecnico di Torino, DET



Forward and backward voltages along a line



- In a homogeneous line, the forward and backward voltages in a point univoquely determine the voltage and currents on the whole line:

$$V(z) = V^+(z) + V^-(z) = V^+(0) \exp(-j\beta z) + V^-(0) \exp(j\beta z)$$

$$\begin{aligned} \frac{V^+(0)}{Z_0} \exp(-j\beta z) - \frac{V^-(0)}{Z_0} \exp(j\beta z) = \\ = I^+(0) \exp(-j\beta z) + I^-(0) \exp(j\beta z) = I^+(z) + I^-(z) = I(z) \end{aligned}$$

$$Z_0 = \frac{V^+(z)}{I^+(z)} = -\frac{V^-(z)}{I^-(z)} \quad \text{characteristic impedance}$$

$$Z(z) = \frac{V(z)}{I(z)} \quad \text{input impedance at section } z$$

The reflection coefficient



- Defined as the ratio between the backward and forward waves:

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} = \frac{V^-(0) \exp(j\beta z)}{V^+(0) \exp(-j\beta z)} = \Gamma(0) \exp(j2\beta z)$$

$$Z(z) = \frac{V(z)}{I(z)} = \frac{V^+(0) \exp(-j\beta z) + V^-(0) \exp(j\beta z)}{\frac{V^+(0)}{Z_0} \exp(-j\beta z) - \frac{V^-(0)}{Z_0} \exp(j\beta z)} = Z_0 \frac{1 + \frac{V^-(0)}{V^+(0)} \exp(j2\beta z)}{1 - \frac{V^-(0)}{V^+(0)} \exp(j2\beta z)} = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

$$z(z) = \frac{Z(z)}{Z_0} = \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$
$$\Gamma(z) = \frac{z(z) - 1}{z(z) + 1} = \frac{Z(z) - Z_0}{Z(z) + Z_0}$$

Mapping between gamma and zeta planes




- The transformation $\gamma \rightarrow \zeta$ and viceversa defines the mapping between the complex planes ζ & γ
- Straight lines in ζ plane become circles or straight lines in γ plane, and viceversa
- In particular, constant resistance lines in ζ plane become circles in γ plane, constant reactance lines in ζ plane become circles in γ plane
- Particular points (origin, unit circle in γ plane):


$$Z = Z_0 \rightarrow \Gamma(z) = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0$$

$$Z = jX \rightarrow \Gamma(z) = \frac{jX - Z_0}{jX + Z_0} \rightarrow |\Gamma(z)| = \frac{\sqrt{X^2 + Z_0^2}}{\sqrt{X^2 + Z_0^2}} = 1$$

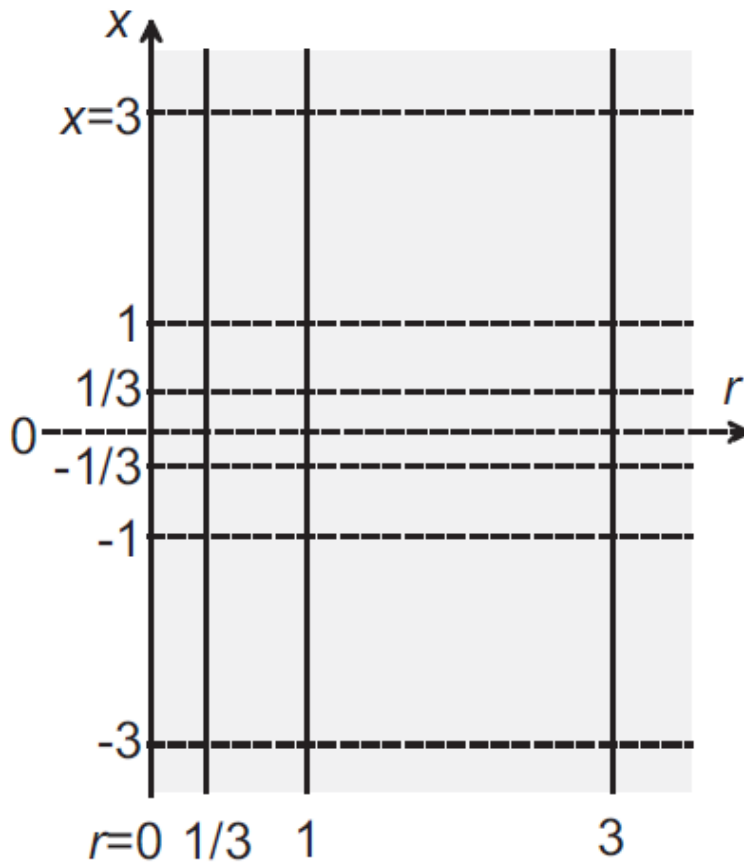Constant resistance (-) and reactance (- -) circles




z plane

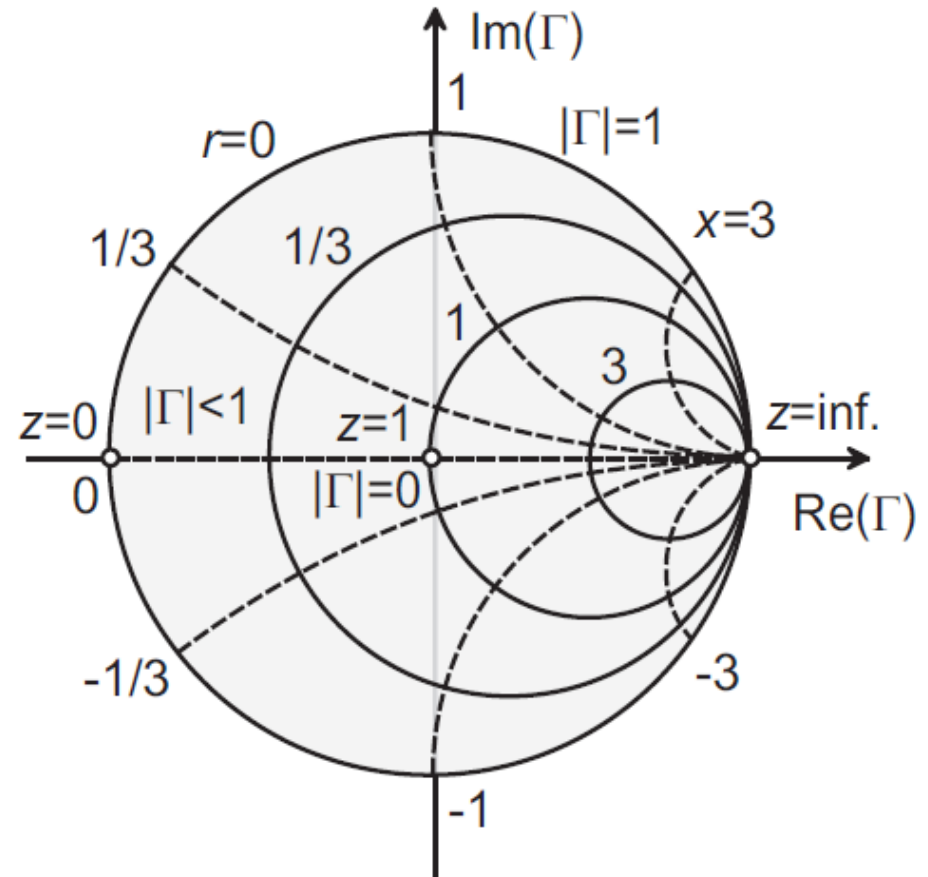

Γ plane

The Smith chart - reminder

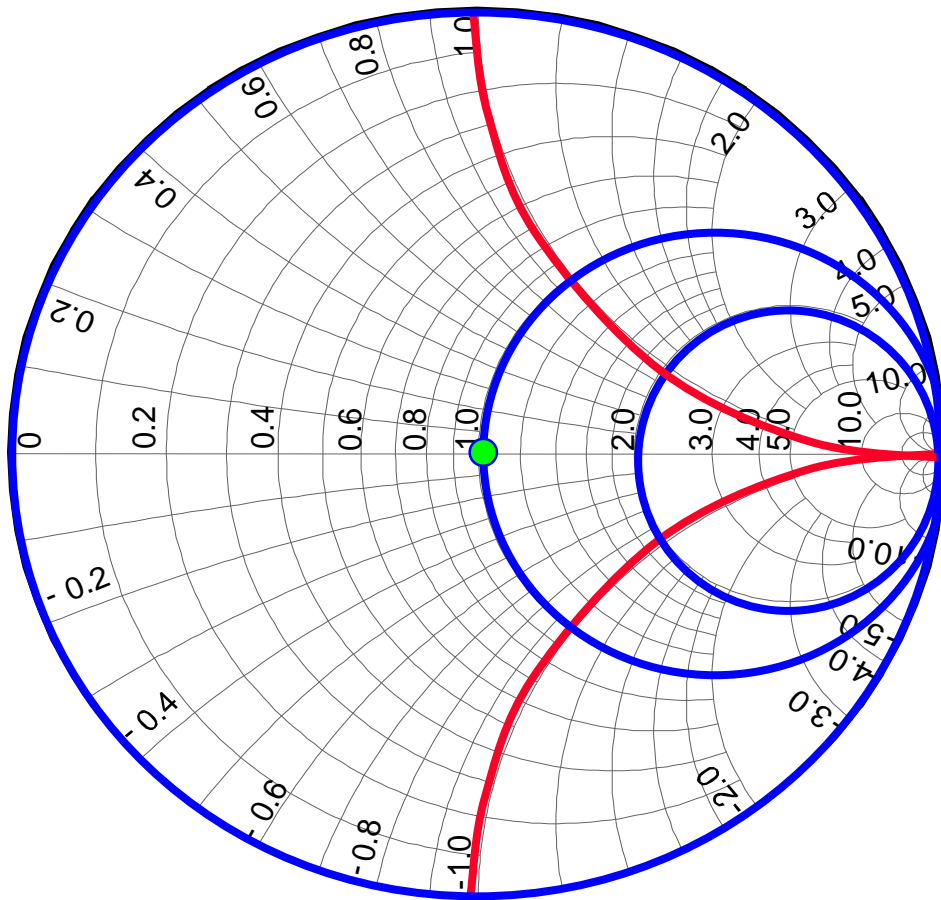


- Graphical representation of the relationship between the reflection coefficient and the normalized impedance ($R=\text{const.}$ and $X=\text{const.}$ lines in gamma plane):

$$\Gamma = \frac{z - 1}{z + 1}$$


$$z = \frac{Z}{Z_0}$$

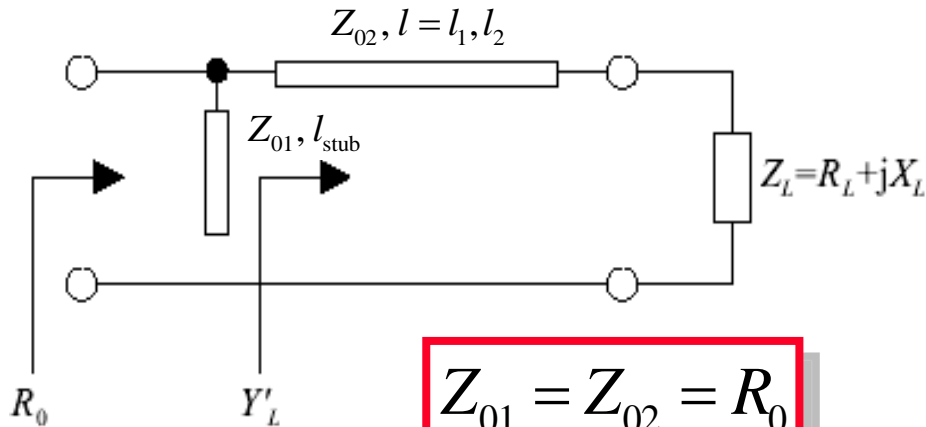The reflection coefficient on the Smith chart & the use of the Smith chart



- Using the Smith chart as a graphical computer is today (almost) a lost art, but the chart still is ubiquitous as a representation tool

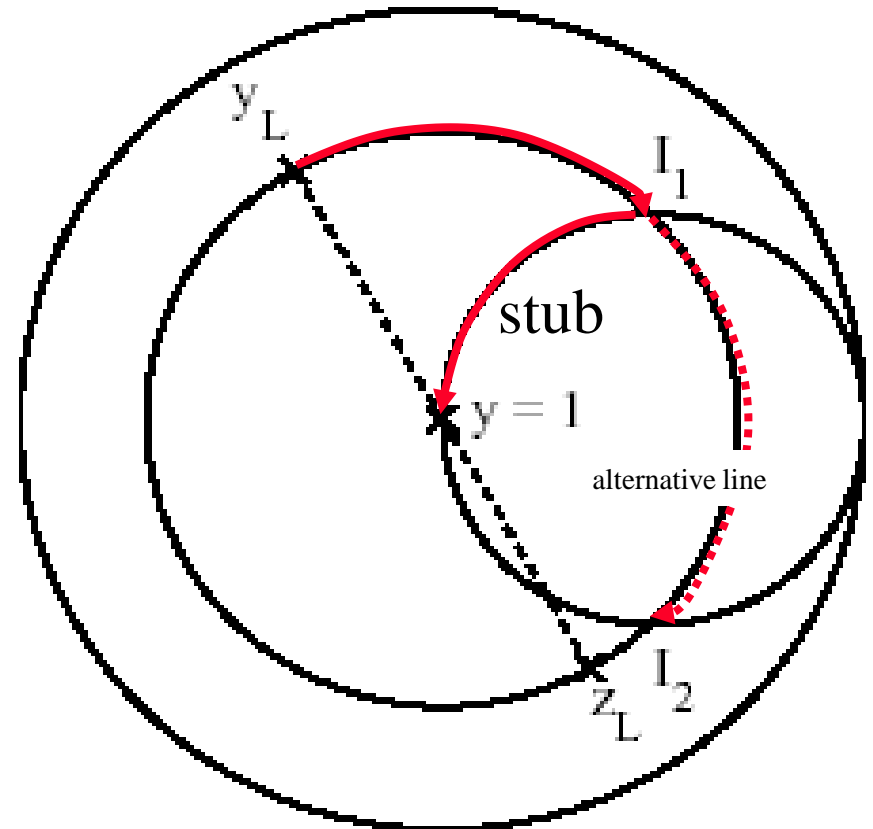
- Gamma rotates on the gamma plane along a line, thus allowing for a simple graphical way to evaluate the line impedance section by section
- Addition of series or parallel elements \rightarrow the Smith chart as a design tool for matching sections (parallel stub here)



Representing a linear n-port



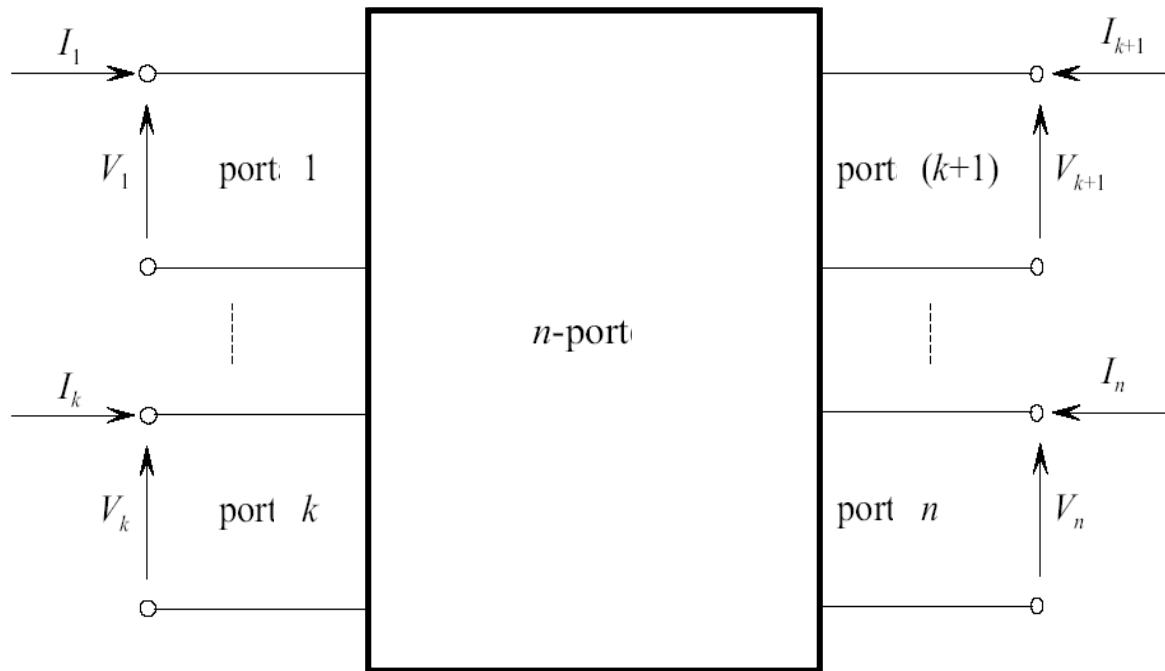- A linear n-port without internal independent generators in sinusoidal steady-state can be described by a matrix relationship between current and voltage phasors



E.g. for a two-port:

Series (impedance)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Parallel (admittance)

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Hybrid

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} H_{11} & H_{12} \\ H_{21} & H_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Why S (scattering) parameters



- Total voltages and currents are difficult to measure at RF and microwaves, and even the definition of these quantities may be questionable in some cases (waveguide).
- In the measurement of conventional ($Z, Y \dots$) two-port parameters, short and open circuits are required. However, they are difficult to realise over a broad band of frequencies.
- Most active devices or circuits are not open- or short circuit stable
- Solution \rightarrow measurement of progressive & regressive waves made on matched load \rightarrow SCATTERING PARAMETERS

Power wave rationale



- All the black box parameters previously introduced are based on the total voltages and currents.
- Note that these total voltages can be considered to be composed out of positive and negative going (progressive and regressive, forward and backward) waves (as in a TX line).
- For higher frequencies it is often more convenient to use a two-port description in terms of forward and backward waves (called power waves)
- Power waves can be formally defined also in a lumped-parameter structure

What are power waves



- Voltage and current phasors in a port can be replaced by two proper linear combinations of them called **power waves** \mathbf{a}_k and \mathbf{b}_k
- Since V and I phasors have different dimensions the combination requires (for each port) a parameter (called *normalization impedance*) having the dimension of an impedance

The normalization impedance for port k , Z_{0k} is arbitrary but typically assumed as real \rightarrow normalization resistance R_{0k}

$$\Re(Z_{0k}) > 0$$

The definition of power waves (real normalization impedance)




$$\mathbf{Z_{0k}=R_{0k} \text{ real and positive}}$$

$$\begin{cases} a_k = \frac{V_k + R_{0k}I_k}{2\sqrt{R_{0k}}} \\ b_k = \frac{V_k - R_{0k}I_k}{2\sqrt{R_{0k}}} \end{cases}$$



$$\begin{cases} V_k = (a_k + b_k)\sqrt{R_{0k}} \\ I_k = \frac{a_k - b_k}{\sqrt{R_{0k}}} \end{cases}$$

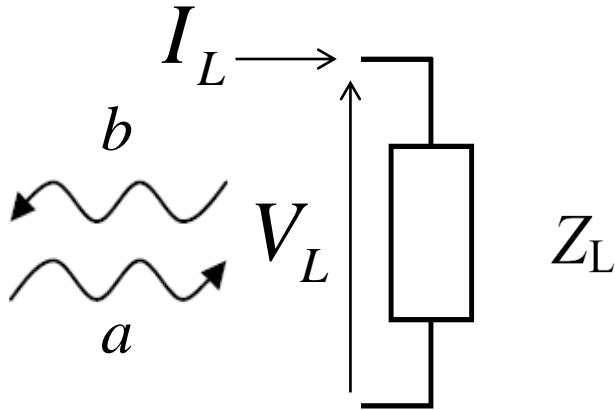Closing a port on its normalization resistance



$$Z_L = R_0 \rightarrow V_L = R_0 I_L$$

$$a = \frac{V_L + R_0 I_L}{2\sqrt{R_0}} = \frac{V_L}{\sqrt{R_0}} = \sqrt{R_0} I_L$$

$$b = \frac{V_L - R_0 I_L}{2\sqrt{R_0}} = 0$$

- In a port closed on its normalization resistance the backward wave b is identically zero!
- This does not generally imply any “matching” in the meaning of maximum power transfer....

Why “power” waves?




- Power entering the k -th port:

$$P_k = \Re(V_k I_k^*) = \Re((a_k + b_k) \cdot (a_k^* - b_k^*))$$

$$P_k = \Re(V_k I_k^*) = |a_k|^2 - |b_k|^2$$

a_k forward power wave

b_k backward power wave

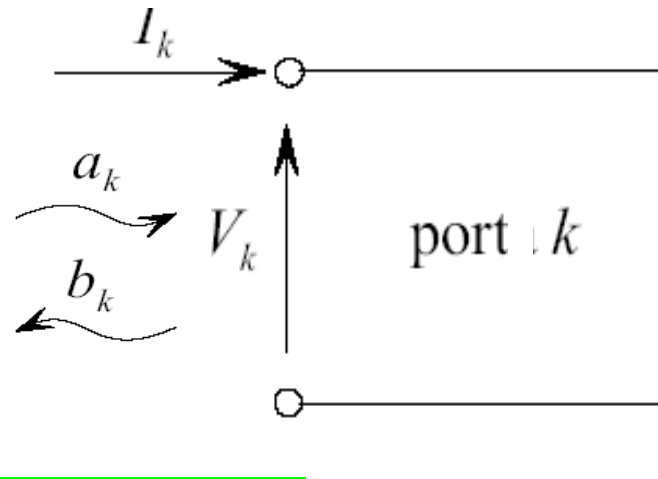


Power wave dimensions: \sqrt{W}

Power waves and transmission lines I



- Given a section z of a T-line of impedance Z_0 power waves are connected to progressive and regressive waves:

$$V(z) = V^+ + V^- = a\sqrt{Z_0} + b\sqrt{Z_0}$$
$$I(z) = I^+ + I^- = \frac{V^+}{Z_0} - \frac{V^-}{Z_0} = \frac{a\sqrt{Z_0}}{Z_0} - \frac{b\sqrt{Z_0}}{Z_0} = \frac{a}{\sqrt{Z_0}} - \frac{b}{\sqrt{Z_0}}$$


$$V^+ = a\sqrt{Z_0}$$
$$V^- = b\sqrt{Z_0}$$

- Power running on the line:

$$P(z) = \operatorname{Re}\{V(z)I^*(z)\} = \frac{|V^+|^2}{Z_0} - \frac{|V^-|^2}{Z_0} = |a|^2 - |b|^2$$

Power waves and transmission lines II



- While in a transmission line power waves exist from a physical standpoint as forward and backward waves, in a n -port their definition is “formal” → no propagation implied
- The normalization impedance does not have a *physical meaning* as the characteristic impedance does

The scattering matrix




In vector form

$$\begin{aligned}\underline{a} &= [a_1, a_2, a_3, \dots]^T \\ \underline{b} &= [b_1, b_2, b_3, \dots]^T \\ \mathbf{R}_0 &= \text{diag}\{R_{01}, R_{02}, R_{03}, \dots\}\end{aligned}$$

&
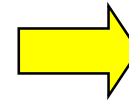
$$\begin{aligned}\underline{V} &= [V_1, V_2, V_3, \dots]^T \\ \underline{I} &= [I_1, I_2, I_3, \dots]^T\end{aligned}$$



$$\begin{aligned}\underline{V} &= \mathbf{R}_0^{1/2} (\underline{a} + \underline{b}) \\ \underline{I} &= \mathbf{R}_0^{-1/2} (\underline{a} - \underline{b})\end{aligned}$$

**Z-matrix
representation**

$$\underline{V} = \mathbf{Z} \underline{I}$$

*Substituting V and I in terms
of power waves a linear relationship
is obtained between a and b*

**Scattering
(S) matrix
representation**

$$\underline{b} = \mathbf{S} \underline{a}$$

S matrix in terms of Z matrix



$$\begin{aligned} \mathbf{S} &\equiv (\mathbf{R}_0^{-1/2} \mathbf{Z} \mathbf{R}_0^{-1/2} + \mathbf{I})^{-1} (\mathbf{R}_0^{-1/2} \mathbf{Z} \mathbf{R}_0^{-1/2} - \mathbf{I}) = \\ &\quad \vdots \\ &= \mathbf{R}_0^{-1/2} (\mathbf{Z} - \mathbf{R}_0) (\mathbf{Z} + \mathbf{R}_0)^{-1} \mathbf{R}_0^{1/2}. \end{aligned}$$

- Take care: matrices functions of the same matrix commute (**$\mathbf{AB}=\mathbf{BA}$** , in general false)!
- If normalization impedances are the same for all ports (typically 50 Ohm):

$$\mathbf{R}_0 = R_0 \mathbf{I} \quad (G_0 = 1/R_0)$$

$$\begin{aligned} \mathbf{S} &= (\mathbf{Z} - R_0 \mathbf{I}) (\mathbf{Z} + R_0 \mathbf{I})^{-1} \\ &= (G_0 \mathbf{I} - \mathbf{Y}) (G_0 \mathbf{I} + \mathbf{Y})^{-1} \end{aligned}$$

Other conversion formulae



$$\mathbf{S} = (\mathbf{I} + \mathbf{R}_0^{1/2} \mathbf{Y} \mathbf{R}_0^{1/2})^{-1} (\mathbf{I} - \mathbf{R}_0^{1/2} \mathbf{Y} \mathbf{R}_0^{1/2})$$

$$\mathbf{Z} = \mathbf{R}_0^{1/2} (\mathbf{I} + \mathbf{S}) (\mathbf{I} - \mathbf{S})^{-1} \mathbf{R}_0^{1/2}$$

$$\mathbf{Y} = \mathbf{R}_0^{-1/2} (\mathbf{I} - \mathbf{S}) (\mathbf{I} + \mathbf{S})^{-1} \mathbf{R}_0^{-1/2}$$

Some S-matrix properties



- Total power dissipated by n-port:

$$P_d = \sum_{i=1}^N \left(|a_i|^2 - |b_i|^2 \right) = \left(\underline{a}^T \cdot \underline{a}^* - \underline{b}^T \cdot \underline{b}^* \right) \stackrel{(\underline{b}=\underline{S}\underline{a})}{=} \underline{a}^T \left(\mathbf{I} - \mathbf{S}^T \mathbf{S}^* \right) \underline{a}^*$$

- Lossless (reactive) device:


$$\mathbf{S}^{T*} \mathbf{S} \equiv \mathbf{S}^\dagger \mathbf{S} = \mathbf{I} \quad \mathbf{S} \text{ hermitian}$$

- Reciprocal device:

$$\mathbf{S} = \mathbf{S}^T \quad \mathbf{S} \text{ symmetric}$$

- For a passive device the eigenvalues of $\mathbf{S}^\dagger \mathbf{S}$ have magnitude < 1

The S-matrix of a one-port

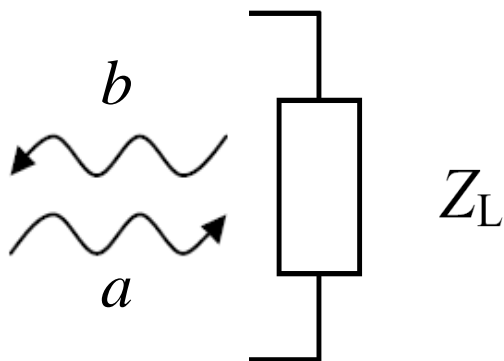

$$S_{11} = \Gamma_L = \frac{b}{a}$$

Γ_L reflection coefficient

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$



$$Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

$$Y_L = \frac{1}{Z_0} \frac{1 - \Gamma_L}{1 + \Gamma_L}$$

Example – Does the choice of Z_0 change the circuit solution? - I




choose $Z_0 = R_L$ (real) $\Rightarrow \Gamma_L = 0$

$$b = \Gamma_L a = 0$$

$$a = \frac{V + Z_0 I}{2\sqrt{Z_0}} = \frac{V + R_L I}{2\sqrt{R_L}} = \frac{V}{\sqrt{R_L}}$$

$$P_d = |a|^2 - |b|^2 = \frac{|V|^2}{R_L}$$

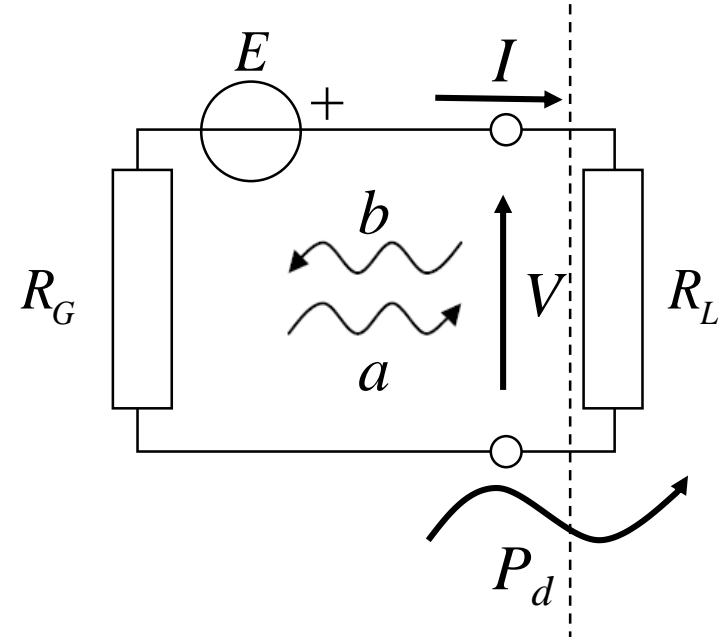

- The normalization impedance “matches” the load

Example – Does the choice of Z_0 change the circuit solution? - II



$$\text{real } Z_0 \neq R_L \Rightarrow \Gamma_L = \frac{R_L - Z_0}{R_L + Z_0};$$

$$a = \frac{V + Z_0 I}{2\sqrt{Z_0}} = \frac{V(1 + Z_0 / R_L)}{2\sqrt{Z_0}}$$

- The normalization impedance is “mismatched”

$$P_d = |a|^2 - |b|^2 = |a|^2 (1 - |\Gamma_L|^2) = \frac{|V|^2 |1 + Z_0 / R_L|^2}{4Z_0} \left(1 - \frac{|1 - Z_0 / R_L|^2}{|1 + Z_0 / R_L|^2} \right) =$$

$$= \frac{|V|^2}{4Z_0} (|1 + Z_0 / R_L|^2 - |1 - Z_0 / R_L|^2) =$$

$$= \frac{|V|^2}{4Z_0} (1 + |Z_0 / R_L|^2 + 2\Re(Z_0 / R_L) - 1 - |Z_0 / R_L|^2 + 2\Re(Z_0 / R_L)) =$$

$$= \frac{|V|^2}{4Z_0} 4(Z_0 / R_L) = \frac{|V|^2}{R_L}$$

n -port with independent sources



Open circuit
voltages $\neq 0$

$$\underline{V} = \underline{Z} \underline{I} + \underline{V}_0$$

Short-circuit
currents $\neq 0$

$$\underline{I} = \underline{Y} \underline{V} + \underline{I}_0$$

b power waves $\neq 0$ when all
ports are closed on the
normalization impedances
(\rightarrow all $a=0$, check!)


$$\underline{b} = \underline{S} \underline{a} + \underline{b}_0$$

$$\underline{b}_0 \equiv (\underline{R}_0^{-1/2} \underline{Z} \underline{R}_0^{-1/2} + \underline{I})^{-1} \underline{R}_0^{-1/2} \underline{V}_0 = \underline{R}_0^{1/2} (\underline{Z} + \underline{R}_0)^{-1} \underline{V}_0 .$$


Forward & backward power wave generators



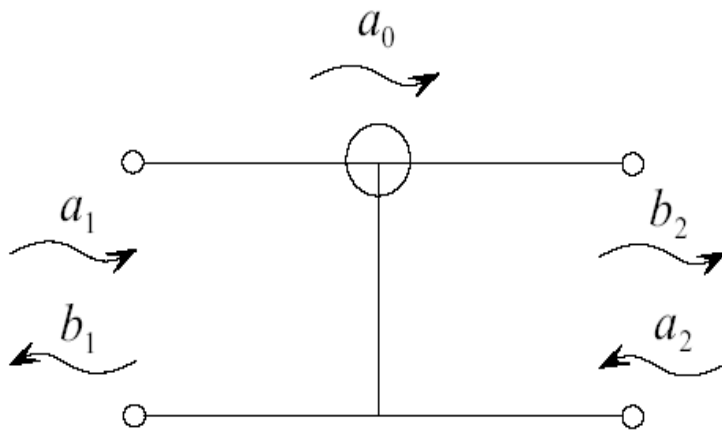- While in series / parallel representations ideal voltage and current sources are introduced, in the power wave representation of non-autonomous n -ports we introduce forward and backward power wave generators


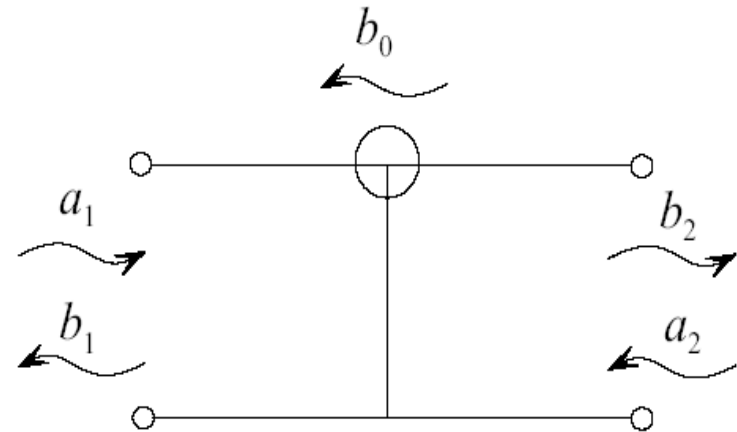
$$\begin{cases} b_1 = a_2 \\ b_2 = a_0 + a_1 \end{cases}$$



$$\begin{cases} b_1 = a_2 + b_0 \\ b_2 = a_1 \end{cases}$$

Why the symbol: forward wave generator = voltage + current source




$$b_1 = a_2 \Rightarrow \frac{V_1 - R_0 I_1}{2\sqrt{R_0}} = \frac{V_2 + R_0 I_2}{2\sqrt{R_0}}$$

$$\Rightarrow V_1 - R_0 I_1 = V_2 + R_0 I_2 \Rightarrow V_1 - V_2 = R_0 I_1 + R_0 I_2$$


$$b_2 = a_1 + a_0 \Rightarrow \frac{V_2 - R_0 I_2}{2\sqrt{R_0}} = \frac{V_1 + R_0 I_1}{2\sqrt{R_0}} + a_0$$

$$\Rightarrow V_2 - R_0 I_2 = V_1 + R_0 I_1 + 2\sqrt{R_0} a_0 \Rightarrow V_1 - V_2 = -R_0 I_2 - R_0 I_1 - 2\sqrt{R_0} a_0$$
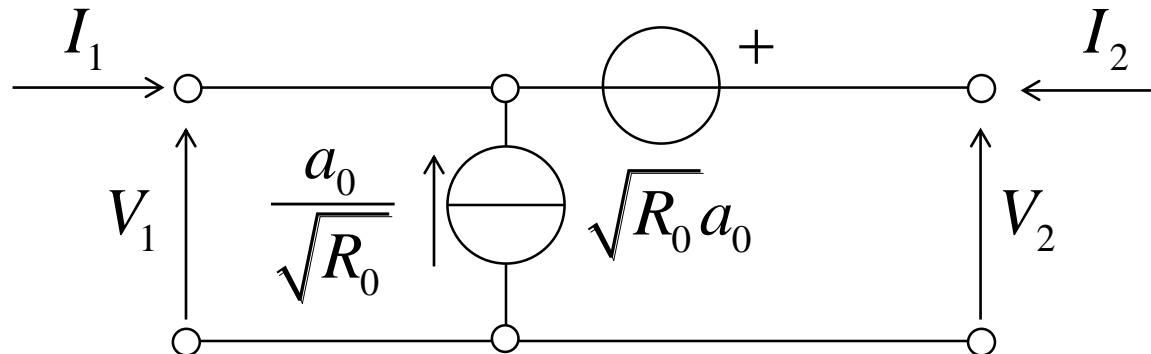
$$\Rightarrow V_2 = V_1 + \sqrt{R_0} a_0, \quad I_2 = -I_1 - \frac{a_0}{\sqrt{R_0}}$$




Equivalent circuit of autonomous n -port

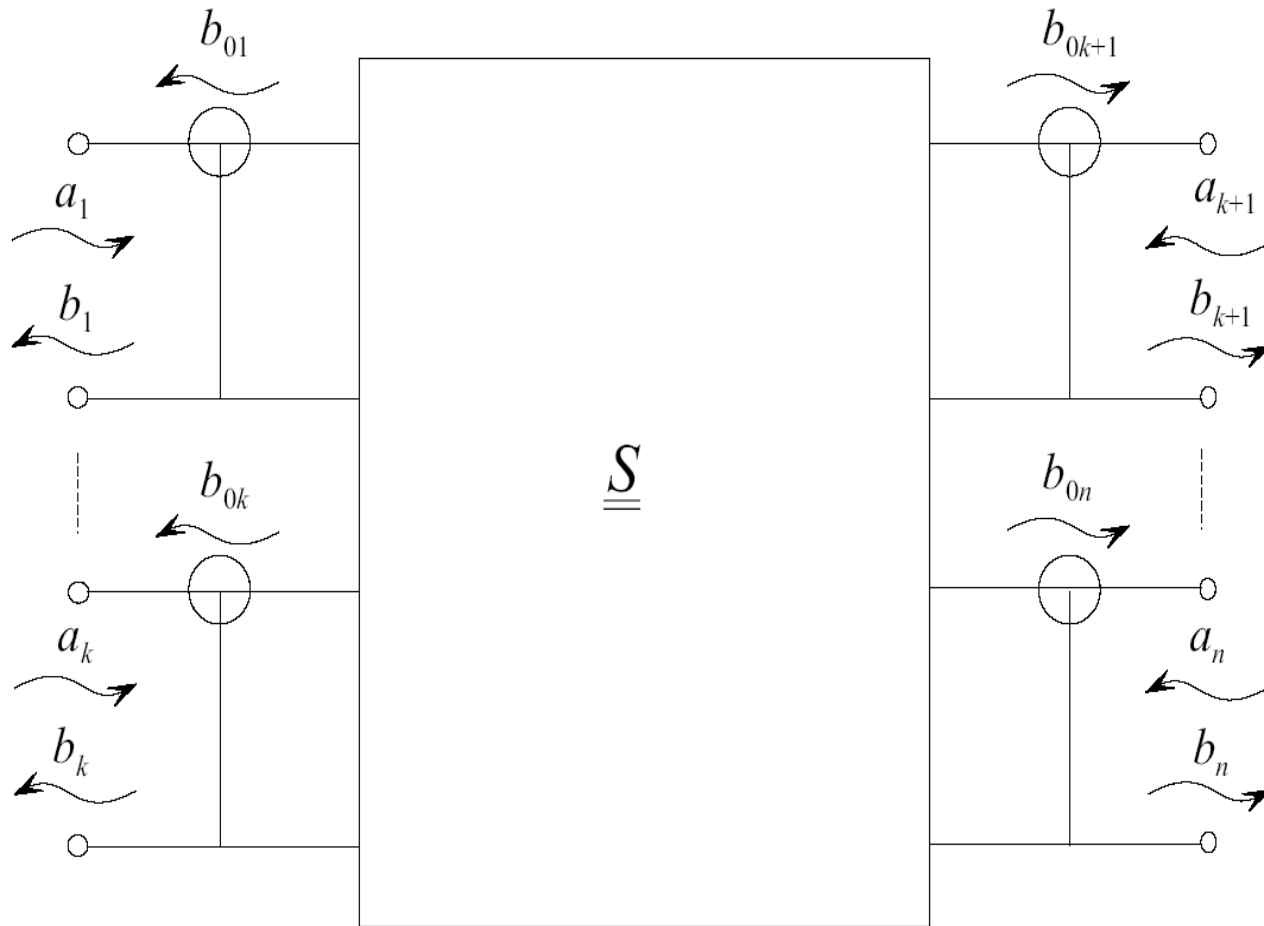

\underline{b}_0 can be derived from open-circuit voltages

Example: real voltage generator I

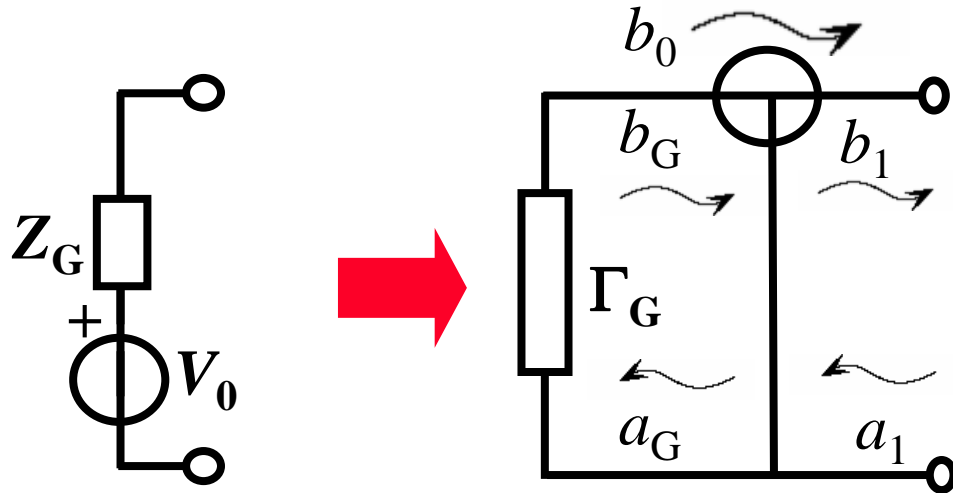

$$a_G = a_1$$


$$b_1 = b_G + b_0$$

$$b_G = \Gamma_G a_G$$

$$b_1 = \Gamma_G a_1 + b_0$$


$$\Gamma_G = \frac{Z_G - R_0}{Z_G + R_0}$$
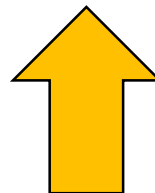
$$b_0 = \frac{\sqrt{R_0}}{Z_G + R_0} V_0$$



Why?

Example: real voltage generator II

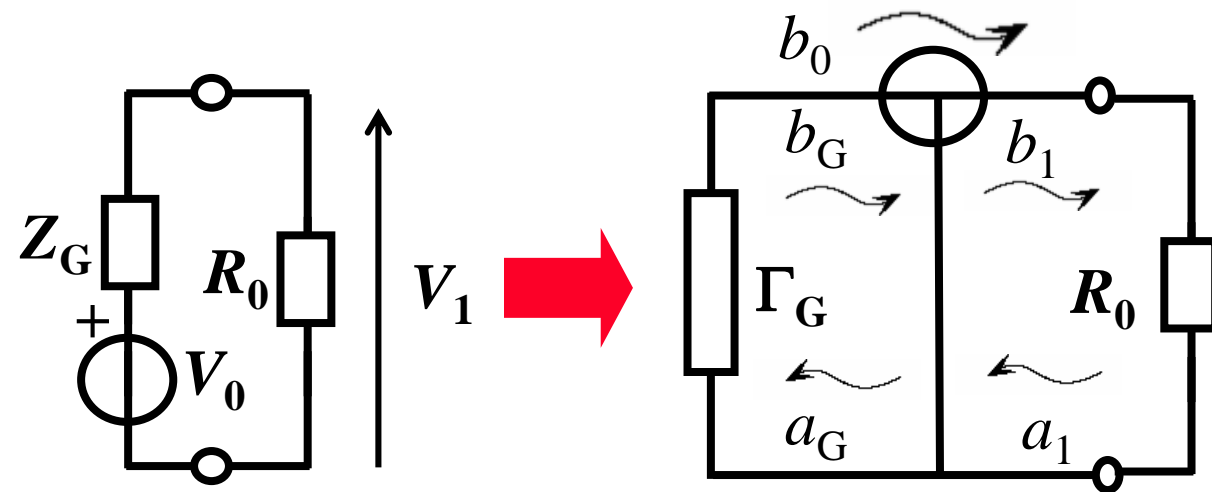

$$a_1 = 0, \quad b_1 = b_0$$

$$V_1 = \frac{V_0 R_0}{Z_G + R_0} = \sqrt{R_0} (a_1 + b_1) =$$

$$= \sqrt{R_0} b_0 \rightarrow b_0 = \frac{V_0}{Z_G + R_0} \sqrt{R_0}$$

if $Z_G = R_0$


$$b_0 = \frac{1}{2\sqrt{R_0}} V_0$$

$$a_G = a_1$$

$$b_G = 0$$

$$b_1 = b_0$$

Measuring the S matrix – two port I

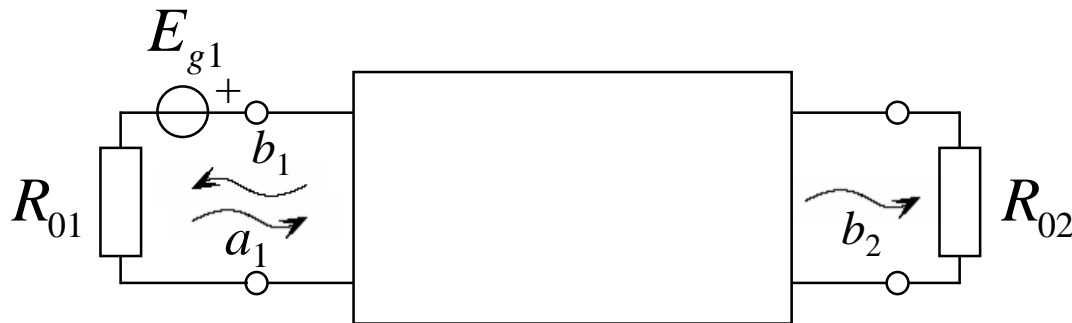


$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0}$$

- We need to **cancel** a_2 and measure the response at port 1
- Port 2 is closed on the normalization resistance, in this case we have (check!):

$$a_2 = 0 \quad b_2 = \frac{V_2}{\sqrt{R_{02}}} \quad a_1 = \frac{E_{g1}}{2\sqrt{R_{01}}}$$

- Therefore scattering parameters are measured on an n -port closed on **resistive loads** (potentially wideband)

Check!

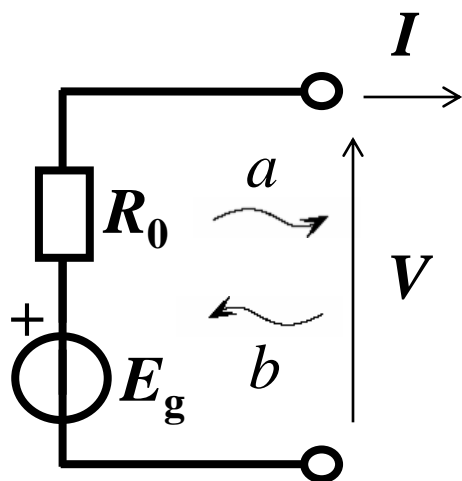

$$V = (a + b)\sqrt{R_0}$$


$$I = \frac{a - b}{\sqrt{R_0}}$$

$$V = -R_0 I + E_g$$

$$(a + b)\sqrt{R_0} = -R_0 \frac{a - b}{\sqrt{R_0}} + E_g$$

$$(a + b + a - b)\sqrt{R_0} = E_g \Rightarrow a = \frac{E_g}{2\sqrt{R_0}}$$

Measuring the S matrix – two port II

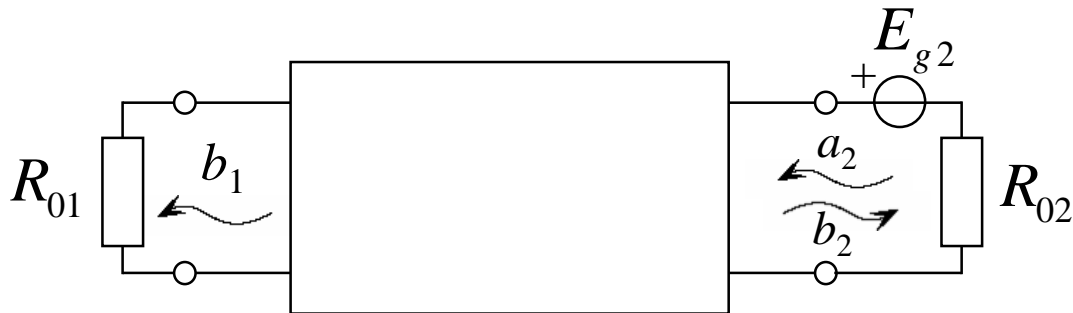


$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} \quad S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

- We need to **cancel** a_1 and measure the response at port 2
- Port 1 is closed on the normalization resistance, in this case we have (check!):

$$a_1 = 0 \quad b_1 = \frac{V_1}{\sqrt{R_{01}}} \quad a_2 = \frac{E_{g2}}{2\sqrt{R_{02}}}$$

- Therefore scattering parameters are measured on an n -port closed on **resistive loads** (potentially wideband)

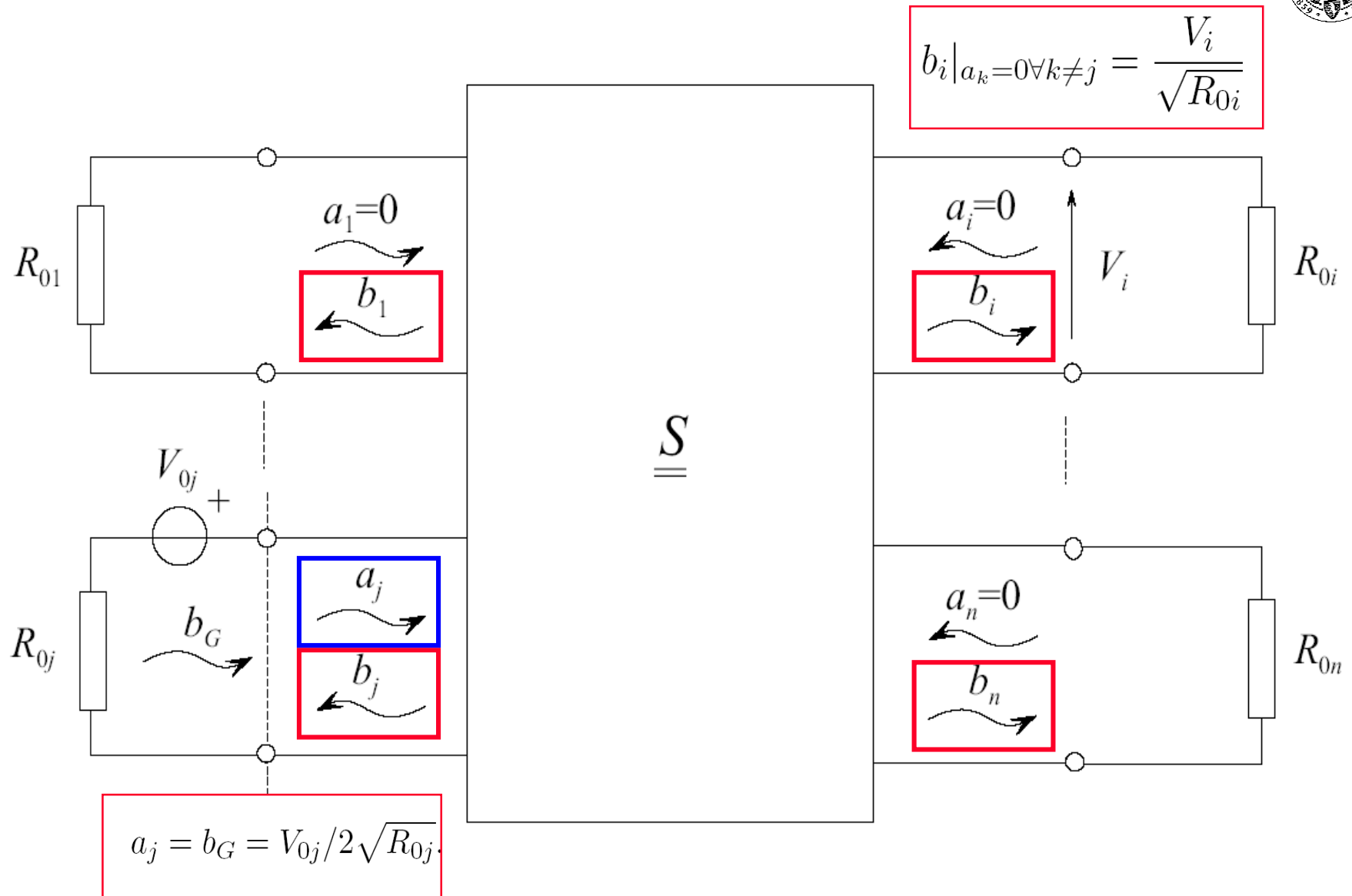Setup to measure the j-th column of S (n-port)



Further remarks



- To evaluate the S parameters we can conveniently make use of a generator with internal impedance equal to the normalization resistance, to change column we only need to change the generator
- The diagonal of \mathbf{S} corresponds to the reflection coefficients seen from each port when all others are closed on the normalization resistances
- For the out-of-diagonal coefficients (transmission coefficients) we have (check!):

$$a_j = b_G = V_{0j}/2\sqrt{R_{0j}}. \quad b_i|_{a_k=0\forall k\neq j} = \frac{V_i}{\sqrt{R_{0i}}}$$

$$S_{ij}|_{i\neq j} = \left. \frac{b_i}{a_j} \right|_{a_k=0\forall k\neq j} = 2\frac{V_i}{V_{0j}}\sqrt{\frac{R_{0j}}{R_{0i}}}.$$

Solving a network made of connected n-ports



- A network deriving from the connection of several n-ports can be solved by exploiting as **unknowns the power waves** and as **constitutive equations the scattering matrices** of each n-port
- For example, in a network with m 2-ports we have $4m$ unknowns but also $2m$ constitutive relationships (from scattering parameters) and **$2m$ continuity relationships** derived from the Kirchhoff voltage and current laws
- Power waves are **not necessarily continuous** across two connected ports \rightarrow only if the normalization impedance is the same on both sides

Connecting n -ports \rightarrow power wave continuity




V and I
continuity

$$V_j = V_i$$
$$I_j = -I_i$$



$$\sqrt{R_{0j}}(a_j + b_j) = \sqrt{R_{0i}}(a_i + b_i)$$
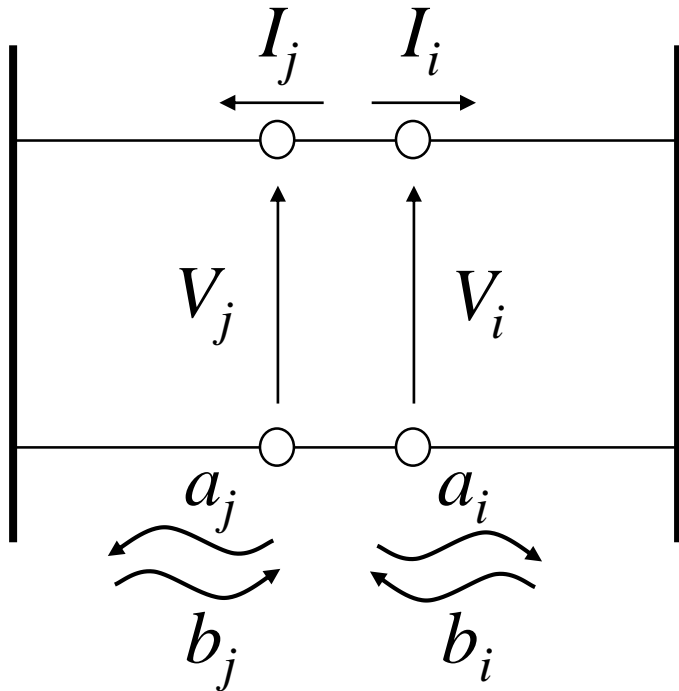
$$(a_j - b_j) / \sqrt{R_{0j}} = -(a_i - b_i) / \sqrt{R_{0i}}$$



- If the normalization impedances are different the linear relationship between power waves is non-diagonal
- If they are equal the simple continuity holds:


$$a_j = b_i$$

$$a_i = b_j$$


Reference plane shift I



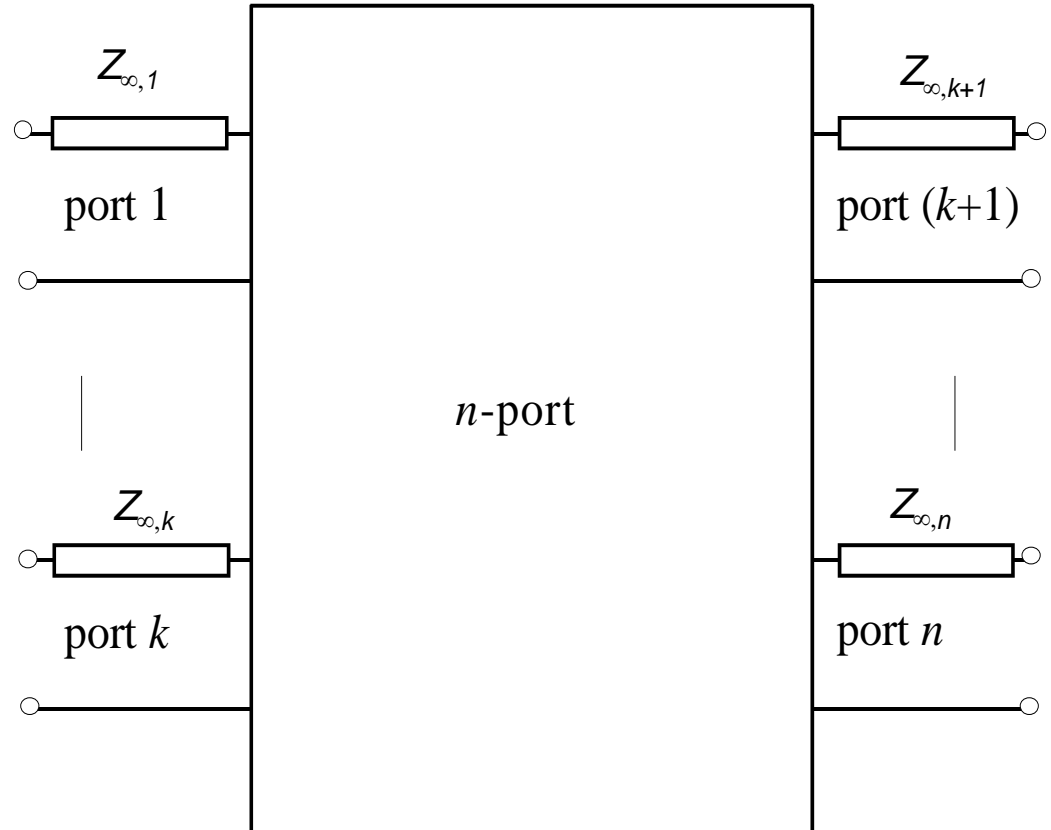
- Suppose we connect to all ports transmission line with characteristic impedance equal to the port normalization impedance, how is the S matrix transformed?



Reference plane shift II

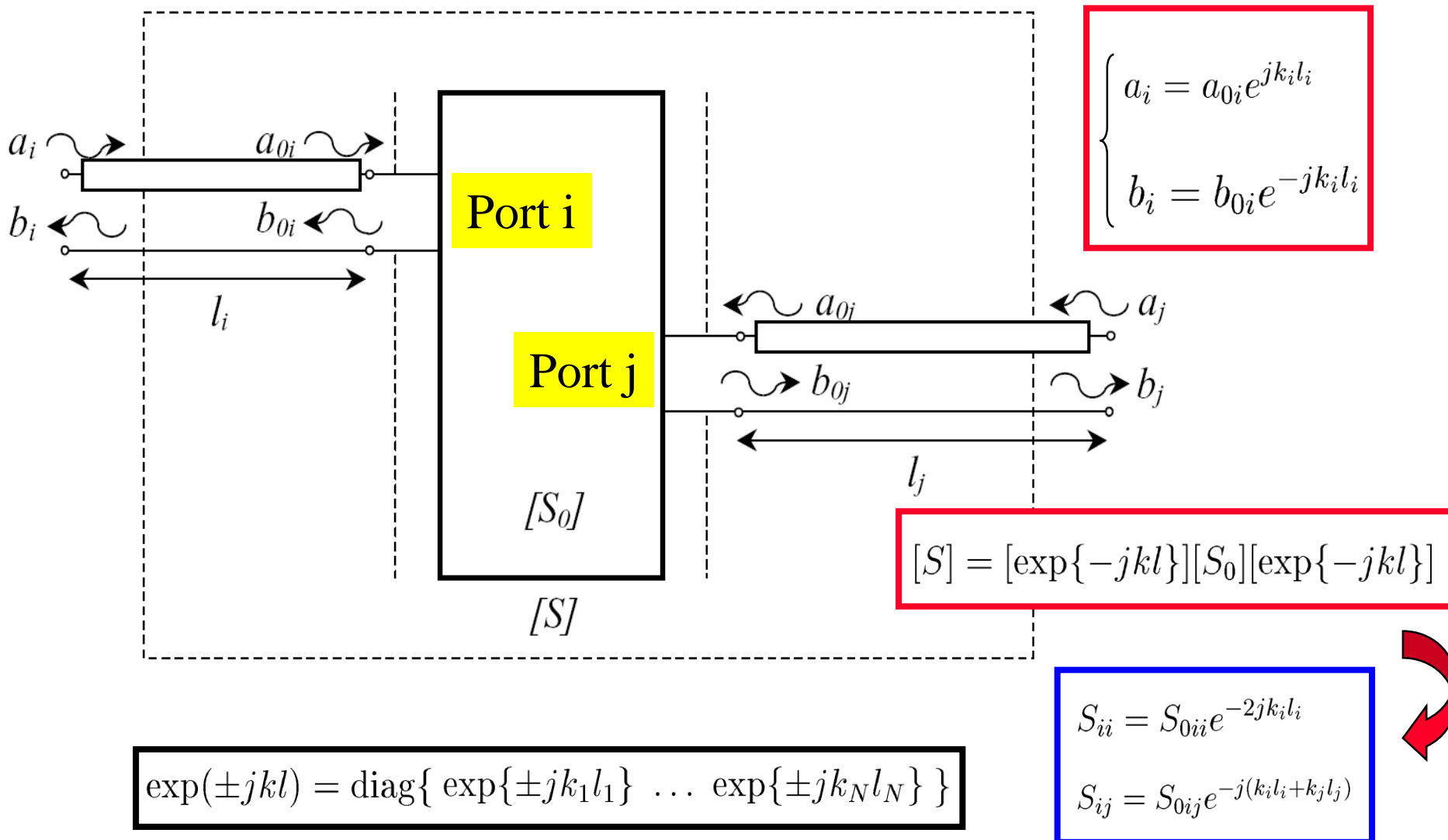

Example: loaded line input impedance

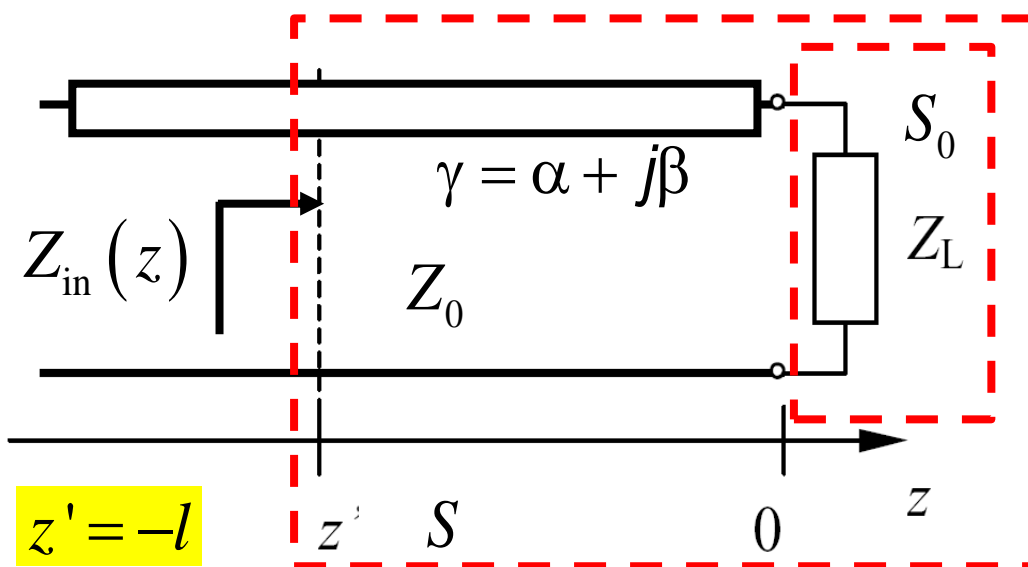

Assume as the reference impedance Z_0 of the line

$$S_0 = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

From line theory

$$\Gamma(z') = \Gamma_L \exp(j2\beta z' + 2\alpha z')$$

$$S = \Gamma(-l) = \Gamma_L \exp(-j2\beta l - 2\alpha l)$$

Reference plane shift

$$S = \exp(-j\beta l - \alpha l) S_0 \exp(-j\beta l - \alpha l)$$


$$Z_{in}(z) = Z_0 \frac{1+S}{1-S} = Z_0 \frac{1+S_0 \exp(-2\gamma l)}{1-S_0 \exp(-2\gamma l)} = Z_0 \frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)}$$

Scattering matrix of a line section



- We choose $R_{01}=R_{02}=Z_{\infty}$
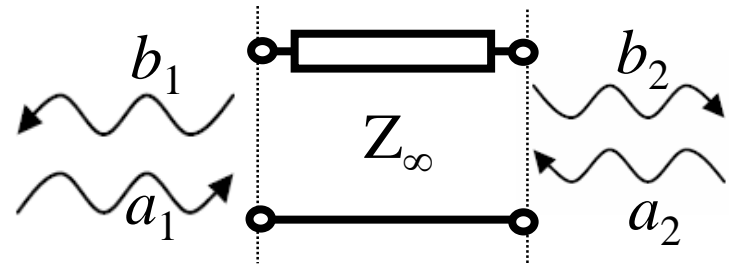
$$S = \begin{pmatrix} 0 & \exp(-j\beta L) \\ \exp(-j\beta L) & 0 \end{pmatrix}$$



- If the normalization resistance is different from Z_{∞}

$$S_{11}^{(R_0)} = S_{22}^{(R_0)} \stackrel{\text{def}}{=} \Gamma_{in}^{(R_0)} = \frac{Z_{\infty} (1 + \Gamma_{in}^{(Z_{\infty})}) - R_0 (1 - \Gamma_{in}^{(Z_{\infty})})}{Z_{\infty} (1 + \Gamma_{in}^{(Z_{\infty})}) + R_0 (1 - \Gamma_{in}^{(Z_{\infty})})}$$


$$S_{21}^{(R_0)} = S_{12}^{(R_0)} = (1 + S_{11}^{(R_0)}) \exp(-j\beta L) \frac{1 + \Gamma_L^{(Z_{\infty})}}{1 + \Gamma_{in}^{(Z_{\infty})}}$$

$$\Gamma_L^{(Z_{\infty})} = \frac{R_0 - Z_{\infty}}{R_0 + Z_{\infty}} \quad (\text{ref. impedance} = Z_{\infty})$$

$$\Gamma_{in}^{(Z_{\infty})} = \Gamma_L^{(Z_{\infty})} \exp(-2j\beta L) \quad (\text{ref. impedance} = Z_{\infty})$$

To evaluate S_{11} close the line on R_0 and evaluate Z_{in}

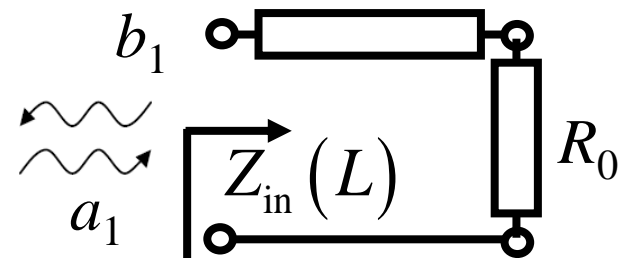
Then: $S_{11} \stackrel{\text{def}}{=} \Gamma_{in}^{(R_0)} = (Z_{in} - R_0) / (Z_{in} + R_0)$



Proof with reference plane shift



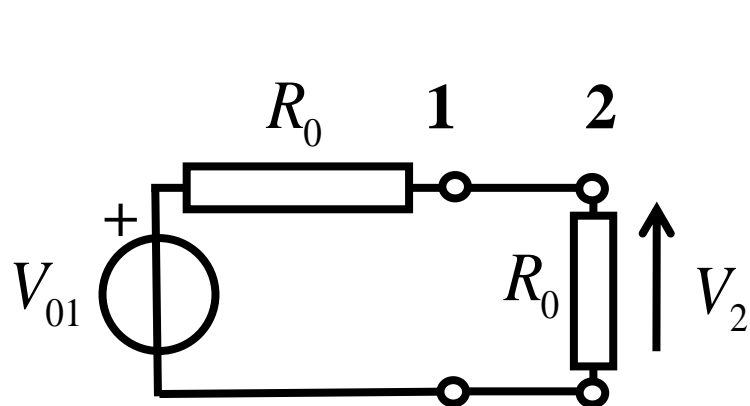- We choose $R_{01}=R_{02}=Z_{\infty}$
- Start with a two-port made of two short circuits.
- Close on the normalization resistance at port 2 and excite at port 1 with a real generator having the normalization resistance as the internal resistance
- The reflection coefficient is 0 because of matching and furthermore (the structure is symmetrical and reciprocal):



$$S_{21} = S_{12} = 2 \frac{V_2}{V_{01}} = 2 \times \frac{1}{2}$$

$$\bar{S} = \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix} \text{ with plane shift at port 1:}$$

$$S = \begin{pmatrix} e^{-j\beta L} & 0 \\ 0 & e^{-j\beta L} \end{pmatrix} \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix} = \begin{pmatrix} 0 & e^{-j\beta L} \\ e^{-j\beta L} & 0 \end{pmatrix}$$