

Noise modeling and low-noise amplifier design

Microwave Electronics

Giovanni Ghione, Marco Pirola


Politecnico di Torino, DET



Noise is a stochastic (random) process



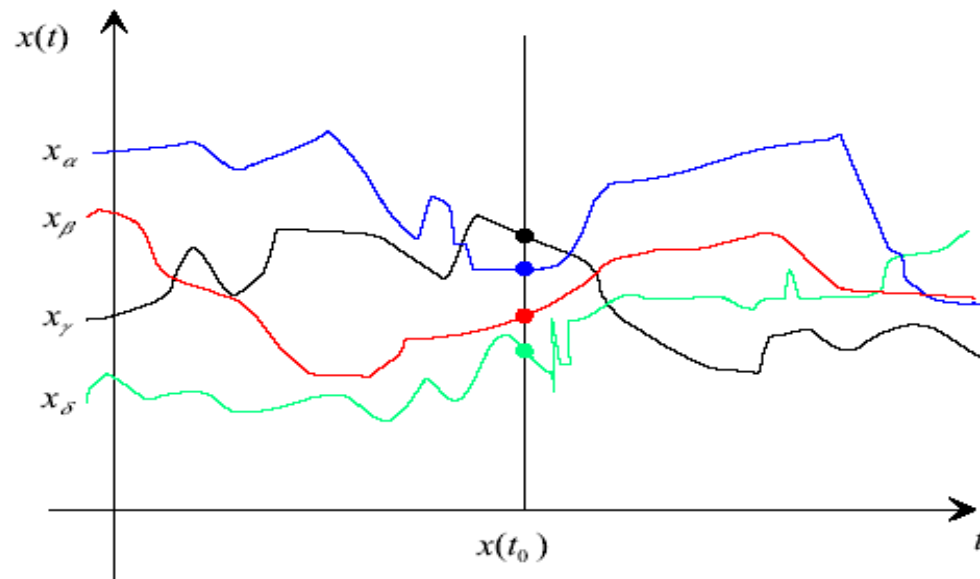- In real world voltages and currents are affected by small-amplitude random fluctuations \rightarrow the actual signal can be modeled as the ideal signal plus a stochastic process called *noise*
- Stochastic process $x(t) \rightarrow$ a bundle of random functions of time (*realizations* of the process)



Characterizing noise



- In circuits we decompose “deterministic” voltages and currents from their “fluctuations”; fluctuations have by definition *zero average value*.
- V and I fluctuations → noise has zero mean but **nonzero mean square value** and **nonzero power spectrum** → **power transfer** within a circuit.
- Since noise is a (zero average) stochastic process it must be characterized statistically through concepts like:
 - **quadratic mean and mean square value**
 - **correlation and self-correlation**
 - **power and correlation spectra**

A reminder on random processes



- A (complex valued) random process $x(t)$ is a set of *process realizations* $x_k(t)$; we can define
 - **time averages** $\langle x_k(t) \rangle$ (random numbers obtained averaging each realization in time)
 - **ensemble averages** $E[x(t)]$ (a function of time obtained taking the statistical average of all realizations at a given time)
 - for an **ergodic & stationary process** time and ensemble averages coincide \rightarrow this will be our case
- Mutual ($m \neq n$) and self ($m = n$) correlation:

$$R_{x_m x_n}(t, \tau) = \left\langle x_m(t) x_n^*(t + \tau) \right\rangle_{\substack{\text{stationary} \\ \text{process}}} = R_{x_m x_n}(\tau)$$

- Quadratic mean and root mean square (rms) value:

$$R_{xx}(0) = \left\langle x(t) x^*(t) \right\rangle = \left\langle |x(t)|^2 \right\rangle \equiv \overline{x^2}, \quad x_{rms} = \sqrt{\overline{x^2}}$$

Power and correlation spectra



- Stationary processes are better characterized in the spectral domain → **correlation spectrum** derived as the Fourier transform of the correlation function

$$S_{x_m x_n}(\omega) = 2 \int_{-\infty}^{+\infty} R_{x_m x_n}(\tau) e^{j\omega\tau} d\tau, \quad \omega \geq 0 \text{ (single-sided!)}$$


- Power spectrum** (Fourier transform of self-correlation):

$$S_{xx}(\omega) \equiv S_x(\omega) = 2 \int_{-\infty}^{+\infty} R_{xx}(\tau) e^{j\omega\tau} d\tau, \quad \omega \geq 0; \quad R_{xx}(\tau) = \frac{1}{2\pi} \int_0^{+\infty} S_{xx}(\omega) e^{-j\omega\tau} d\omega$$

- Spectral formulation of **signal power**:

$$P_{x,av} = \overline{x^2} = R_{xx}(0) = \frac{1}{2\pi} \int_0^{+\infty} S_{xx}(\omega) d\omega = \int_0^{+\infty} S_{xx}(f) df = \int_0^{+\infty} p_x(f) df$$

Noise spectral density and white noise

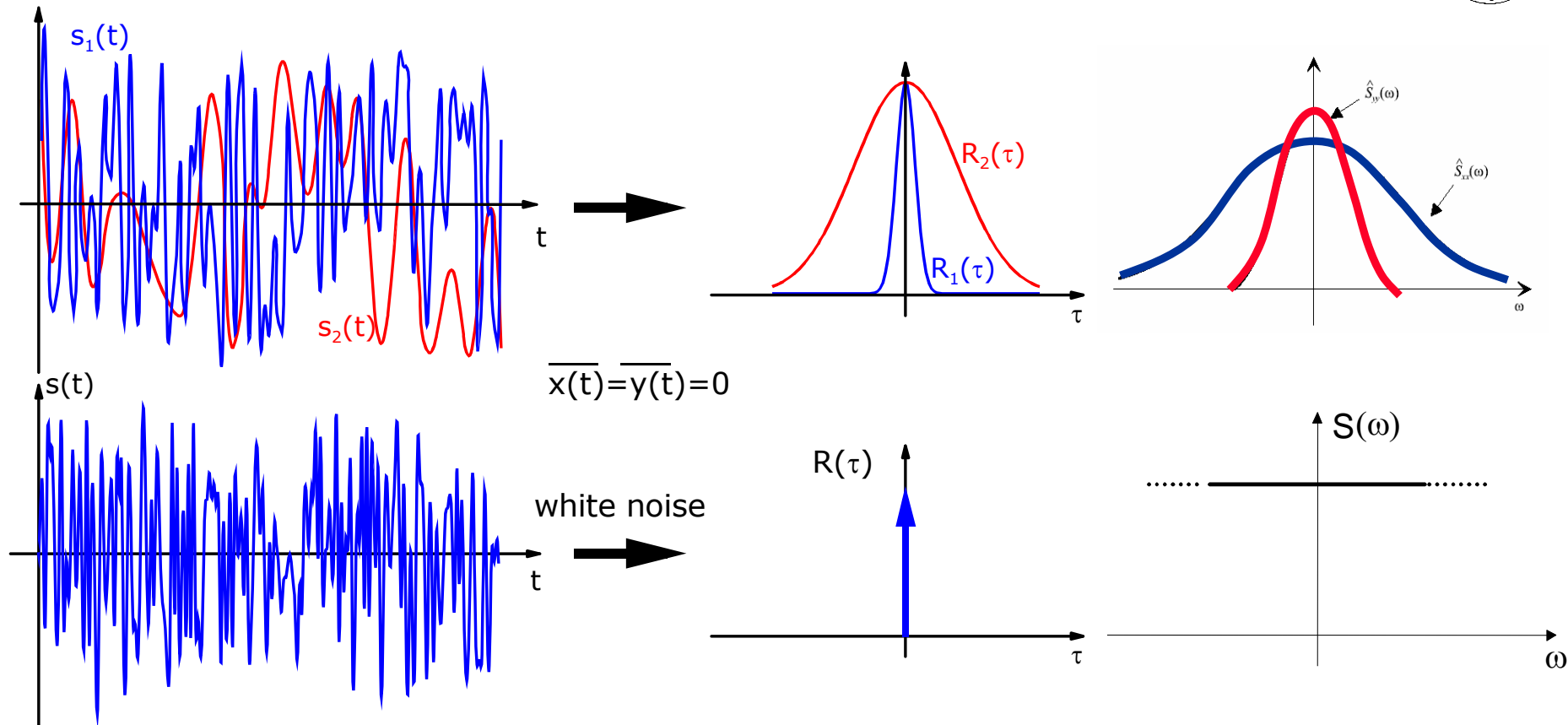


- **White noise has** (theoretically) a constant spectral density
- **Coloured noise** a low-pass spectral density

Equivalent circuit of a noisy one-port




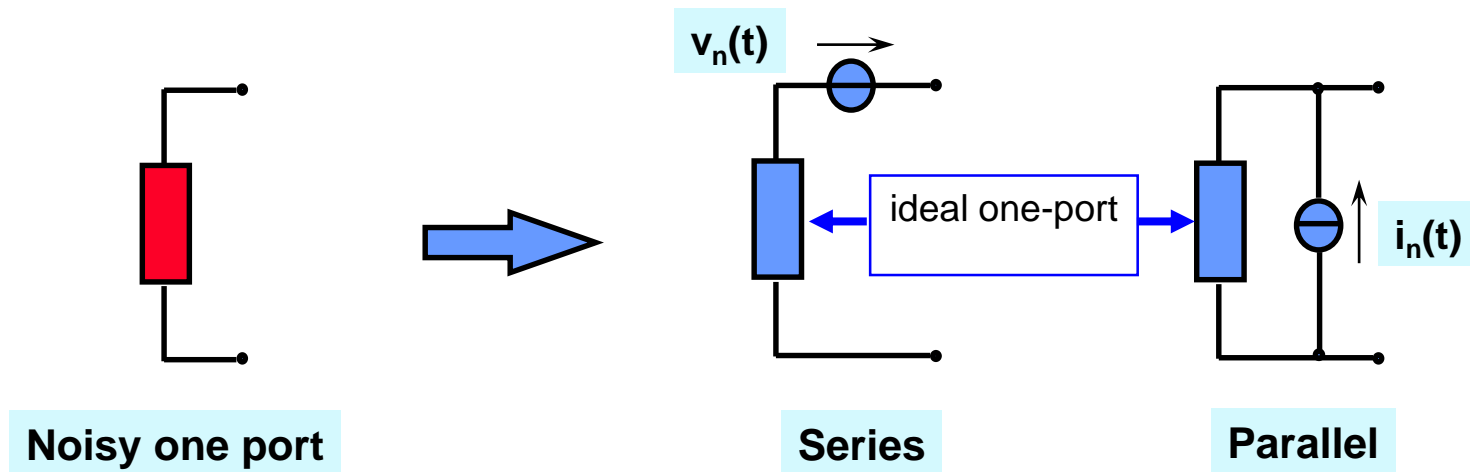
- A noisy one-port is a noiseless equivalent plus a random noise generator (series \rightarrow Thevenin, parallel \rightarrow Norton)



- Available noise power and noise generator spectra (V^2/Hz , A^2/Hz):

$$P_{n,av} = \frac{\overline{v_n^2}}{4R} = \int_0^{+\infty} \frac{S_{v_n}(f)}{4R} df = \frac{\overline{i_n^2}}{4G} = \int_0^{+\infty} \frac{S_{i_n}(f)}{4G} df = \int_0^{+\infty} p_n(f) df$$

Noisy two-ports

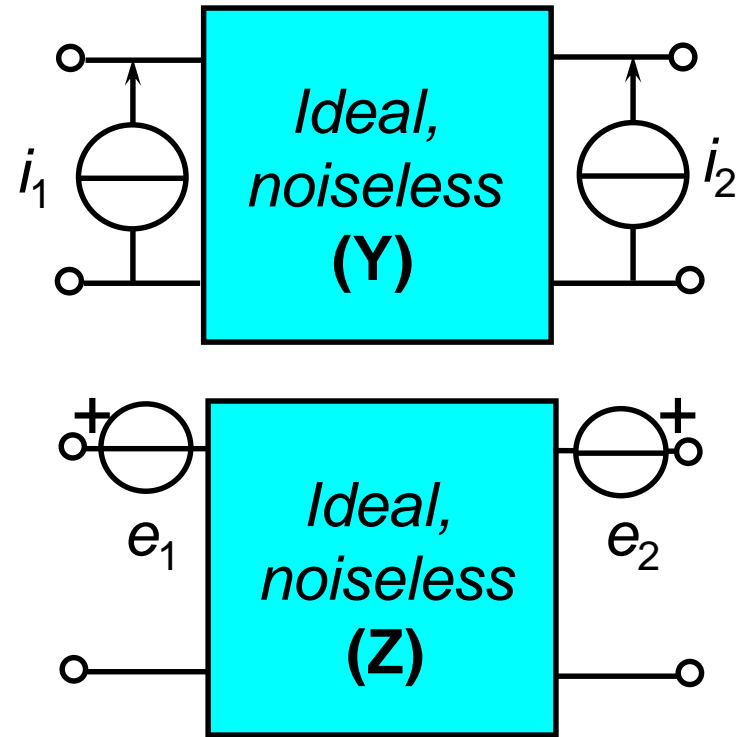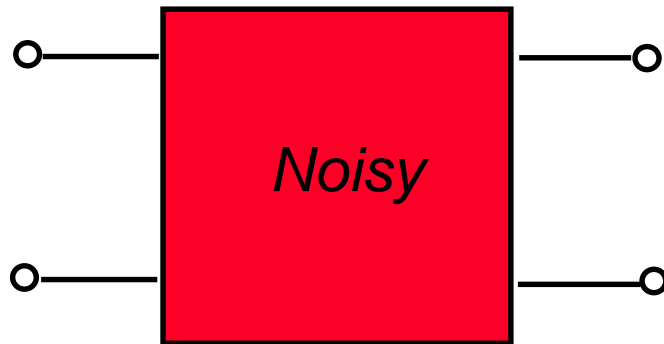

i_1, i_2
 e_1, e_2 random correlated sources



$$\begin{matrix} S_{i_1}(\omega), & S_{i_1 i_2}(\omega), & S_{i_2}(\omega) \\ S_{e_1}(\omega), & S_{e_1 e_2}(\omega), & S_{e_2}(\omega) \end{matrix}$$

Power spectra are **real**,
correlation spectra **complex**
→ 4 real numbers each
frequency

The cause of noise



- In a semiconductors noise is caused by *velocity fluctuations* and *population fluctuations* of carriers, e.g. in *n*-type conductor:

$$\underline{J}_n + \delta \underline{J}_n = q(n + \delta n)(\underline{v}_n + \delta \underline{v}_n) \approx \underbrace{qn\underline{v}_n}_{\text{population fluctuations}} + \underbrace{q\delta n\underline{v}_n}_{\text{velocity fluctuations}} + qn\delta \underline{v}_n$$

- Velocity fluctuations** exist in any conductor → thermal noise (diffusion noise out of equilibrium) → white
- Population fluctuations** (also connected with surfaces) are the main cause of 1/f and flicker noise → coloured
- Noise due to population fluctuations vanishes if no current (excess noise)
- In linear RF applications **white noise** dominates

Noise models: resistor (Nyquist law)



- In a resistor the power spectrum of (thermal) noise generators is given by **Nyquist law** (T temperature, k_B Boltzmann constant):

$$S_{v_n} = 4k_B T R \quad \text{V}^2/\text{Hz}, \quad S_{i_n} = 4k_B T G \quad \text{A}^2/\text{Hz}$$

- Noise power spectral density and rms values:**

$$p_n(f) = \frac{S_{v_n}(f)}{4R} = \frac{S_{i_n}(f)}{4G} = k_B T \quad \text{W/Hz}$$

$$v_{n,rms} = \sqrt{4k_B T R B}, \quad i_{n,rms} = \sqrt{4k_B T G B} \quad B \text{ system bandwidth}$$

- In a **passive one-port** one has the **generalized Nyquist law**:

$$S_{v_n} = 4k_B T \Re[Z(\omega)] \quad \text{V}^2/\text{Hz}, \quad S_{i_n} = 4k_B T \Re[Y(\omega)] \quad \text{A}^2/\text{Hz}$$

Semiconductor device noise models




- For passive networks the Nyquist law holds
- Junction devices (diodes, bipolar transistors) exhibit *shot noise*, e.g. for a diode the short-circuit noise current is:

$$S_i = 2q(I_D + 2I_0) \approx 2qI_D$$

- In FET devices noise is thermal or diffusion, but no exact theoretical model exists relating noise generators to small-signal parameters; however, compact noise FET models synthesize the noise generators with a low number of parameters (e.g. the PRC model)

FET noise model (PRC)

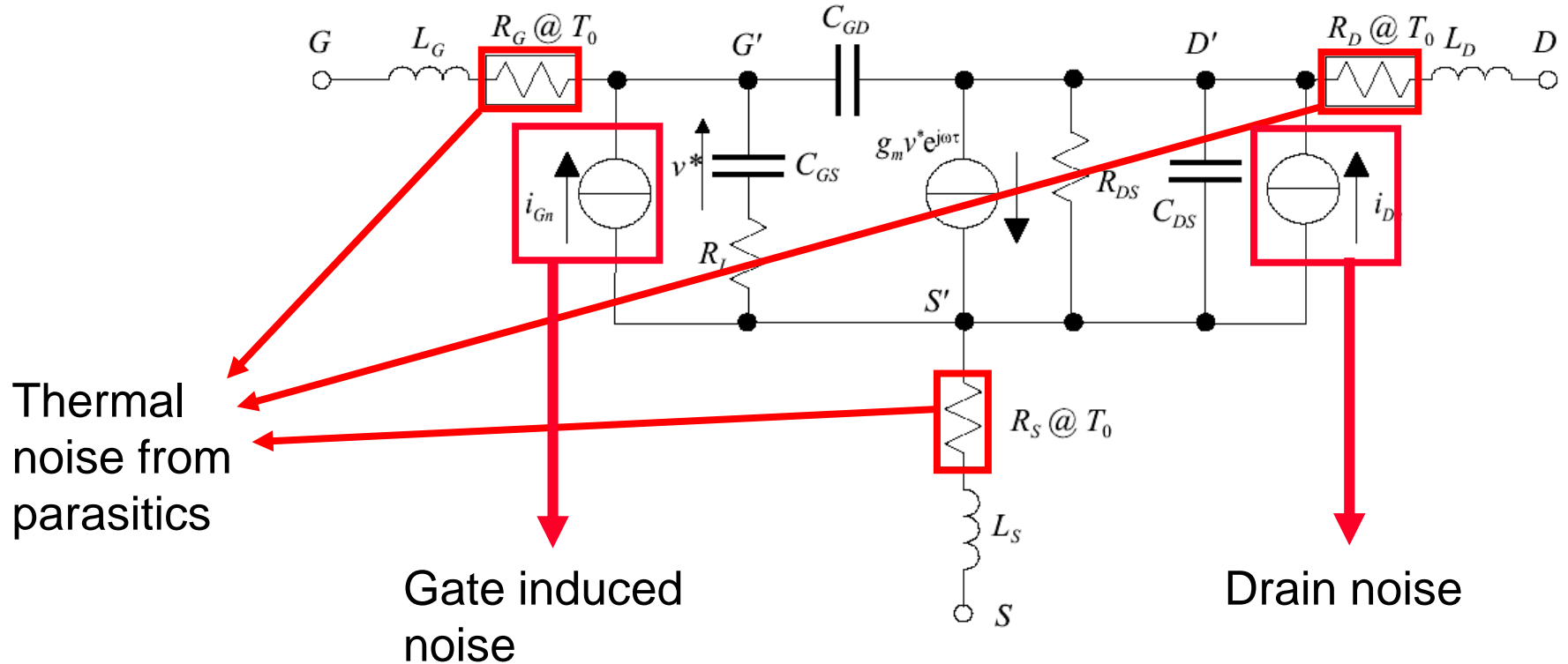


$$S_{i_{Dn}i_{Dn}} \approx 4k_B T_0 g_m P \quad \gamma (\sim 2/3)$$

$$S_{i_{Gn}i_{Gn}} \approx 4k_B T_0 \frac{\omega^2 C_{GS}^2}{g_m} R \quad \sim \beta, \delta \sim 0.12$$

$$S_{i_{Gn}i_{Dn}} \approx jC \sqrt{S_{i_{Dn}i_{Dn}} S_{i_{Gn}i_{Gn}}} \quad \text{Correlation}$$

Two-temperature noise model

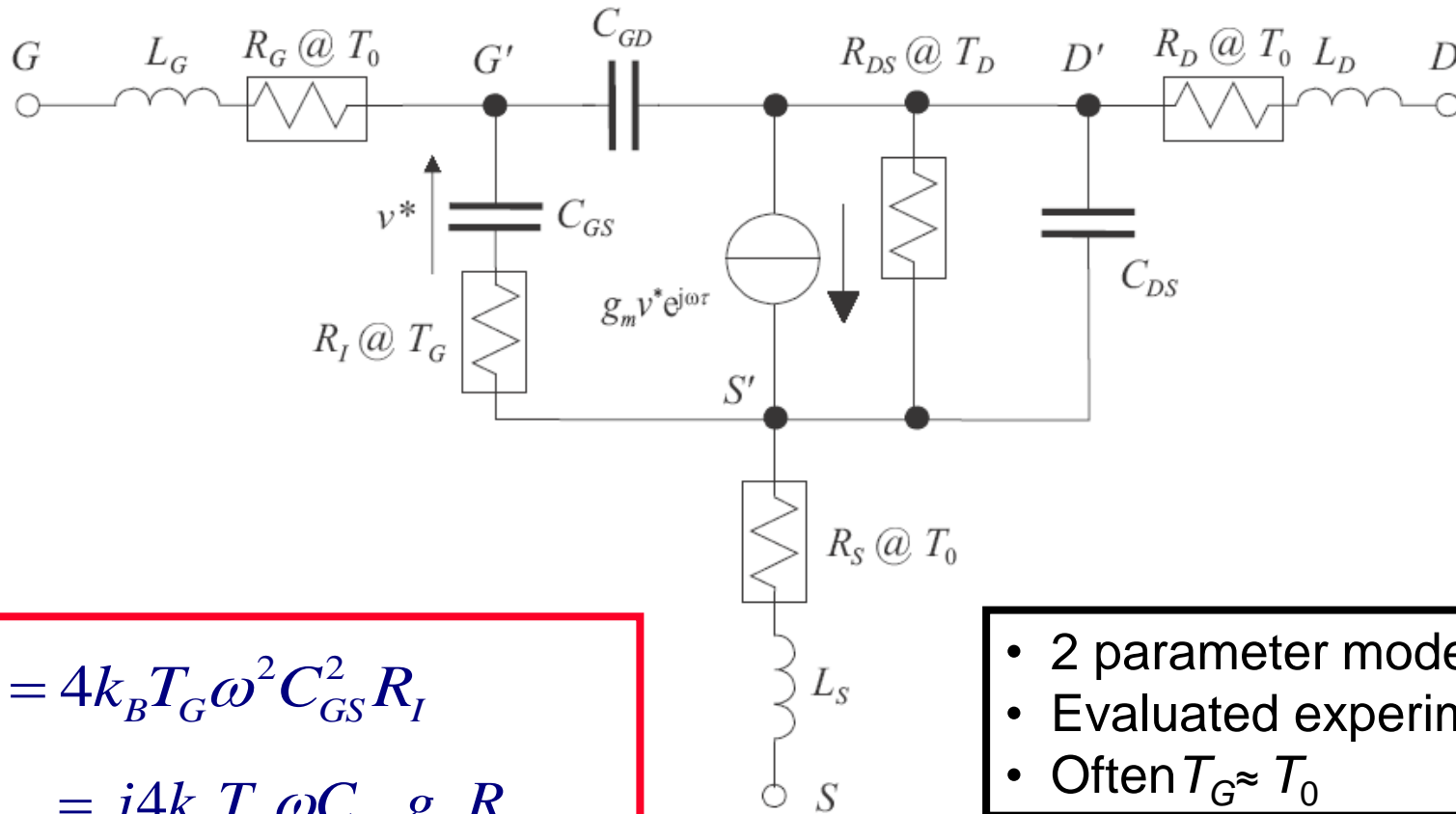

$$S_{i_{nG}} = 4k_B T_G \omega^2 C_{GS}^2 R_I$$

$$S_{i_{nG}, i_{nD}} = j4k_B T_G \omega C_{GS} g_m R_I$$

$$S_{i_{nD}} \approx 4k_B (T_G g_m^2 R_I + T_D G_{DS})$$

- 2 parameter model
- Evaluated experimentally
- Often $T_G \approx T_0$



1 parameter model

Solving circuits with noise generators - I



- Suppose a linear circuit includes **a set of (correlated and/or uncorrelated) noise generators**, how can we compute the total noise power on a load or the power spectrum of a given voltage or current?
- We have better work in the **frequency domain** associating to each process $x(t)$ its “Fourier transform” or “associated phasor” $X(\omega)$ and exploiting the symbolic definitions:

$$S_{xx}(\omega) = \overline{XX^*}, \quad S_{xy}(\omega) = \overline{XY^*} = S_{yx}^*(\omega)$$

- This definition is consistent with the *transformation rules* of the power spectrum of a random process through a linear system:

$$Y(\omega) = H(\omega)X(\omega); \quad S_{yy} = \overline{YY^*} = \overline{HXH^*X^*} = HH^* \overline{XX^*} = |H|^2 S_{xx}$$

Solving circuits with noise generators - II



- Procedure:
 - Associate to each random voltage or current generator a voltage or current phasor
 - The circuit is solved in frequency domain with the phasor technique
 - Power and correlation spectra are evaluated through the symbolic definitions as a function of the (supposedly known) power and correlation spectra of the noise sources
 - The average power exchanged are recovered by integrating the power densities on the system bandwidth (often to be specified separately → remember the presence of bandpass filters!)

Example



- Association random process & phasor $e_{n2} \leftrightarrow E_{n2}$ e $i_{n1} \leftrightarrow I_{n1}$, $v_L \leftrightarrow V_L$;
- The power spectra $S_{e_{n2}}$, $S_{i_{n1}}$, $S_{e_{n2}i_{n1}}$ are known
- From the circuit:


$$V_L = \frac{(I_{n1}Z_1 + E_{n2})Z_L}{Z_1 + Z_L} \rightarrow S_{v_L} = \overline{V_L V_L^*} = \frac{\overline{(I_{n1}Z_1 + E_{n2})(I_{n1}Z_1 + E_{n2})^*} |Z_L|^2}{|Z_1 + Z_L|^2}$$

- i.e.:

$$S_{v_L} = \overline{V_L V_L^*} = \frac{\left(\overline{I_{n1}I_{n1}^*} |Z_1|^2 + \overline{E_{n2}E_{n2}^*} + Z_1 \overline{I_{n1}E_{n2}^*} + Z_1^* \overline{E_{n2}I_{n1}^*} \right) |Z_L|^2}{|Z_1 + Z_L|^2} =$$

$$= \frac{|Z_L|^2}{|Z_1 + Z_L|^2} \left(|Z_1|^2 S_{i_{n1}} + S_{e_{n2}} + Z_1 S_{e_{n2}i_{n1}}^* + Z_1^* S_{e_{n2}i_{n1}} \right)$$

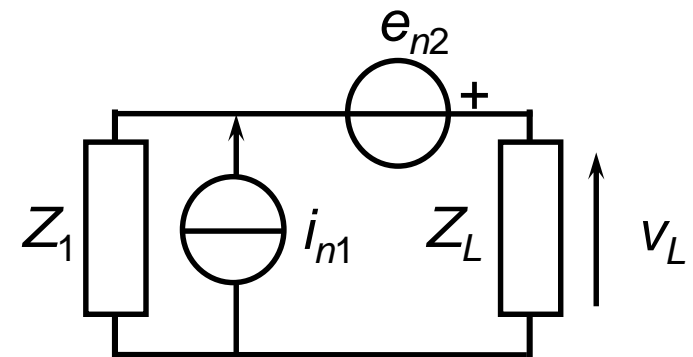- To evaluate the total noise power one must integrate on the system bandwidth



The two-port noise figure



- From a system standpoint a commonly used amplifier noise figure of merit is the *noise figure* NF:

$$\text{NF} = \frac{P_{nav,L}}{p'_{nav,L}} = \frac{\text{Noise available power spectral density on load}}{\text{Noise available power spectral density on load with **noiseless** two-port}}$$

- In the standard NF definition the input noise is thermal noise at T_0 (conventionally ~ 290 K, at that temperature $kT=25$ meV)
- This definition as the ratio of power spectral densities is called the **spot noise figure**; we can also define NF considering power and noise on a certain system bandwidth:

$$\text{NF} = \frac{\int_{f_0-B/2}^{f_0+B/2} P_{nav,L}(f) df}{\int_{f_0-B/2}^{f_0+B/2} p'_{nav,L}(f) df} = \frac{P_{nav,L}}{P'_{nav,L}}$$

System definition of noise figure




- The noise figure can be also shown to admit the alternative system definition involving the input and output **signal over noise ratios**:

$$\text{NF} = \frac{(S / N)_{in}}{(S / N)_L}$$

- In fact:

$$\begin{aligned} \text{NF} &= \frac{P_{nav,L}}{P'_{nav,L}} \equiv \frac{N_L}{N_{in} G_{av}} = \frac{N_L S_{in}}{N_{in} G_{av} S_{in}} = \\ &= \frac{N_L S_{in}}{N_{in} S_L} = \frac{(S / N)_{in}}{(S / N)_L} \end{aligned}$$

Spot noise figure in terms of (S/N)

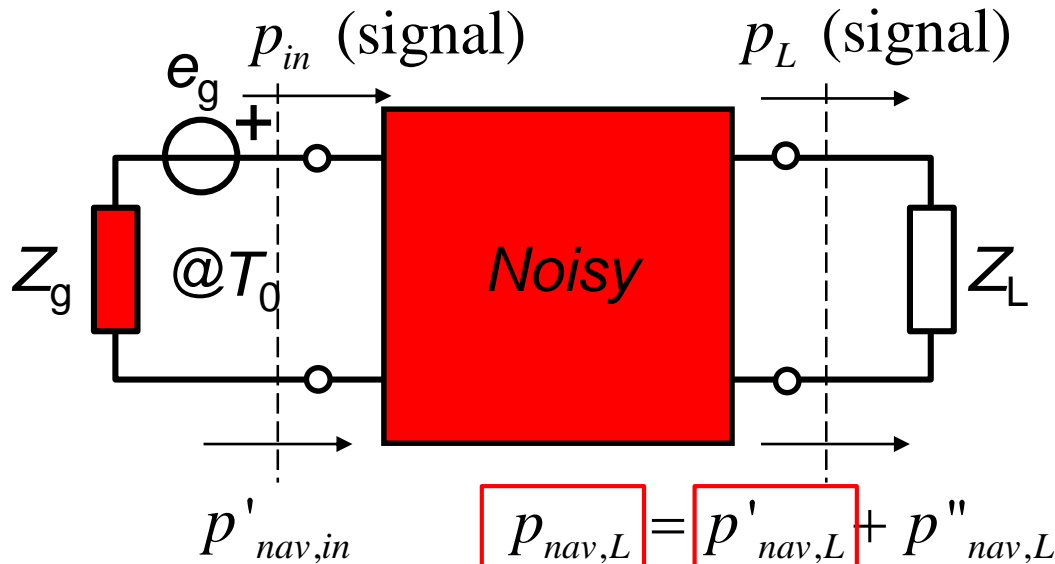

- All powers (signal and noise) are available powers
- Definition of the output available noise power due to generator:

$$p'_{nav,L} = G_{av} p'_{nav,in}$$

Total output noise available power

Output noise available power generated from generator noise available power

$$\begin{aligned} NF &= \frac{p_{nav,L}}{p'_{nav,L}} = \frac{p_{nav,L}}{p'_{nav,in} G_{av}} = \frac{p_{nav,L} p_{in}}{p'_{nav,in} G_{av} p_{in}} = \\ &= \frac{p_{nav,L} p_{in}}{p'_{nav,in} p_L} = \frac{p_{in}}{p'_{nav,in}} \times \frac{p_{nav,L}}{p_L} = \frac{(S/N)_{in}}{(S/N)_L} \end{aligned}$$

Noise temperature



- In a noiseless two-port $NF=1$ (e.g.: reactive two-port)
- If $p''_{nav,L}$ is the noise available power density on the load because of the effect of the noisy two port only:

$$NF = 1 + \frac{p''_{nav,L}}{p'_{nav,L}}$$



$$NF = 1 + \frac{G_{av} p''_{nav,in}}{G_{av} p'_{nav,in}} = 1 + \frac{p''_{nav,in}}{k_B T_0}$$

- Supposing that the input referred noise available power density $p''_{nav,in}$ be expressed as: $p''_{nav,in} = k_B T_n$


$$T_n = T_0 (NF - 1)$$

Noise temperature of two-port

Noise temperature




Noisy two-port and input

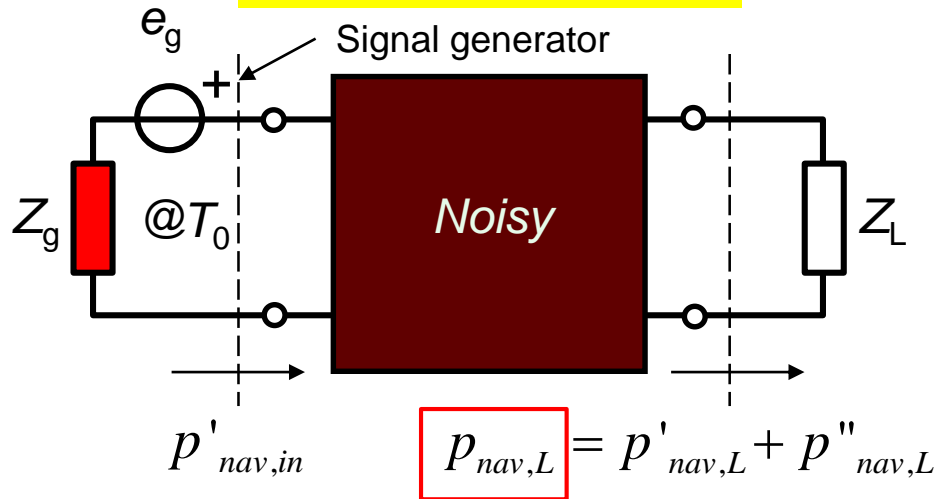


$$\begin{aligned} NF &= \frac{p_{nav,L}}{p'_{nav,L}} = \frac{p'_{nav,L} + p''_{nav,L}}{p'_{nav,L}} = \\ &= 1 + \frac{p''_{nav,L}}{p'_{nav,L}} = 1 + \frac{p''_{nav,L} / G_{av}}{p'_{nav,L} / G_{av}} = \\ &= 1 + \frac{p''_{nav,in}}{p'_{nav,in}} = 1 + \frac{k_B T_n}{k_B T_0} = 1 + \frac{T_n}{T_0} \end{aligned}$$



Noise referred to input

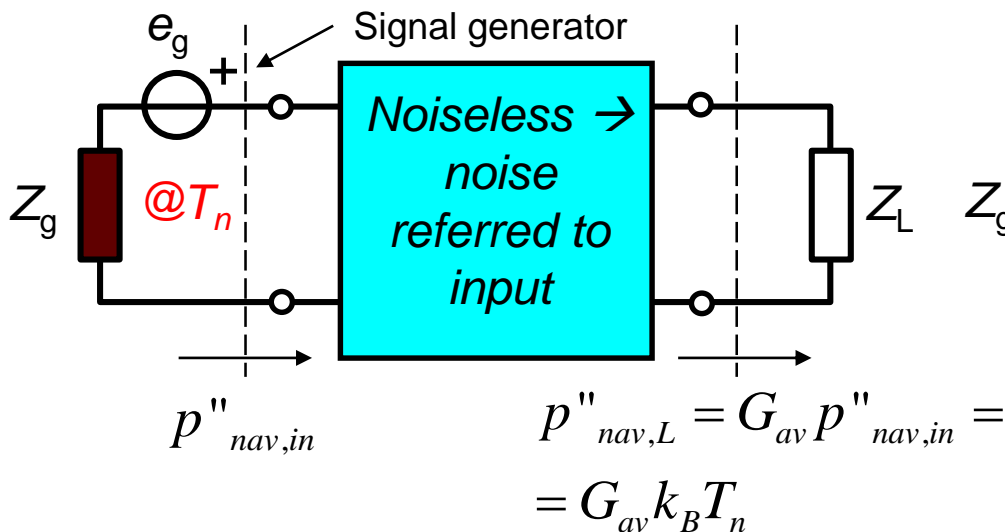

Noiseless two-port

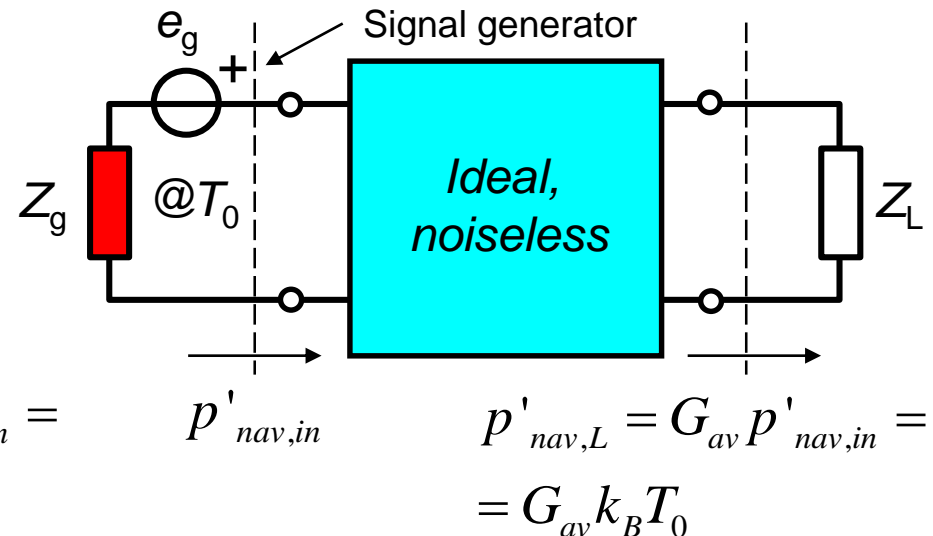





Noise figure in terms of I/V spectra - I

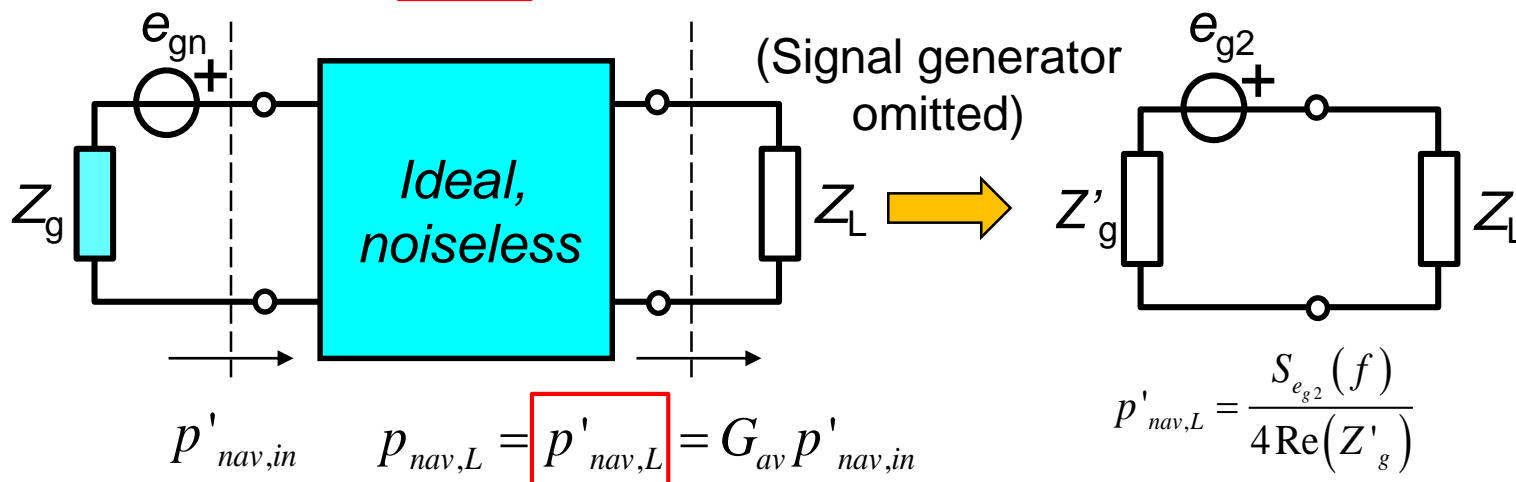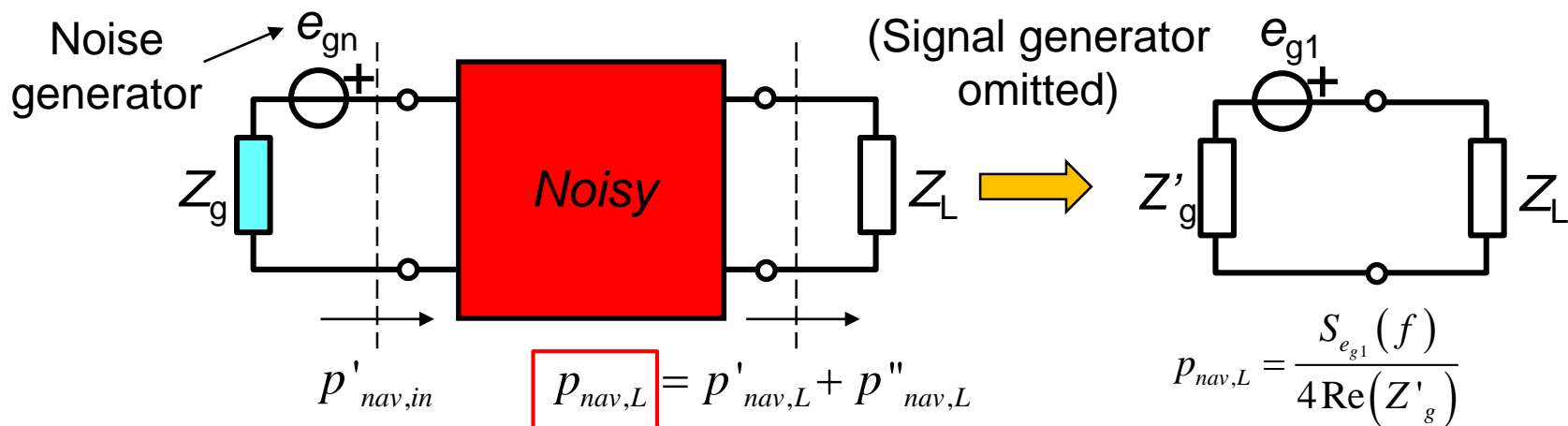

$$NF = \frac{p_{nav,L}}{p'_{nav,L}} = \frac{S_{e_{g1}}(f) / 4\text{Re}(Z'_g)}{S_{e_{g2}}(f) / 4\text{Re}(Z'_g)} = \frac{S_{e_{g1}}(f)}{S_{e_{g2}}(f)}$$

Ratio of open-circuit
output voltage spectra

Noise figure in terms of I/V spectra - I

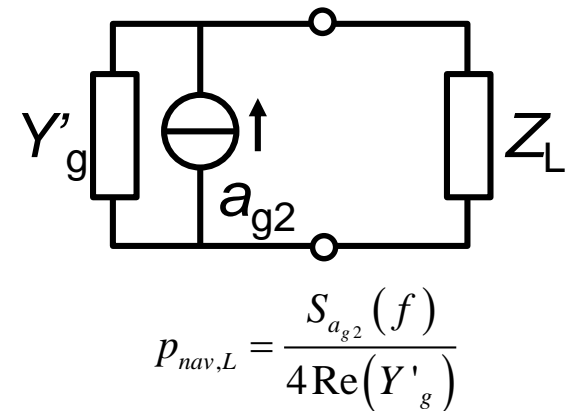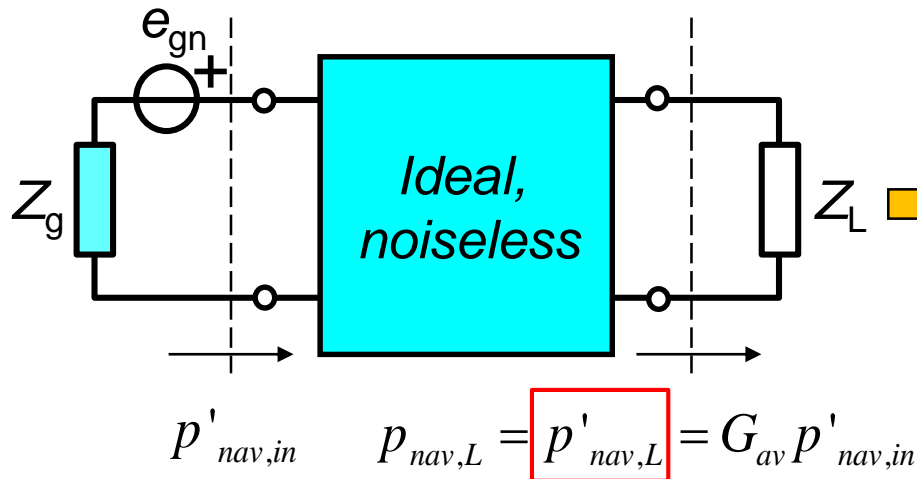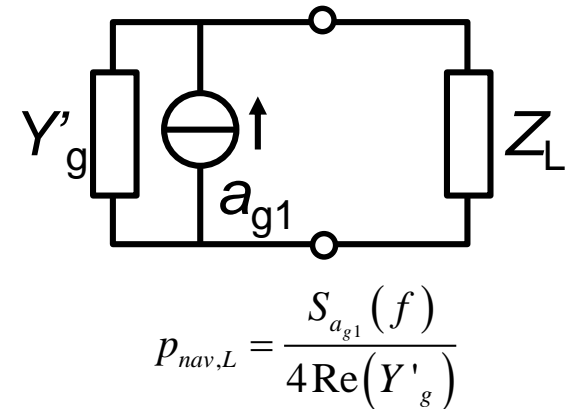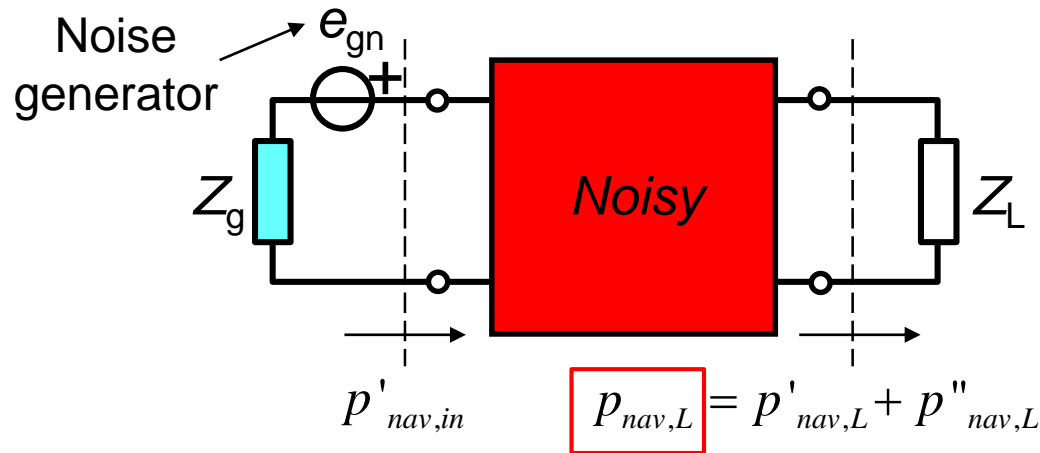

$$\text{NF} = \frac{p_{nav,L}}{p'_{nav,L}} = \frac{S_{a_{g1}}(f) / 4\text{Re}(Y'_g)}{S_{a_{g2}}(f) / 4\text{Re}(Y'_g)} = \frac{S_{a_{g1}}(f)}{S_{a_{g2}}(f)}$$


Ratio of short-circuit output current spectra

Looking for the minimum noise figure



- The noise figure of a two-port is a ratio of available powers at port 2 \rightarrow it only depends on the two port SS and noise parameters and on the **source impedance**
- It can be shown that an **optimum source impedance** exists which **minimizes the noise figure** (but of course does not maximize the available power gain!)
- The sensitivity of the NF with respect to the minimum is a further noise parameter (see later)
- A simplified example of the minimization process is presented in the next slides

Example of minimum NF - I

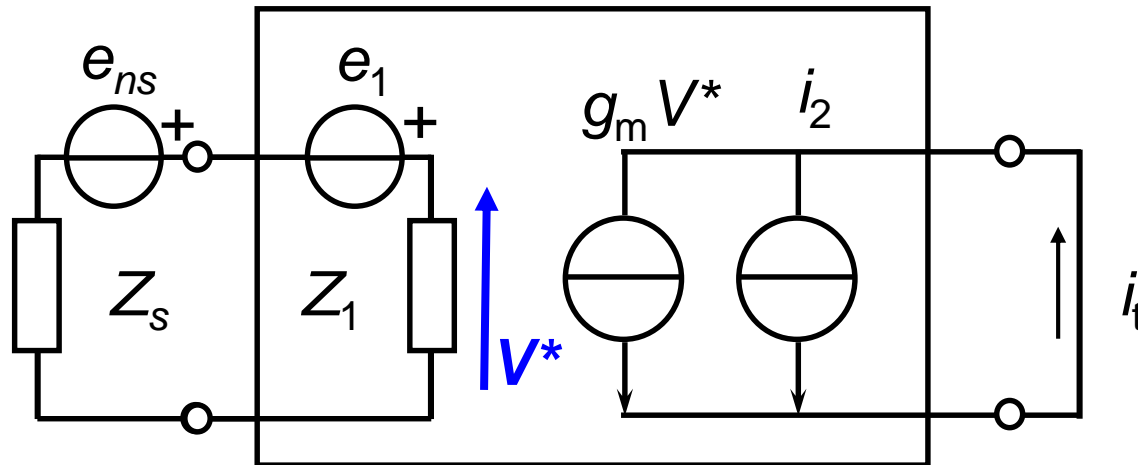

All noise sources are uncorrelated

$$I_t = g_m v^* + I_2 = (E_{ns} + E_1) \frac{g_m Z_1}{Z_s + Z_1} + I_2$$

$$S_{i_t} = \overline{I_t I_t^*} = (\overline{E_{ns} E_{ns}^*} + \overline{E_1 E_1^*}) \frac{g_m^2 |Z_1|^2}{|Z_s + Z_1|^2} + \overline{I_2 I_2^*}$$

$$\overline{E_{ns} E_{ns}^*} = 4k_B T_0 R_s$$

$$\overline{E_1 E_1^*} = 4k_B T_0 R_n$$

$$\overline{I_2 I_2^*} = 4k_B T_0 G_n$$

Nyquist for resistor, pseudo-Nyquist for 2-port sources

Example of minimum NF - II



NF as the ratio
of short-circuit
current power
spectra

$$\begin{aligned} \text{NF} &= \frac{(4k_B T_0 R_s + 4k_B T_0 R_n) \frac{g_m^2 |Z_1|^2}{|Z_s + Z_1|^2} + 4k_B T_0 G_n}{4k_B T_0 R_s \frac{g_m^2 |Z_1|^2}{|Z_s + Z_1|^2}} = \\ &= 1 + \frac{R_n}{R_s} + \frac{|Z_s + Z_1|^2}{g_m^2 |Z_1|^2} \frac{G_n}{R_s} = \\ &= 1 + \frac{R_n}{R_s} + \frac{(R_s + R_1)^2 + (X_s + X_1)^2}{g_m^2 |Z_1|^2} \frac{G_n}{R_s} \end{aligned}$$

optimum source reactance

$$X_{so} = -X_1$$

Resulting NF:

$$\begin{aligned} \text{NF} &= 1 + \frac{R_n}{R_s} + \frac{(R_s + R_1)^2}{g_m^2 |Z_1|^2} \frac{G_n}{R_s} = \\ &= 1 + \frac{R_n}{R_s} + \frac{R_1^2 G_n}{R_s g_m^2 |Z_1|^2} + \frac{2R_1 G_n}{g_m^2 |Z_1|^2} + \frac{G_n R_s}{g_m^2 |Z_1|^2} \end{aligned}$$

Example of minimum NF - III



Function:

$$NF = 1 + \frac{a}{R_s} + b + cR_s$$

$$\frac{dNF}{dR_s} = -\frac{a}{R_s^2} + c = 0 \rightarrow R_{so} = \sqrt{\frac{a}{c}}$$

$$NF_{\min} = 1 + 2\sqrt{ac} + b$$

Introducing values:




$$NF_{\min} = 1 + 2\sqrt{\left(R_n + \frac{R_1^2 G_n}{g_m^2 |Z_1|^2}\right) \frac{G_n}{g_m^2 |Z_1|^2}} + \frac{2R_1 G_n}{g_m^2 |Z_1|^2}$$
$$R_{so} = \sqrt{\frac{R_n + \frac{R_1^2 G_n}{g_m^2 |Z_1|^2}}{\frac{G_n}{g_m^2 |Z_1|^2}}} = \sqrt{R_1^2 + \frac{g_m^2 |Z_1|^2 R_n}{G_n}}$$

- if the device input is capacitive (FETs) the minimum noise figure increases with f , if it has a resistive component (BJT) with f^2

Evaluating and minimizing NF: how to do it



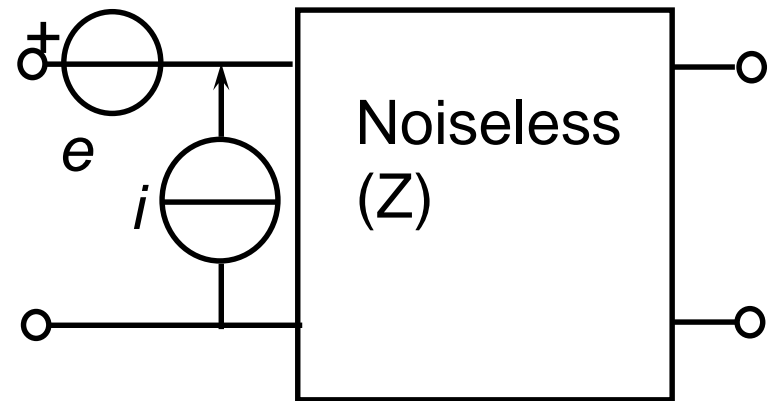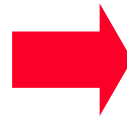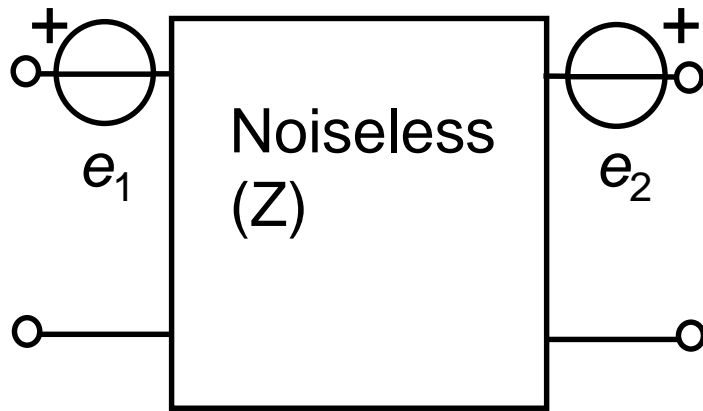- Referring noise generators to the input:



$$S_{e_1 e_1}(\omega), S_{e_1 e_2}(\omega), S_{e_2 e_2}(\omega)$$

$$S_{ee}(\omega), S_{ei}(\omega), S_{ii}(\omega)$$


- By imposing the equivalence of the two representations we obtain the correlation matrix of the two generators i and e .

Representation with input uncorrelated generators



- It is expedient to introduce instead of e and i (correlated) a voltage generator uncorrelated from i
- The equivalence is obtained by imposing that the short-circuit current and open circuit-voltage of the two sets is the same
- Imposing that e_{nc} and i be uncorrelated we obtain:

Z_c correlation impedance

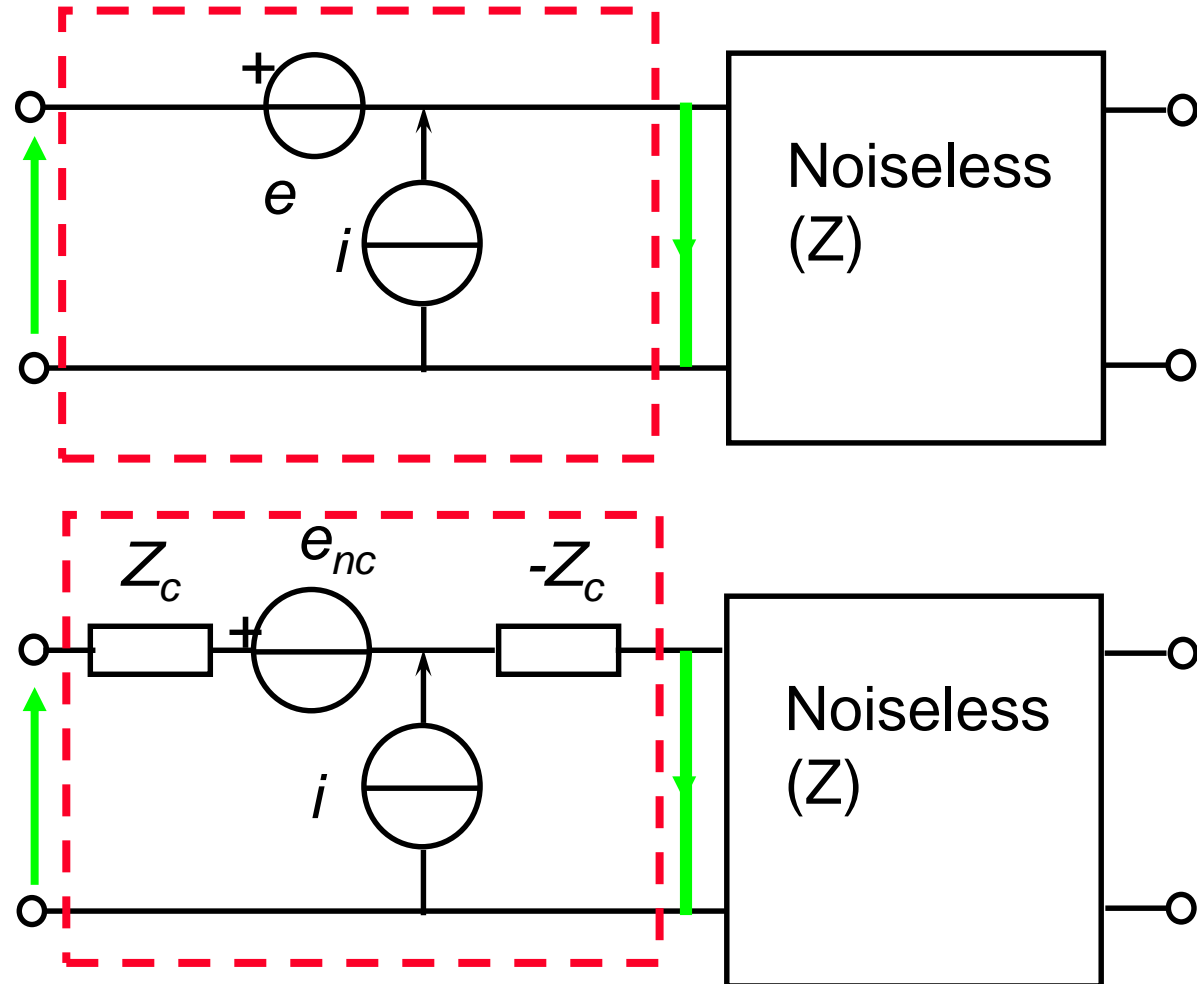

Power spectra of uncorrelated generators



- The power spectra of the two uncorrelated generators can be for brevity expressed introducing the **series noise resistance and conductance**; the info on correlation is in Z_c

$$S_{e_{nc}, e_{nc}} = 4k_B T_0 r_n$$

$$S_{i,i} = 4k_B T_0 g_n$$

$$Z_c$$


- Starting from a parallel (Norton) two-port representation we obtain a dual circuit with uncorrelated generators having as parameters the **parallel noise resistance and conductance and the correlation admittance**:

$$R_n, \quad G_n, \quad Y_c \neq 1/Z_c$$

Noise figure



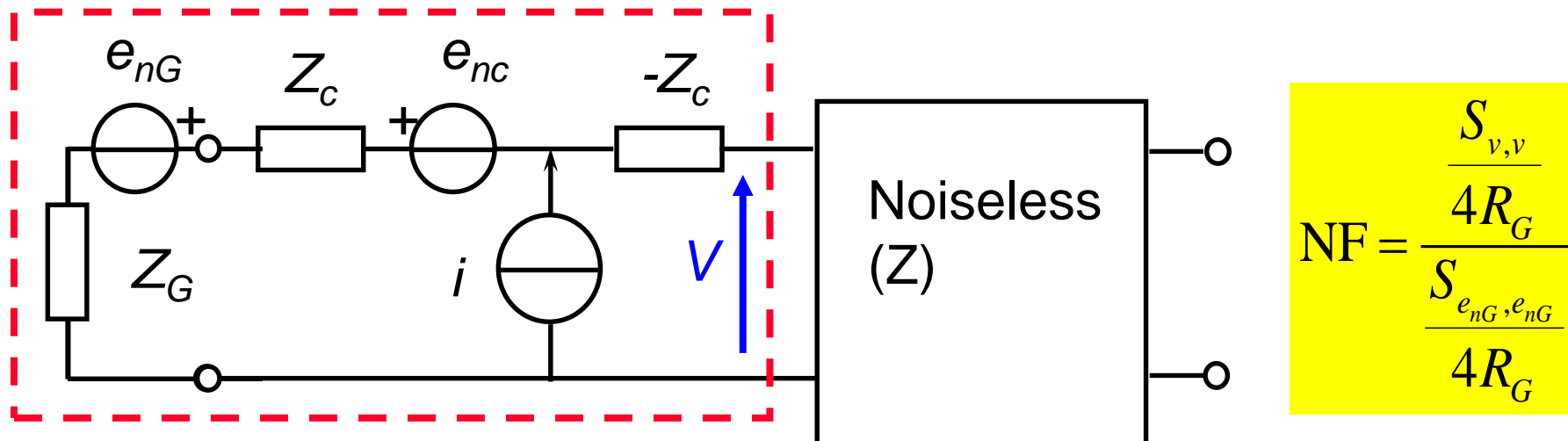- Starting from the input referred generators we find the noise figure as the ratio of the input open-circuit voltage power spectra: full/due to generator noise only:



$$NF = \frac{S_{e_{nG}, e_{nG}} + S_{e_{nc}, e_{nc}} + S_i |Z_c + Z_G|^2}{S_{e_{nG}, e_{nG}}}$$



$$NF = 1 + \frac{r_n}{R_G} + \frac{g_n}{R_G} |Z_c + Z_G|^2$$

Minimum noise figure & Z_{Go}



- NF does not depend on load
- Minimizing NF vs. R_G and X_G we generally find the *optimum source impedance* Z_{Go}
- The minimum noise figure results:

$$R_{Go} = \sqrt{\frac{r_n}{g_n} + R_c^2}$$

$$X_{Go} = -X_c$$

$$NF_{min} = 1 + 2g_n R_c + 2g_n \sqrt{\frac{r_n}{g_n} + R_c^2}$$


System characterization of two-port



- The two-port noise is therefore characterized by four real parameters, which can be also evaluated directly through measurements:
 - **Minimum noise figure** NF_{\min}
 - **Series noise conductance** g_n
 - **Optimum source impedance** $Z_{\text{sopt}} = R_{\text{sopt}} + jX_{\text{sopt}}$
- Meaning of series noise conductance: sensitivity of NF with respect to minimum:

$$NF = NF_{\min} + \frac{4g_n}{R_G} \frac{|Z_G - Z_{Go}|^2}{|Z_{Go}|^2}$$

FET noise parameters with PRC model

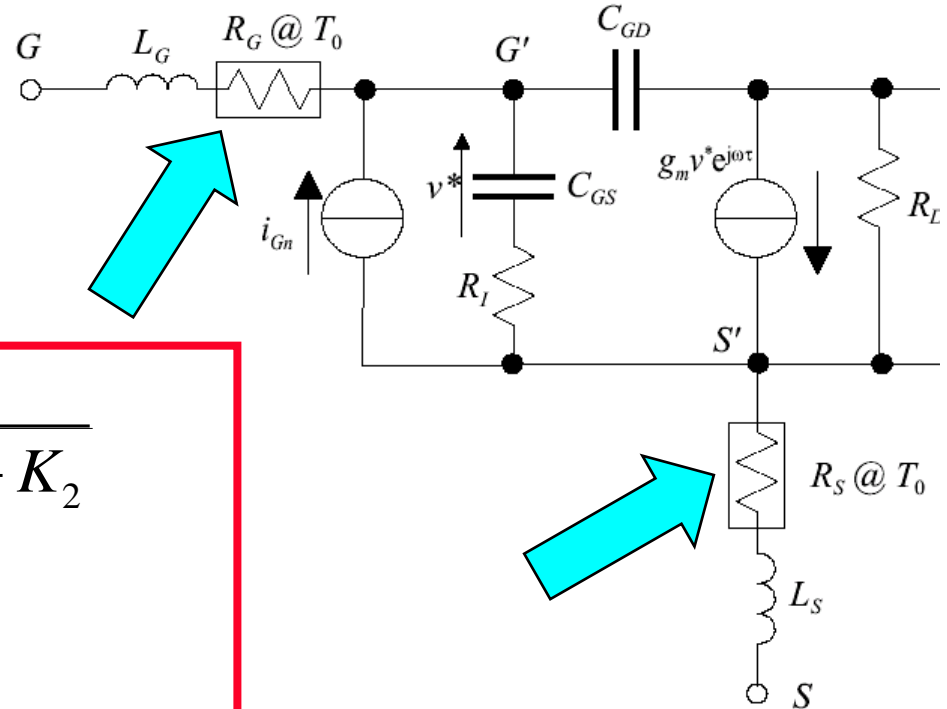

$$NF_{\min} \approx 1 + 2K_1 \frac{f}{f_T} \sqrt{g_m (R_G + R_S) + K_2}$$

$$g_n \approx g_m K_1 \left(\frac{f}{f_T} \right)^2$$

$$Z_{So} = \frac{\sqrt{g_m (R_G + R_S) + K_2}}{\omega C_{GS} K_1} + j \frac{P - C \sqrt{RP}}{\omega C_{GS} K_1^2}$$

$$K_1 = \sqrt{P + R - 2C \sqrt{PR}}$$

$$K_2 = PR (1 - C^2) / K_1^2$$

$$f_T = g_m / 2\pi C_{GS}$$

Fukui formula



- If the contribution of the R_G and R_S parasitic resistances is dominant, the noise figure can be approximated as (**Fukui formula**)

$$NF_{\min} \approx 1 + 2K_1 \frac{f}{f_T} \sqrt{g_m (R_G + R_S)} = 1 + 2KL_G f \sqrt{g_m (R_G + R_S)}$$

- For a HEMT $K \sim 0.1$, for a MESFET ~ 0.3 same gate length
- NF deteriorates with frequency and with resistive parasitics, improves by increasing the cutoff frequency

Frequency behaviour of noise figure and associate gain




One-temperature model, neglecting gate noise:

$$p_{n,L} = k_B T_D + G_{ass} k_B T_0$$

$$p'_{n,L} = G_{ass} k_B T_0$$

$$NF_{min} = 1 + \frac{T_D}{G_{ass} T_0}$$

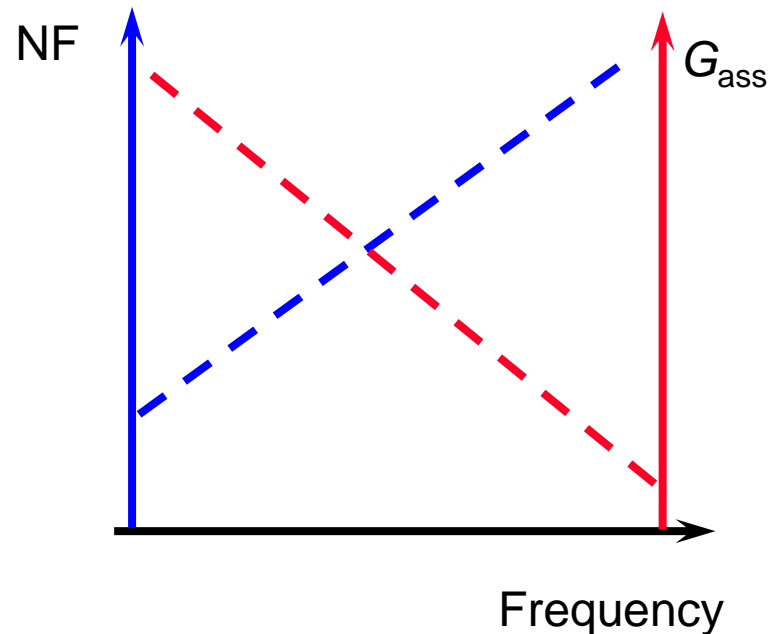
$$G_{ass} \cdot (NF_{min} - 1) \approx \frac{T_D}{T_0}$$




Constant noise circles and noise-gain tradeoff



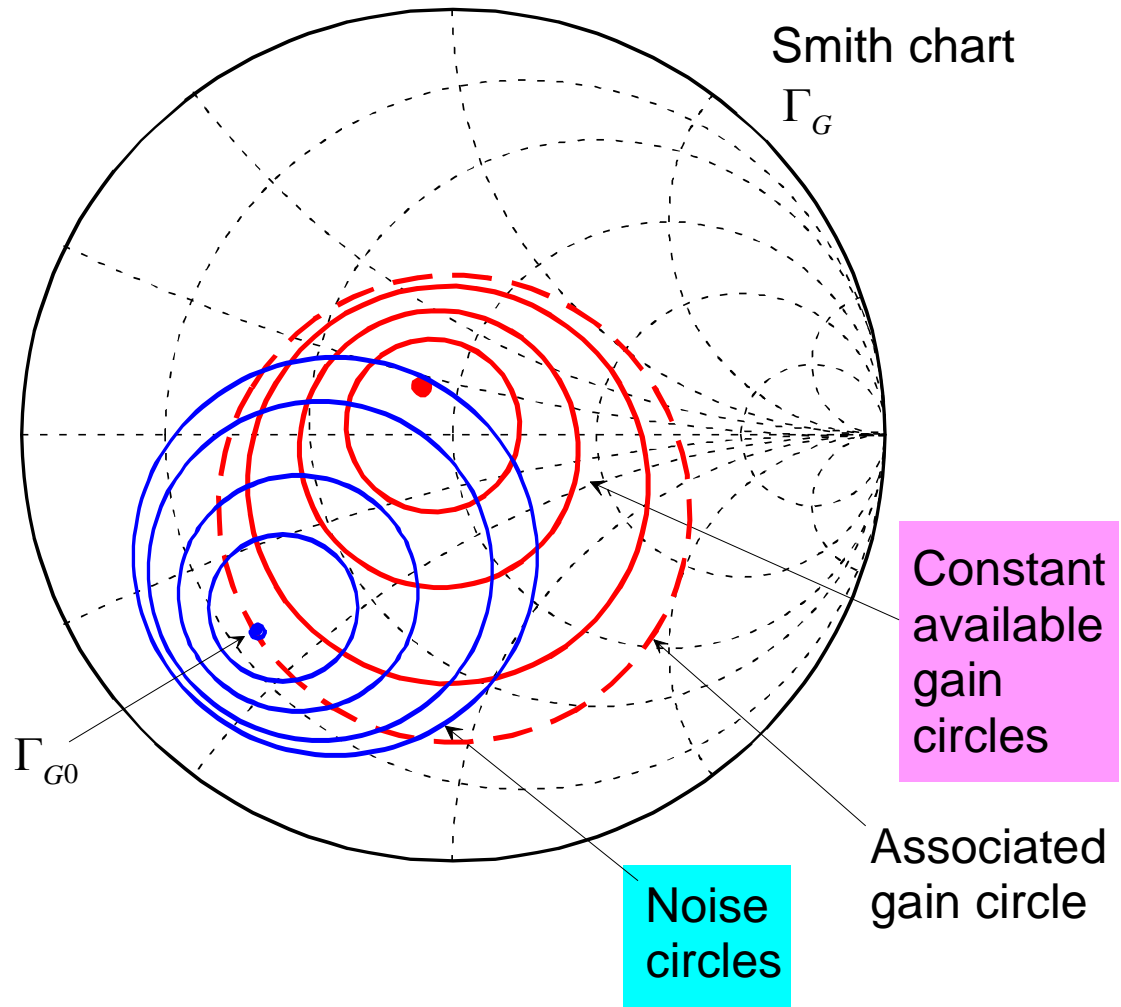- On the Γ_G Smith chart constant NF curves are again circles
- Constant noise circles and constant available gain circles allow for a tradeoff between gain and noise




Low-noise active device bias

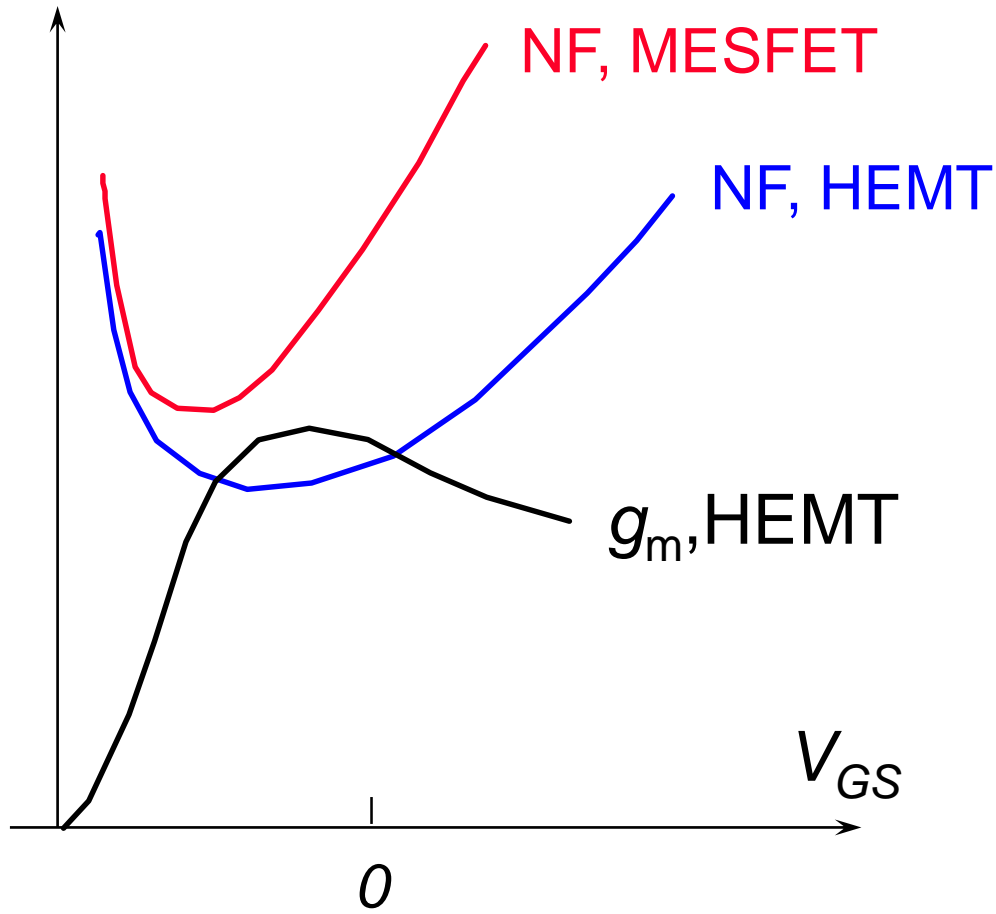

- Typically the optimum low-noise bias corresponds to low to average currents and low drain-to-source voltage
- Better compromise in some devices (e.g. HEMTs) with respect to gain

Noise in a receiver chain

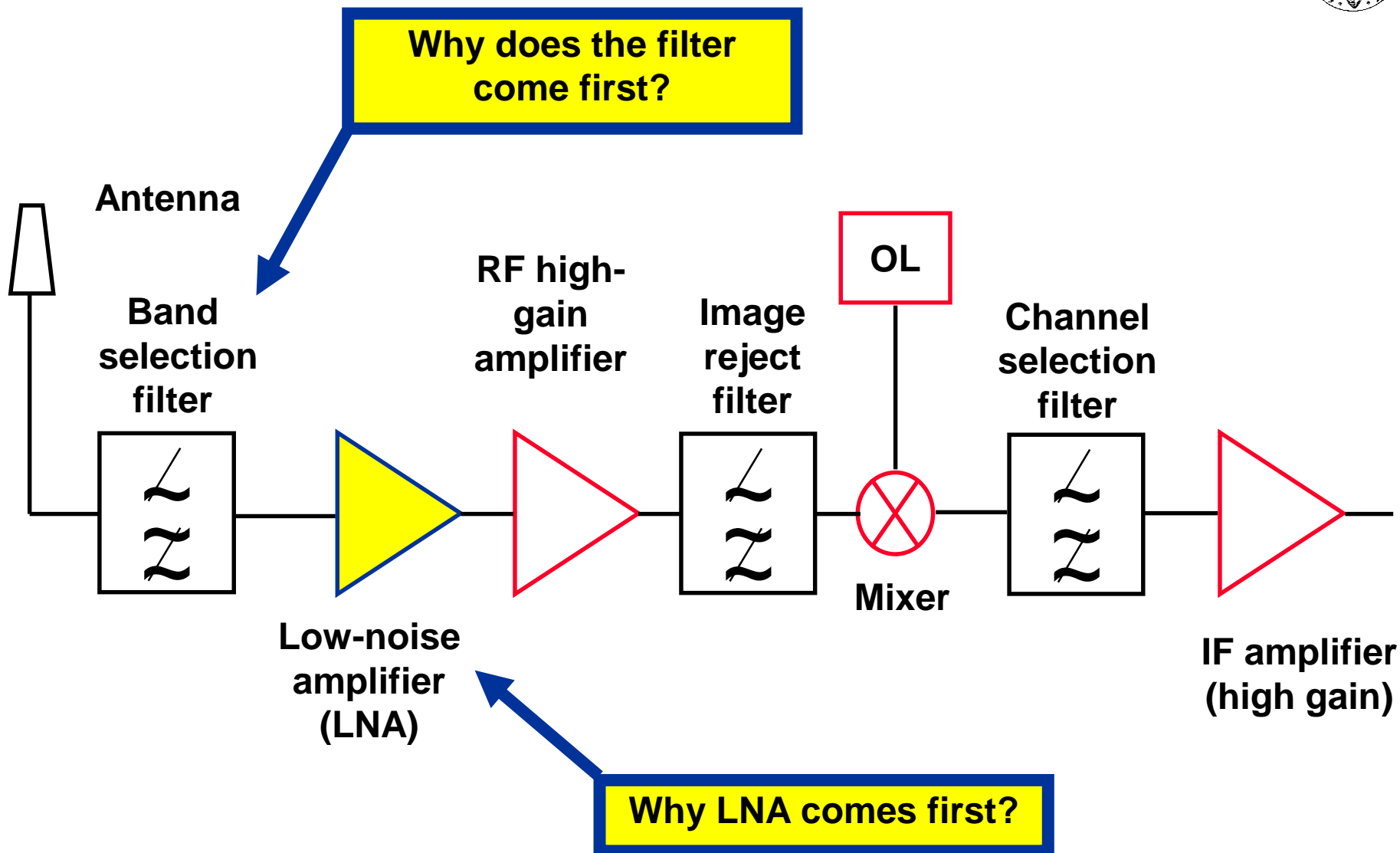

Noise in cascaded two-ports - The Friis formula



$$NF_{\text{tot}} = 1 + (NF_1 - 1) + \frac{(NF_2 - 1)}{G_1} + \frac{(NF_3 - 1)}{G_1 G_2} + \frac{(NF_4 - 1)}{G_1 G_2 G_3} + \dots$$

- From the Friis formula, the first stage should be low noise, high gain
- Lossy stages in the first position are usually unavoidable but should be minimized (for a lossy two-port $NF=L$ where L is the loss > 1 – why? See next slide)
- A passband filter before the LNA is indispensable because it reduces the noise bandwidth of the amplifier (and also rejects spurious interferers from outside the system bandwidth)

The noise figure of a lossy two-port




$$\text{NF} = \frac{p_{nav,L}}{p'_{nav,L}} = \frac{k_B T_0}{G_{av} p'_{nav,in}} = \frac{k_B T_0}{G_{av} k_B T_0} = L_{av}$$

$$L_{av} = \frac{1}{G_{av}} \text{ available power loss of the two port}$$

$$p_{nav,L} = k_B T_0 \text{ since the output behaves as a resistor}$$

Proof of Friis formula

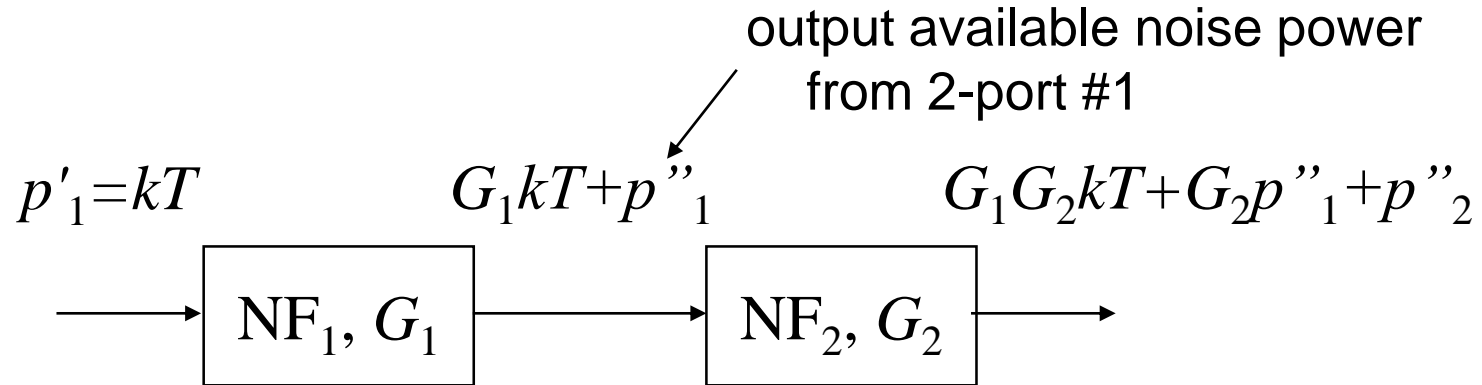

$$NF_1 = 1 + \frac{p''_1}{G_1 kT} \rightarrow p''_1 = G_1 kT (NF_1 - 1)$$

$$NF_2 = 1 + \frac{p''_2}{G_2 kT} \rightarrow p''_2 = G_2 kT (NF_2 - 1)$$

$$NF_{\text{tot}} = \frac{G_1 G_2 kT + G_2 p''_1 + p''_2}{G_1 G_2 kT} = 1 + \frac{p''_1}{G_1 kT} + \frac{p''_2}{G_1 G_2 kT} =$$

$$= 1 + \frac{G_1 kT (NF_1 - 1)}{G_1 kT} + \frac{G_2 kT (NF_2 - 1)}{G_1 G_2 kT} \rightarrow NF_{\text{tot}} = 1 + (NF_1 - 1) + \frac{NF_2 - 1}{G_1}$$


Low noise design and Associated gain




- In LNA design the *source impedance* is the optimum impedance, the *load is power matched*
- The optimum source impedance for noise does not generally yield input power match and therefore the corresponding available power gain (“**associate gain**”) is lower than the MAG

- **Power match** at input: $Z_g = Z_i^*$
- **Power match** at output
- Gain = MAG

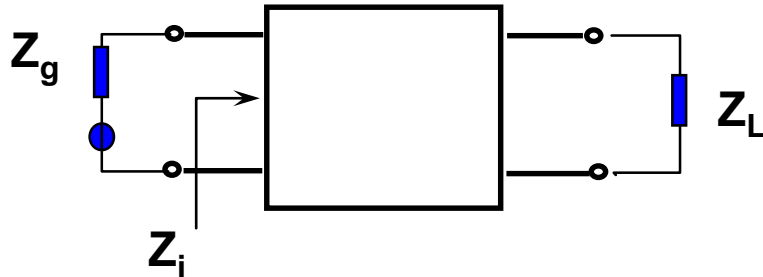- **Noise match** at input: $Z_g = Z_{opt}$
- **Power match** at output
- Associate gain < MAG



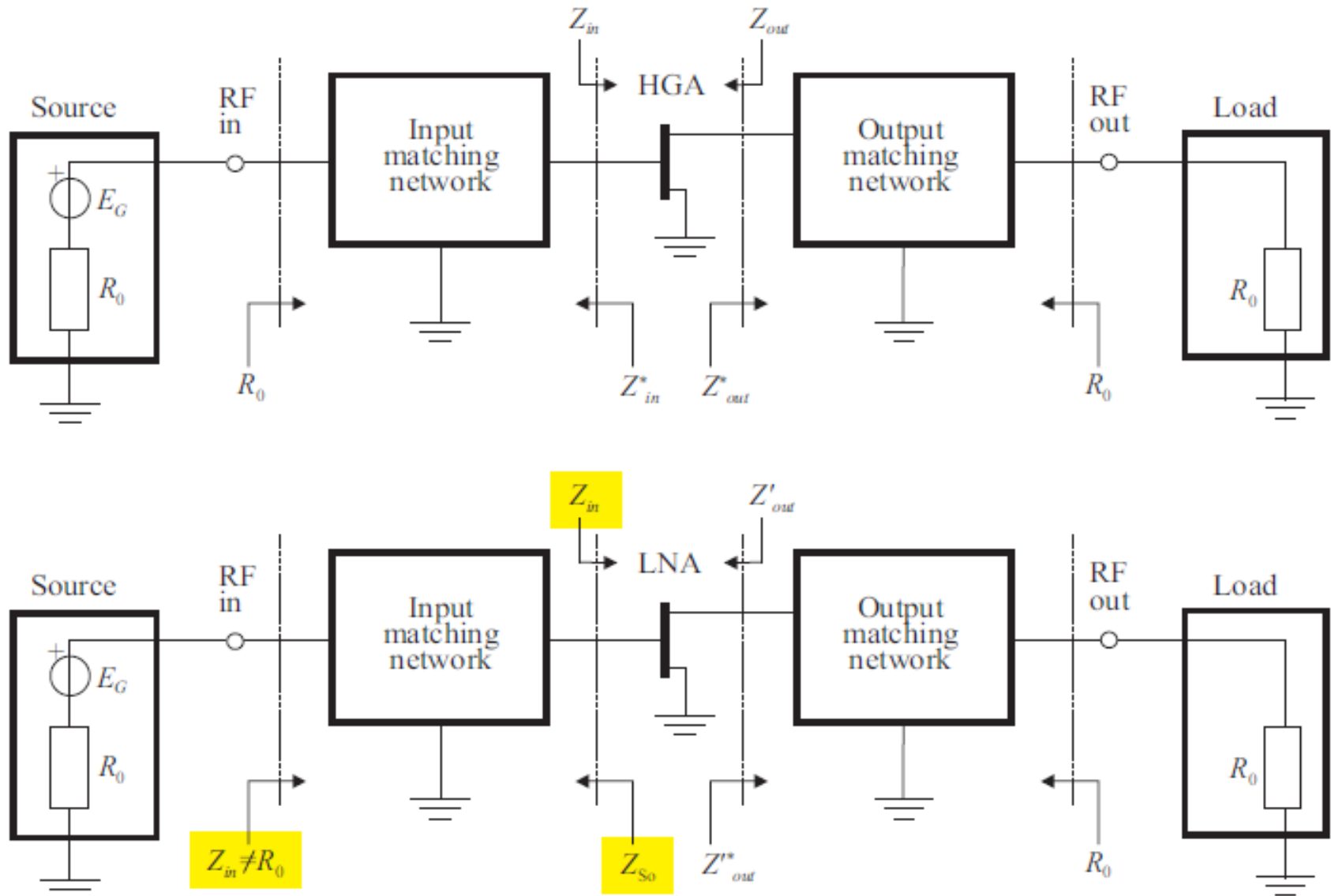Low-noise design does not grant input matching!!



The traditional low-noise design strategy



- In traditional low-noise design we have $NF = NF_{\min}$
- **1st step**: choice of device and device optimum working point
- **2nd step**: input matching network so as to obtain from the generator impedance (e.g. 50 Ω) the optimum noise impedance Z_{G_0}
- **3rd step**: output matching network implementing output power match
- The amplifier has minimum NF, associated gain
- In many cases the classical strategy is unsatisfactory because input mismatching is unacceptable \rightarrow alternative input matching strategies allow for improvements in the input match without overly deteriorating NF \rightarrow particularly popular in RF

Popular FET LNA topologies




- Common gate (base) stage → input matching through bias or periphery design, high noise figure
- Inductive source (emitter) feedback → noise figure marginally worse than the minimum, reasonable gain, narrowband input matching; can also use a cascade stage
- The cascode configuration has advantages in LNAs thanks to the better isolation → improved stability → however in some cases LNAs use potentially unstable devices (in-band!)
- The classical design can be input matched by using a balanced configuration or through an input circulator

Common gate FET stage



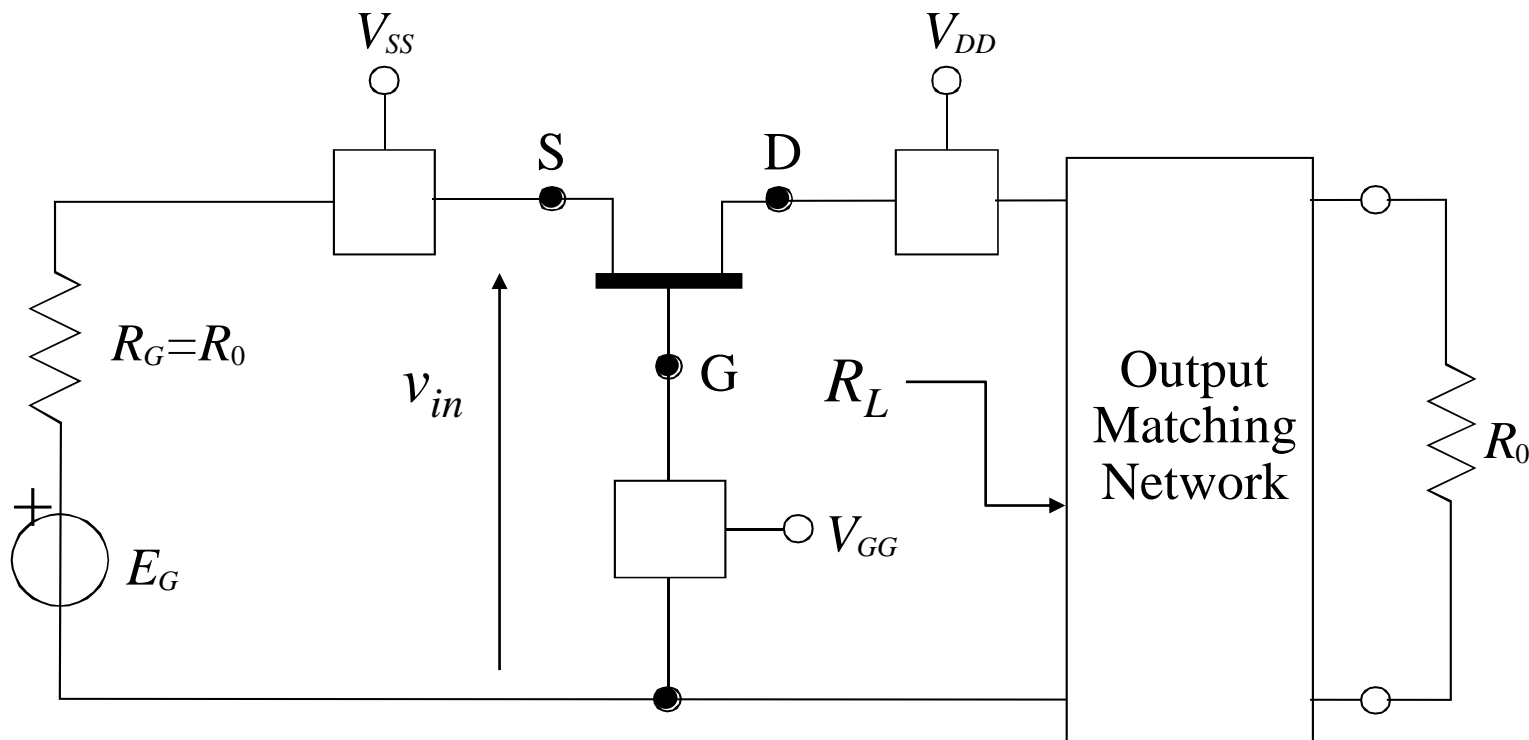- Noninverting amplifier, can be input matched by proper transconductance design (\rightarrow bias)
- For ideal parameters the noise figure is 2.2 dB ☹



Common gate FET stage



- The formulae hold if the input capacitance is negligible
- For ideal parameters the noise figure is 2.2 dB ☹️


$$Z_{in} = \frac{1}{g_m}$$

$$A_V = \frac{V_D}{V_{in}} = g_m R_L$$

$$NF = \frac{4k_B T R_G g_m^2 + 4k_B T P g_m}{4k_B T R_G g_m^2} = 1 + \frac{P}{R_G g_m}$$

$$\xrightarrow{1/g_m = R_G} 1 + P \approx 1 + \frac{2}{3} = \frac{5}{3} \rightarrow NF_{dB} = 2.22 \text{ dB}$$

Input impedance and amplification

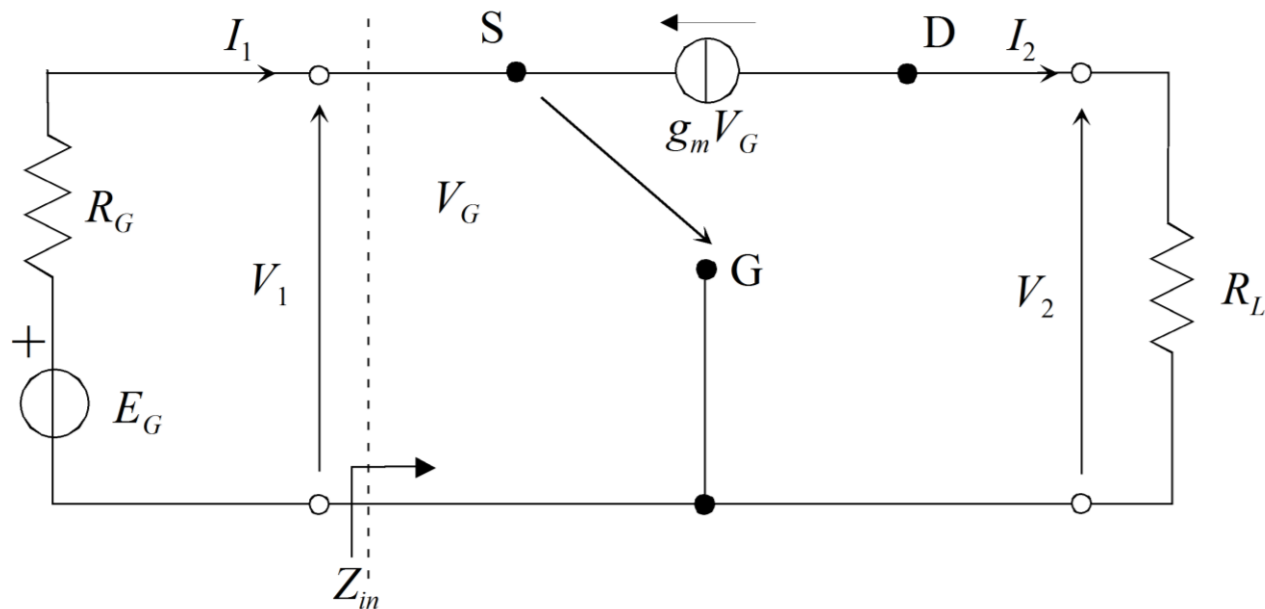


$$I_1 = -g_m V_G \quad V_2 = -g_m V_G R_L \quad V_1 = -V_G$$

$$Z'_{in} = I_2 R_L = \frac{V_1}{I_1} = \frac{-V_G}{-g_m V_G} = \frac{1}{g_m}$$

$$A_V = \frac{V_2}{V_1} = \frac{-g_m V_G R_L}{-V_G} = g_m R_L$$

Noise figure - I

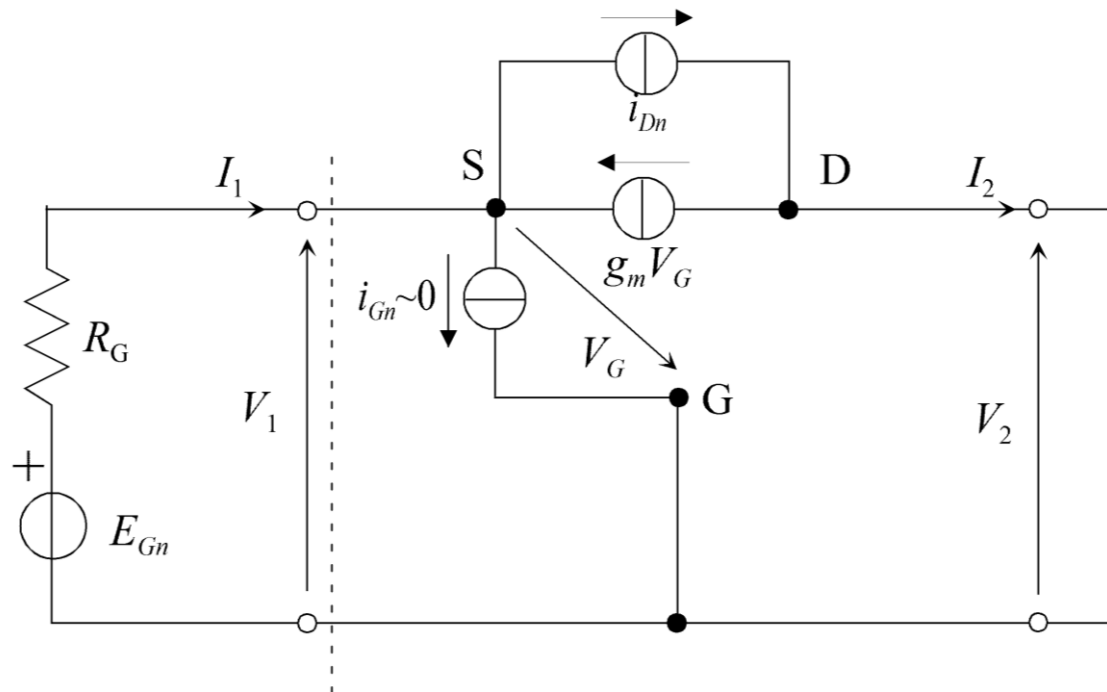


$$I_2 = I_1 = -g_m V_G + I_{Dn}$$

$$V_G = R_G I_1 - E_{Gn} \rightarrow I_1 = -g_m R_G I_1 + g_m E_{Gn} + I_{Dn}$$

$$I_1 = I_2 = \frac{g_m E_{Gn} + I_{Dn}}{1 + g_m R_G}$$

Noise figure - II

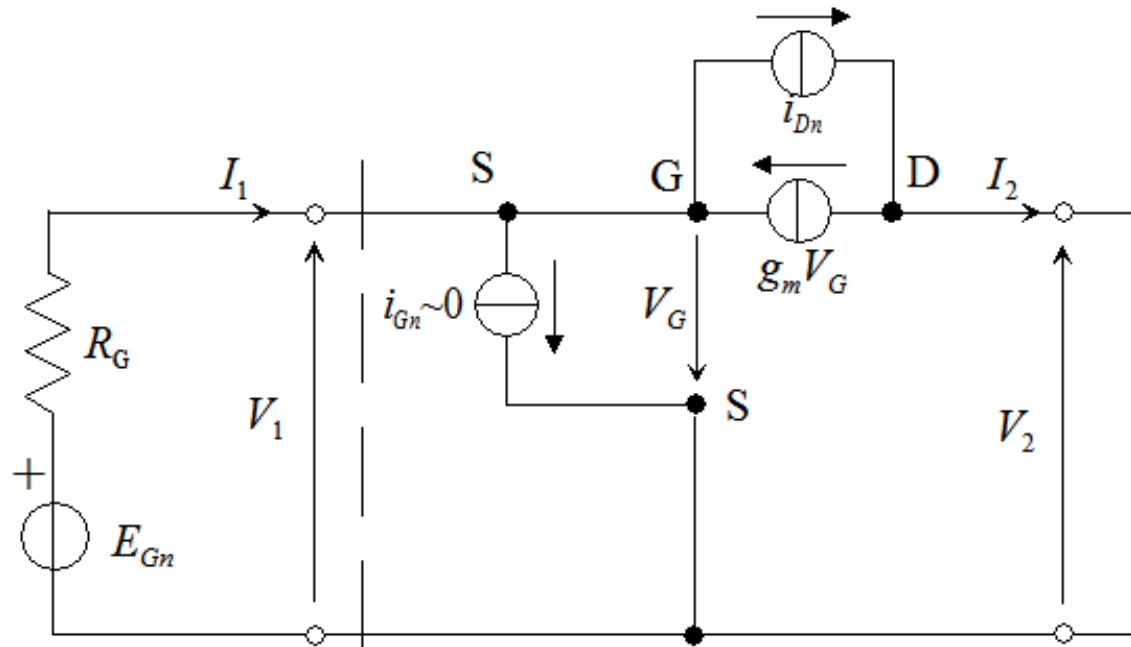


$$\overline{I_2 I_2^*} = \frac{g_m^2 \overline{E_{Gn} E_{Gn}^*} + \overline{I_{Dn} I_{Dn}^*}}{(1 + R_G g_m)^2}$$

$$\text{NF} = \frac{g_m^2 \overline{E_{Gn} E_{Gn}^*} + \overline{I_{Dn} I_{Dn}^*}}{g_m^2 \overline{E_{Gn} E_{Gn}^*}} = 1 + \frac{4k_B T_0 g_m P}{g_m^2 4k_B T_0 R_G} = 1 + \frac{P}{g_m R_G} \xrightarrow{R_G = 1/g_m} \text{NF} = 1 + P$$

Series inductive feedback LNA




Series inductor on FET source

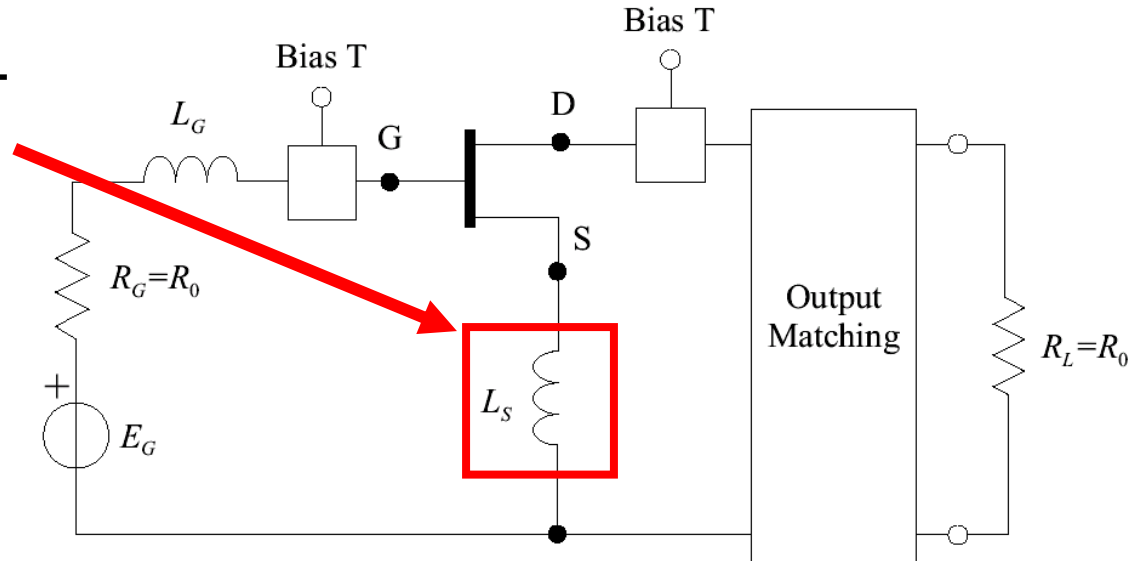

- An example of popular RF LNA design approach, where the input matching is obtained through a lossless network and the noise figure can be only marginally worse than the minimum one, but with reasonable and low input reflection coefficient
- Remember that cascading a stage with reactive networks does not change the minimum NF, but a source inductor does (sometimes marginally)!

Series Inductive Feedback LNA

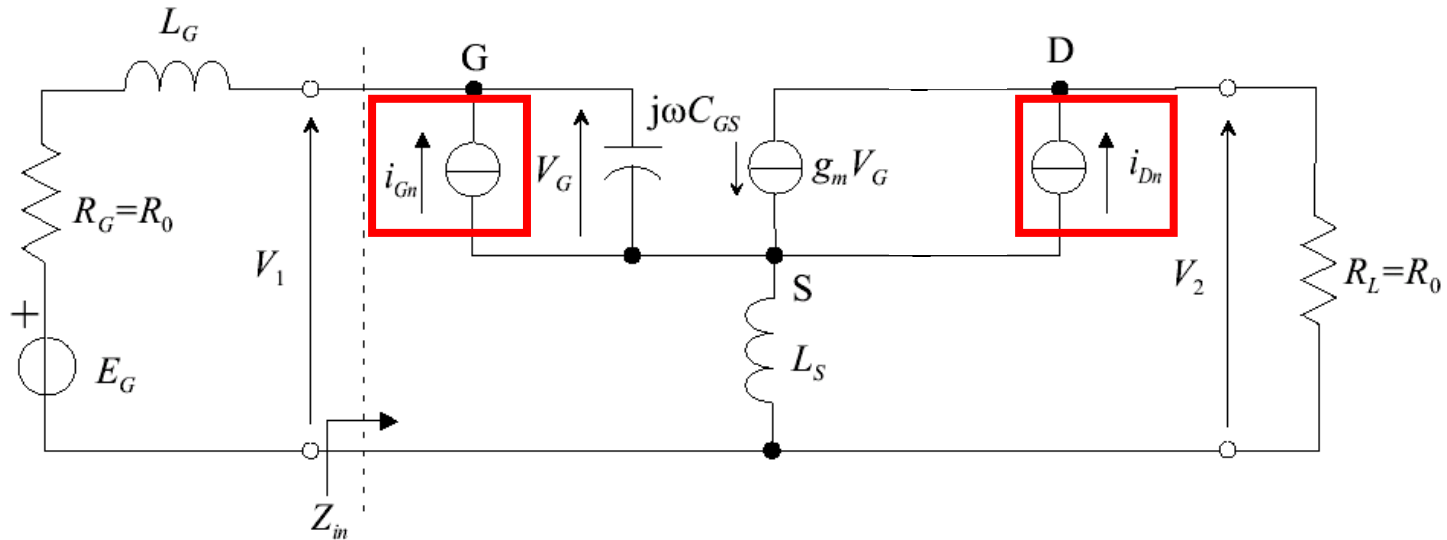

- Input impedance:

$$Z_{in} = Z_{11} - \frac{Z_{12}Z_{21}}{Z_{22} + R_0} = -\frac{j}{\omega C_{GS}} + j\omega L_S - \frac{j\omega L_S \left(j\frac{g_m}{\omega C_{GS}G_{DS}} + j\omega L_S \right) G_{DS}}{1 + (j\omega L_S + R_0) G_{DS}} \approx$$

$$\approx \underbrace{-\frac{j}{\omega C_{GS}} + j\omega L_S}_{\text{can be cancelled through resonance} \rightarrow L_G} + \underbrace{\frac{g_m L_S}{C_{GS}}}_{\text{can be designed to 50 Ohm}}$$

LNA design



- Matching corresponds to conditions:

$$\begin{aligned} L_S &= \frac{C_{GS} R_0}{g_m} = \frac{R_0}{\omega_T} \\ \omega (L_G + L_S) &= \frac{1}{\omega C_{GS}} \end{aligned}$$

- In input matching conditions the NF can be shown to be:

$$\text{NF} = 1 + \frac{\omega}{\omega_T} \left[Q_L R + \frac{1}{Q_L} \left(R - 2C\sqrt{PR} + P \right) \right]$$

- where:

$$Q_L = \frac{\omega (L_G + L_S)}{R_0} = \frac{1}{\omega C_{GS} R_0}$$

“Power optimization”



- The NF can be now be optimized with respect to the Q factor → since the gate noise contribution R is small usually this corresponds to large values of Q
- This can be obtained by changing the device periphery in order to set the input capacitance → reducing this also the **power dissipation is reduced**
- Optimum (not minimum!) Q & NF:

$$Q_{Lo} = \sqrt{\frac{R - 2C\sqrt{PR} + P}{R}}$$
$$NF_o = 1 + 2\frac{\omega}{\omega_T} \sqrt{R(R - 2C\sqrt{PR} + P)}$$