

Two-port Stability

Microwave Electronics

Giovanni Ghione, Marco Pirola

Politecnico di Torino, DET



Summary



- **Stability**
- Stability criteria
- Examples

Stability issues in a two-port



- A loaded two-port is here a model for a linear amplifier, including an active device → in certain conditions the structure can be unstable, i.e. it can oscillate
- Instability and oscillations correspond to **nonzero solution with zero forcing term**, i.e. zero system determinant:

$$\begin{vmatrix} 1 & -\Gamma_G & 0 & 0 \\ -S_{11} & 1 & -S_{12} & 0 \\ -S_{21} & 0 & -S_{22} & 1 \\ 0 & 0 & 1 & -\Gamma_L \end{vmatrix} = (1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L = 0$$

- This condition can be expressed equivalently:

$$(1 - S_{11}\Gamma_G)(1 - \Gamma_L\Gamma_{out}) = 0 \quad \longleftrightarrow \quad (1 - S_{22}\Gamma_L)(1 - \Gamma_G\Gamma_{in}) = 0$$

Unconditional & conditional stability - I



- We assume that load and generator are *passive* (gamma with magnitude <1) and that the two-port is *stable when closed on the normalization impedances* (reasonable, why?), i.e.:

$$|S_{11}| < 1 \quad |S_{22}| < 1$$

- it follows that:

$$\begin{aligned} |S_{11}\Gamma_G| < 1, \quad |S_{22}\Gamma_L| < 1 &\rightarrow \\ \rightarrow |1 - S_{11}\Gamma_G| > 0, \quad |1 - S_{22}\Gamma_L| > 0 \end{aligned}$$

- Therefore the instability condition **can only derive from**:

$$(1 - \Gamma_G \Gamma_{in}) = 0 \iff (1 - \Gamma_L \Gamma_{out}) = 0$$

Unconditional & conditional stability - II



$$\boxed{\Gamma_G \Gamma_{in} = 1} \longleftrightarrow \boxed{\Gamma_L \Gamma_{out} = 1}$$


Diagram showing the relationship between input and output reflection coefficients. A green double-headed arrow connects two equations. Below the left equation, a yellow arrow points from a yellow box containing the expression $\frac{S_{11} - \Delta_S \Gamma_L}{1 - S_{22} \Gamma_L}$ to the Γ_{in} term. Similarly, below the right equation, a yellow arrow points from a yellow box containing the expression $\frac{S_{22} - \Delta_S \Gamma_G}{1 - S_{11} \Gamma_G}$ to the Γ_{out} term.

- Two possibilities (generator and load gamma are considered as **passive** \rightarrow magnitude < 1 , within the unit circle in Smith chart):
 - For every possible Γ_L we have $|\Gamma_{in}| < 1$ & for every possible Γ_G we have $|\Gamma_{out}| < 1 \rightarrow$ **unconditional stability**
 - For some $\Gamma_L \rightarrow |\Gamma_{in}| \geq 1$ or for some $\Gamma_G \rightarrow |\Gamma_{out}| \geq 1 \rightarrow$ **conditional stability or potential instability**


Graphical representation: unconditional stability



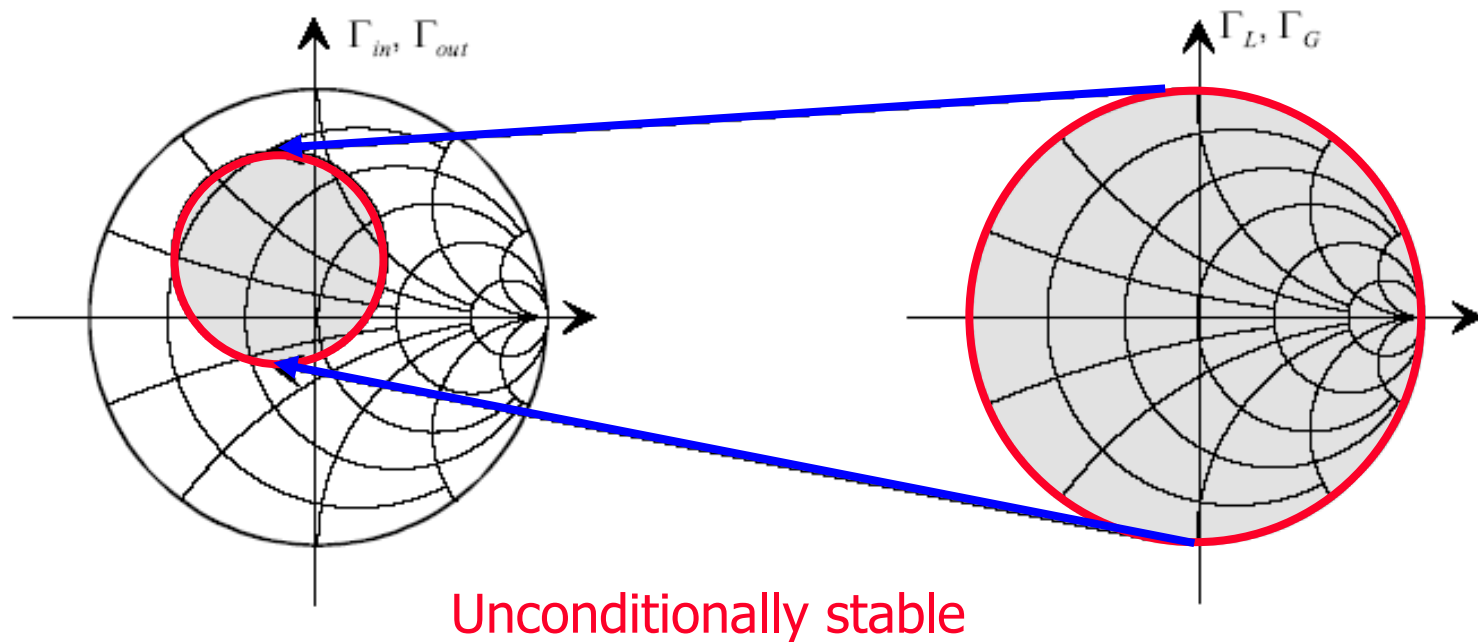- Taking into account that $\Gamma_{in}(\Gamma_L)$ and $\Gamma_{out}(\Gamma_G)$ are *bilinear transformations of complex variables* that turn circles into circles in the respective complex planes we have the graphical interpretation:



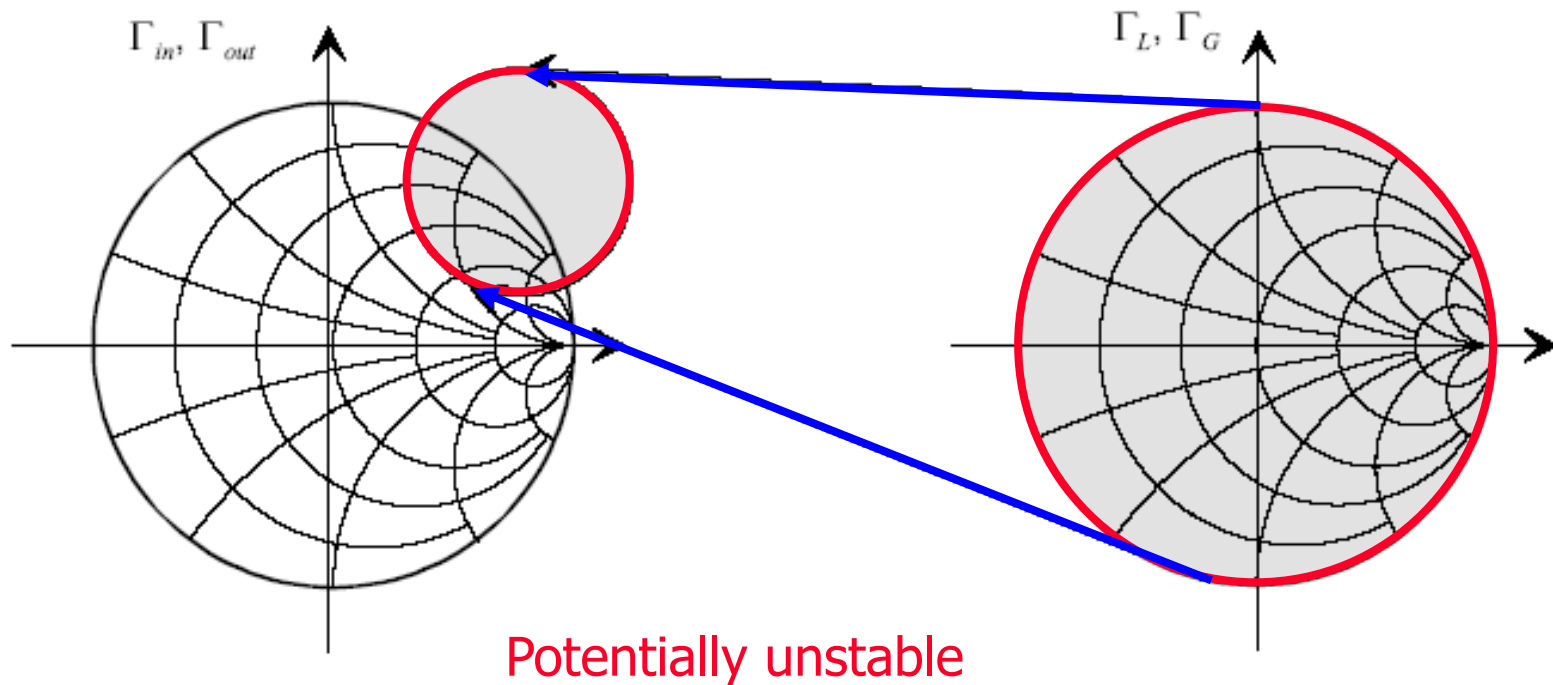
Graphical representation: conditional stability



Stability circles - I



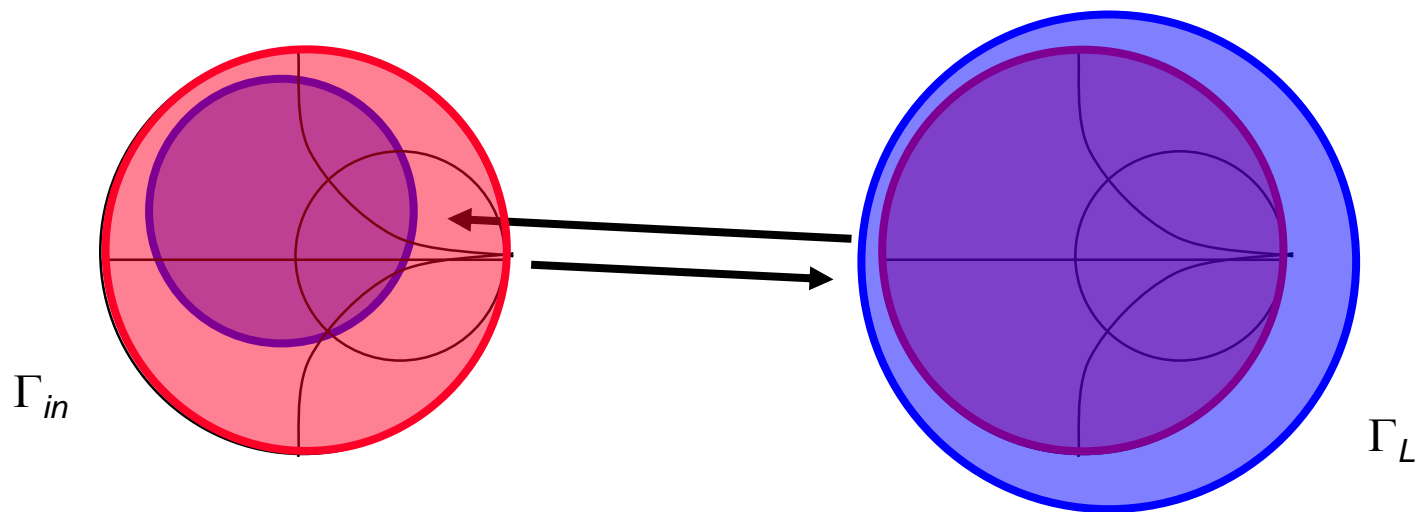
- In practice we prefer to consider the *counterimage* of the interior of the unit circle in the Γ_{in} (Γ_{out}) in the plane Γ_L (Γ_G) \rightarrow **output (input) stability circles**, e.g.:



Stability circles - II



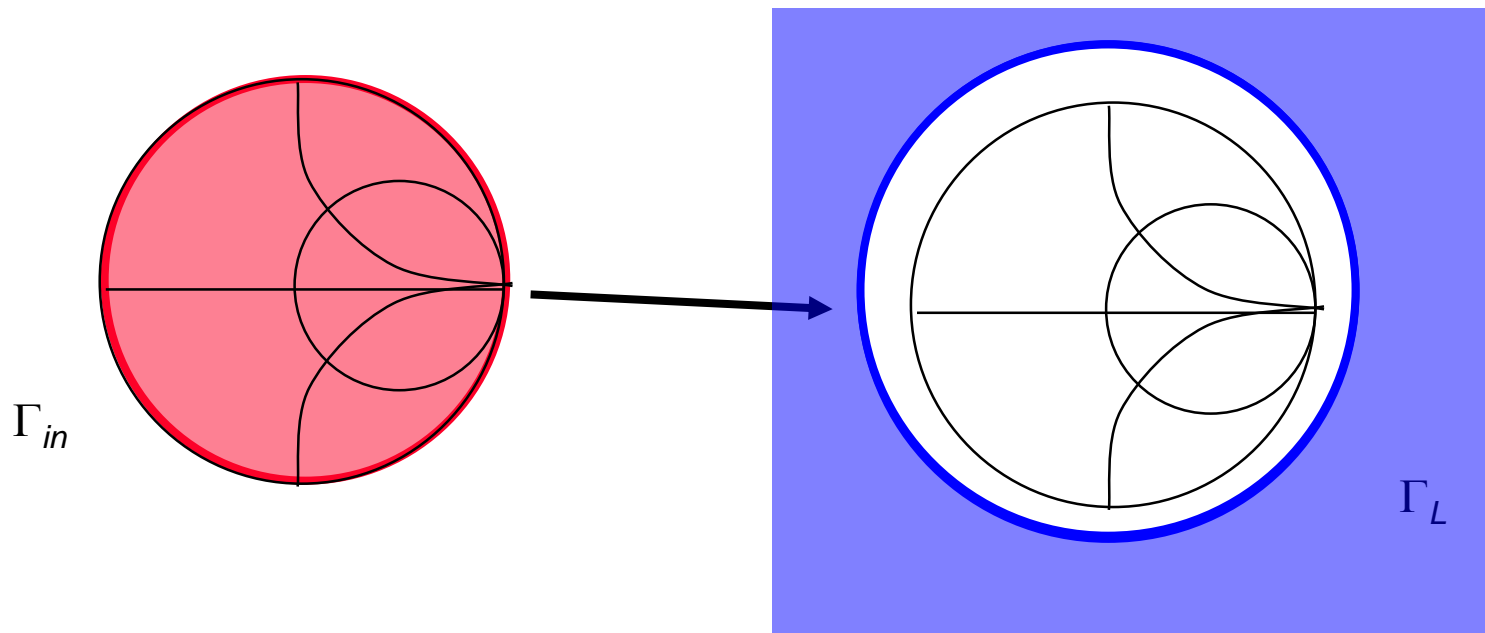
- **!!! WARNING !!!** The counterimage of the interior of the unit circle of the plane Γ_{in} (Γ_{out}) in plane Γ_L (Γ_G) can be **the interior** but also **the exterior** of the output (input) stability circle:




Stability circles - III



- To solve the ambiguity, take into account that:
 - to $\Gamma_L=0$ ($\Gamma_G=0$) a $|\Gamma_{in}| < 1$, $|\Gamma_{out}| < 1$ should correspond.
 - Why? because in this case $\Gamma_{in} = S_{11}$, $\Gamma_{out} = S_{22}$ and we suppose that those have **magnitude** **<1**
- The center of the Smith chart is in the stable zone (in light blue)

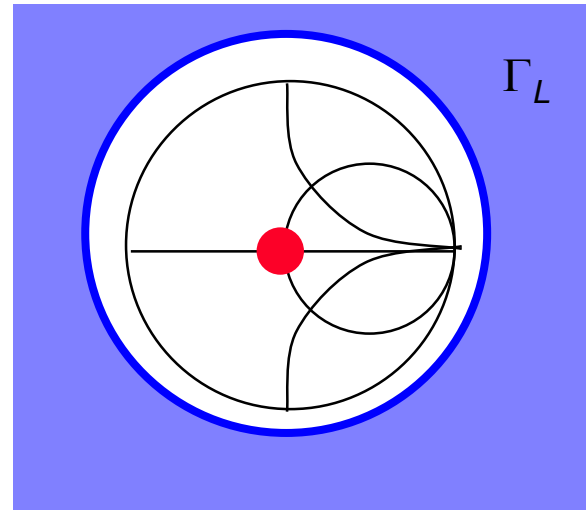

NO!

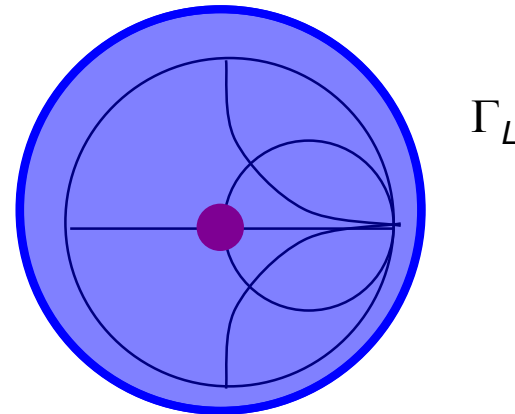


OK!

Example – output stability circle




Unconditionally stable

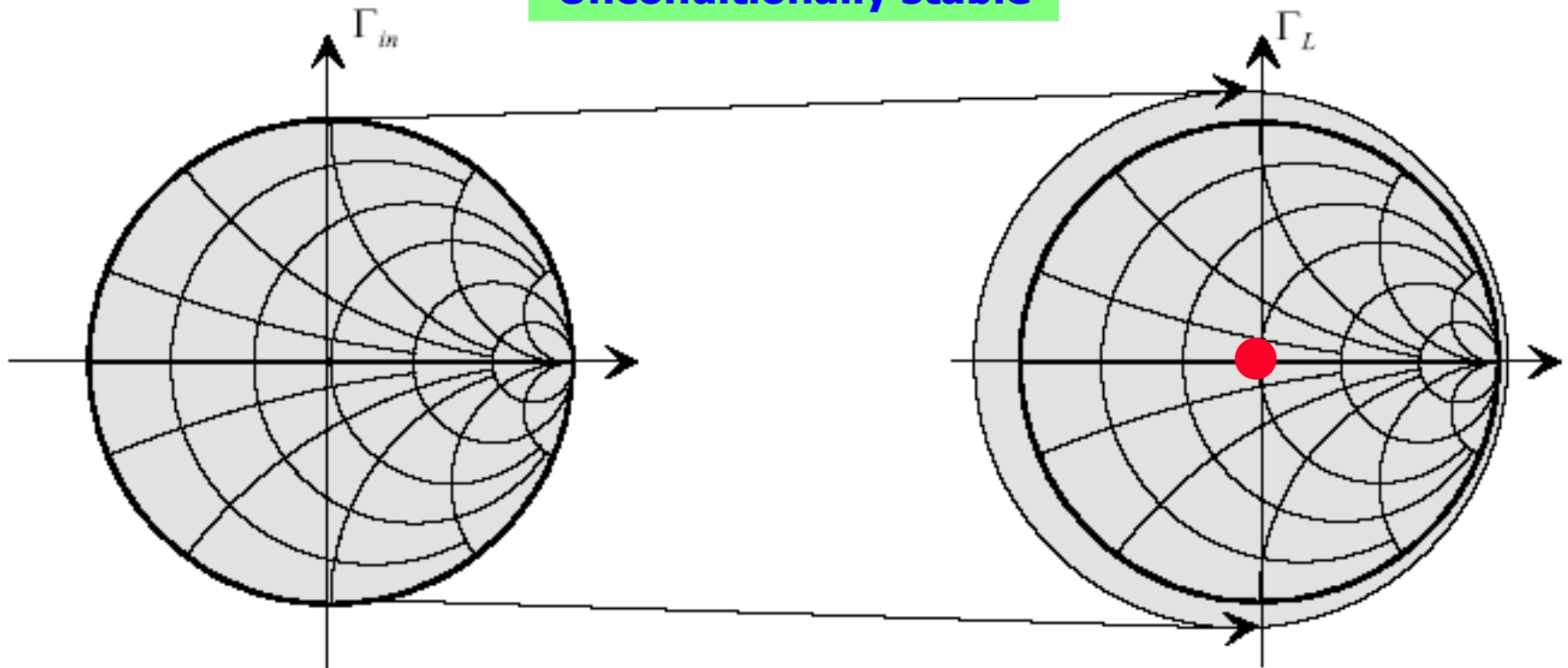

Example – input stability circle



Potentially unstable

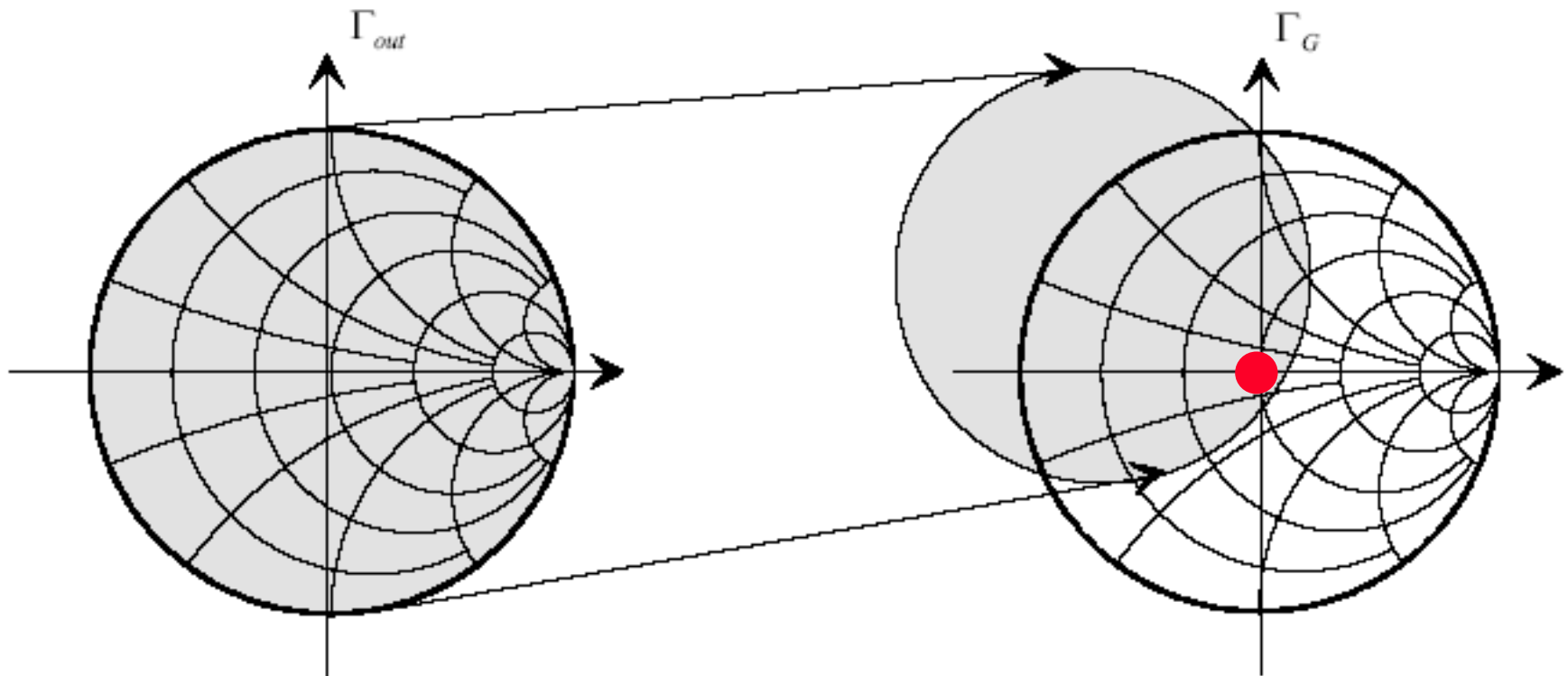


Other examples




Unconditionally stable


unstable

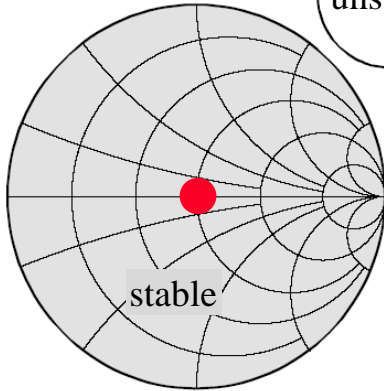

Potentially unstable

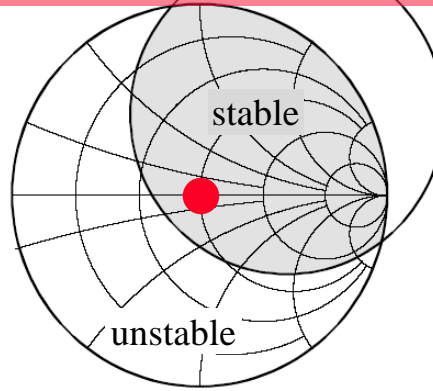


unstable
Unconditionally stable

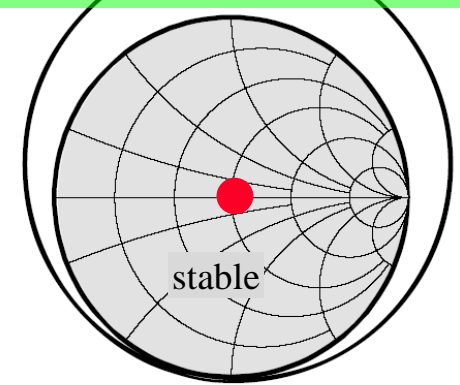


Potentially unstable


unstable

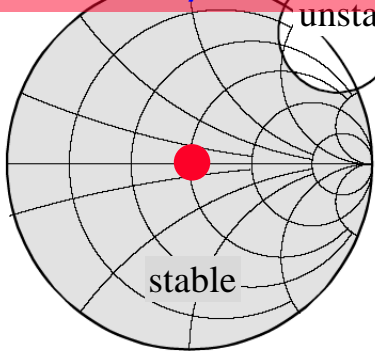

Potentially unstable

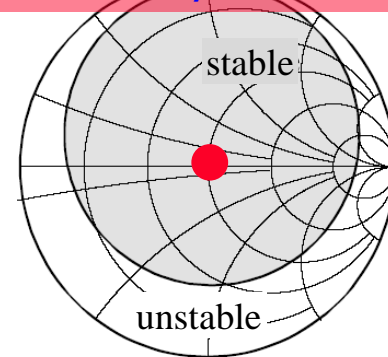

Potentially unstable

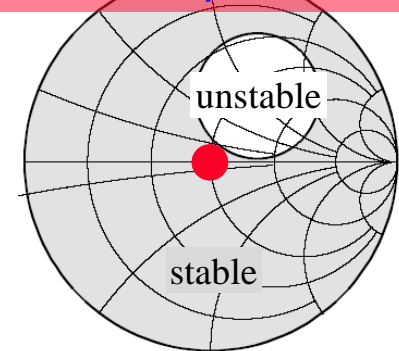

Stability and gain - I





- The two sets corresponding to the potential instability condition:

$$|\Gamma_{in}(\Gamma_L)| = \left| \frac{S_{11} - \Delta_S \Gamma_L}{1 - S_{22} \Gamma_L} \right| \geq 1 \quad |\Gamma_{out}(\Gamma_G)| = \left| \frac{S_{22} - \Delta_S \Gamma_G}{1 - S_{11} \Gamma_G} \right| \geq 1$$

are (in the Γ_L or Γ_G plane) **circles ($|\Gamma|=1$) + their internal or external region**

- Examples:

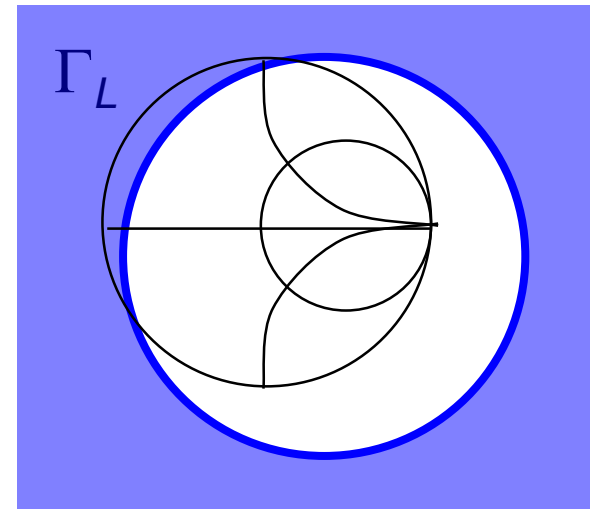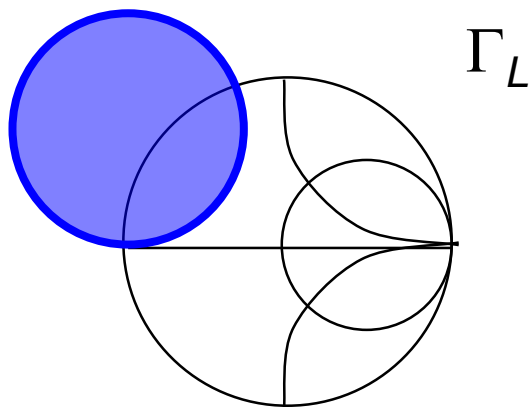

Stability and gain - II



- On the circles corresponding to the limit of potential instability condition the related gains \rightarrow infinity (check, see next slide):

$$\left| \Gamma_{in}(\Gamma_L) \right| = 1 \rightarrow G_{op} = \infty \quad \left| \Gamma_{out}(\Gamma_G) \right| = 1 \rightarrow G_{av} = \infty$$

- In an unconditionally stable two-port the “unstable” region fall outside the Smith chart and the gains have a **well defined maximum (MAG)**
- In a potentially unstable two-port the “unstable” region falls in part within the Smith chart and therefore a maximum gain does not exist any more, **gain becomes infinity on a set of points within the Smith chart**

Stability and gain - III




$$G_{op} = \frac{P_L}{P_{in}}$$

$$P_{in} = \frac{|b_0|^2 (1 - |\Gamma_{in}|^2)}{|1 - \Gamma_{in} \Gamma_G|^2} \rightarrow P_{in}|_{|\Gamma_{in}|=1} = 0, \quad P_L \neq 0, \rightarrow G_{op} = \infty$$


$$G_{av} = \frac{P_{av,out}}{P_{av,in}}$$

$$P_{av,out} = \frac{|b_0|^2 |S_{21}|^2}{(1 - |\Gamma_{out}|^2) |1 - S_{11} \Gamma_G|^2} \rightarrow P_{av,out}|_{|\Gamma_{out}|=1} = \infty, \rightarrow G_{av} = \infty$$

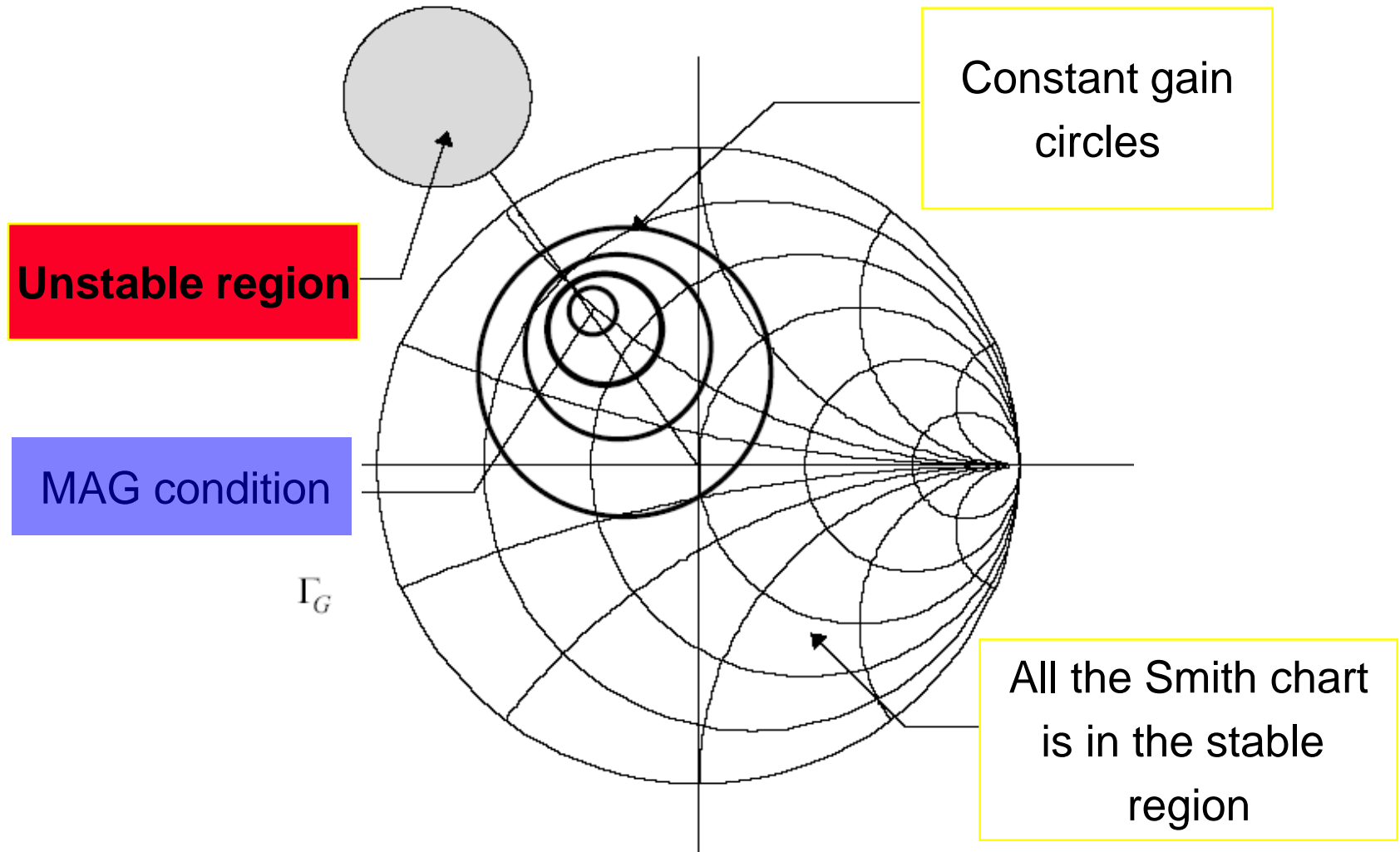
Example: available gain, unconditionally stable



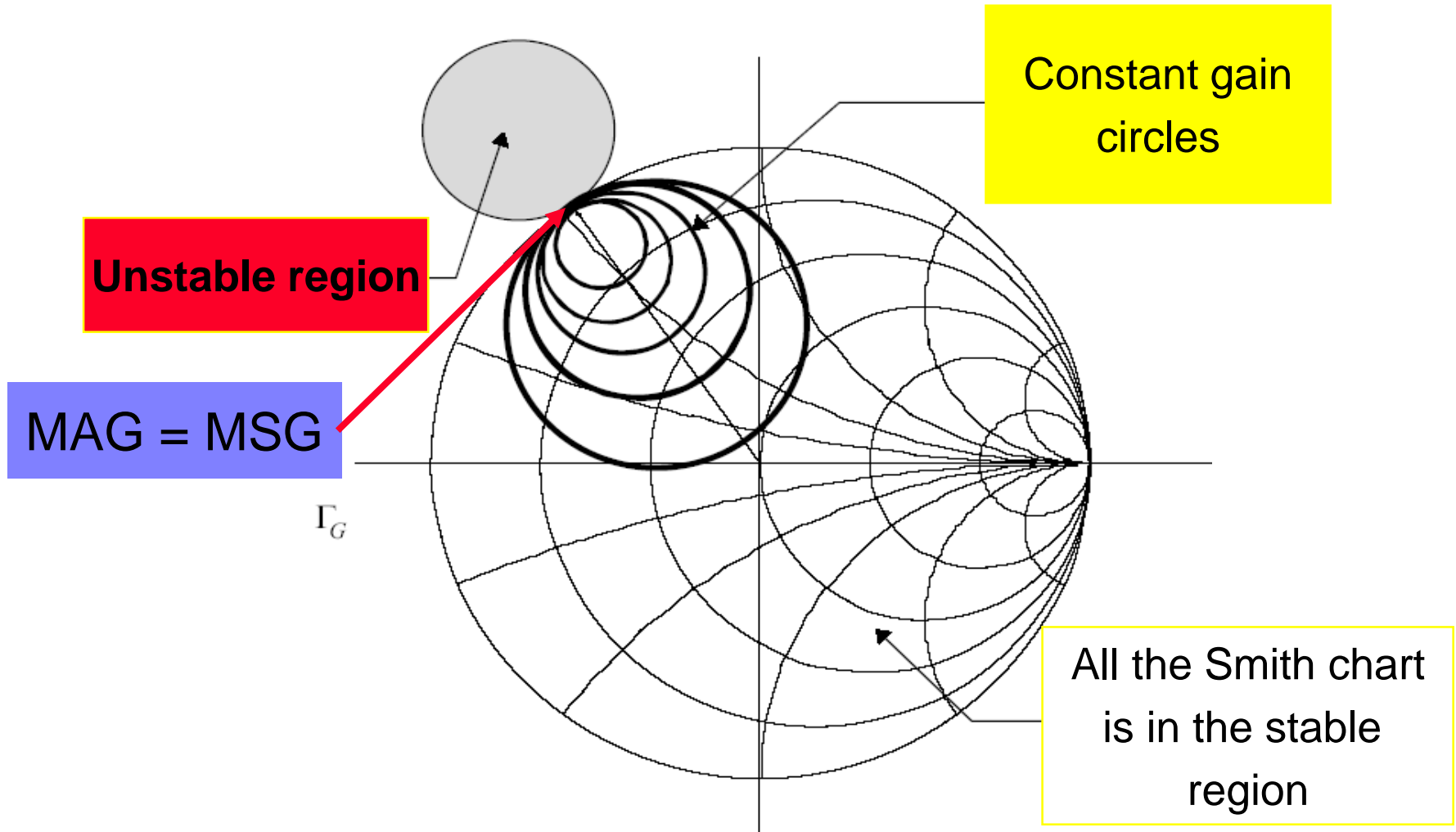Example: available gain, almost potentially unstable



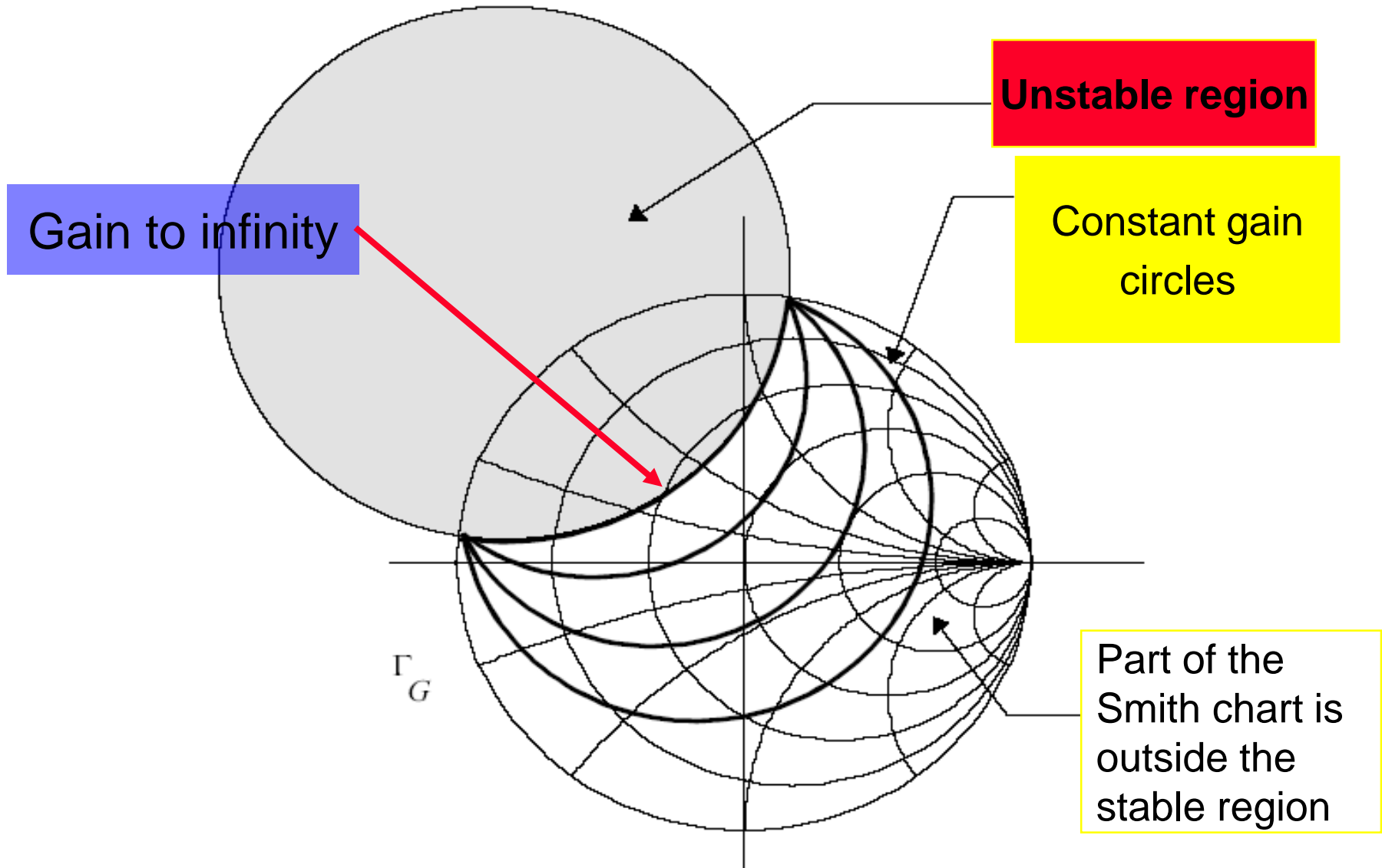Example: available gain, potentially unstable



Stability and amplifier design



- The maximum gain design is possible through **simultaneous conjugate matching** only if the two-port is unconditionally stable on the operating bandwidth
- If the two-port is potentially unstable we have to choices:
 - Choose a load and generator condition far enough away from the unstable region (critical!)
 - Stabilize the two-port through resistive networks (safer, our choice always)
- Low-frequency (out-of-band) stability is always to be checked and made sure of (why? See next slides, the problem lies with amplifier saturation due to “self jamming”)
- How do you know that a two-port is unconditionally stable? See “stability criteria”

An amplifier (approximate) system model



- The model is nonlinear and is often called “descriptive function model”; it goes beyond the small-signal linear approximation


$$\text{input} \rightarrow x(t) = \text{Re} \{ \hat{x}(t) \exp(j\omega_c t) \}$$

$$\text{output} \rightarrow y(t) = \text{Re} \{ \hat{y}(t) \exp(j\omega_c t) \}$$

$$\hat{y}(t) = G(|\hat{x}(t)|) \hat{x}(t)$$

- \mathbf{G} is the complex “descriptive function” (of a real variable) relating the input and output signal **envelopes**.
- Note that the **input envelope** can be a **constant + a sinusoidal signal** so that the total input is made of **two frequencies**.
- The model accounts for **gain compression** and **intermodulation distortion**

Descriptive function - example

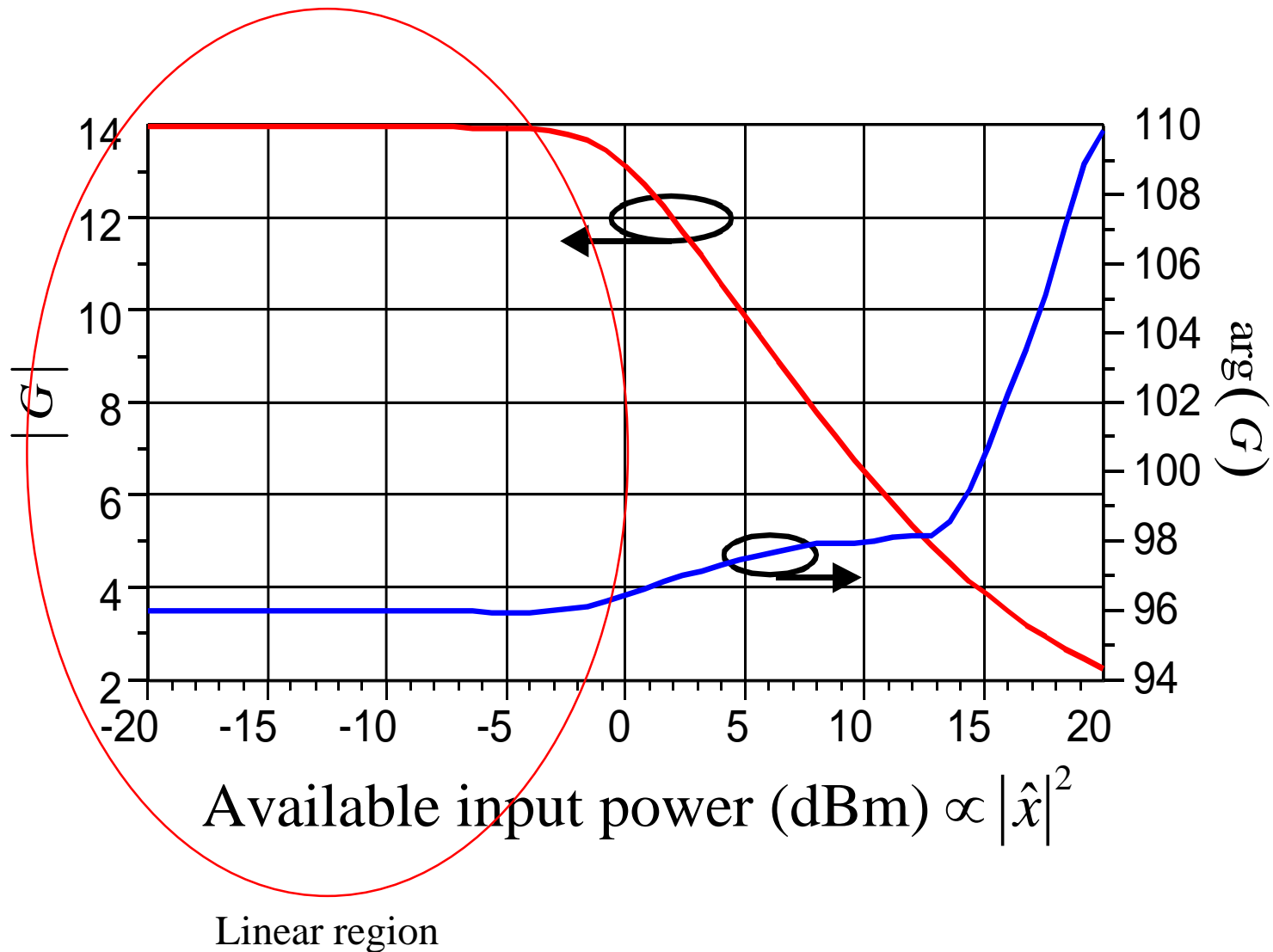

Effect of out-of-band oscillations



- Suppose the signal input x of the amplifier is affected by a large interferer X generated by self-oscillations:

$$\hat{x}_{tot} = \hat{x}(t) + \hat{X}(t)$$

- While the gain for x is large, the gain for X is small:

$$G(|\hat{x}(t)|) = G_{ss}, \quad G(|\hat{X}(t)|) = G_1, \quad |G_1| \ll |G_{ss}|$$

- The gain for the “good” part of the total signal will be also small \rightarrow the amplifier is desensitized, i.e. dominated by out-of-band oscillations:

$$G(|\hat{x} + \hat{X}|) \approx G_1 \rightarrow \hat{y} \approx \underbrace{G_1 \hat{x}(t)}_{\text{negligible}} + \underbrace{G_1 \hat{X}(t)}_{\text{dominant}}$$

Summary



- Stability
- **Stability criteria**
- Examples

Stability criteria (classical)



- It can be shown that a necessary and sufficient condition for stability is the set made by the following two conditions (other equivalent choices exist for the second condition):

$$K = \frac{1 - |S_{22}|^2 - |S_{11}|^2 + |\Delta_S|^2}{2 |S_{21} S_{12}|} > 1$$

$$|\Delta_S| < 1$$

Example: reactive two-port



- For a reactive two-port $SS^* = 1$ since the S-matrix is symmetrical
- It follows $|\Delta_S|^2 = 1$ (determinant of product of two matrices)
- Moreover expanding $SS^* = 1$ one has:

$$|S_{11}|^2 + |S_{12}|^2 = 1$$

$$|S_{22}|^2 + |S_{12}|^2 = 1$$

- Thus:

$$\begin{aligned} K &= \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta_S|^2}{2|S_{12}|^2} = \\ &= \frac{1 - (1 - |S_{12}|^2) - (1 - |S_{12}|^2) + 1}{2|S_{12}|^2} = 1 \end{aligned}$$

Single-parameter stability criterion



- More recently a single-parameter, completely equivalent stability criterion was introduced, based on verifying **one** of the two following conditions (the other one follows):

$$\mu_1 = \frac{1 - |S_{11}|^2}{|S_{22} - S_{11}^* \Delta_S| + |S_{12} S_{21}|} > 1$$

$$\mu_2 = \frac{1 - |S_{22}|^2}{|S_{11} - S_{22}^* \Delta_S| + |S_{12} S_{21}|} > 1$$

Single-frequency stability: examples



	$ S_{11} $	ph(S_{11}), degrees	$ S_{12} $	ph(S_{12}), degrees	$ S_{21} $	ph(S_{21}), degrees	$ S_{22} $	ph(S_{22}), degrees
1	0.2	20	0.05	120	3	30	0.5	-50
2	0.75	-60	0.3	70	6	90	0.5	60
3	1.05	20	0.05	120	3	40	0.5	-50
4	0.5	0	0.025	180	2	0	0.1	0
5	0.95	-22	0.04	80	3.5	165	0.61	-13
6	0.69	-123	0.11	48	1.29	78	0.52	-77
7	0.1	0	0	0	0	0	0.3	0
8	1.2	0	0	0	0	0	0.3	0
9	0.1	0	0	0	0	0	1.3	0

Stable or potentially unstable?



	K	$ \Delta_S $	TYPE	$ \Gamma_{G_{opt}} $	$\text{ph}(\Gamma_{G_{opt}})$, degrees	$ \Gamma_{L_{opt}} $	$\text{ph}(\Gamma_{L_{opt}})$, degrees	G_{MAX} , dB
1	2.57	0.249	ST	0.10	-20	0.48	50	10.8
2	1.34	2.156	UNST	undef.	undef.	undef.	undef.	undef.
3	0.34	0.673	UNST	undef.	undef.	undef.	undef.	undef.
4	7.50	0.1	ST	0.50	0	0.07	0	7.3
5	0.19	0.572	UNST	undef.	undef.	undef.	undef.	undef.
6	1.12	0.254	ST	0.88	127	0.82	86	8.6
7	$+\infty$	0.03	ST	0.1	0	0.3	0	0
8	$-\infty$	0.36	UNST	undef.	undef.	undef.	undef.	undef.
9	$-\infty$	0.13	UNST	undef.	undef.	undef.	undef.	undef.

Stability as a function of frequency




- In general stability changes with frequency, at low frequency devices have high gain and are potentially more unstable, gain decreases with frequency finally leading to an unconditionally stable device
- In the transition from the stable to the potentially unstable regions there is a frequency at which $K=1 \rightarrow$ at that frequency $MAG=MSG$
- In the potentially unstable frequency range MSG is used as a figure of merit
- High-frequency devices typically need low-frequency stabilization to prevent out-of-band oscillations

Summary



- Stability
- Stability criteria
- **Examples**

Stability vs. frequency in a MESFET

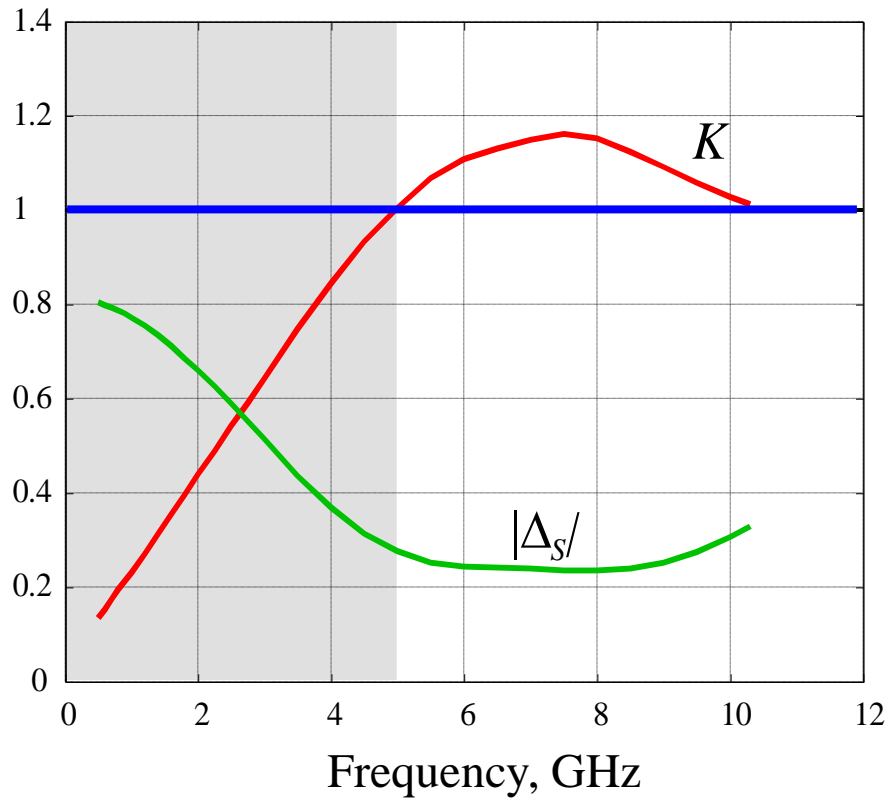

f , GHz	$ S_{11} $	ϕ_{11}	$ S_{21} $	ϕ_{21}	$ S_{12} $	ϕ_{12}	$ S_{22} $	ϕ_{22}
1.000	0.949	-29.8	4.825	151.1	0.038	72.1	0.781	-14.4
2.000	0.821	-59.8	4.531	123.8	0.070	56.0	0.696	-28.9
3.000	0.648	-94.2	4.092	97.6	0.092	41.4	0.600	-42.4
4.000	0.512	-133.0	3.516	73.9	0.102	30.5	0.518	-51.8
5.000	0.472	-165.2	3.025	54.7	0.108	25.3	0.444	-57.8
6.000	0.464	176.0	2.714	38.4	0.118	23.7	0.367	-65.4
7.000	0.441	158.2	2.505	22.1	0.134	20.2	0.302	-80.8
8.000	0.411	127.5	2.321	4.0	0.151	15.0	0.281	-105.9
9.000	0.454	91.4	2.093	-15.1	0.168	7.0	0.300	-134.2
10.000	0.551	66.6	1.836	-34.5	0.181	-2.8	0.328	-169.8

Gain parameters versus frequency

