

RF power amplifiers – Class A to class C

Microwave Electronics

Giovanni Ghione, Marco Pirola

Politecnico di Torino, DET




RF amplifiers




- Receiver chain:
 - Low-noise amplifiers → optimized with respect to noise figure & gain
 - High gain amplifiers → optimized with respect to gain
- Transmitter chain:
 - High gain amplifiers
 - **Power amplifiers** → optimized vs. output power, linearity, efficiency

PA with “resistive” load

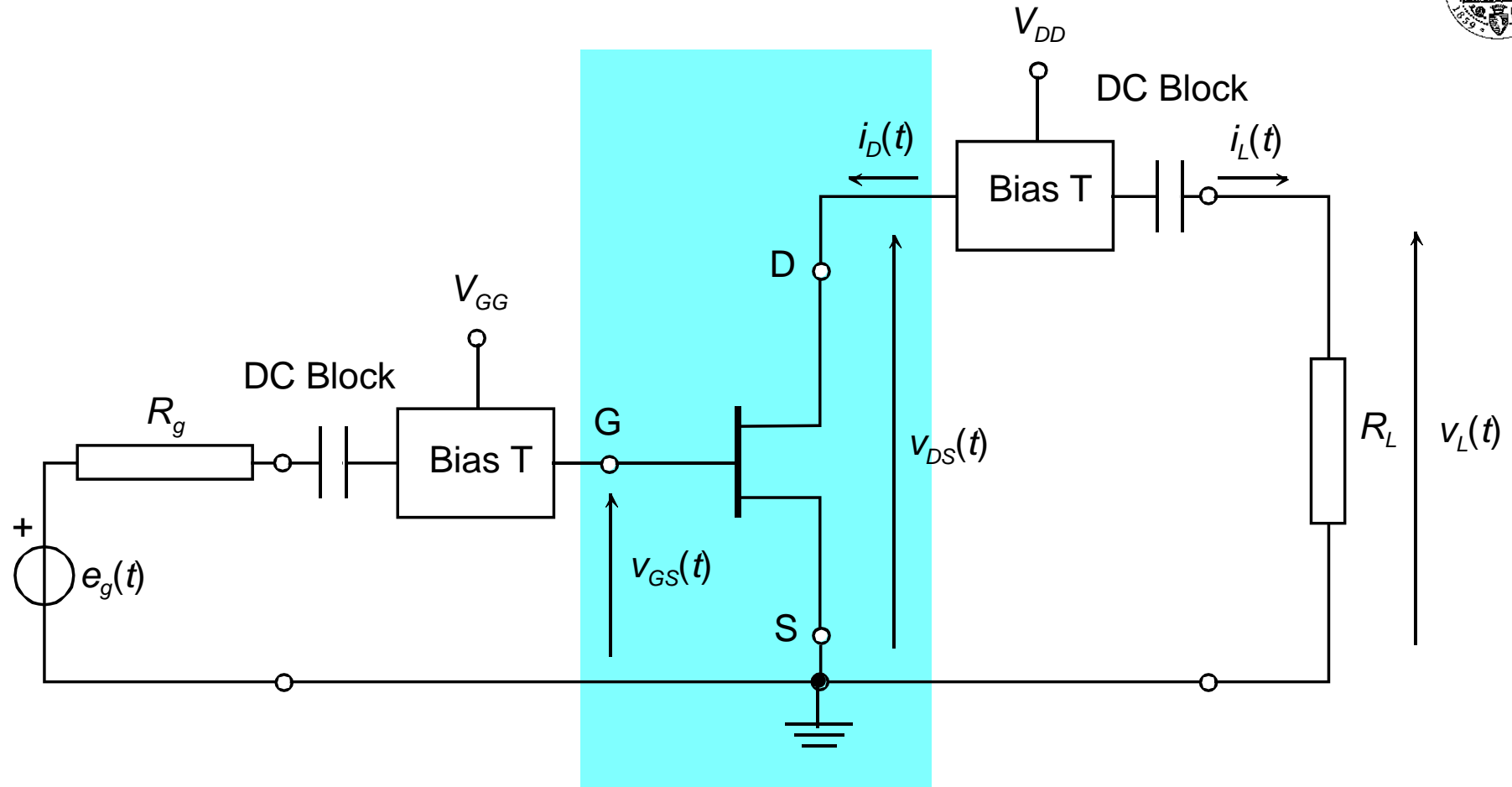

PA with “tuned” load

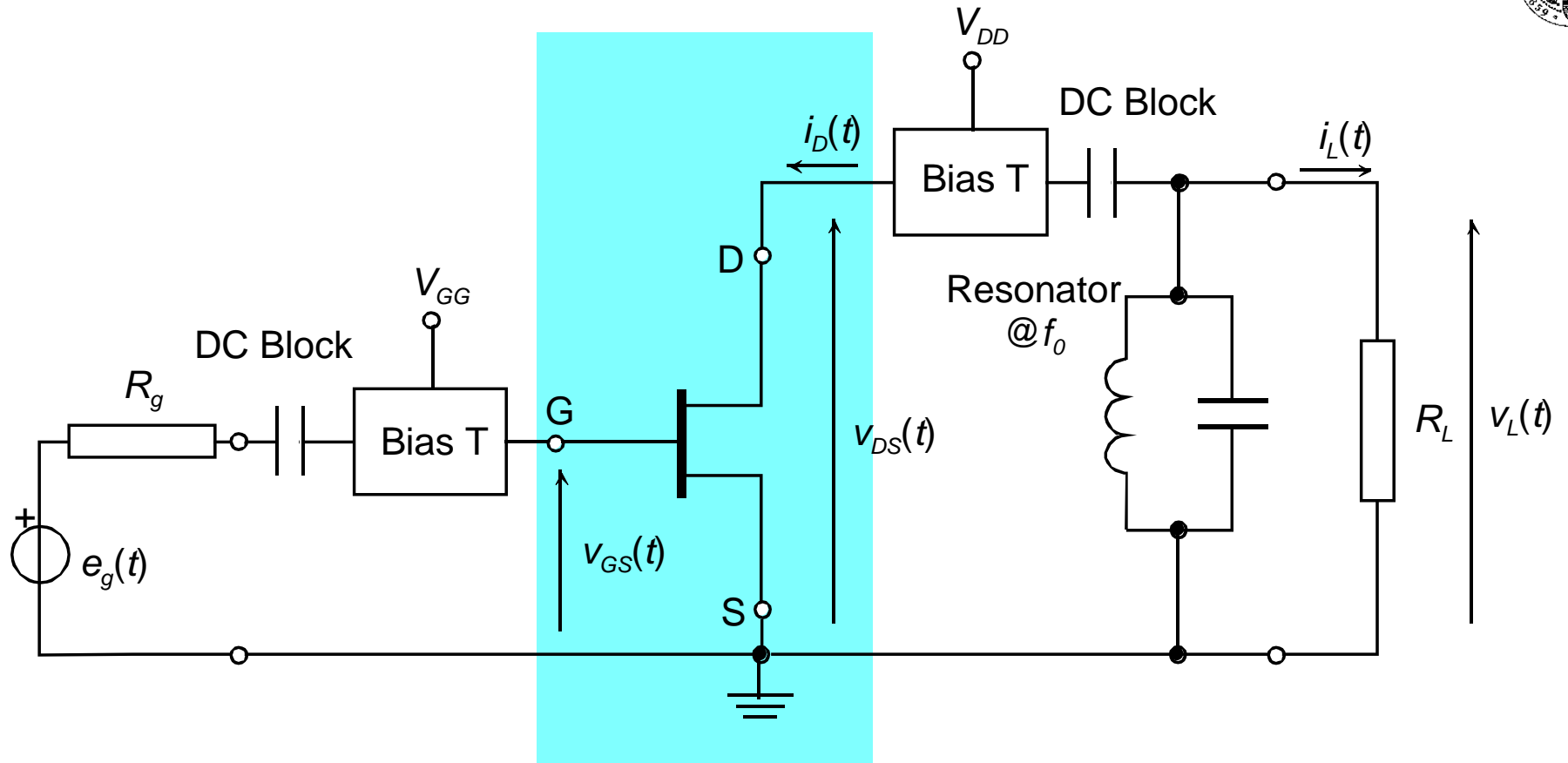


PA – Classes (traditional)




- Suppose to apply a sinusoidal input signal of period T to the power amplifier; cases:
 - Class A (quasi-linear): the active device is always ON
 - Class AB: the active device is ON for more than 50% of the time
 - Class B: the active device is ON for exactly 50% of the time
 - Class C: the active device is ON for less than 50% of the time

From class A to class C: device current

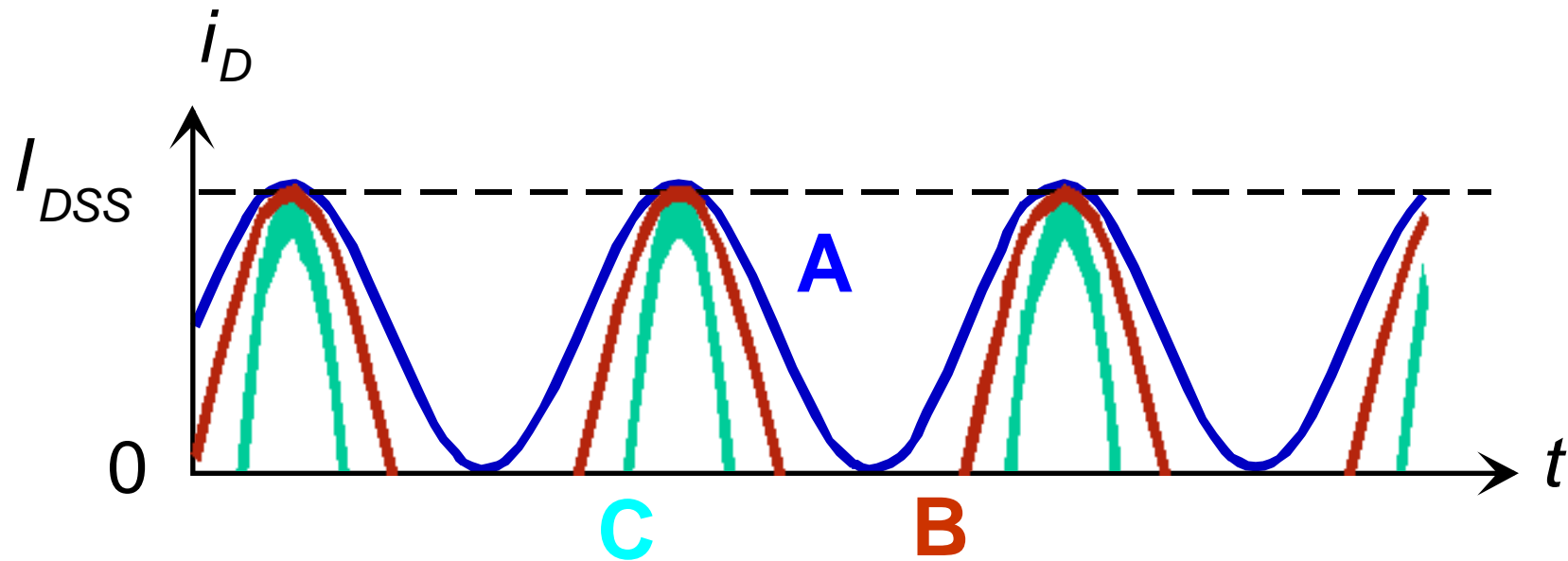

Tuned PA output loop equations

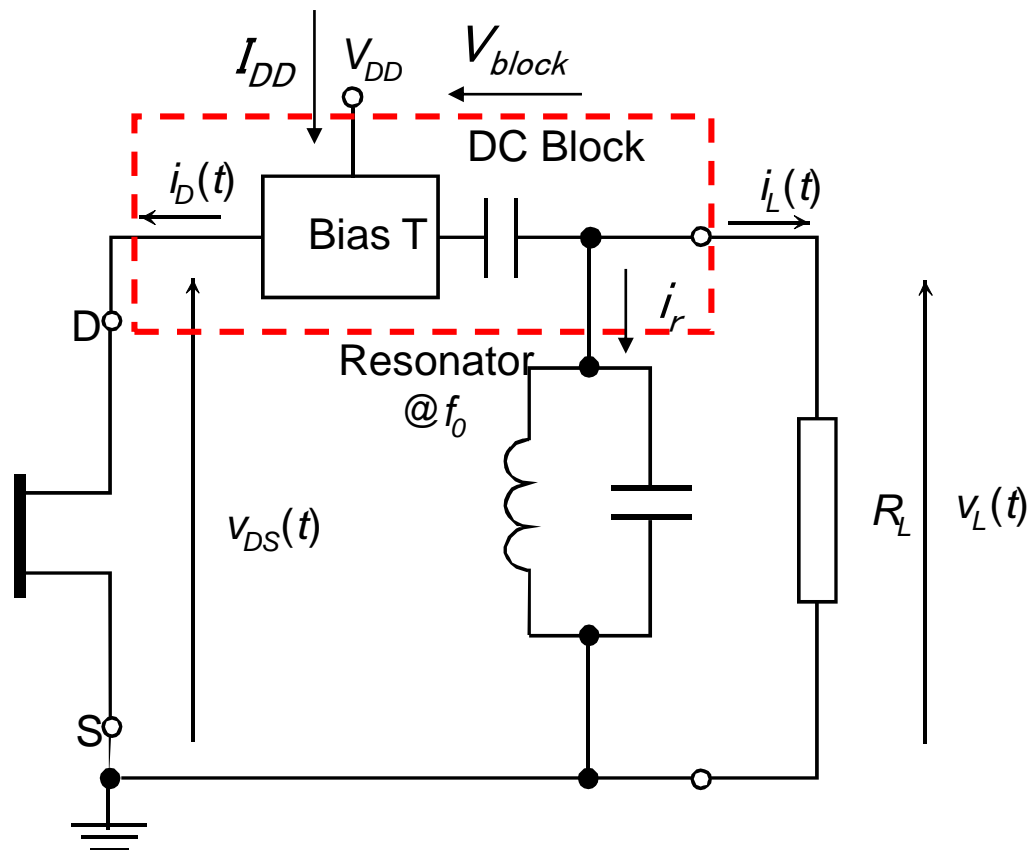

Time domain:

$$v_L(t) + V_{block} = v_{DS}(t)$$

$$i_L(t) + i_D(t) + i_r(t) = I_{DD}$$

Frequency domain

$$V_{DS}(DC) = V_{block}(DC) = V_{DD}$$

$$V_{DS}(f_0) = V_L(f_0)$$

$$V_{DS}(nf_0) = V_L(nf_0) = 0$$

$$I_D(DC) = I_{DD} \quad I_L(DC) = I_r(DC) = 0$$

$$I_L(f_0) = -I_D(f_0)$$

$$I_L(nf_0) = 0, \quad I_r(nf_0) = -I_D(nf_0)$$


Load line (generally a curve)

$$V_{DS}(f_0) = V_L(f_0) = R_L I_L(f_0) = -R_L I_D(f_0)$$

$$v_{DS}(t) = V_{DD} - R_L I_D(f_0) \cos \omega_0 t$$

$$i_D(t) = I_{DD} + I_D(f_0) \cos \omega_0 t + I_D(2f_0) \cos 2\omega_0 t + \dots$$

Bias T voltages & currents

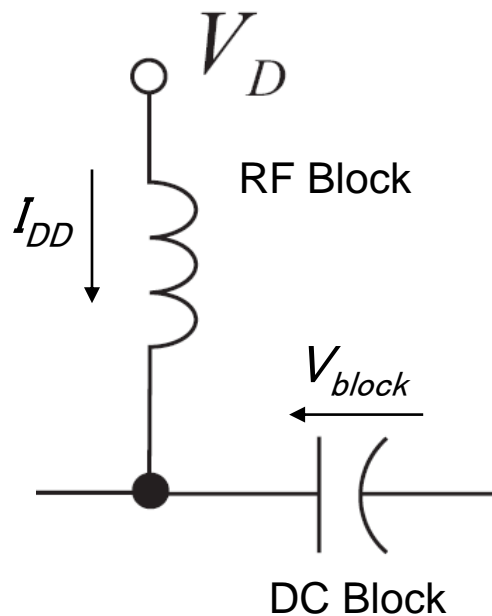

- Ideally the RF block is a very large inductor \rightarrow only the DC component of the current can pass, the block blocks all frequencies above DC
- The DC block is a very large capacitor \rightarrow only the DC component of voltage exists, all other frequencies above DC are shorted

Load line & output device $I_D(V_{DS})$



Load line + device characteristics

$$v_{DS}(t) = V_{DD} - R_L I_D(f_0) \cos \omega_0 t$$

$$i_D(t) = I_{DD} + I_D(f_0) \cos \omega_0 t +$$

$$I_D(2f_0) \cos 2\omega_0 t + \dots$$

$$i_D(t) = I(v_{DS}(t), v_{GS}(t))$$


No harmonics (e.g. class A before saturation)

$$v_{DS}(t) = V_{DD} - R_L I_D(f_0) \cos \omega_0 t$$

$$i_D(t) = I_{DD} + I_D(f_0) \cos \omega_0 t$$

$$\rightarrow (i_D - I_{DD}) = -(v_{DS} - V_{DD}) / R_L$$

$$i_D(t) = I(v_{DS}(t), v_{GS}(t))$$

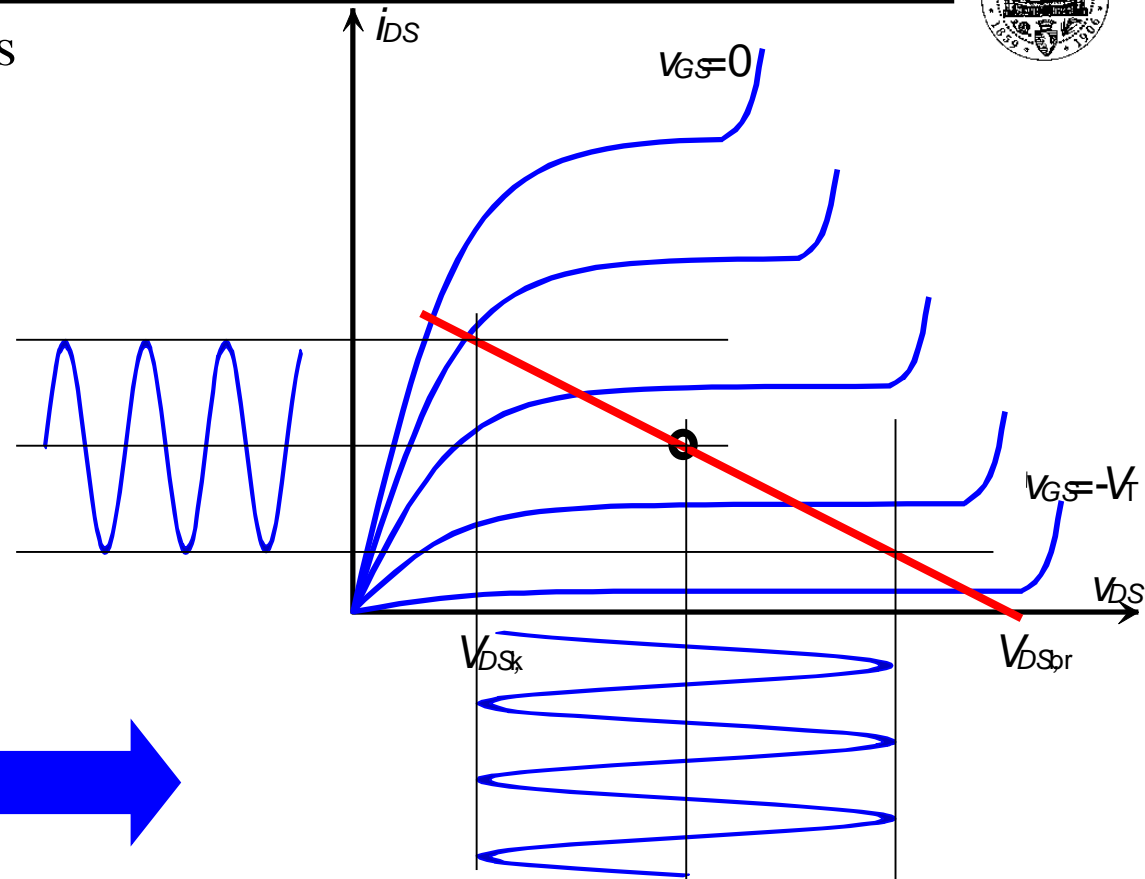


Class A amplifier analysis



- PA dynamics limited by
 - current saturation
 - triode (linear) region
 - cutoff
 - breakdown
- Optimum DC bias point:

$$I_{D,DC} = I_{DSS} / 2$$
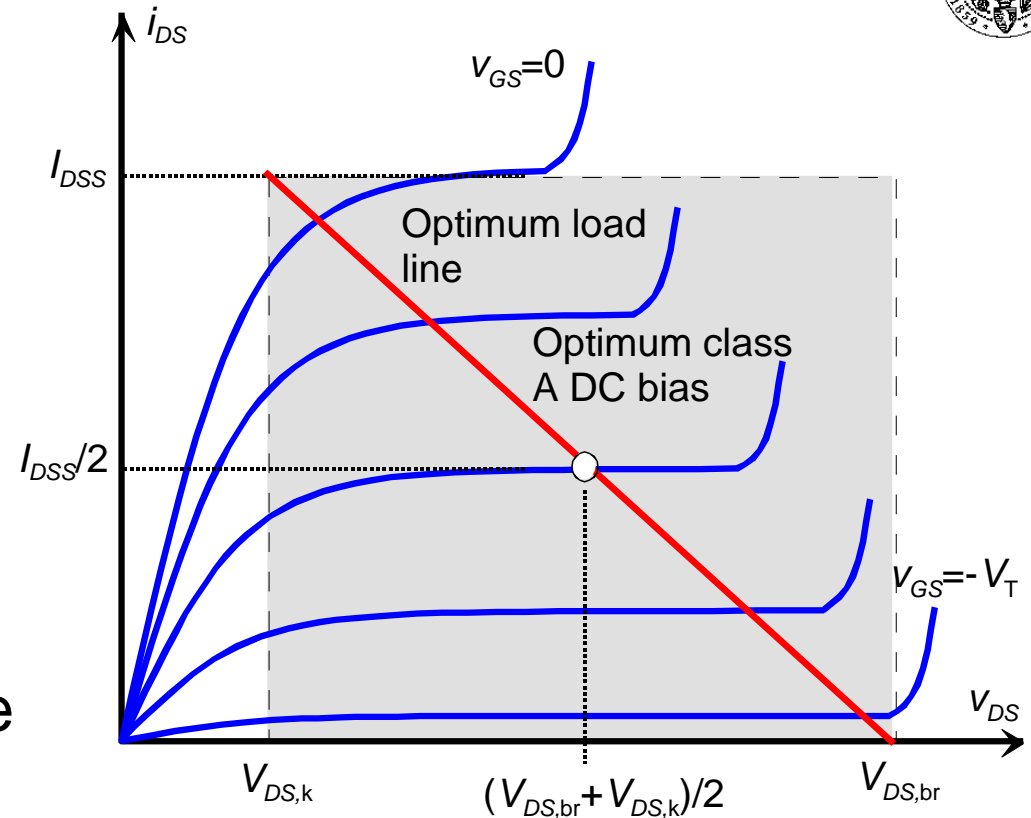
$$V_{DS,DC} \approx V_{DS,br} / 2$$
- Maximum (peak) AC voltage and current amplitude



$$v_{DS,M} = \frac{V_{DS,br} - V_{DS,k}}{2} \approx \frac{V_{DS,br}}{2} \quad i_{D,M} = \frac{I_{DSS}}{2}$$

Power amplifier gain



- Power amplifier power gain:

- Transducer: $G_{tr} = \frac{P_{out}}{P_{disp,in}}$

- Operational: $G_{op} = \frac{P_{out}}{P_{in}}$

- Available power ????


PA Efficiency & PAE



- Total DC power from bias $P_{DC} = V_{DC} I_{DC} \rightarrow$ no DC power to load!
- Only in class A amplifiers = to DC power without applied signal!
- Efficiency:
- Power-added efficiency (PAE):

$$\eta = \frac{P_{out}(f_0)}{P_{DC}}$$
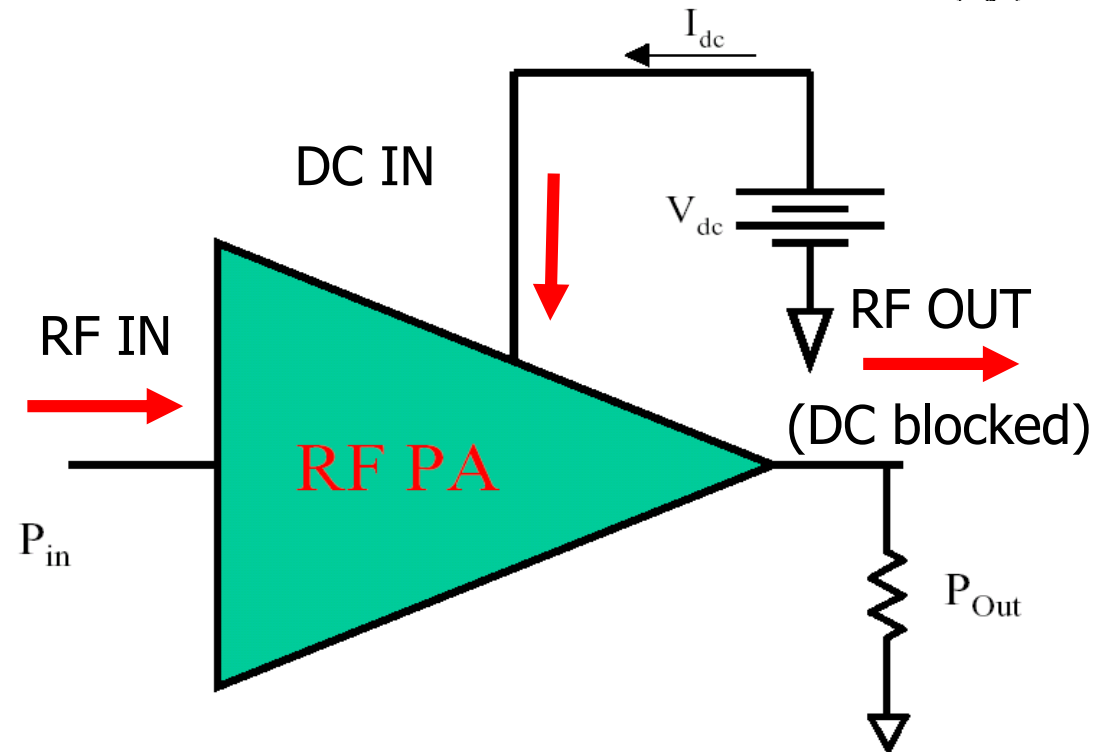
$$PAE = \frac{P_{out}(f_0) - P_{in}(f_0)}{P_{DC}} = \eta \left(1 - \frac{1}{G_{op}} \right)$$



Class A power, efficiency, waveforms



- Optimum load resistance


$$R_{Lo} = \frac{V_{DS,br}}{I_{DSS}}$$

- Average RF power to load

$$\begin{aligned} P_{RF,M} &= \frac{1}{2} v_{L,M} i_{L,M} \cos \theta = \\ &= \frac{1}{2} v_{DS,M} i_{D,M} \approx \frac{V_{DS,br} I_{DSS}}{8} \end{aligned}$$

- DC power & efficiency

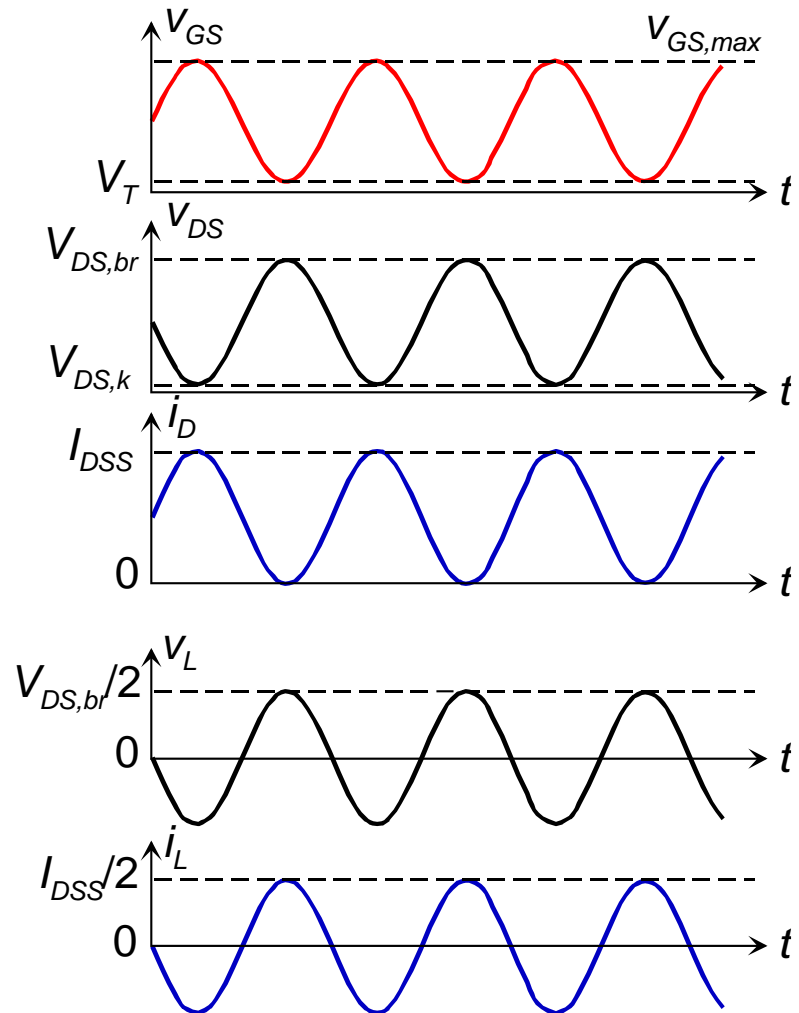
$$P_{DC} = \frac{V_{DS,br} I_{DSS}}{4} \quad \eta_A = \frac{P_{RF,M}}{P_{DC}} = 0.5$$



Class A design



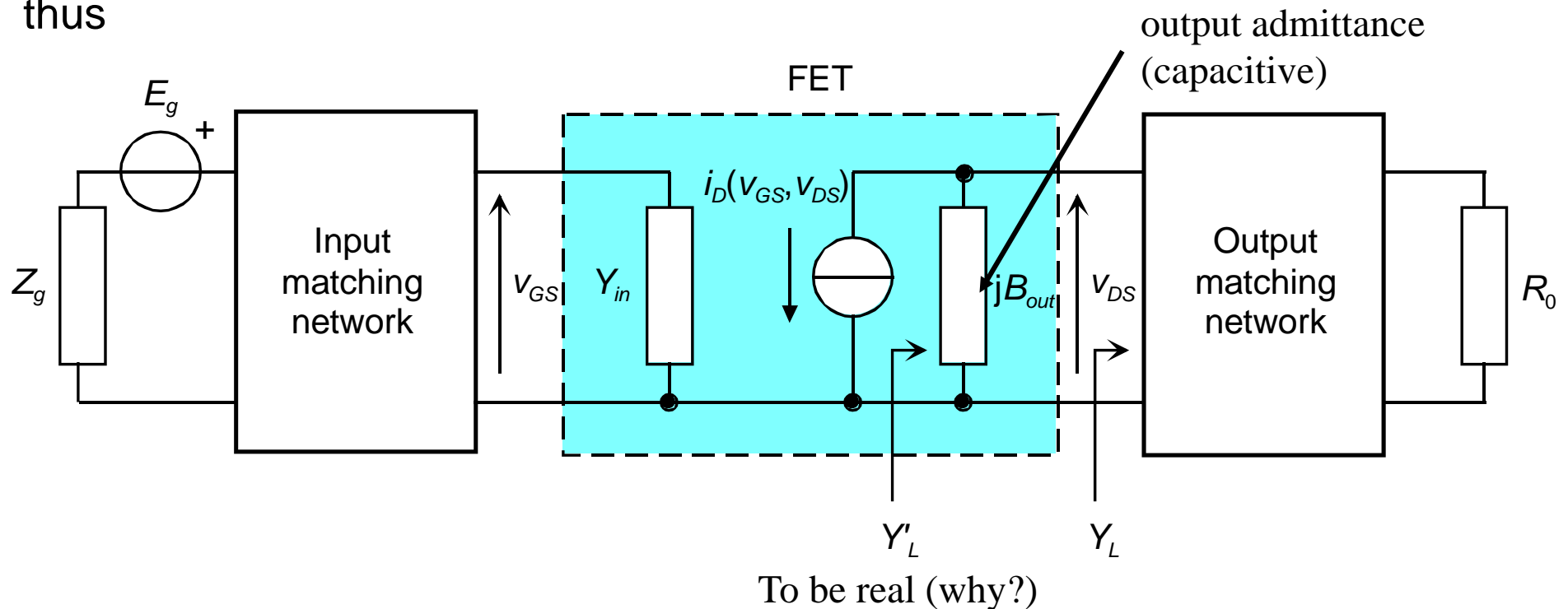- Optimum A bias point
- IMN: input matching (input admittance \rightarrow generator) $Y'_L = 1/R_{Lo}$
- OMN: transform load into $Y_L \rightarrow Y_L = 1/R_{Lo} - jB_{out}$
- thus



Deviation from optimum load






$$P_{RF} = \frac{1}{2} i_{L,M}^2 R'_L$$


$$= P_{RF,M} \frac{R'_L}{R_{Lo}}$$

$$P_{RF} = \frac{1}{2} v_{L,M}^2 \frac{1}{R'_L}$$


$$= P_{RF,M} \frac{R_{Lo}}{R'_L}$$

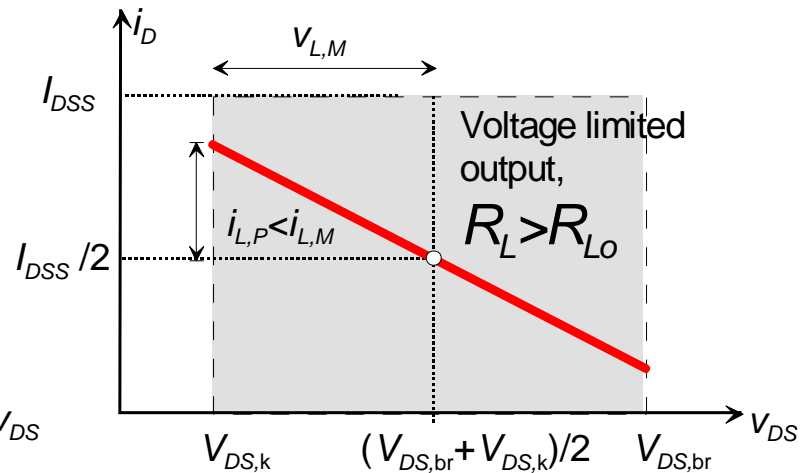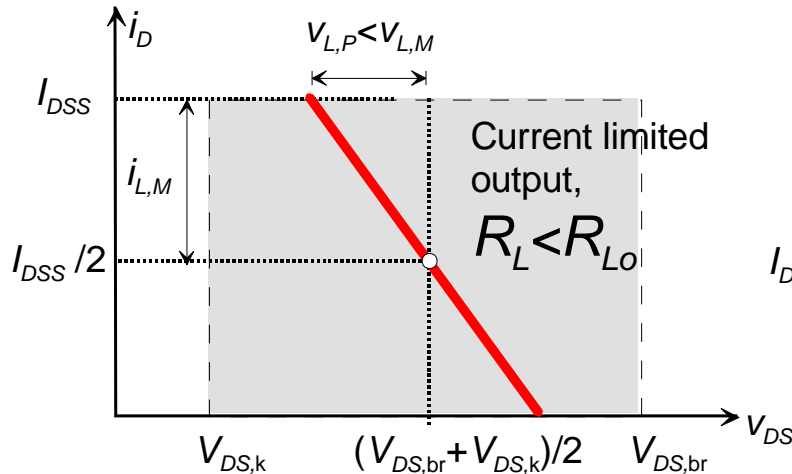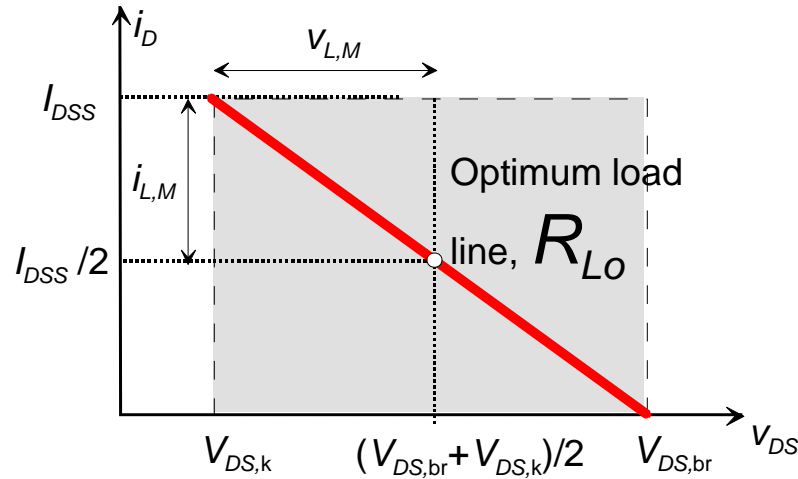


Power vs. optimum, res. load

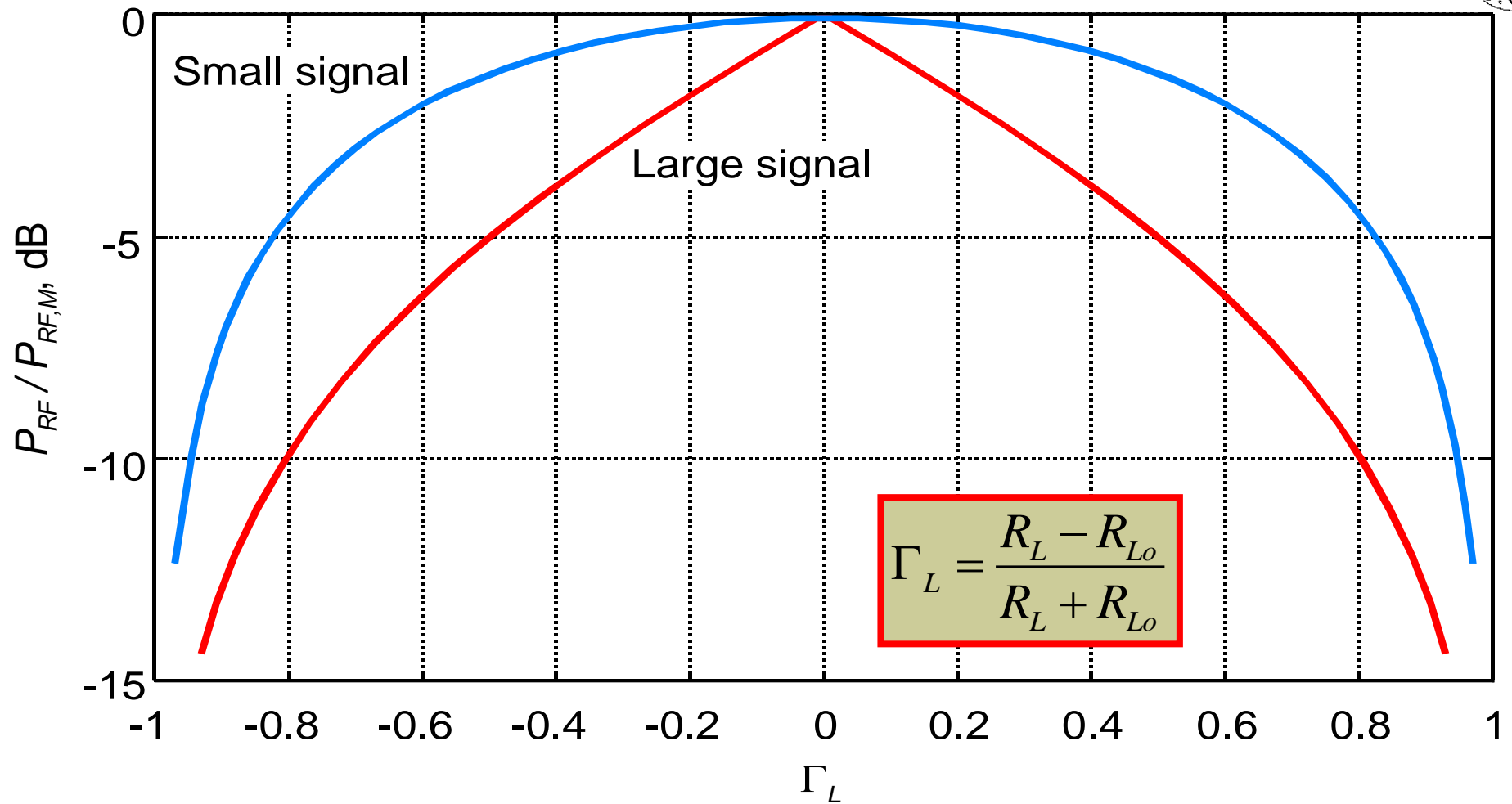

Deviations on Pin-Pout

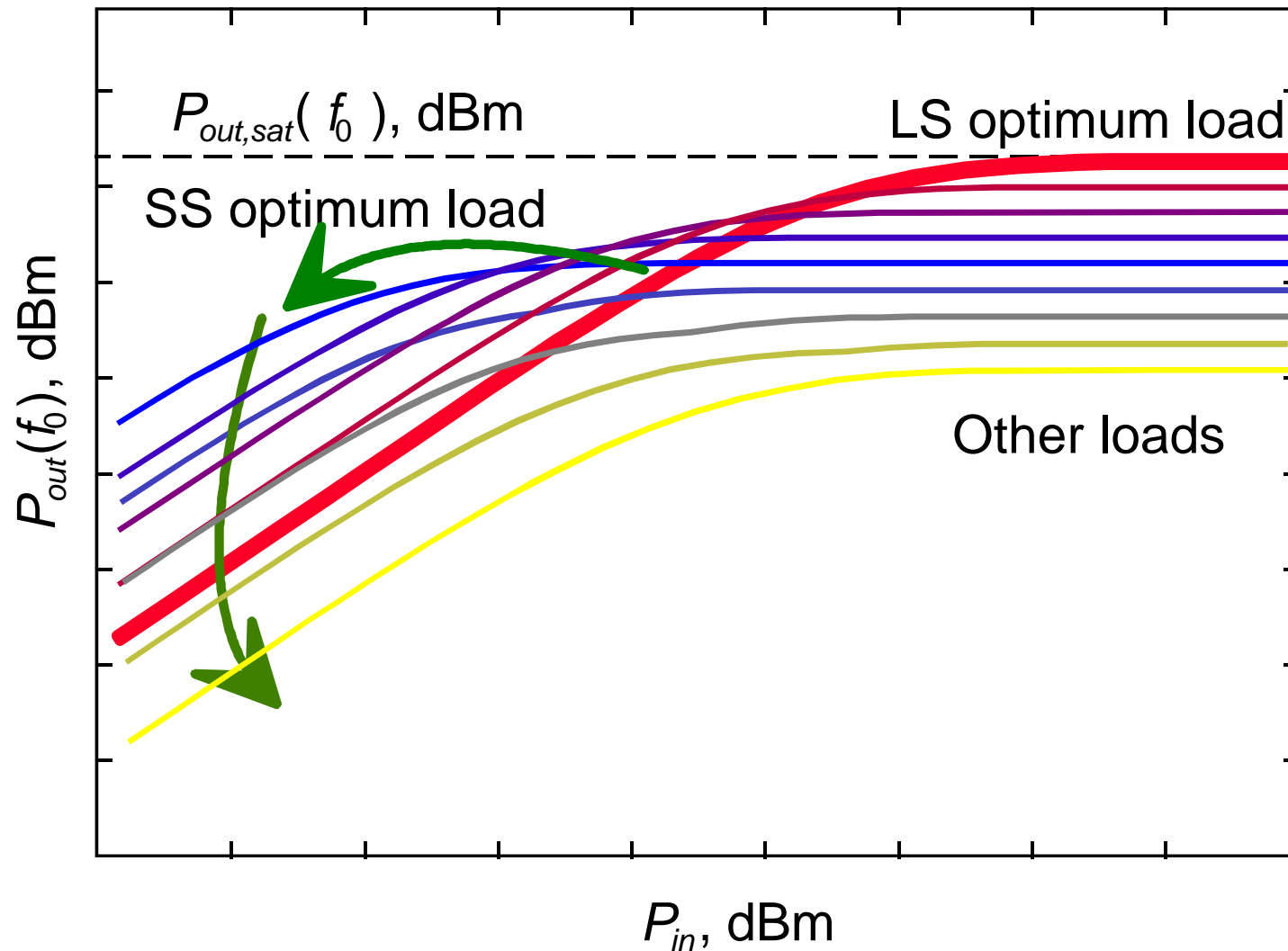

Class A Load-Pull (Cripps)

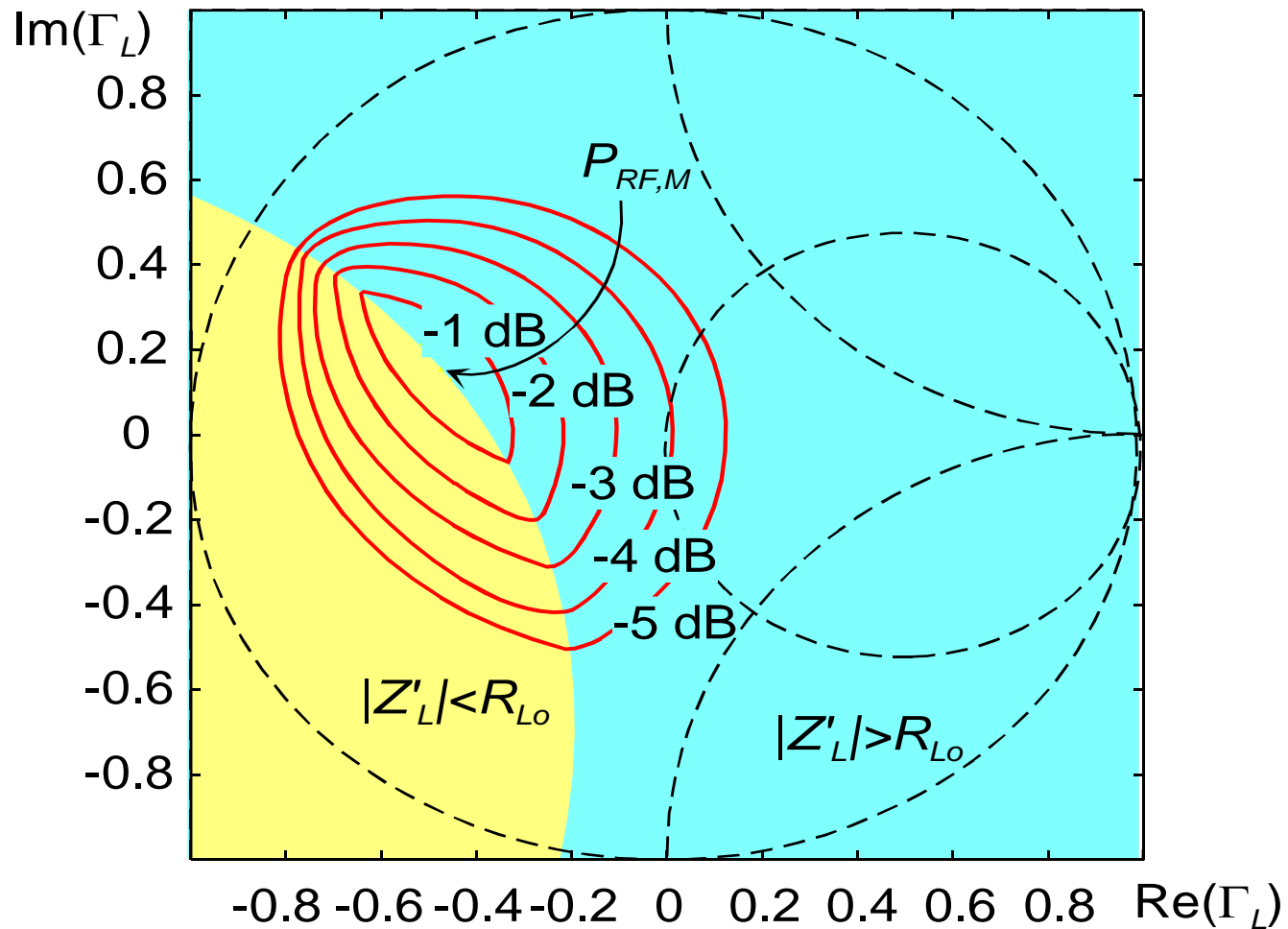

Load pull design




- The load-pull procedure can be carried out experimentally by changing the load seen by the device with a mechanical or electronic tuner; in this way the optimum load impedance can be detected, also for other parameters (IMPs, efficiency etc.)
- Also a source-pull approach is feasible, but less effective at least in FETs (low sensitivity with respect to source impedance)

Power amplifier performances I



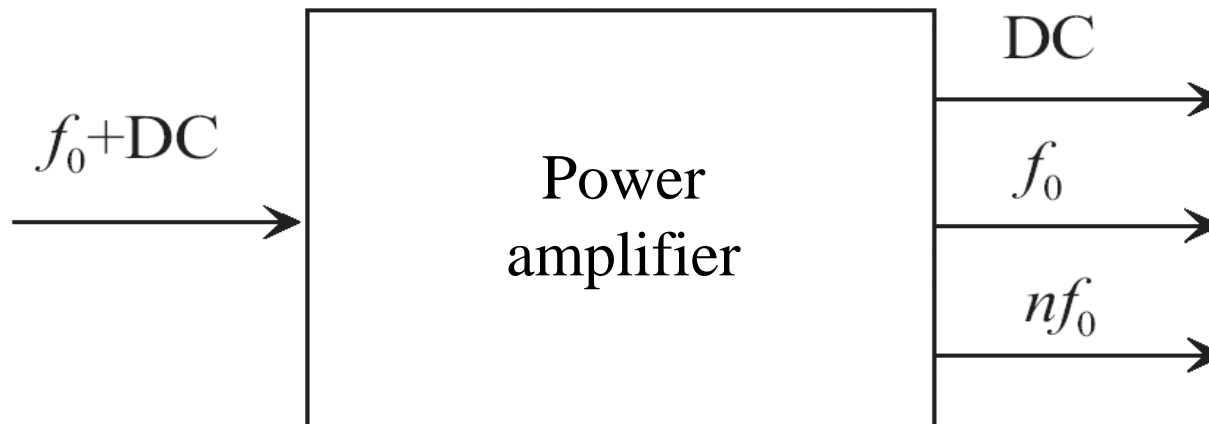- Power amplifier: *quasi-linear system (class A)*
- Single-frequency input + DC (bias): output @ fundamental + DC + harmonics



Power amplifier performances II



- Power amplifier power gain:


- Transducer: $G_{tr} = \frac{P_{out}}{P_{av,in}}$

- Operational: $G_{op} = \frac{P_{out}}{P_{in}}$

- Conversion (fundamental \rightarrow harmonics & DC; defined in small-signal):

$$P_{out}(nf_0) = K_n P_{in}^n(f_0)$$

Single-tone Pin-Pout

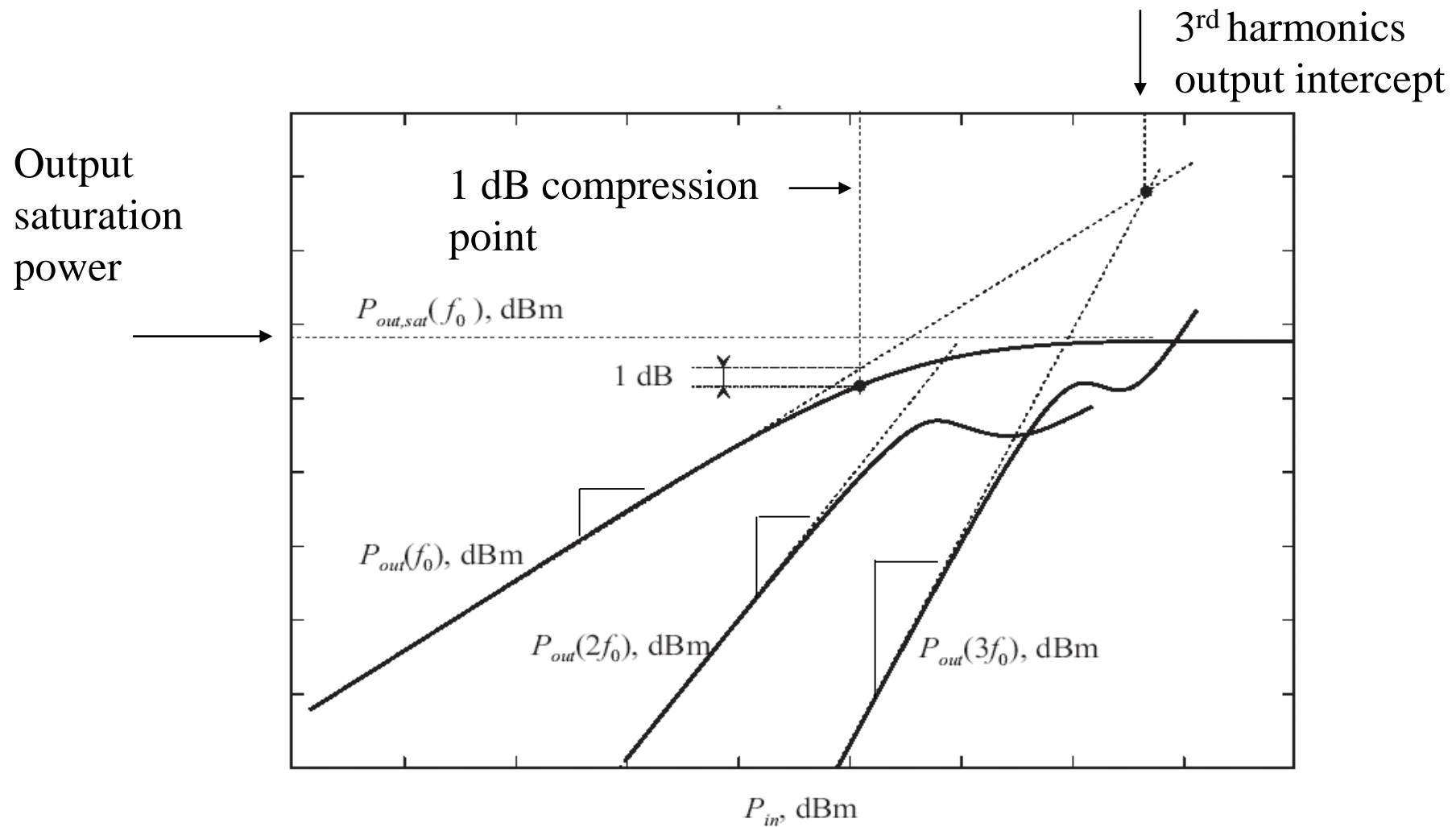

3rd, 5th... harmonics intercept



- Output power @ nth harmonic = linear output power at fundamental


$$G_{op,SS} P_{in,n} = K_n P_{in,n}^n$$

- Corresponding input intercept power:


$$P_{in,n} = \left(\frac{G_{op,SS}}{K_n} \right)^{\frac{1}{n-1}}$$

- Sometimes defined with reference to output power.

Pout and gain vs. Pin

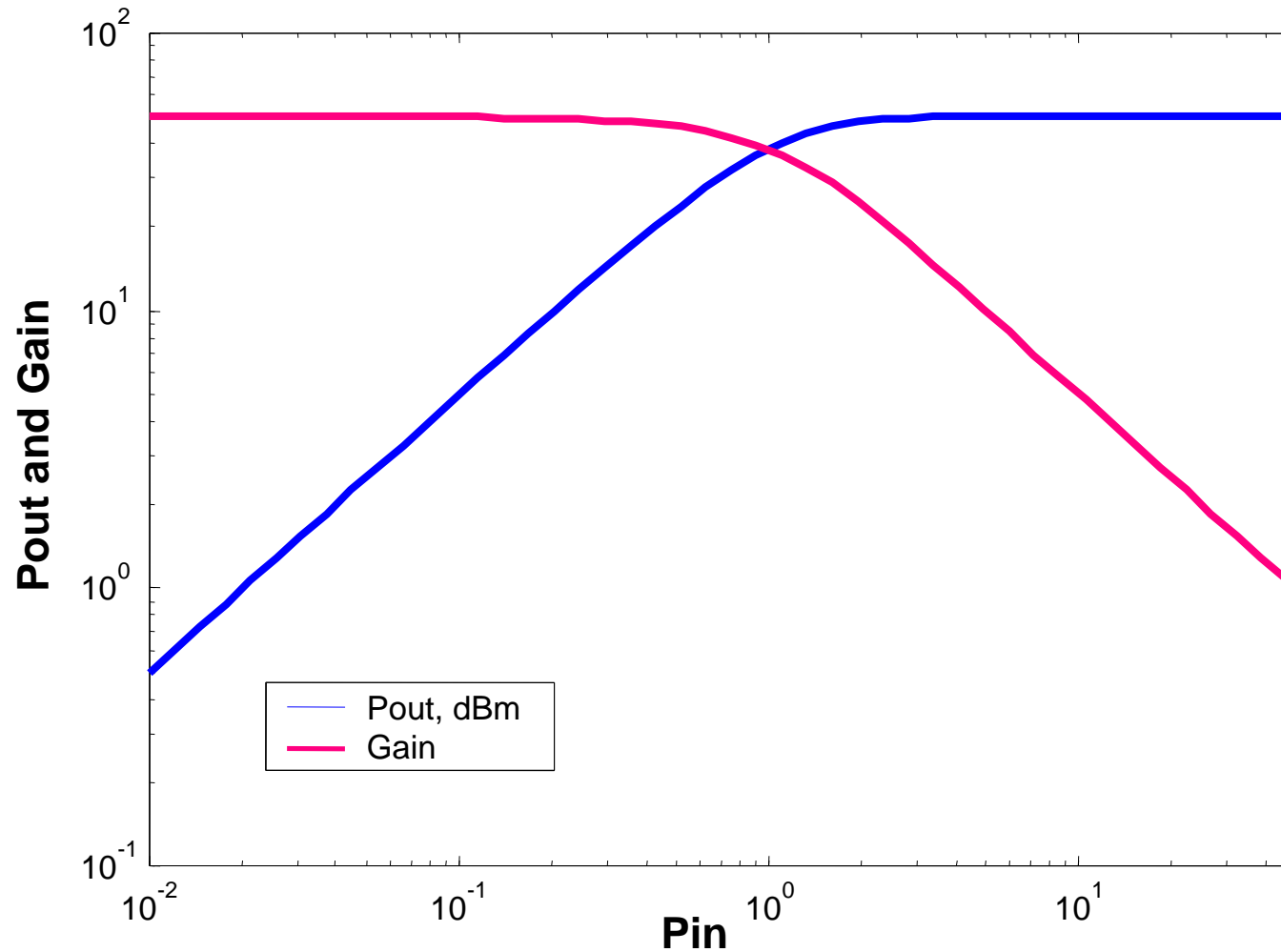


Efficiency & PAE vs. P_{in}

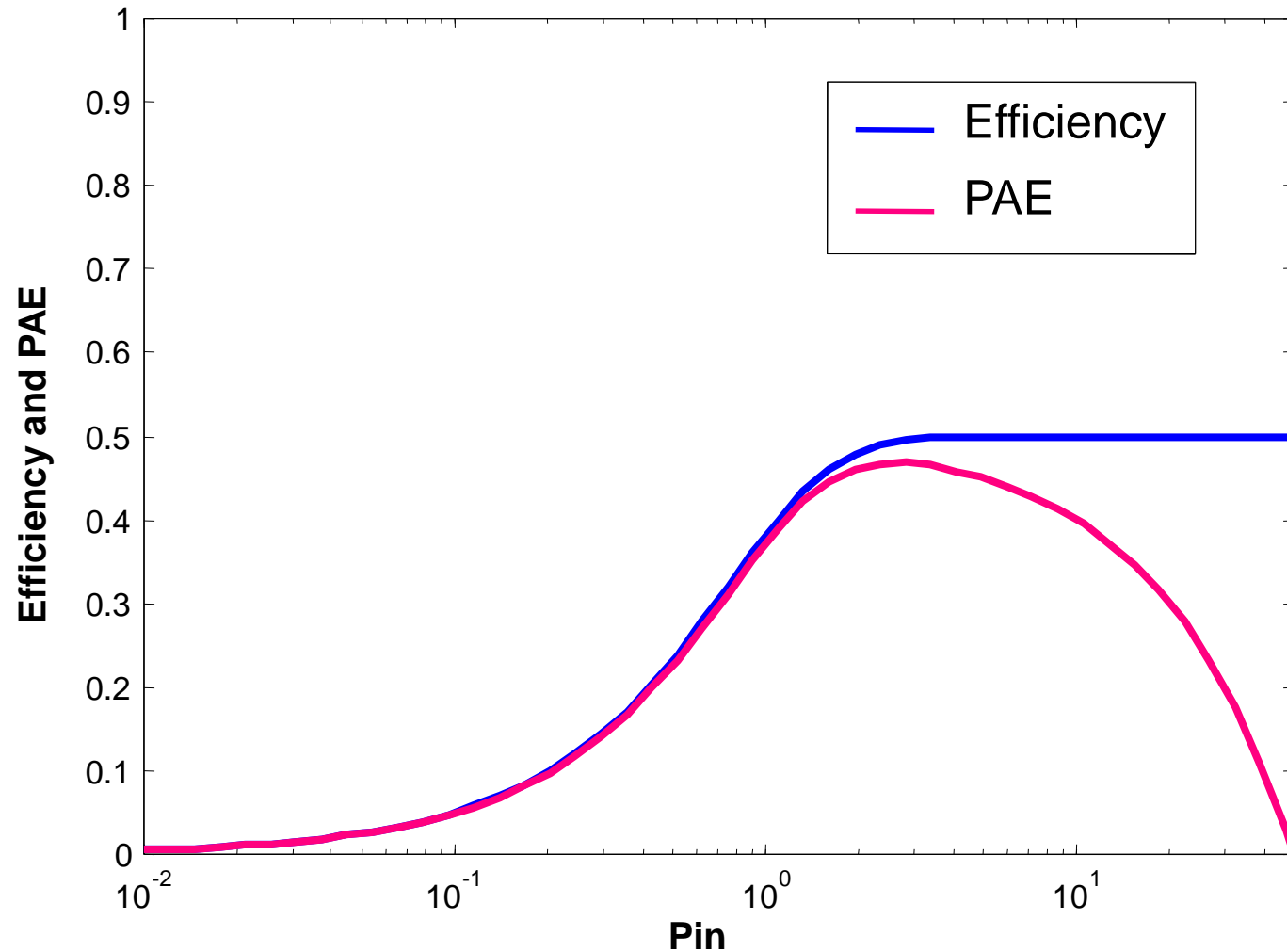


Two-tone PA operation I



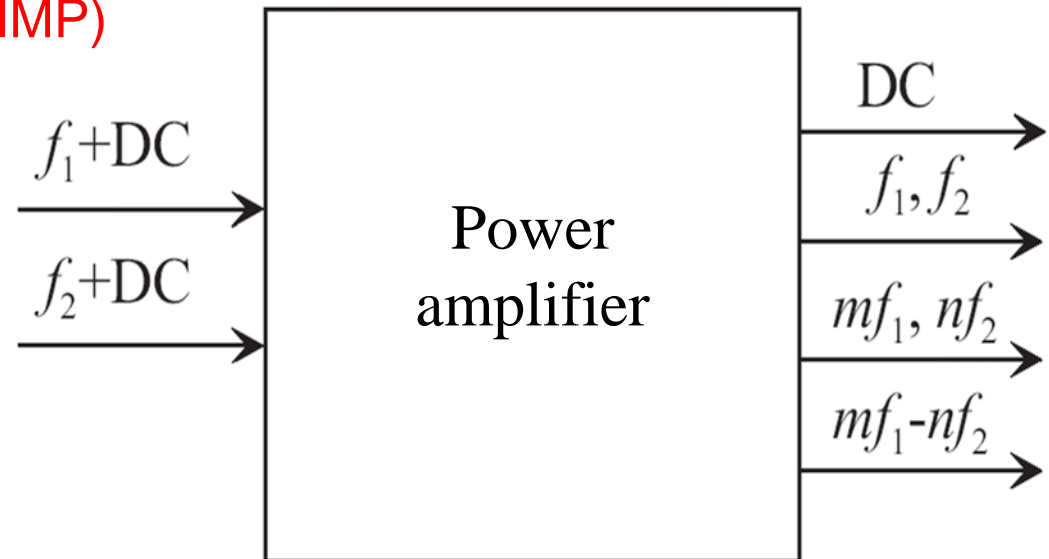- Rationale: two-tone operation **simulates** narrowband operation on a continuous band $f_1 - f_2$
- PA output:
 - fundamentals + DC
 - harmonics of two tones
 - Intermodulation products (IMP)



Two-tone PA operation II

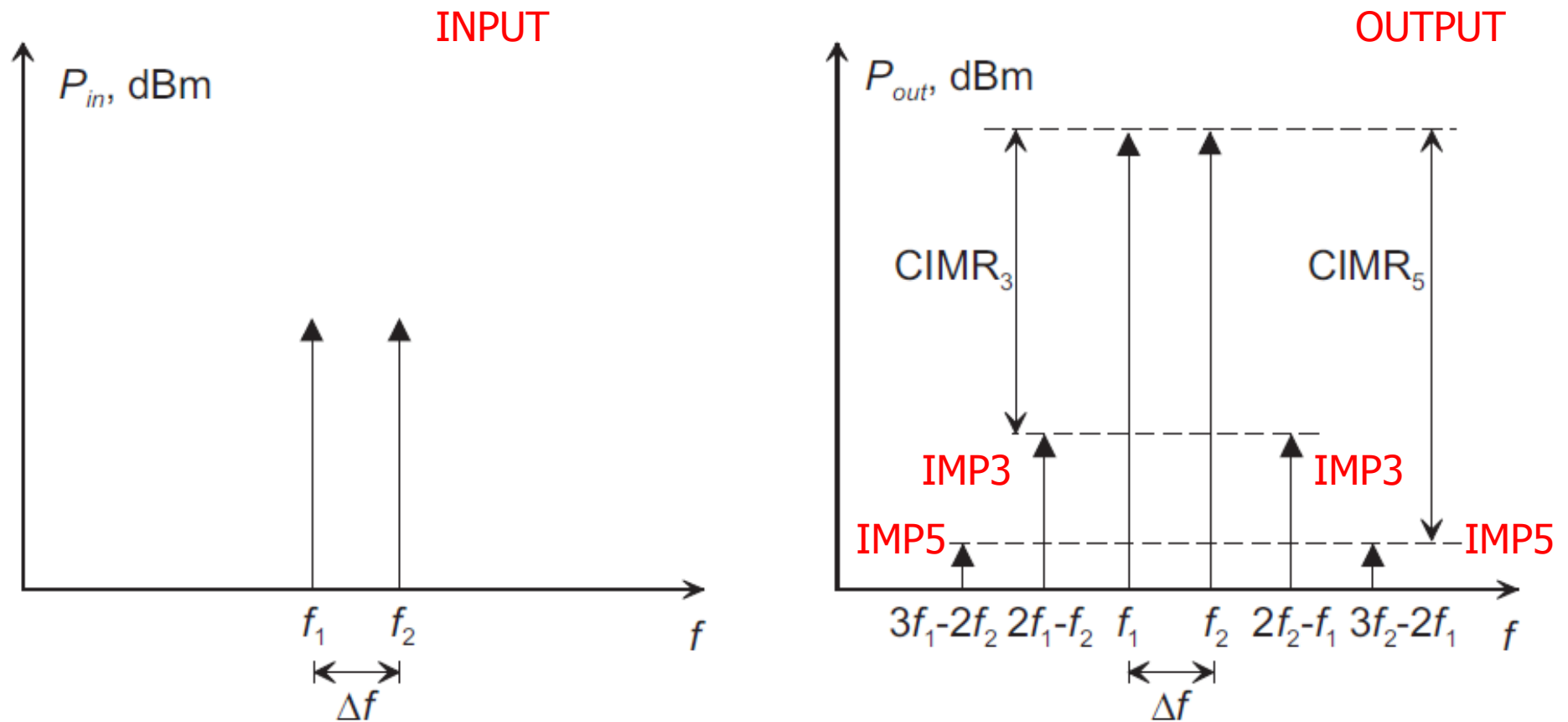

3rd order IMPs



- Intermodulation products $mf_1 \pm nf_2$ falling close to the input tones \rightarrow within the same bandwidth (potentially) \rightarrow interferers to nearby channel

$$f_a = 2f_1 - f_2 = f_1 - \Delta f$$

$$f_b = 2f_2 - f_1 = f_2 + \Delta f$$

with


$$f_2 = f_1 + \Delta f$$

Two-tone Intermodulation Test




- Standard procedure for intermodulation experimental evaluation of power amplifier
- Input signal: two tones with same power, small spacing (e.g. 10 MHz at RF)
- Output: fundamental tones + intermodulation products of different order
- If the PA is a narrowband system the two output IMPs have the same power

Carrier-to-IM3 Ratio (CIM3)

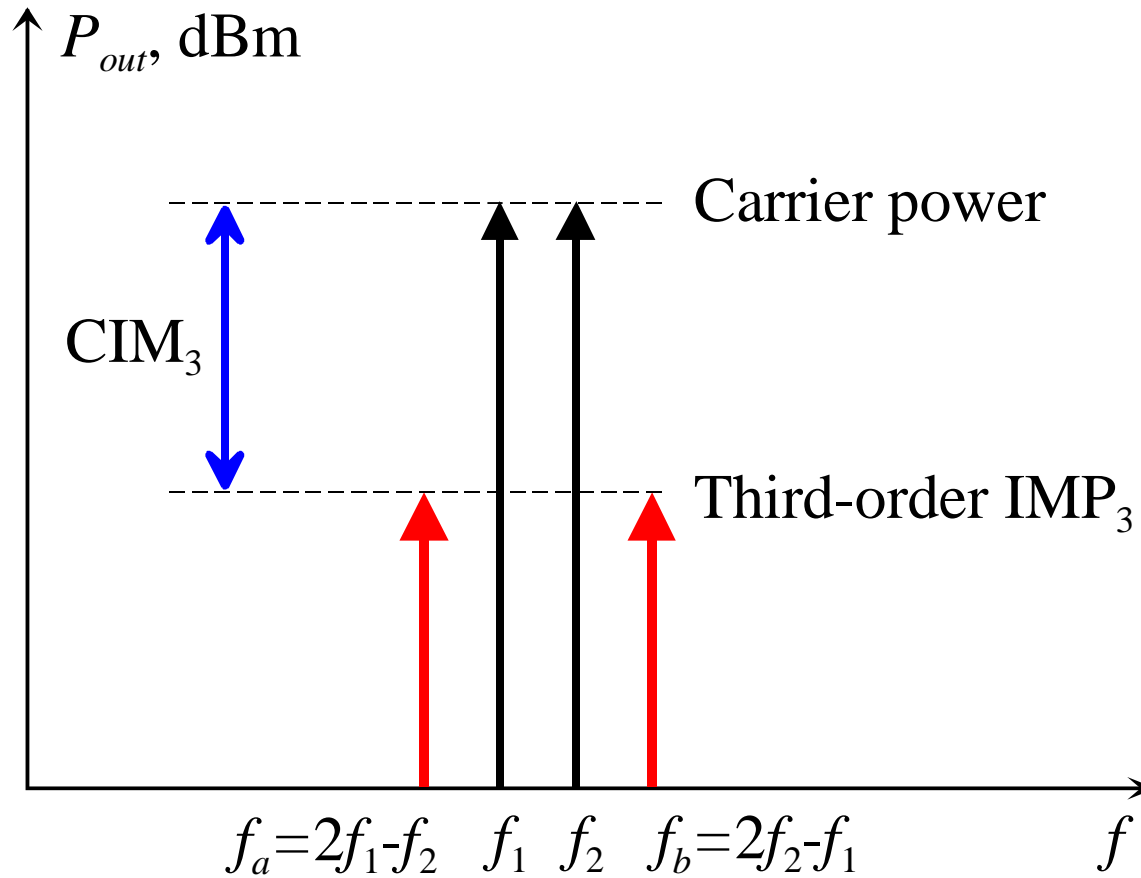

$$\text{CIM}_3 = \frac{P_{out}(f_0)}{P_{\text{int},3}}$$

3rd order IMP intercept – IP_3

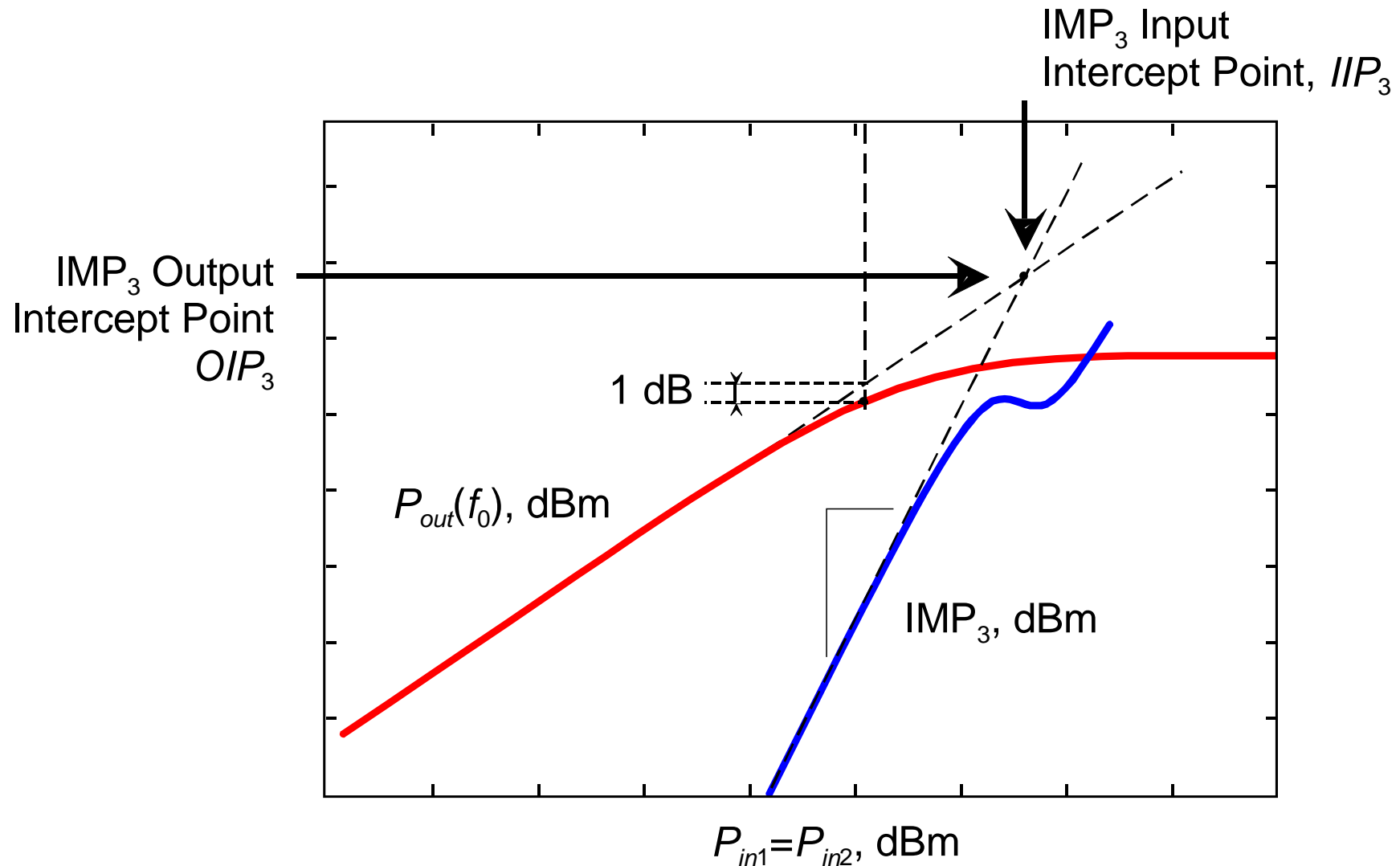


IP₃ from SS measurements I



- The third-order intercept cannot be measured directly, but can be extrapolated from low-power measurements; in fact:

$$\underbrace{P_{\text{IM3,out}}}_{\text{IM3 power for an arbitrary input power } P_{in}} = \underbrace{GP_{in}}_{\text{output power in linearity}} \times \left(\frac{P_{in}}{IIP_3} \right)^2 \Rightarrow IIP_3 = \frac{(P_{in})^{3/2} G^{1/2}}{(P_{\text{IM3,out}})^{1/2}}$$


 IMP3 input intercept point


- output IP₃:

$$OIP_3 = G \times IIP_3 = \frac{(P_{in})^{3/2} G^{3/2}}{(P_{\text{IM3,out}})^{1/2}} = \frac{(P_{out})^{3/2}}{(P_{\text{IM3,out}})^{1/2}}$$

IP₃ from SS measurements II




- Log scale: $OIP_3|_{\text{dBm}} = \frac{3}{2} P_{out}|_{\text{dBm}} - \frac{1}{2} P_{IM3,out}|_{\text{dBm}}$

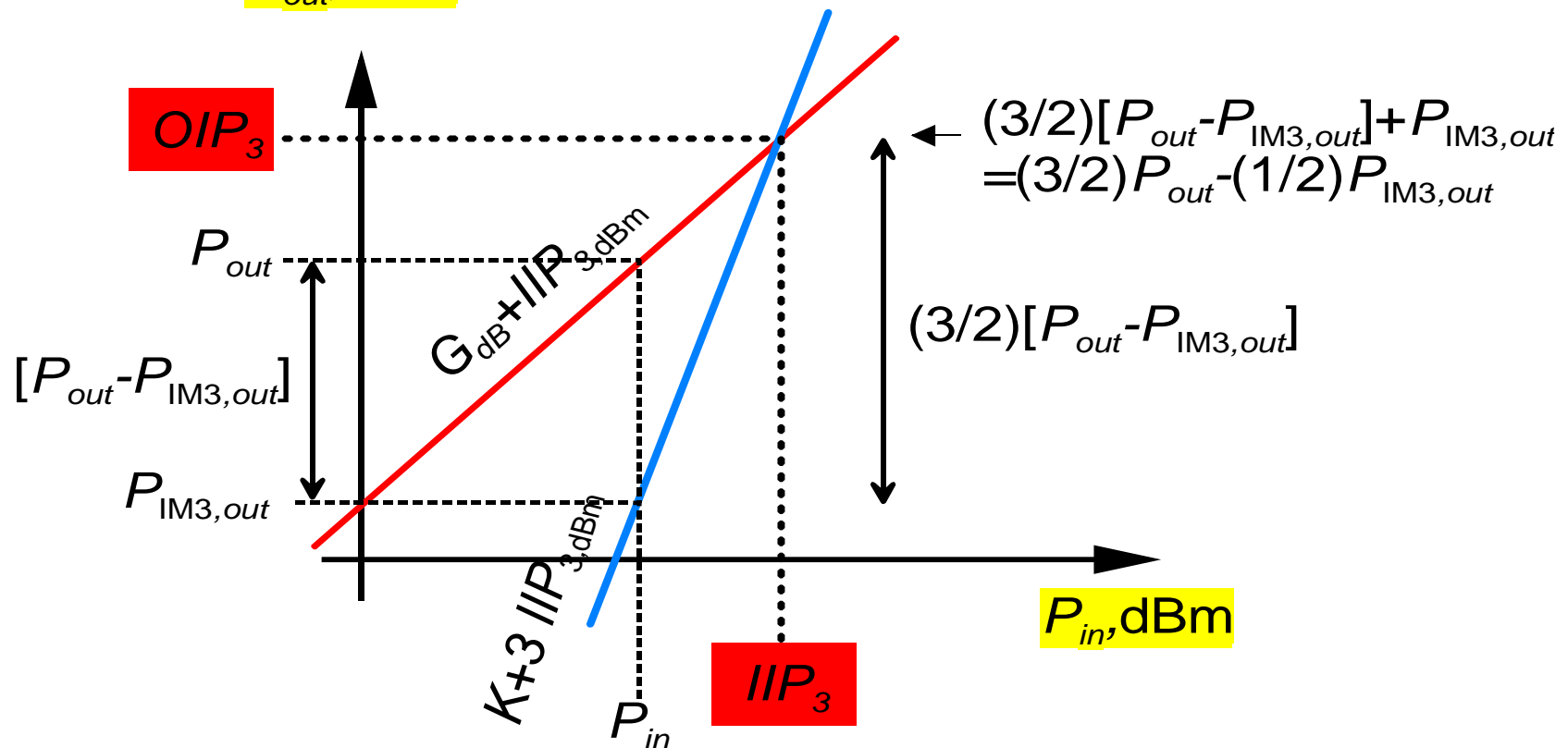


Intermodulation in a real channel



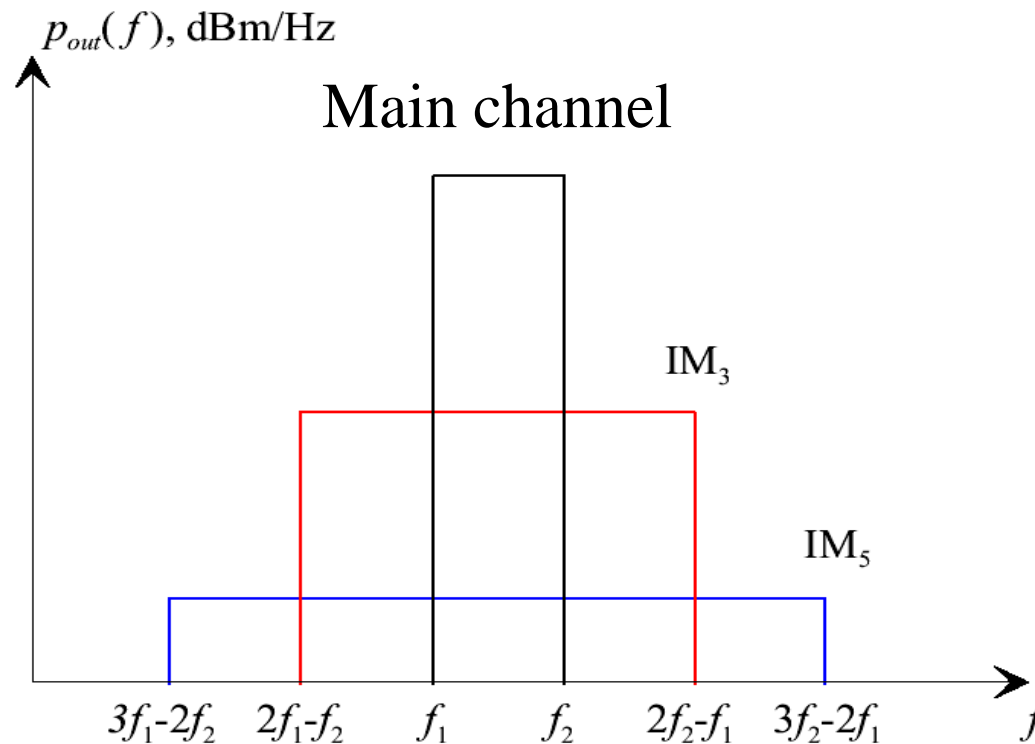- Two-tone excitation \rightarrow IMP3, IMP5 etc. as single tones
- Narrowband (continuous) excitation \rightarrow IMP3, IMP5 etc. as (wider) band signals entering nearby channels



“Spectral Regrowth”

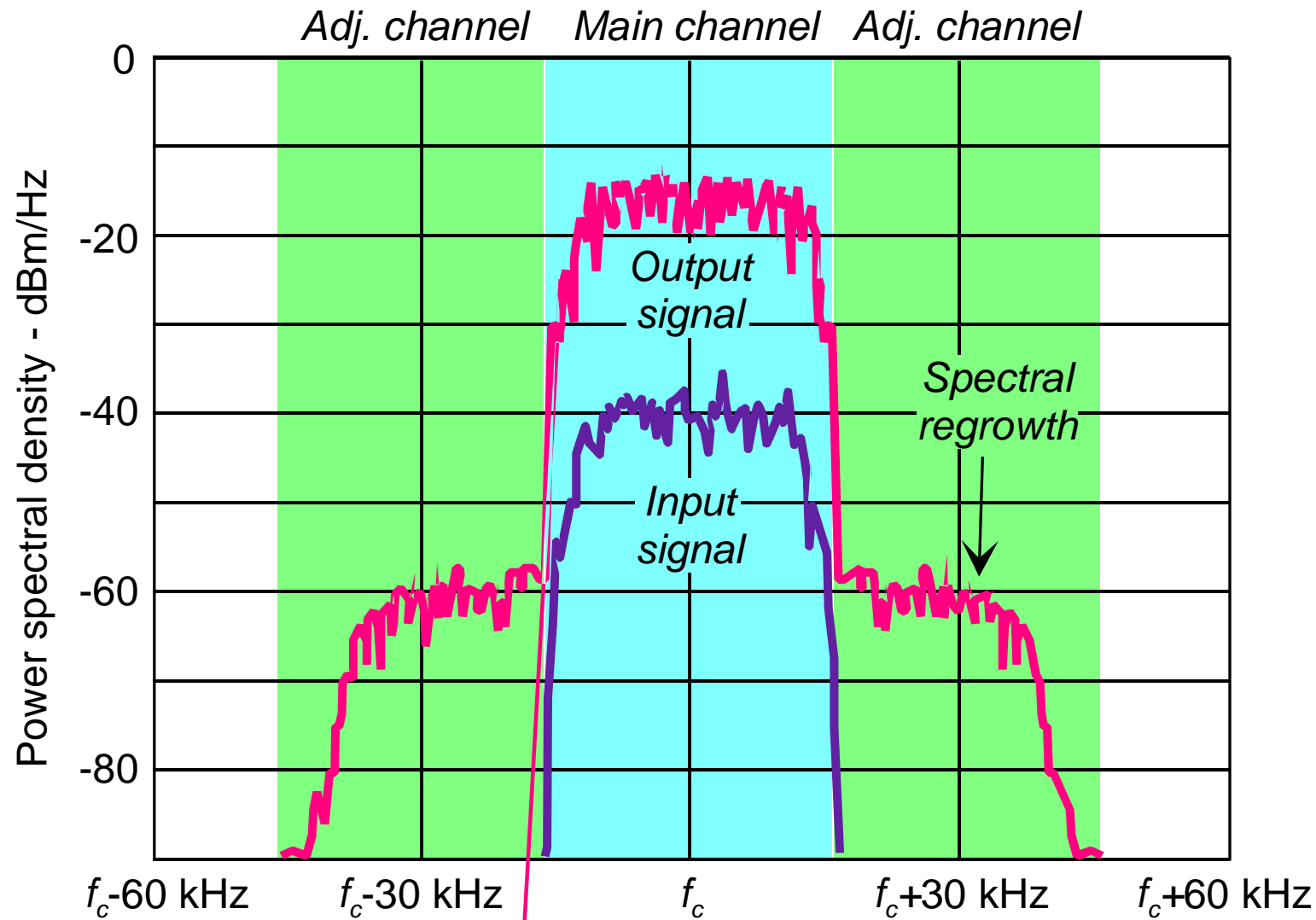

Adjacent Channel Power Ratio



- The ACPR is a quantitative measure of spectral regrowth as an interference to a nearby channel
- ACPR definition (MC → Main Channel; C_k → k-th adjacent channel):

$$\text{ACPR}_k = \frac{\int_{MC} p_{out}(f) df}{\int_{C_k} p_{out}(f) df}$$

- ACPR sensitive to the signal format:
 - Constant envelope (e.g. analog FM) → less sensitive
 - Variable envelope (e.g. multilevel digital, see later) → more sensitive

Dynamic range - qualitative definition



- For an amplifier (power, small signal, low noise...) the dynamic range (also called Spurious Free Dynamic Range, SFDR) is the input power range providing operation “within specs”
- SFDR limits:
 - Lower limit: related to noise → **minimum input power able to provide at the amplifier output the required signal over noise ratio (SNR)**
 - Upper limit: related to distortion → **maximum input power providing acceptable distortion at amplifier output**