

# Coupled line components: directional couplers and power dividers

***Microwave Electronics***

**Giovanni Ghione, Marco Pirola**

**Politecnico di Torino, DET**




# Outline

---




- **Coupled lines**
- Directional couplers
- Power dividers and combiners

# Coupled lines

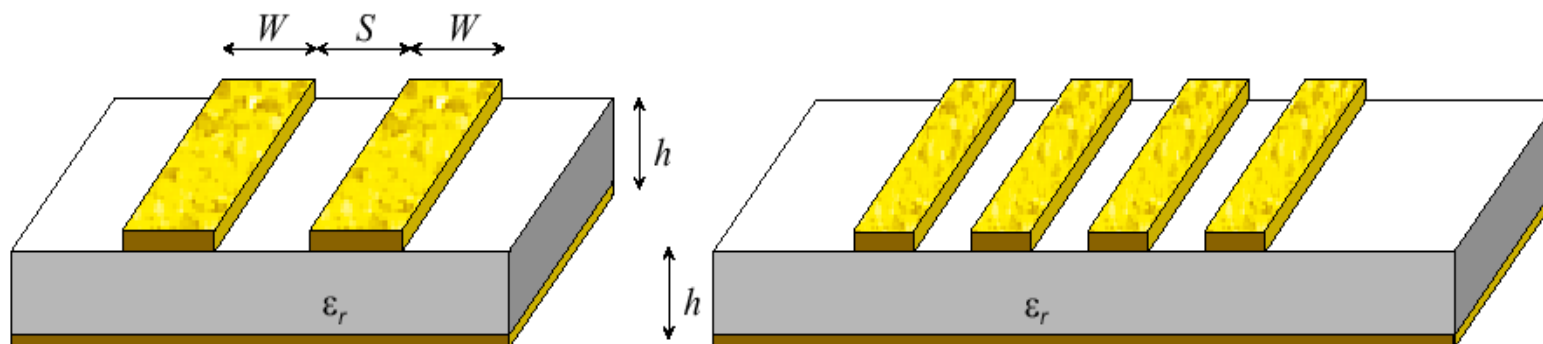


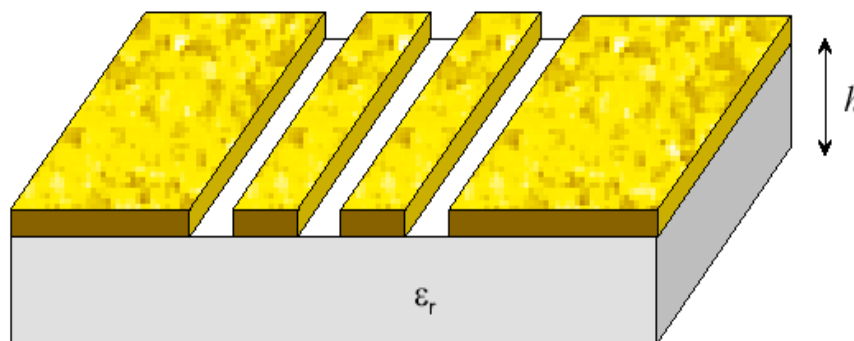Two and four-conductor microstrip coupled lines



Coupled two-conductor coplanar lines
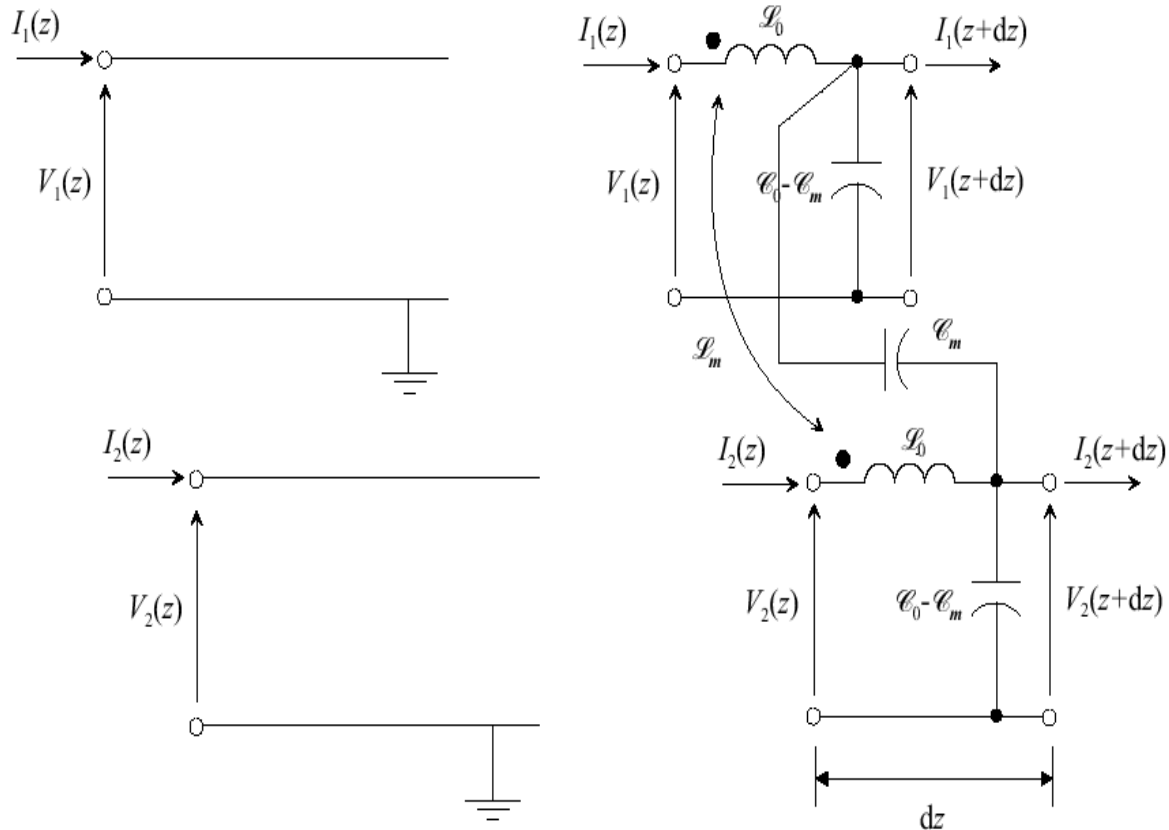
# Equivalent circuit of lossless symmetric coupled lines



- Capacitance matrix

$$\mathbf{C} = \begin{pmatrix} \mathcal{C}_0 & -\mathcal{C}_m \\ -\mathcal{C}_m & \mathcal{C}_0 \end{pmatrix}$$

- Inductance matrix


$$\mathbf{L} = \begin{pmatrix} \mathcal{L}_0 & \mathcal{L}_m \\ \mathcal{L}_m & \mathcal{L}_0 \end{pmatrix}.$$

- A line with  $N$  conductors + ground carries  $N$  quasi-TEM propagation modes
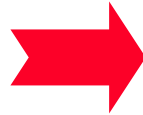
# Generalized telegraphers' equation and modal solution




- Voltage and current vectors on the two lines




$$\underline{V} = \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}, \quad \underline{I} = \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

- Generalized telegraphers' equations

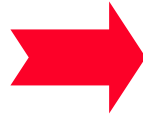

$$\begin{aligned} \frac{d\underline{V}(z)}{dz} &= j\omega \mathbf{L} \underline{I} \\ \frac{d\underline{I}(z)}{dz} &= j\omega \mathbf{C} \underline{V} \end{aligned}$$

- Second-order system

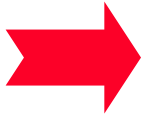

$$\frac{d^2 \underline{V}(z)}{dz^2} = -\omega^2 \mathbf{L} \mathbf{C} \underline{V}$$

- Trial solutions




$$\underline{V}(z) = \underline{V}_0 \exp(-j\beta z)$$
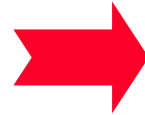
# Solutions in terms of even (p) and odd (d) modes



- Two modes, even and odd (p, d) with different propagation constants



$$(\beta^2 \mathbf{I} - \omega^2 \mathbf{LC}) \underline{V}_0 = 0$$




- Each mode has a **progressive** and **regressive** wave

$$\beta_1 = \beta_e = \frac{\omega}{c_0} \sqrt{\frac{C_e}{C_{ea}}}$$
$$\beta_2 = \beta_o = \frac{\omega}{c_0} \sqrt{\frac{C_o}{C_{oa}}}$$


$$C_e = C_0 - C_m$$
$$C_o = C_0 + C_m$$

- Even mode: both line have **the same voltage**
- Odd mode: the line voltages are **equal but opposite**
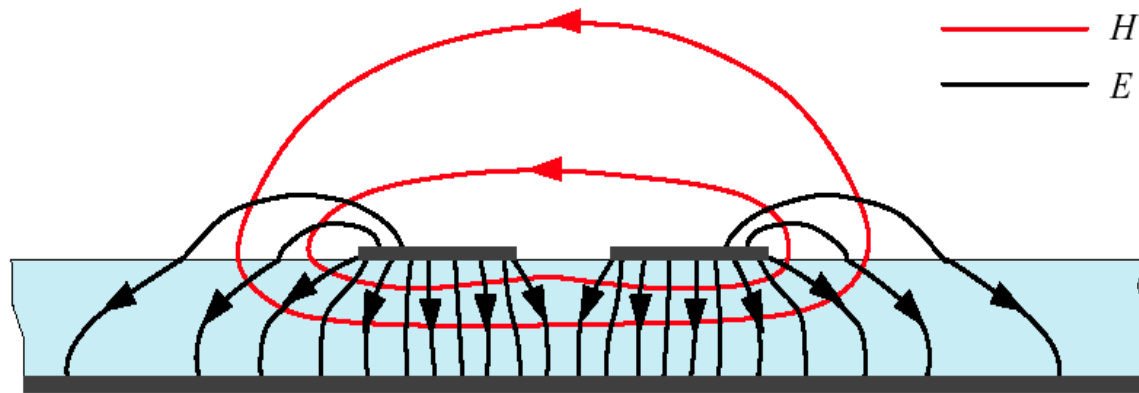
# Even and odd mode topology in coupled lines



*Even mode*

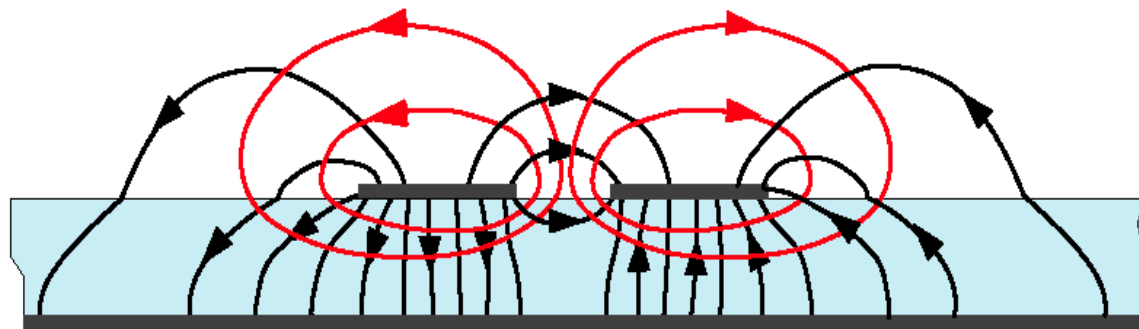

*Odd mode*

# Even (p) and odd (d) mode parameters



- Effective permittivity:

$$\epsilon_{\text{eff}e} = \frac{C_e}{C_{ea}}$$

$$\epsilon_{\text{eff}o} = \frac{C_o}{C_{oa}}$$

- Characteristic impedance:

$$Z_{0e} = \frac{1}{c_0 \sqrt{C_e C_{ea}}} = \frac{Z_{0ea}}{\sqrt{\epsilon_{\text{eff}e}}}$$



$$Z_{0o} = \frac{1}{c_0 \sqrt{C_o C_{oa}}} = \frac{Z_{0oa}}{\sqrt{\epsilon_{\text{eff}o}}}$$

- Since the odd mode capacitance > than the even mode capacitance the odd mode impedance < than the even mode impedance ( $Z_0$  is the uncoupled line impedance):


$$Z_{0e} \geq Z_0 \geq Z_{0o}$$



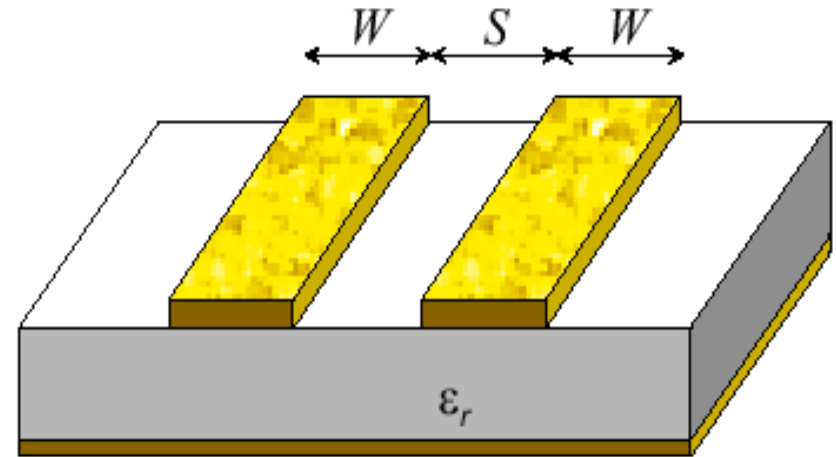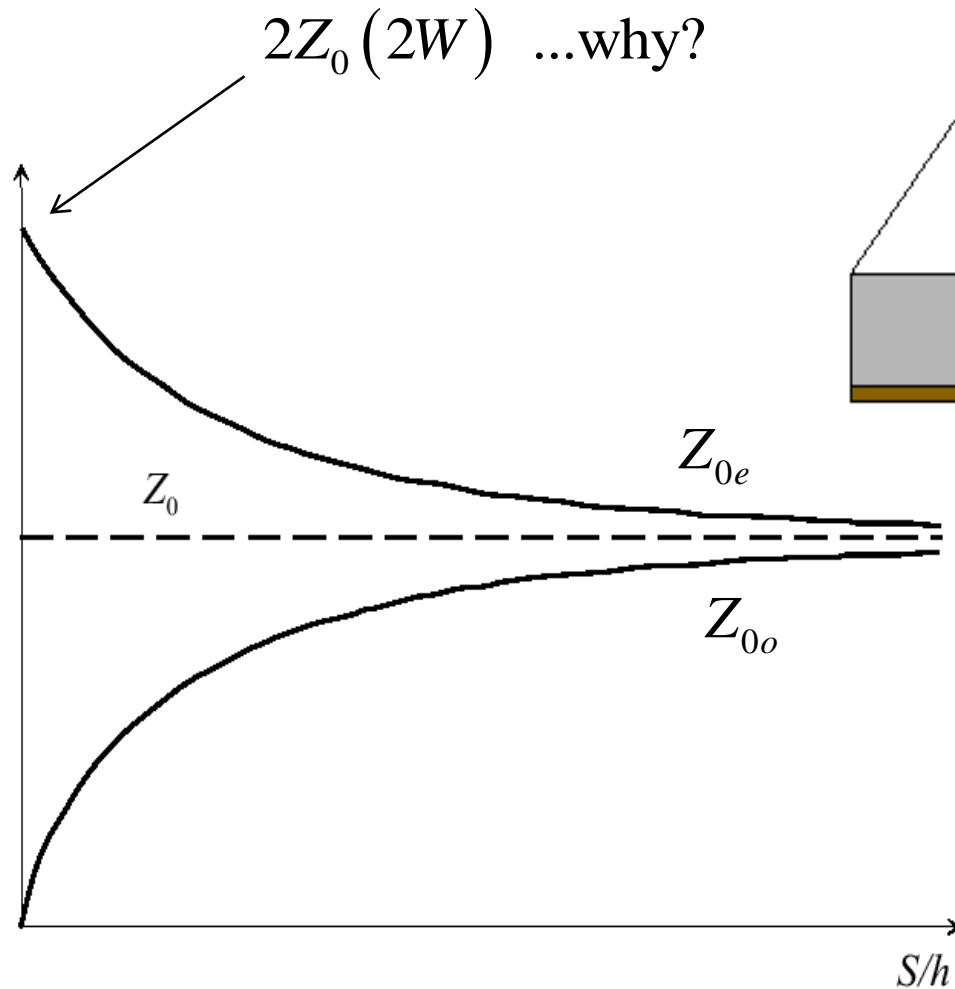
# Even and odd mode parameters vs. line spacing $S$


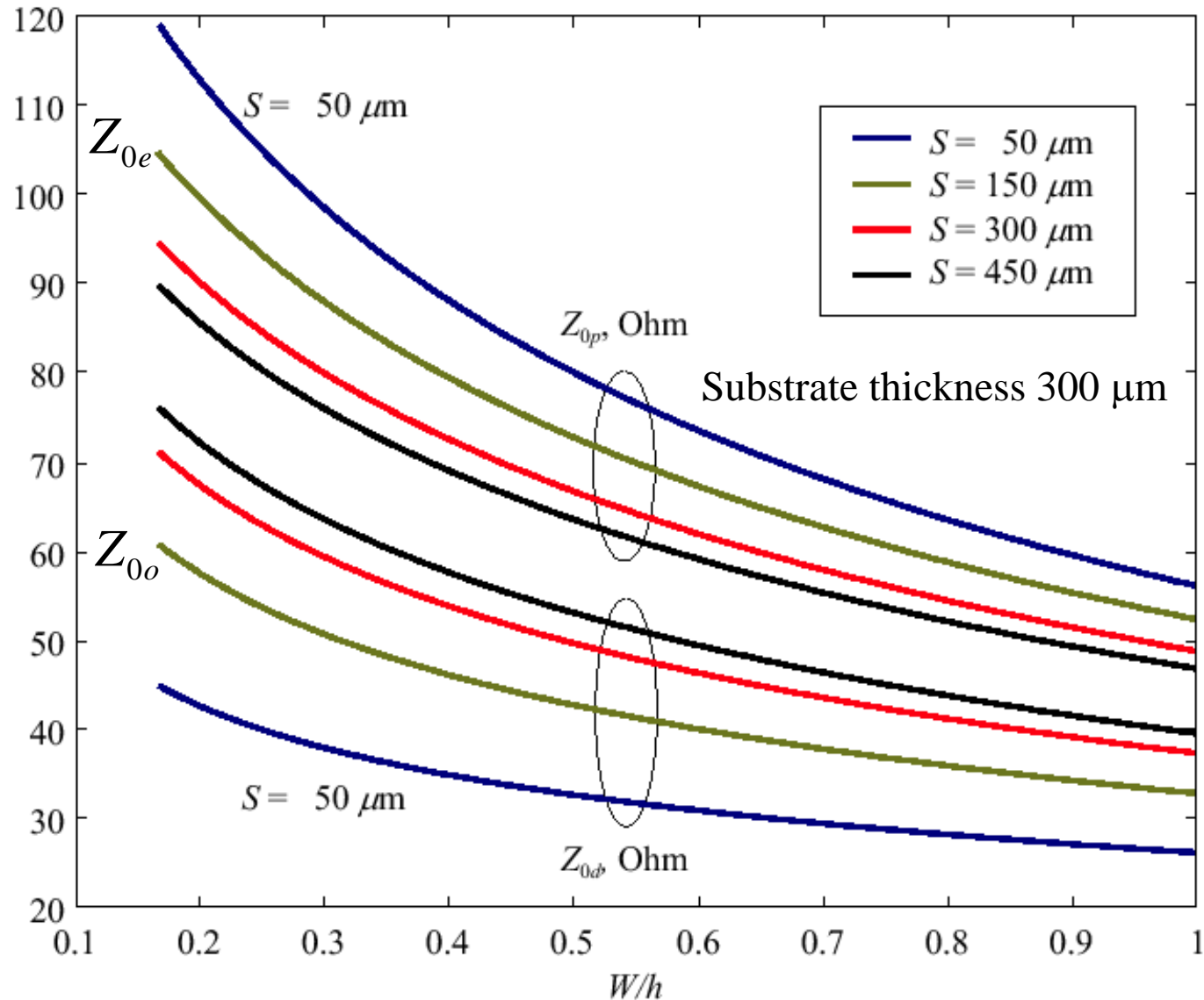
# Coupled microstrip impedances (on GaAs, $\epsilon=13$ )


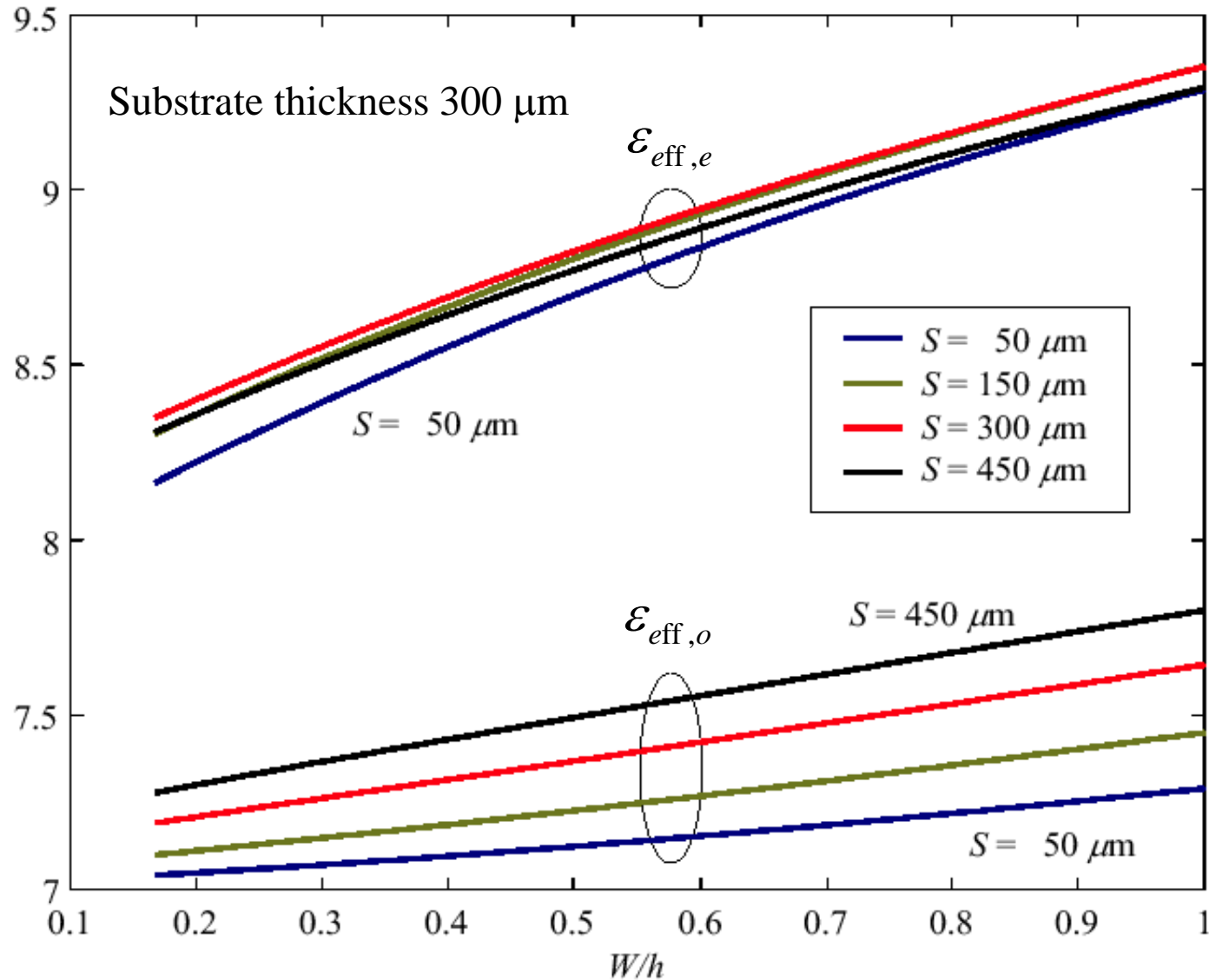
# Effective permittivities (on GaAs, $\epsilon=13$ )



# Outline

---




- Coupled lines
- **Directional couplers**
- Power dividers and combiners
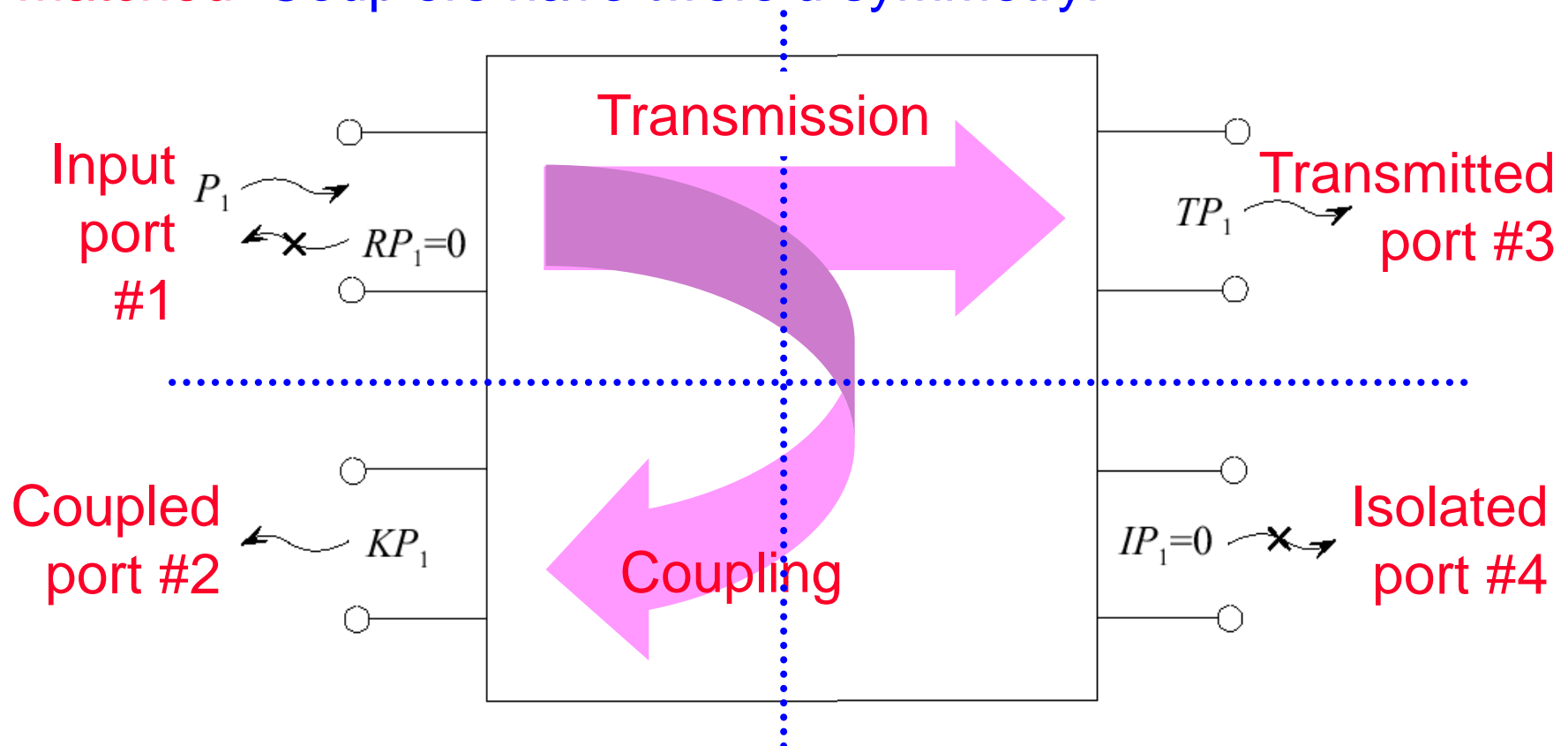
# Directional coupler



- Is a four-port dividing the **input power** at port 1 into **two parts** (generally not the same  $\rightarrow$  3dB coupler if same) (port 3 and 2) with 90 or 180 phase difference (90 and 180 **hybrids**) between the two ports; port 4 is **isolated** and all ports are **matched**. Couplers have twofold symmetry!



# Coupler parameters



$$R|_{\text{dB}} = 20\log_{10}|S_{11}| \text{ reflection coefficient } \approx 0$$

$$K|_{\text{dB}} = -10\log_{10}\left(\frac{P_2}{P_1}\right) \equiv |C|_{\text{dB}} = -20\log_{10}\left|\frac{b_2}{a_1}\right| \text{ coupling}$$

$$T|_{\text{dB}} = -10\log_{10}\left(\frac{P_3}{P_1}\right) \text{ transmission coefficient}$$

$$I|_{\text{dB}} = -10\log_{10}\left(\frac{P_4}{P_1}\right) \text{ isolation}$$

$$D|_{\text{dB}} = 10\log_{10}\left(\frac{P_2}{P_4}\right) \text{ directivity}$$


**Couplers are reactive!**

$$P_1 = P_2 + P_3 = KP_1 + TP_1$$


$$\rightarrow K + T = 1 \rightarrow T = 1 - |C|^2$$

(often  $C$  is taken as real, e.g. coupling =  $jC$ )

# Directional coupler implementations

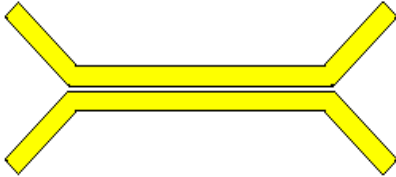


uniform coupled line coupler

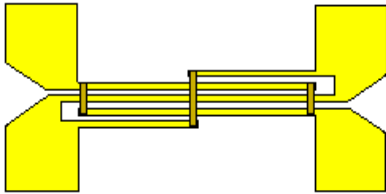


Lange coupler

- Coupled line couplers:
  - simple (two coupled lines), achieving 3 dB coupling is difficult (equal power division)
  - interdigitated (Lange), technologically more difficult, 3 dB couplers can be obtained
  - Coupled line couplers can easily obtain low coupling (what for?)

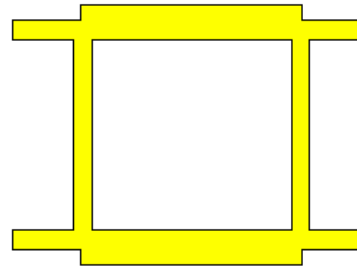- Interference couplers:
  - Easy 3 dB couplers
  - Difficult low-coupling couplers
  - Large area



Branch line coupler

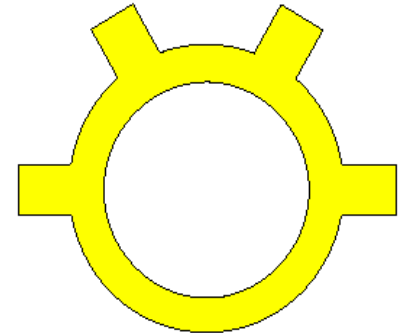

Rat race coupler


*Size: quarter wavelength at centerband*

# Coupled line couplers



$$S(\pi/2) = \begin{pmatrix} 0 & C & -j\sqrt{1-C^2} & 0 \\ C & 0 & 0 & -j\sqrt{1-C^2} \\ -j\sqrt{1-C^2} & 0 & 0 & C \\ 0 & -j\sqrt{1-C^2} & C & 0 \end{pmatrix}$$

Centerband scattering matrix

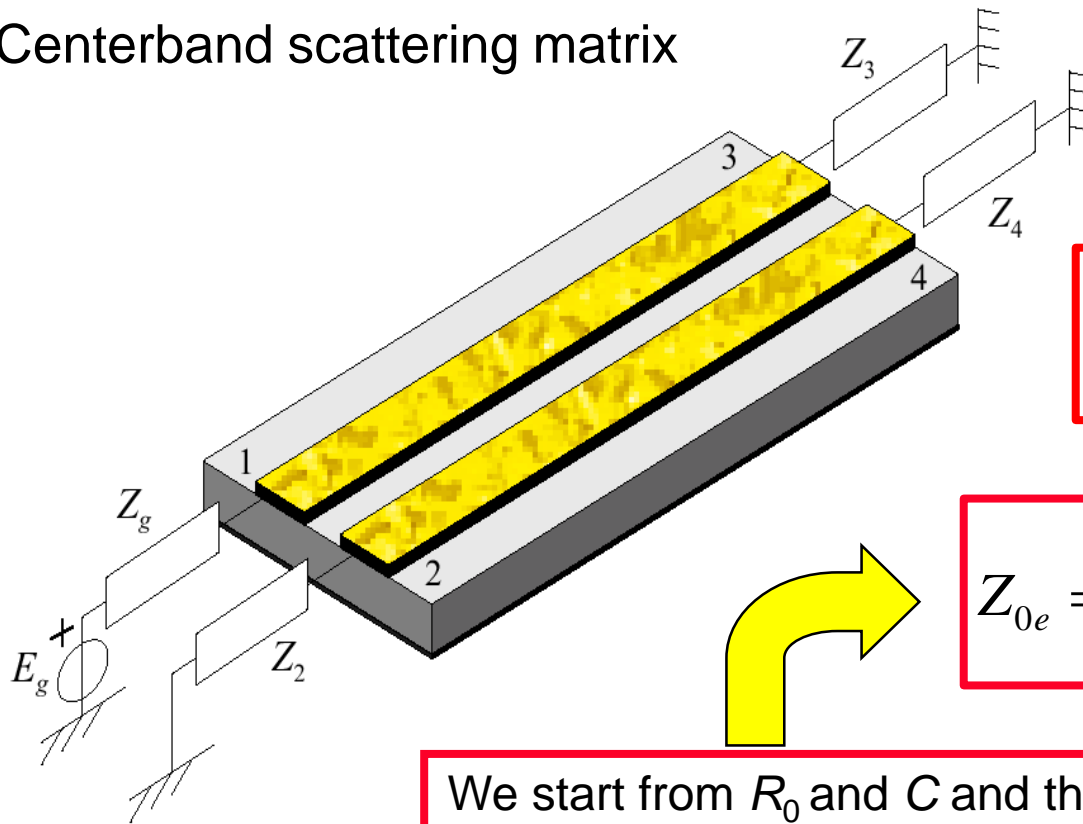

- The centerband coupler length is  **$\lambda_g/4$**
- To have matching (port 1), isolation (port 4), coupling  $C$  (port 2) the following conditions should be met:

$$C = \frac{Z_{0e} - Z_{0o}}{Z_{0e} + Z_{0o}} \quad R_0 = \sqrt{Z_{0e} Z_{0o}}$$

$$Z_{0e} = R_0 \sqrt{\frac{1+C}{1-C}} \quad Z_{0o} = R_0 \sqrt{\frac{1-C}{1+C}}$$


We start from  $R_0$  and  $C$  and the design of coupled lines follows




# Ideal 3dB coupler response (synchronous even and odd modes)



Magnitude

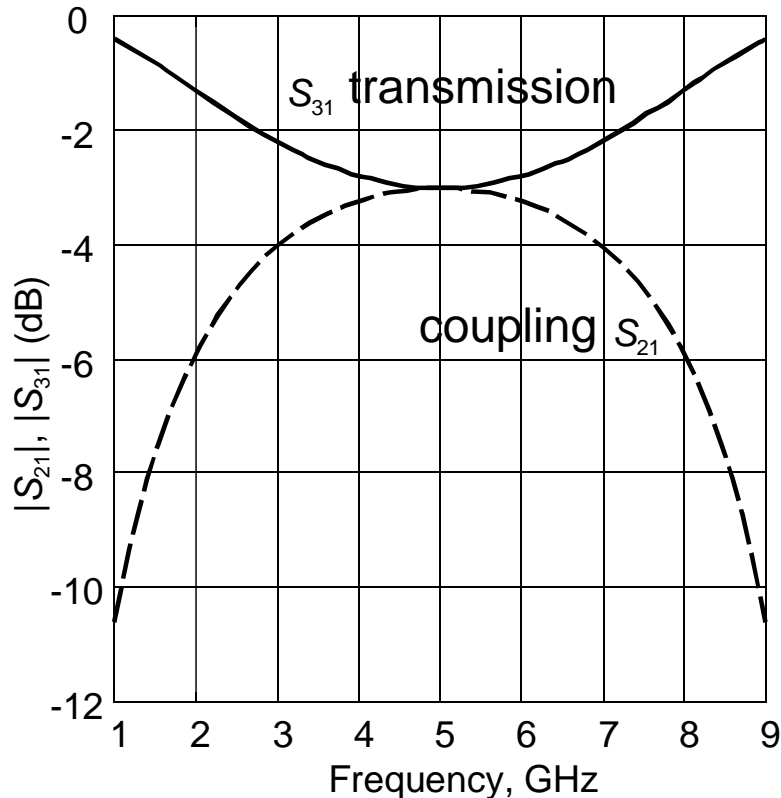


Phase, degrees

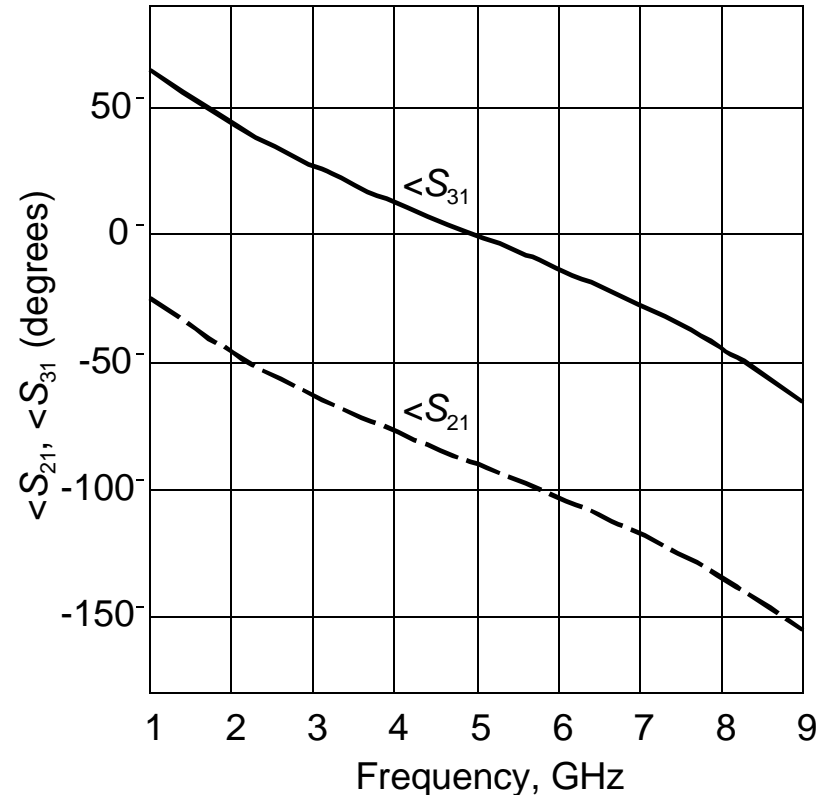


Ideal matching and isolation achieved on the whole band!
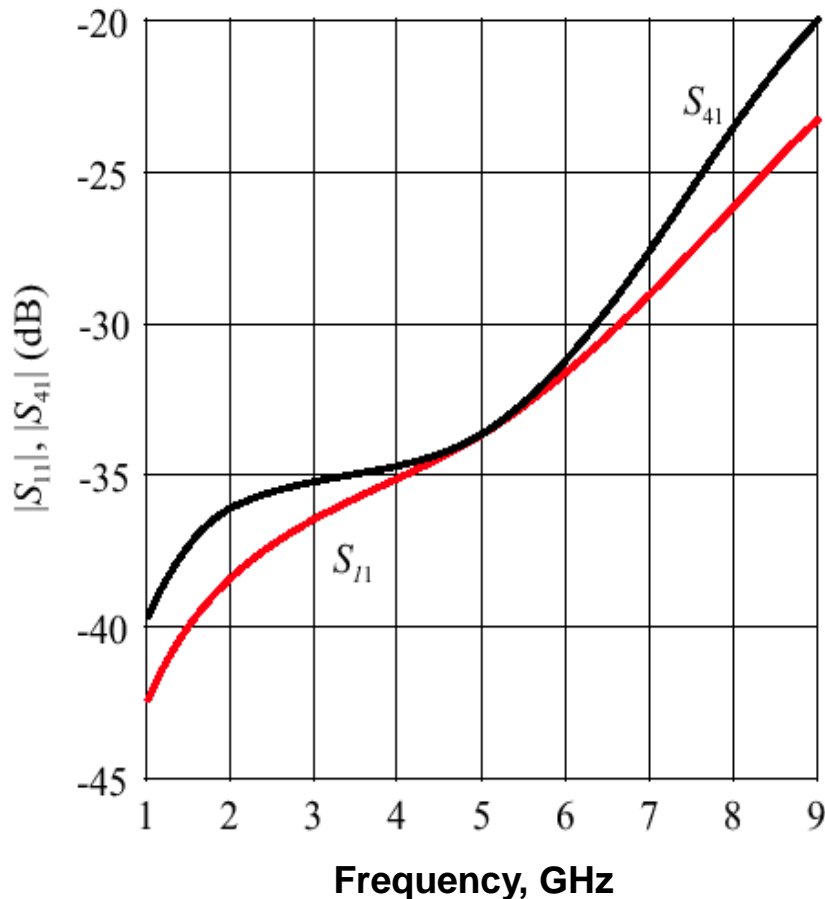
# Isolation and matching in a real coupler



- In real couplers the even and odd modes do not have the same propagation velocity
- As a result, **matching** and **isolation** deteriorate, **coupling** and **transmission** are almost unchanged
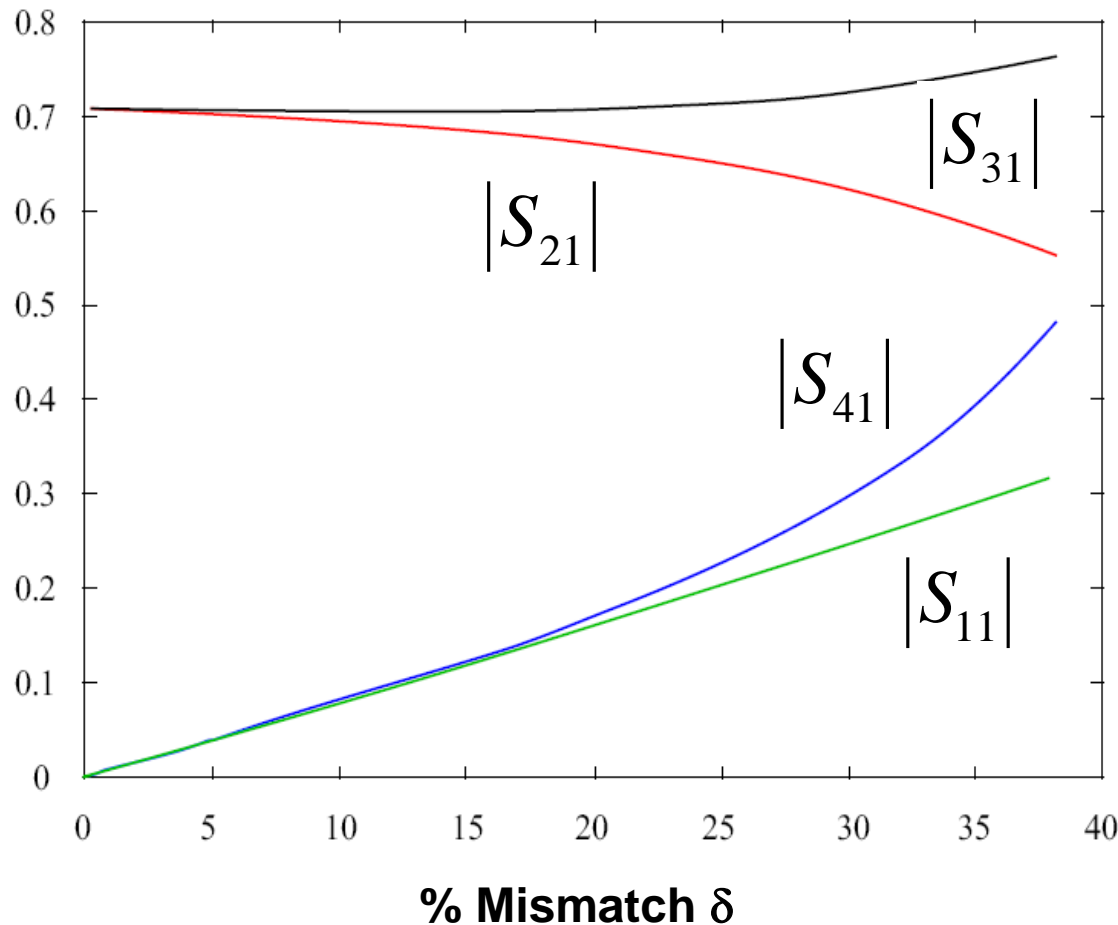
# Centerband S parameters as a function of velocity mismatch




- In several applications the loss in isolation can be a serious problem
- Approximately:


$$S_{41} \approx \delta(1 - C^2)$$

$$\delta = \frac{|v_e - v_o|}{v_e + v_o}$$


# Compensated couplers

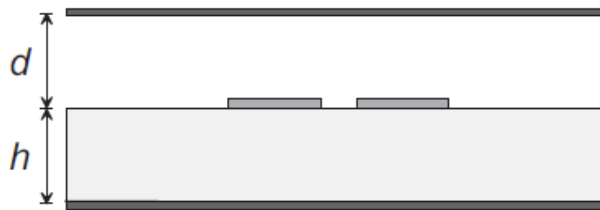


(a)

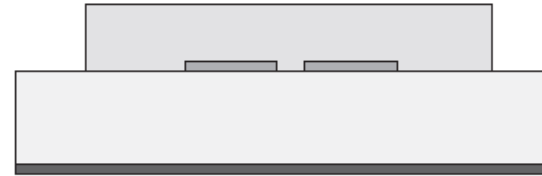

(b)

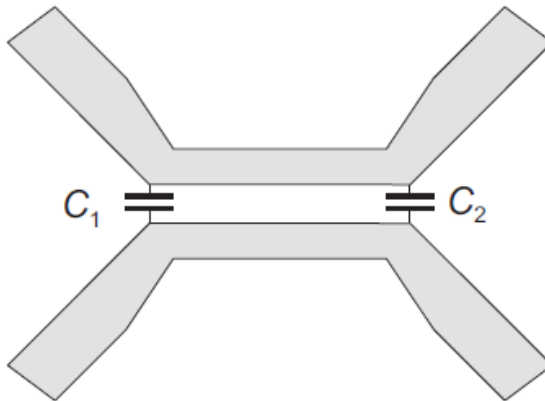

(c)

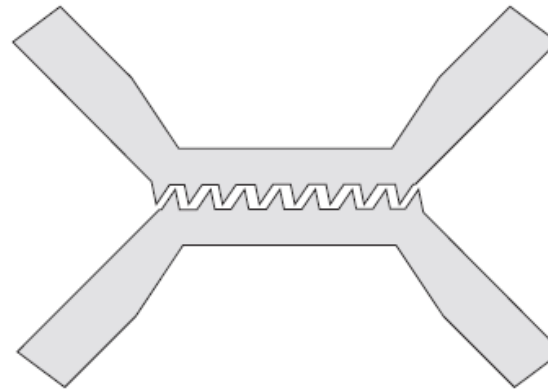

(d)

Velocity compensation techniques: shielded directional coupler (a) and with dielectric overlay (b); compensation through concentrated capacitances (c) and line wiggly (d).

# Integrated 3dB couplers

---




- 3dB couplers can be in principle implemented with two coupled microstrips; however, the slot width in a 50 Ohm system turns out to be technologically impossible to realize (a few microns)
- Unfortunately 3dB couplers with 90 degrees phase shift are required in many applications (e.g. balanced amplifiers)
- A solution that is technologically manageable is given by the **multiconductor couplers** → Lange couplers

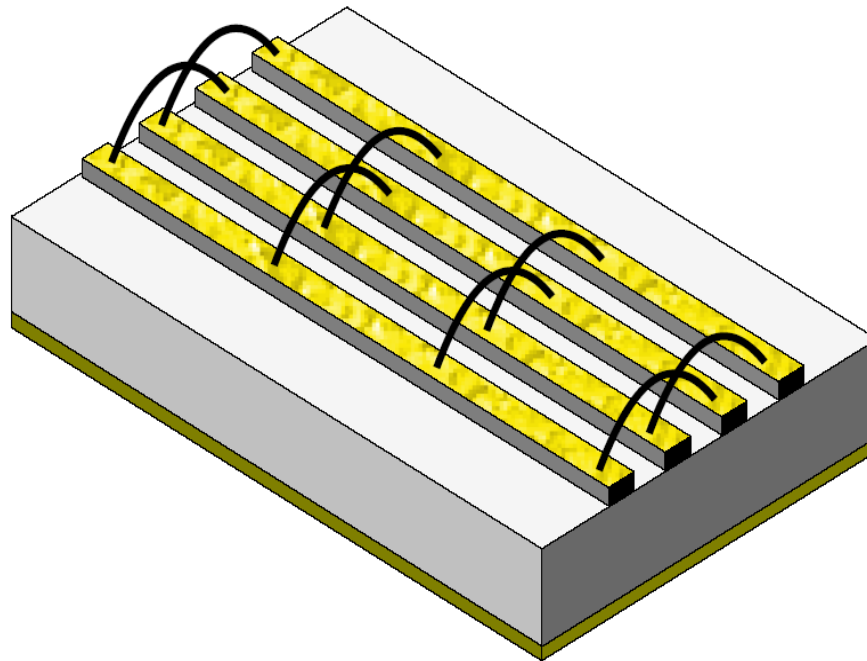
# Multiconductor microstrip and equivalent two-conductor line



- A multiconductor line is equivalent to a two-conductor line if the conductors are periodically connected
- The mutual capacitance of the equivalent two lines increases  $\rightarrow$  coupling increases also for widely spaced lines
- 3 dB couplers can be implemented with 4, 6, 8 conductors (typically 4)
- Increasing the number of conductors the closing impedance decreases


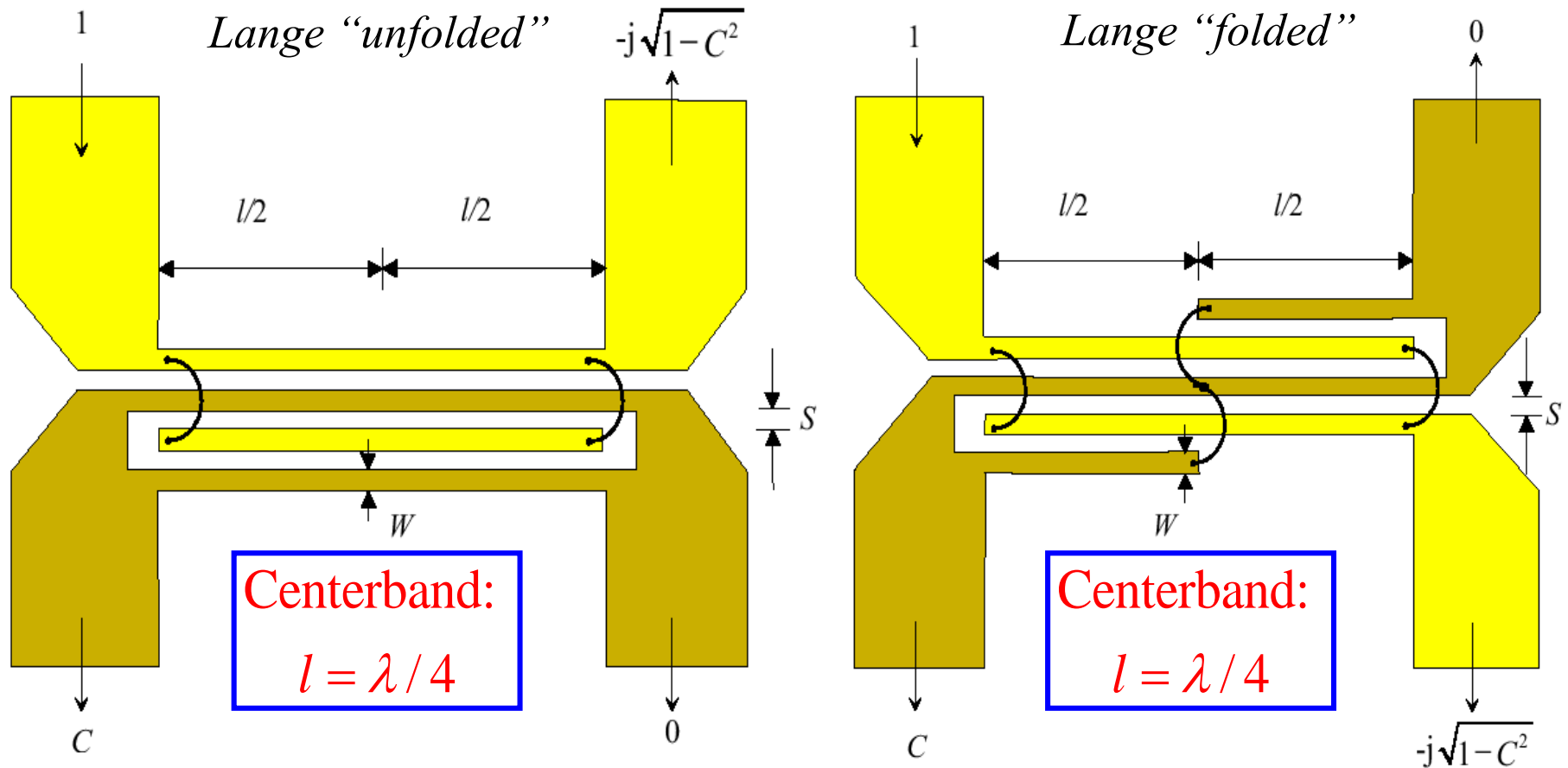
# Interdigitated four-conductor 3dB Lange couplers



- In principle directional couplers can also be made with two-conductor coupled microstrips, but for technological limits 3dB couplers can only be interdigitated

# Designing a multiconductor coupler



- Assume we know the **centerband coupling**  $C$ , the **closing impedance**  $R_0$  (e.g. 50 Ohm) and the **number of lines**  $k$ .
- It can be shown that:

$$C(k) = \frac{(k-1)(1-R^2)}{(k-1)(1+R^2) + 2R}, \quad R_0^2 = r \frac{(1+R)^2}{[(k-1)R + 1][(k-1) + R]}$$

- where  $R = Z_{0o}(2) / Z_{0e}(2)$ ,  $r = Z_{0o}(2) Z_{0e}(2)$ ;  $Z_{0o}(2)$  and  $Z_{0e}(2)$  are the odd and even mode impedances of a two-conductor line with the **same** geometrical parameters  $w$  and  $G$ , substrate etc.
- The two previous equations can be solved in order to find
  - the impedance ratio  $R = Z_{0o}(2) / Z_{0e}(2)$
  - the impedance product  $r = Z_{0o}(2) Z_{0e}(2)$
- From these we obtain  $Z_{0o}(2)$  and  $Z_{0e}(2)$ , synthesis formulae exist giving the slot and line width needed to implement the two impedances.
- Of course the same formulae can be exploited for analysis



# Example: 3dB 50 Ohm Lange coupler on GaAs



- With  $k=4$  and  $C=1/\sqrt{2}$  we obtain (from first equation):


$$3\left(1 + \frac{1}{\sqrt{2}}\right)R^2 + 2\frac{1}{\sqrt{2}}R - 3\left(1 - \frac{1}{\sqrt{2}}\right) = 0$$

- i.e. solving for  $R$  and substituting (second equation, closing impedance 50 Ohm):


$$R = \frac{Z_o}{Z_e} = 0.3; \quad r = Z_e Z_o = 9275$$

- The two-strip impedance is:
  - Odd mode 53 Ohm
  - Even mode 177 Ohm
- An idea of the required spacing and strip thickness can be obtained from the graph in the next slide; for the 2 conductor plain coupler the odd and even mode impedances were around 120 and 20 Ohm, much less favourable

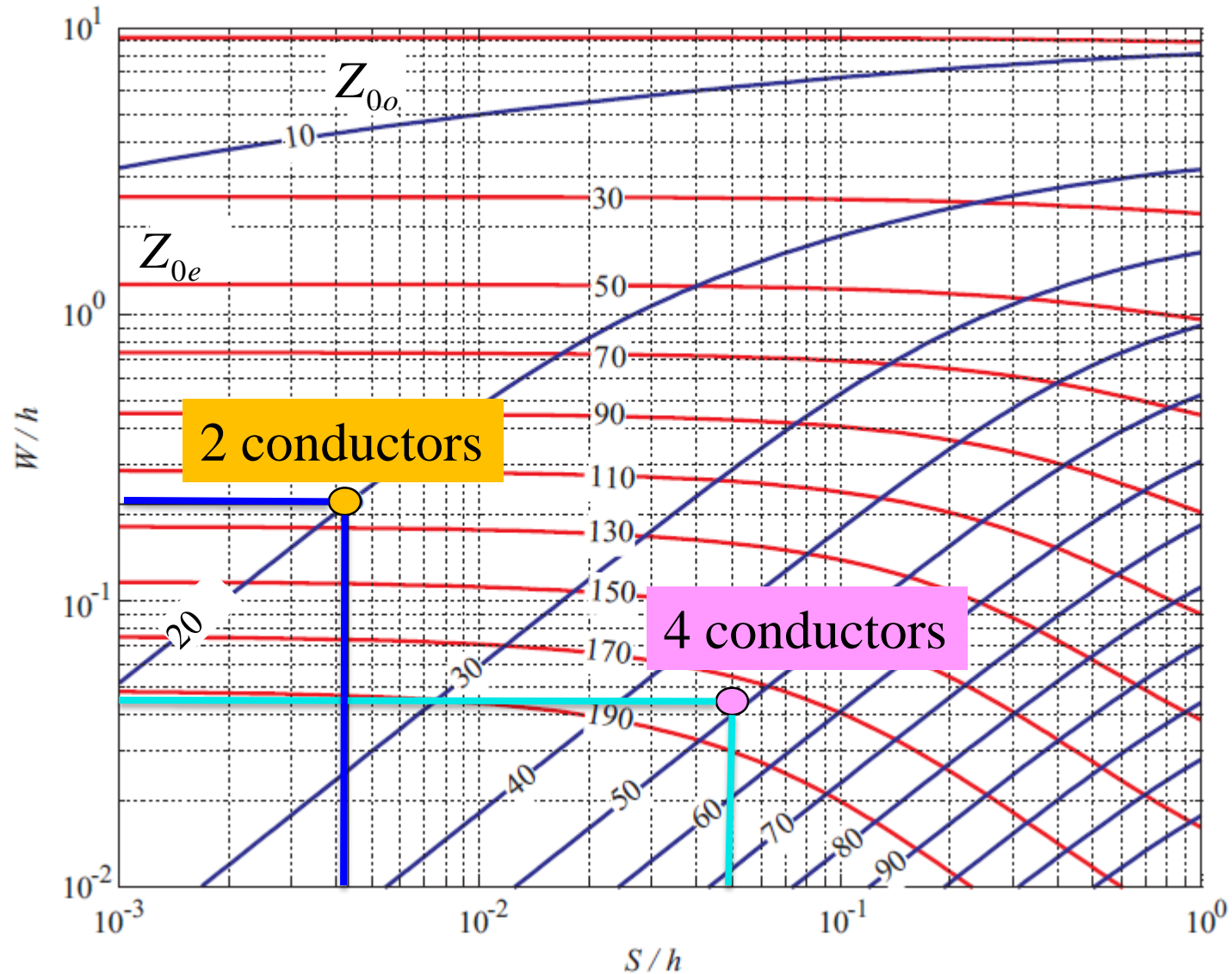
# Design chart for the coupler (epsilon\_r=13)


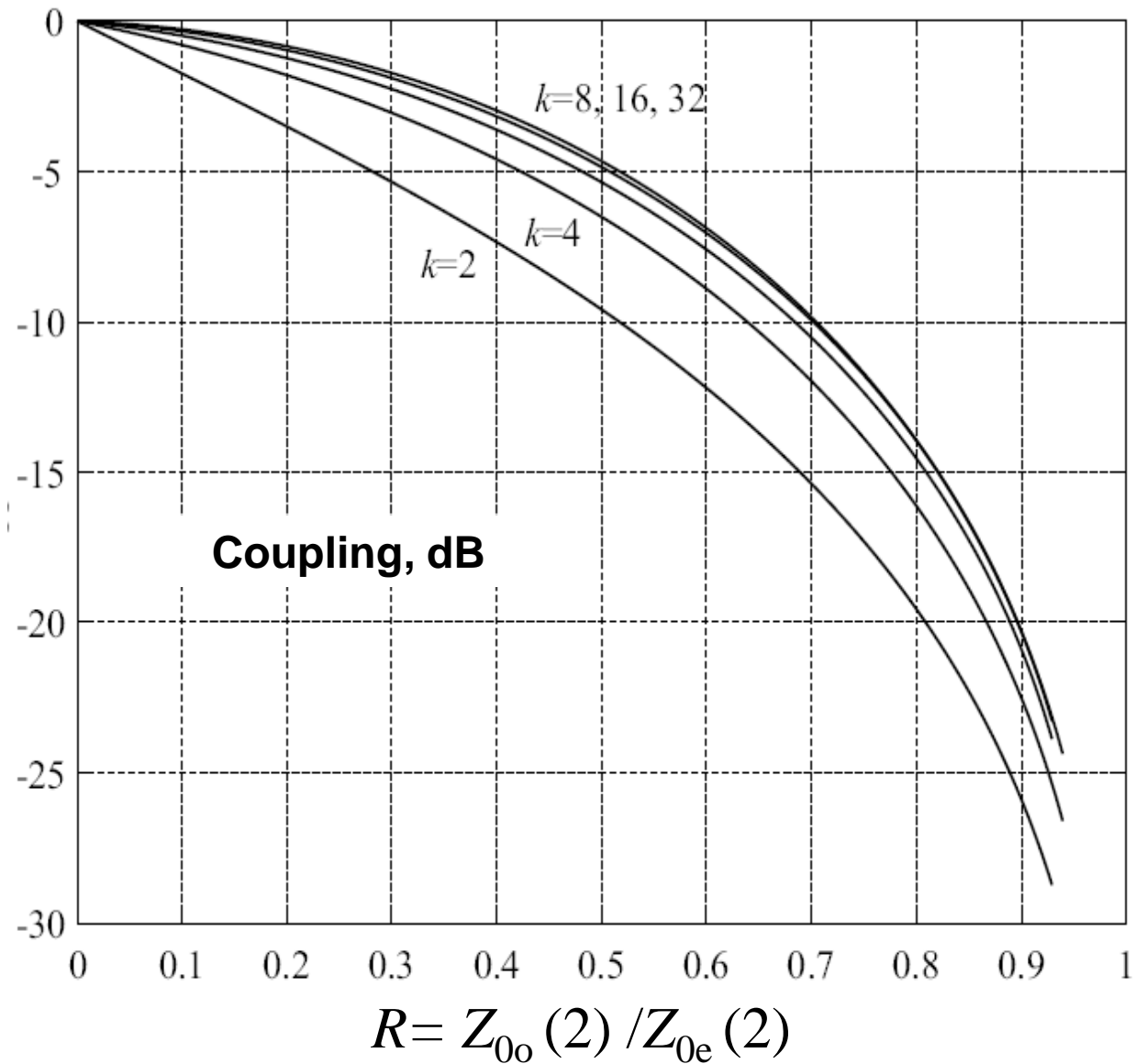
# Coupling vs. $R=Z_{\text{odd}}/Z_{\text{even}}$



# Matching impedance vs. $R$

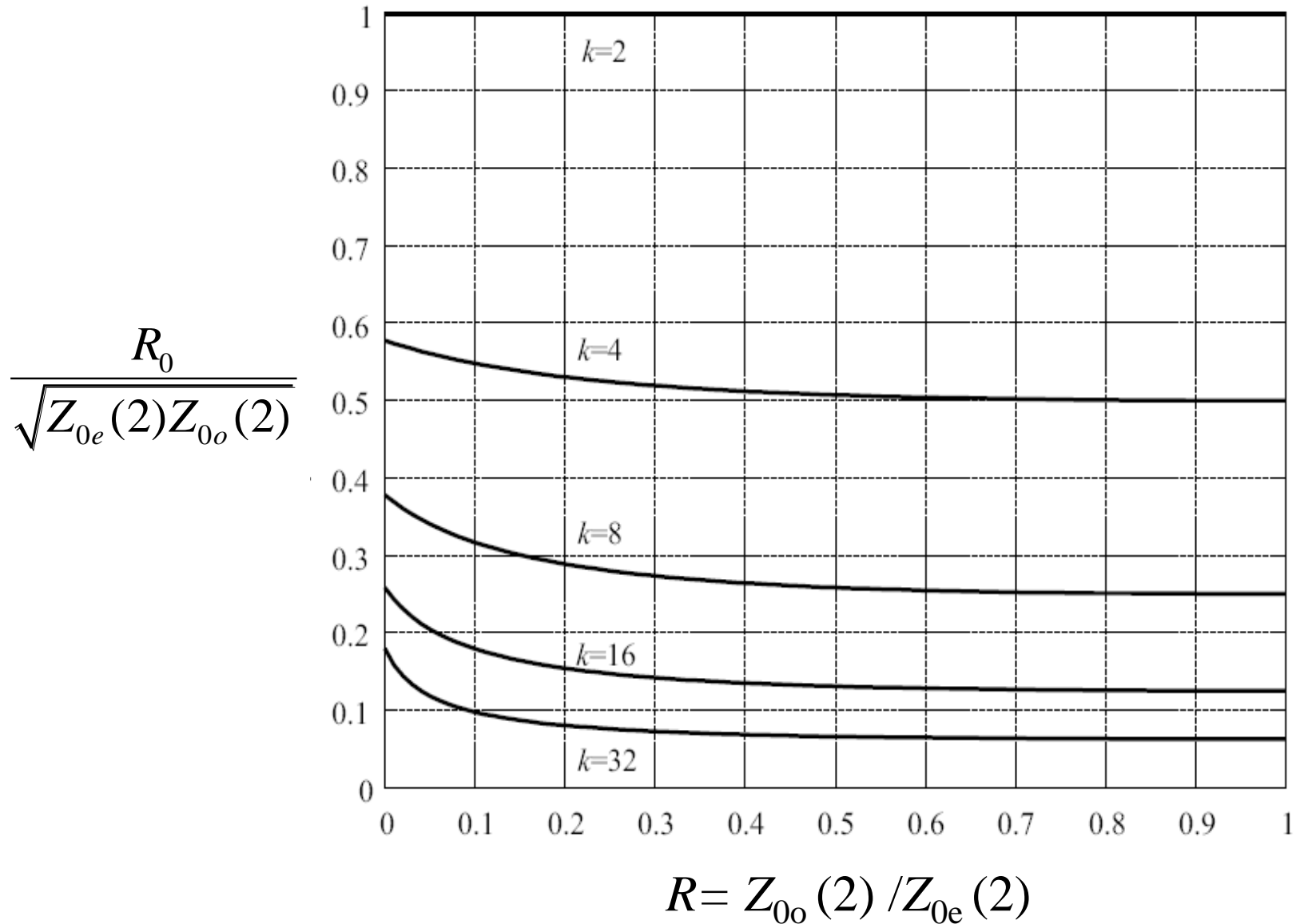

# Interference couplers




## Branch line coupler

$$Z_{02} = \frac{CZ_0}{\sqrt{1-C^2}}$$

$$Z_{01} = CZ_0$$

$$Z_{02} = Z_0$$

$$Z_{01} = \frac{Z_0}{\sqrt{2}}$$

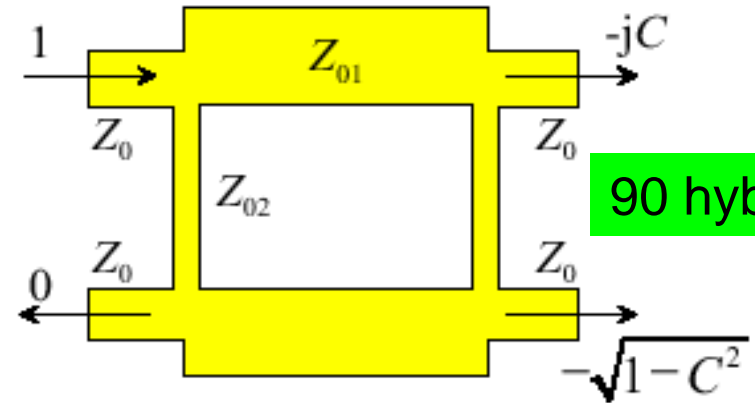

90 hybrid


## Rat race or hybrid ring coupler

$$Z_{01} = \frac{Z_0}{\sqrt{1-C^2}}$$

$$Z_{02} = \frac{Z_0}{C}$$

$$Z_{01} = Z_0\sqrt{2}$$

$$Z_{02} = Z_0\sqrt{2}$$

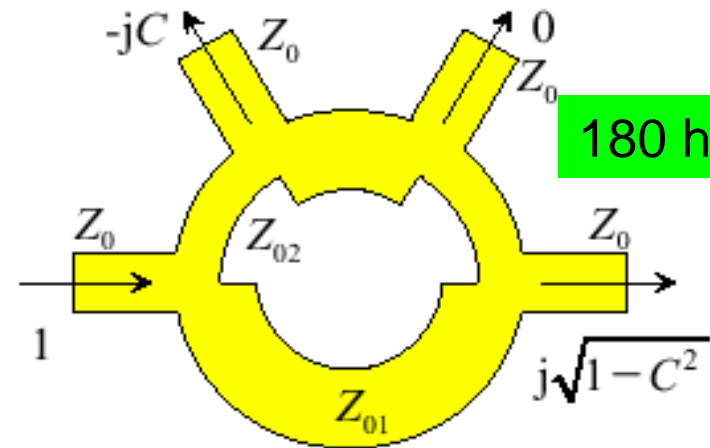


180 hybrid

*Generic coupling*



*3dB*

Centerband: branch coupler side  $\lambda/4$ , hybrid ring periphery  $3\lambda/2$

# Lumped interference couplers

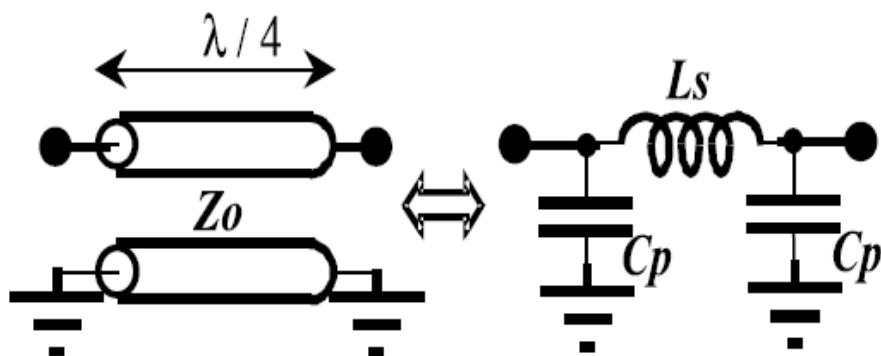


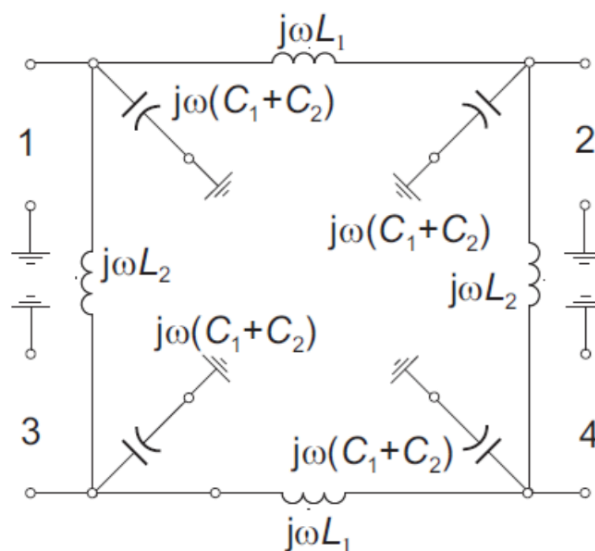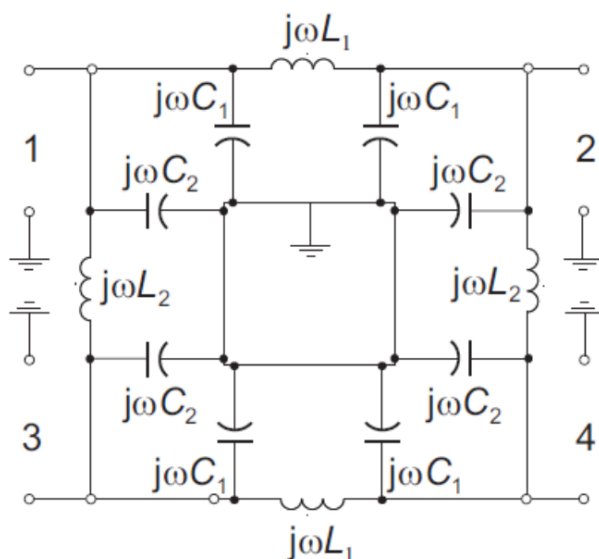- Idea: replace at centerband a lambda/4 section with a pi lumped section
- ~Same behavior around centerband



Lumped parameter branch-line coupler: left, implementation from  $n$  sections; right, practical implementation.
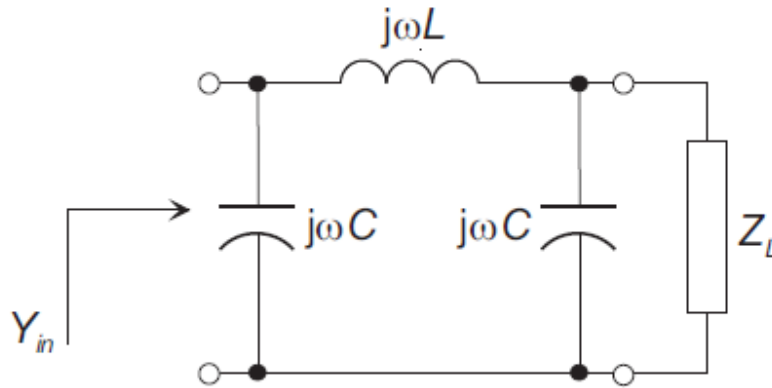
# Example: lumped section as quarter-wave transformer



At centerband suppose resonance  $j\omega_0 L = -\frac{1}{j\omega_0 C} = jX$ ;

$$Z_1 = \frac{-jX \times Z_L}{-jX + Z_L} \quad Z_2 = Z_1 + jX$$


$$Z_2 = \frac{-jX \times Z_L}{-jX + Z_L} + jX = \frac{X^2}{-jX + Z_L}; \quad Y_2 = -j\frac{1}{X} + \frac{Z_L}{X^2};$$

$$Y_{in} = Y_2 + j\frac{1}{X} = \frac{Z_L}{X^2} \quad Z_{in} = \frac{X^2}{Z_L}$$
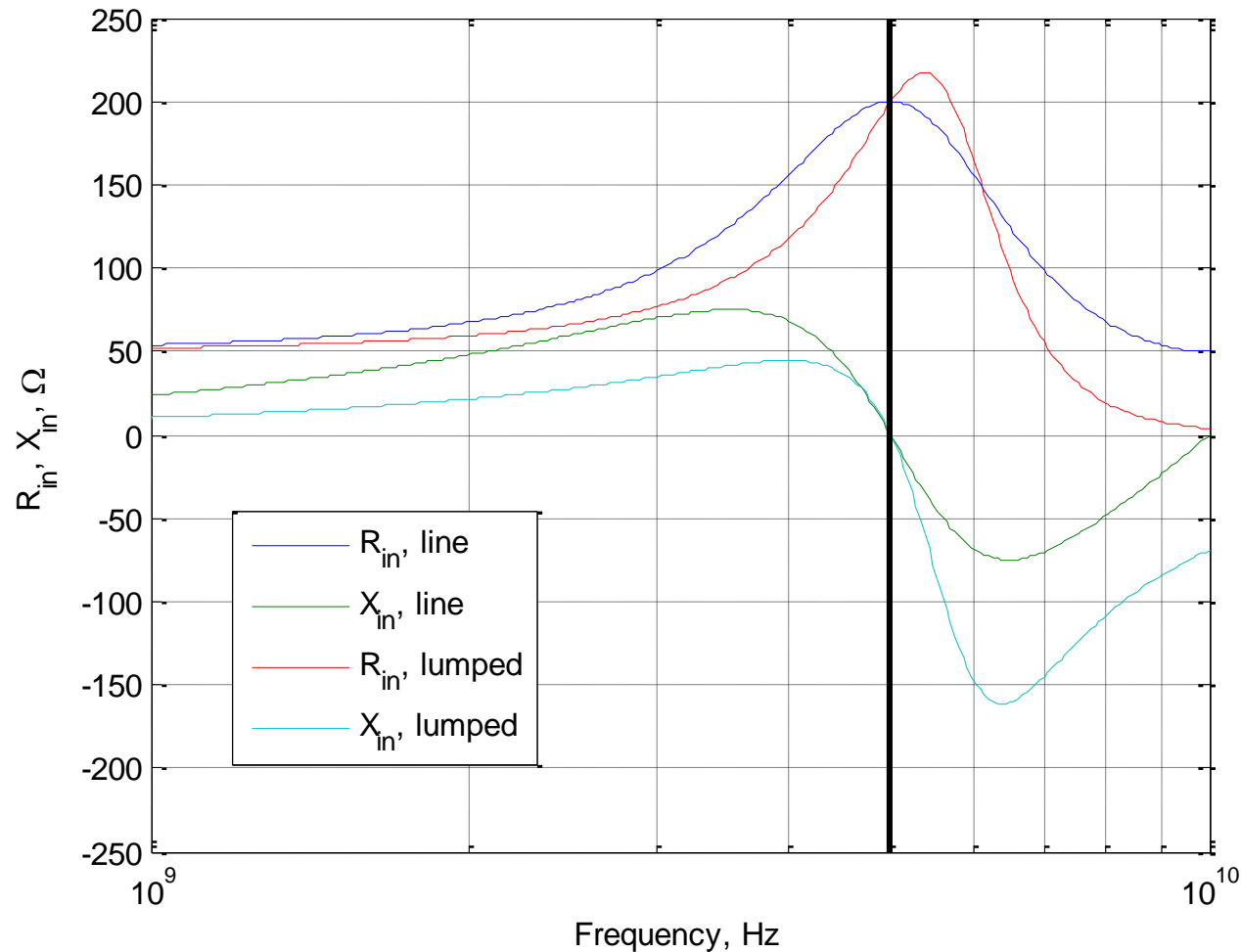
# Example: 50→200 Ohm transformer at 5 GHz



- 50 Ohm load, 100 Ohm line,  $\lambda/4$  @5 GHz






# Features of interference couplers

---





- **Large layout size** (square or circular layout, side of the order of  $\lambda/4$  at centerband)
- **Lumped implementations** possible in integrated form till ~25-30 GHz
- Compact implementations based on coupled transmission line sections are also possible
- **180 degrees hybrids possible besides 90 degrees hybrids**
- 3dB couplers easy to implement, low coupling couplers almost impossible to implement
- Narrowband couplers anyway.
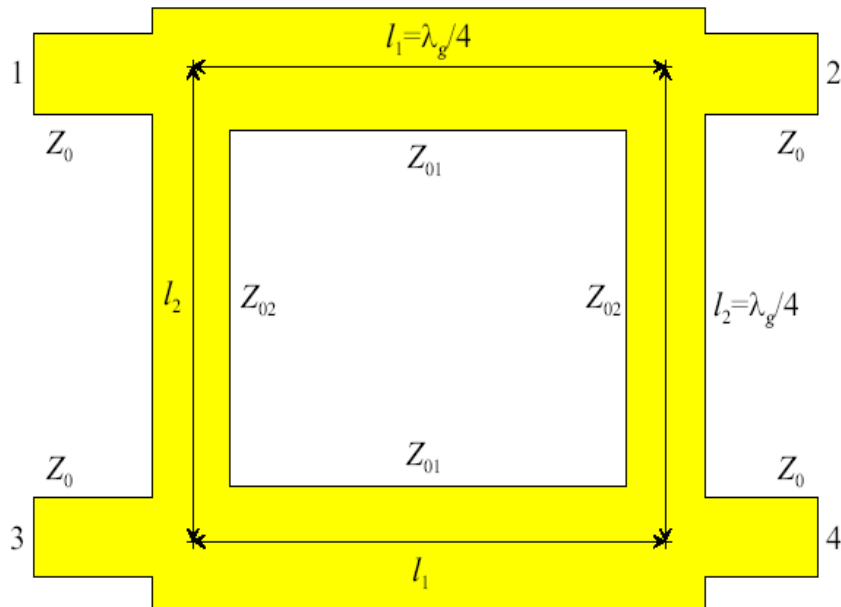
# Branch-line couplers, frequency behavior vs. Lange coupler



$$Z_{01} = CZ_0$$

$$Z_{02} = \frac{CZ_0}{\sqrt{1 - C^2}}$$

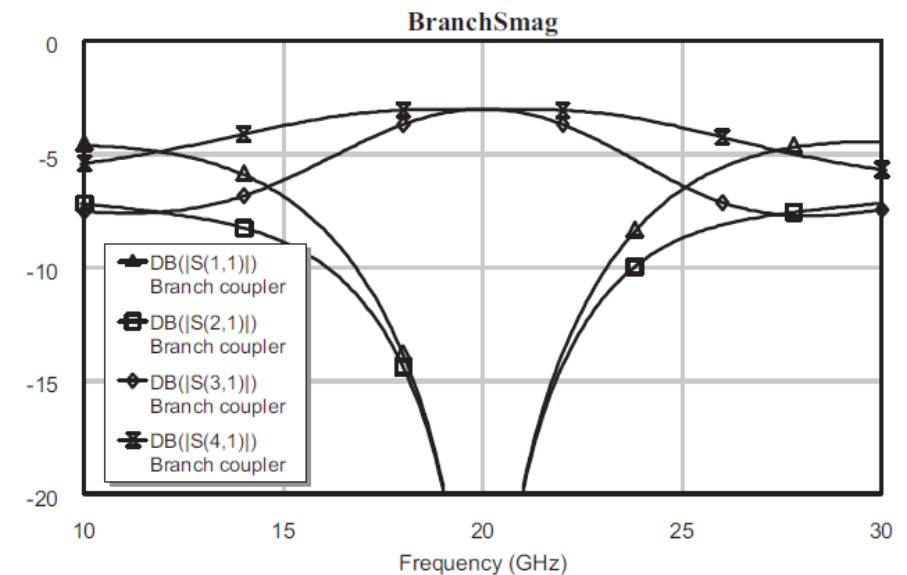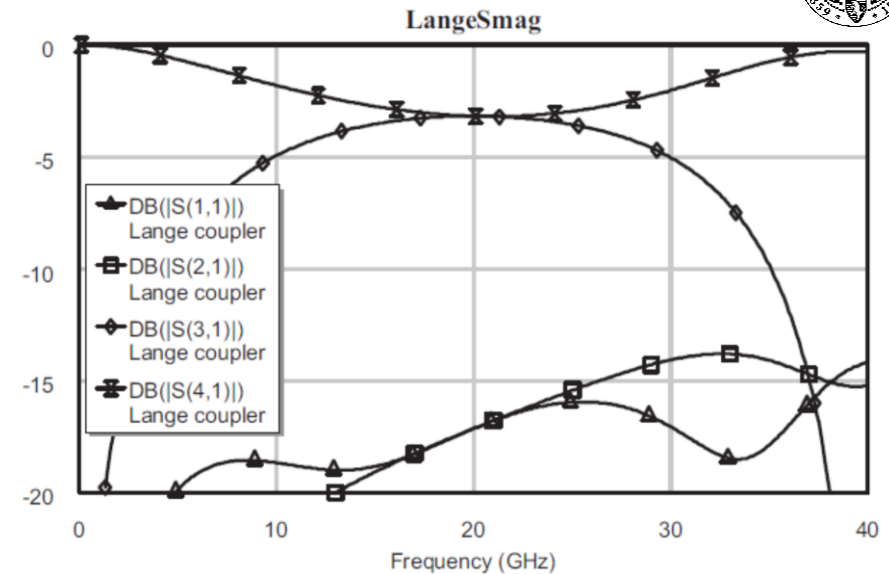

# Outline

---



- Coupled lines
- Directional couplers
- **Power dividers and combiners**


# Power dividers and combiners

---



- The aim is to **divide the input power** (dividers) or **combine several output powers** (combiners) uniformly, granting impedance matching at all ports.
- Usually narrowband, can be made wideband by multisection structures
- Directional couplers can be exploited but ad hoc combiners are preferred → several solutions available, a classical example is **the Wilkinson combiner / divider**.
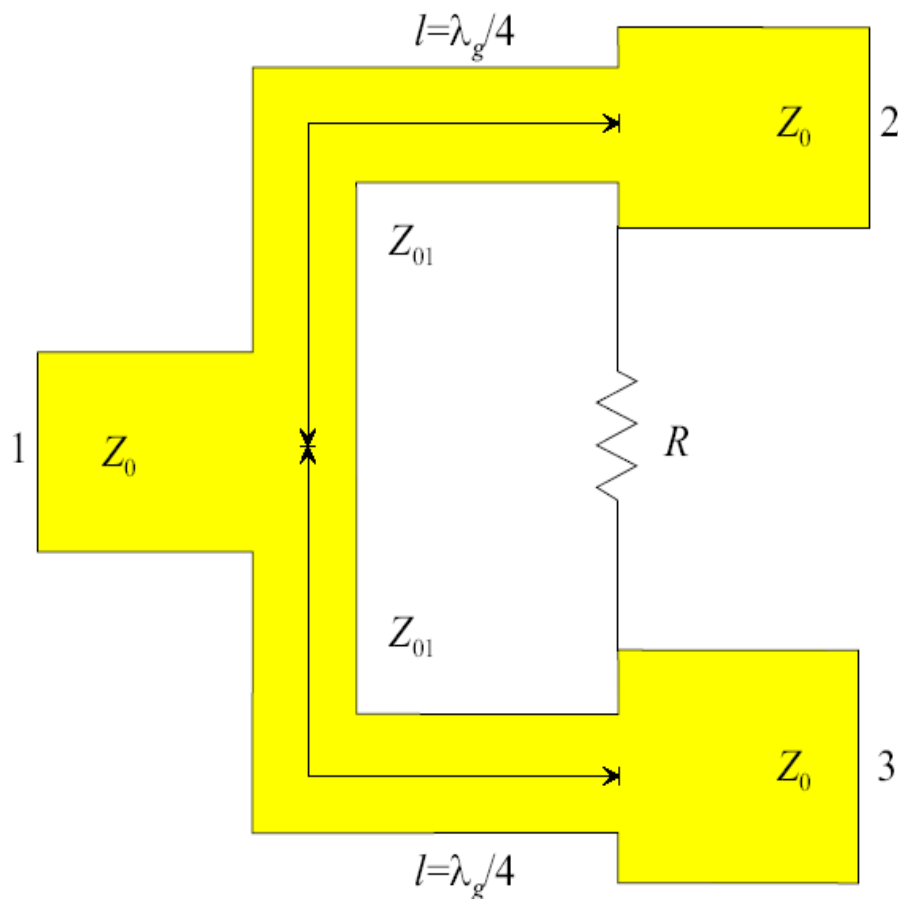
# Wilkinson divider – Layout and Y matrix



$$Y = \begin{pmatrix} 2Y_{11}^l & Y_{12}^l & Y_{12}^l \\ Y_{12}^l & Y_{11}^l + Y_{11}^R & Y_{12}^R \\ Y_{12}^l & Y_{12}^R & Y_{11}^l + Y_{11}^R \end{pmatrix}$$

$$Y_{11}^l = Y_{22}^l = -jY_{01} \cot \theta$$

$$Y_{12}^l = Y_{21}^l = jY_{01} / \sin \theta$$

$$Y_{11}^R = Y_{22}^R = G$$

$$Y_{12}^R = Y_{21}^R = -G.$$


# Wilkinson power divider (combiner)



- The two lines are a **quarter wavelength** at centerband
- The divider is narrowband and splits in two the input power
- If the structure is perfectly balanced at the output the resistor is redundant

$$Z_{01} = Z_0 \sqrt{2}$$


$$R = 2Z_0$$

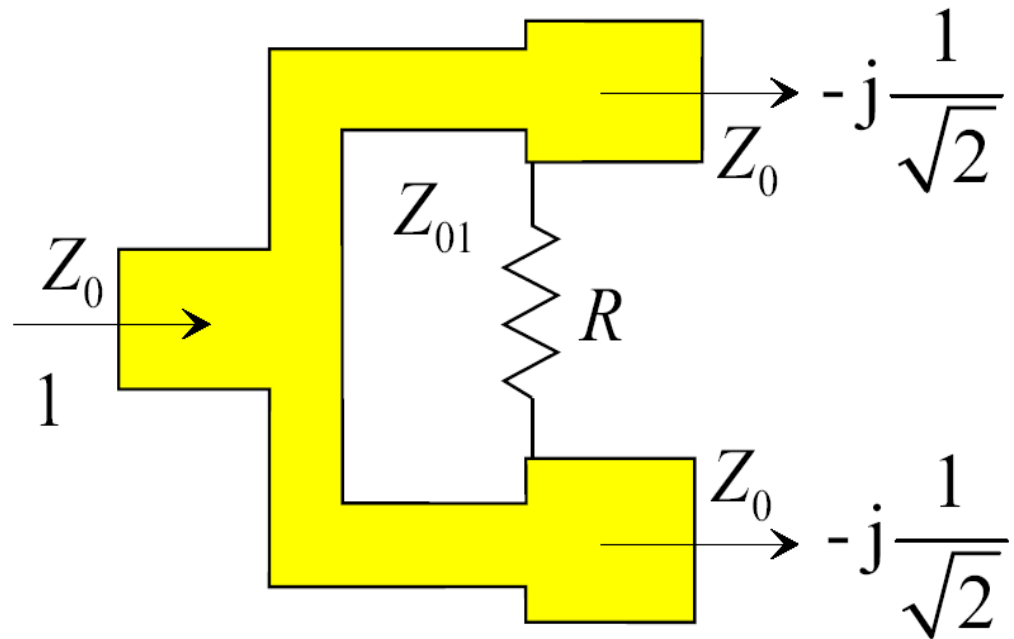
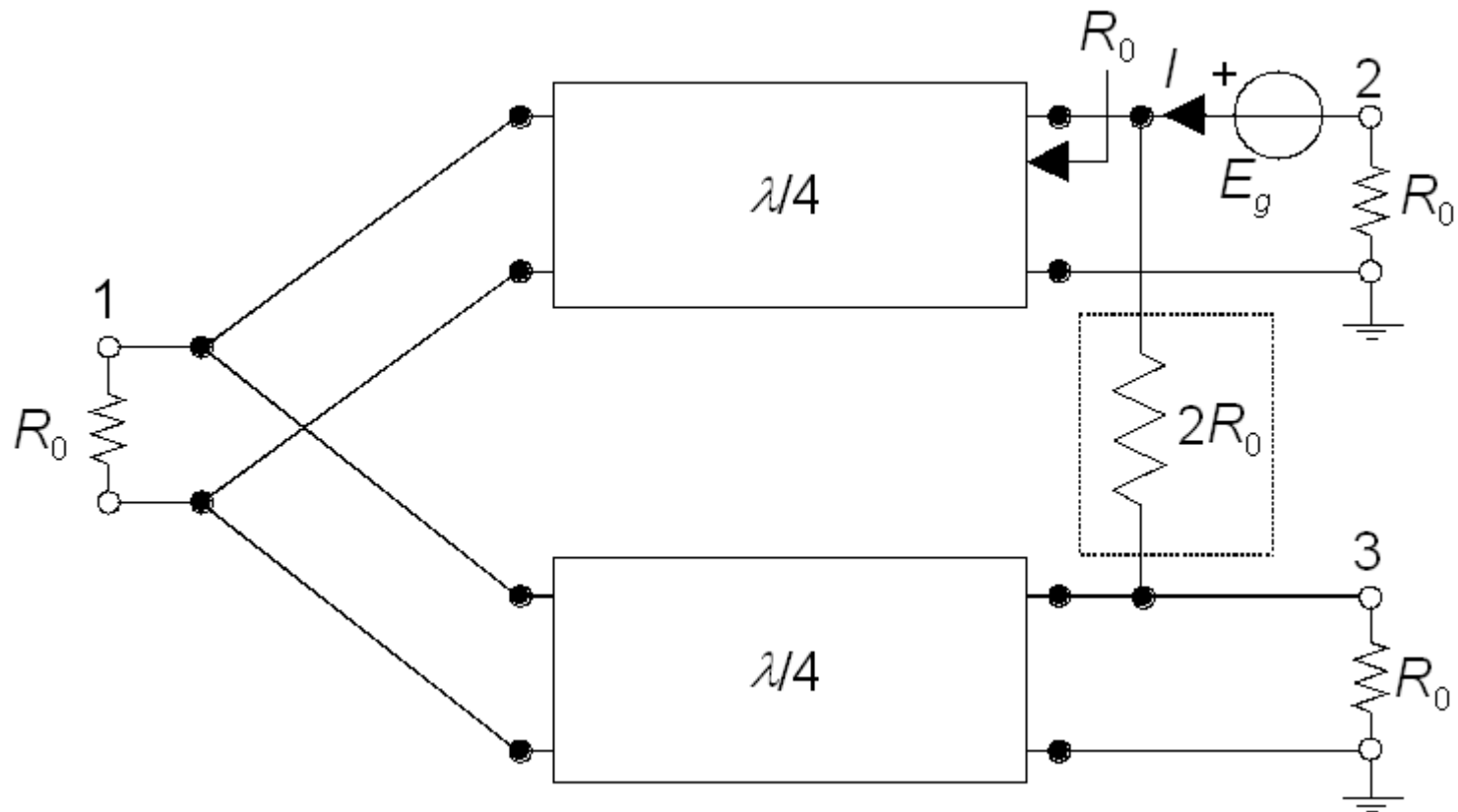
# Even-odd proof of $R = 2Z_0 - I$




- We want to check that the parallel resistance grants matching in port 2 and 3


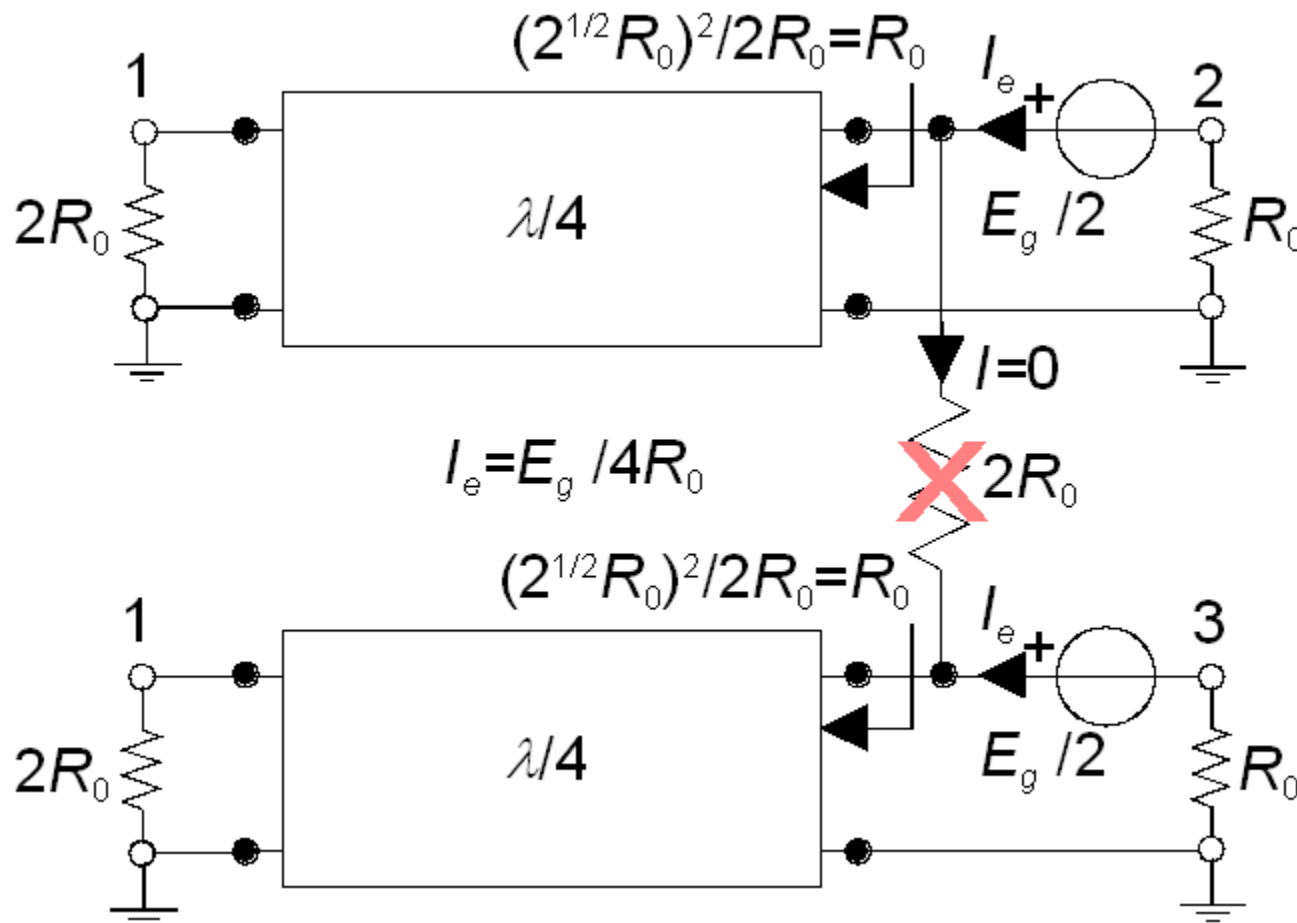
# Even-odd proof of $R = 2Z_0 - \Gamma$



- Decomposition into even and odd mode excitation:  
**even**





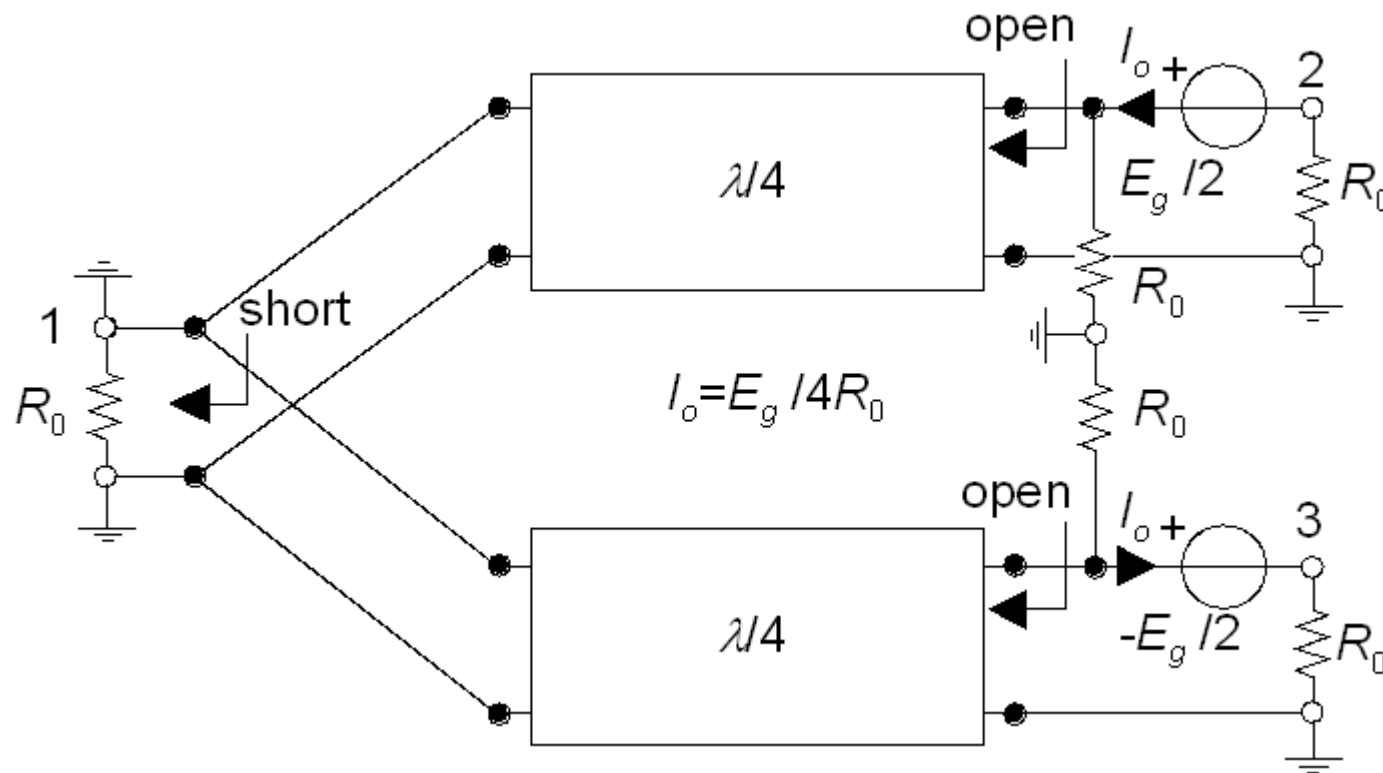
# Even-odd proof of $R = 2Z_0$ - III




- Decomposition into even and odd mode excitation:  
**odd**




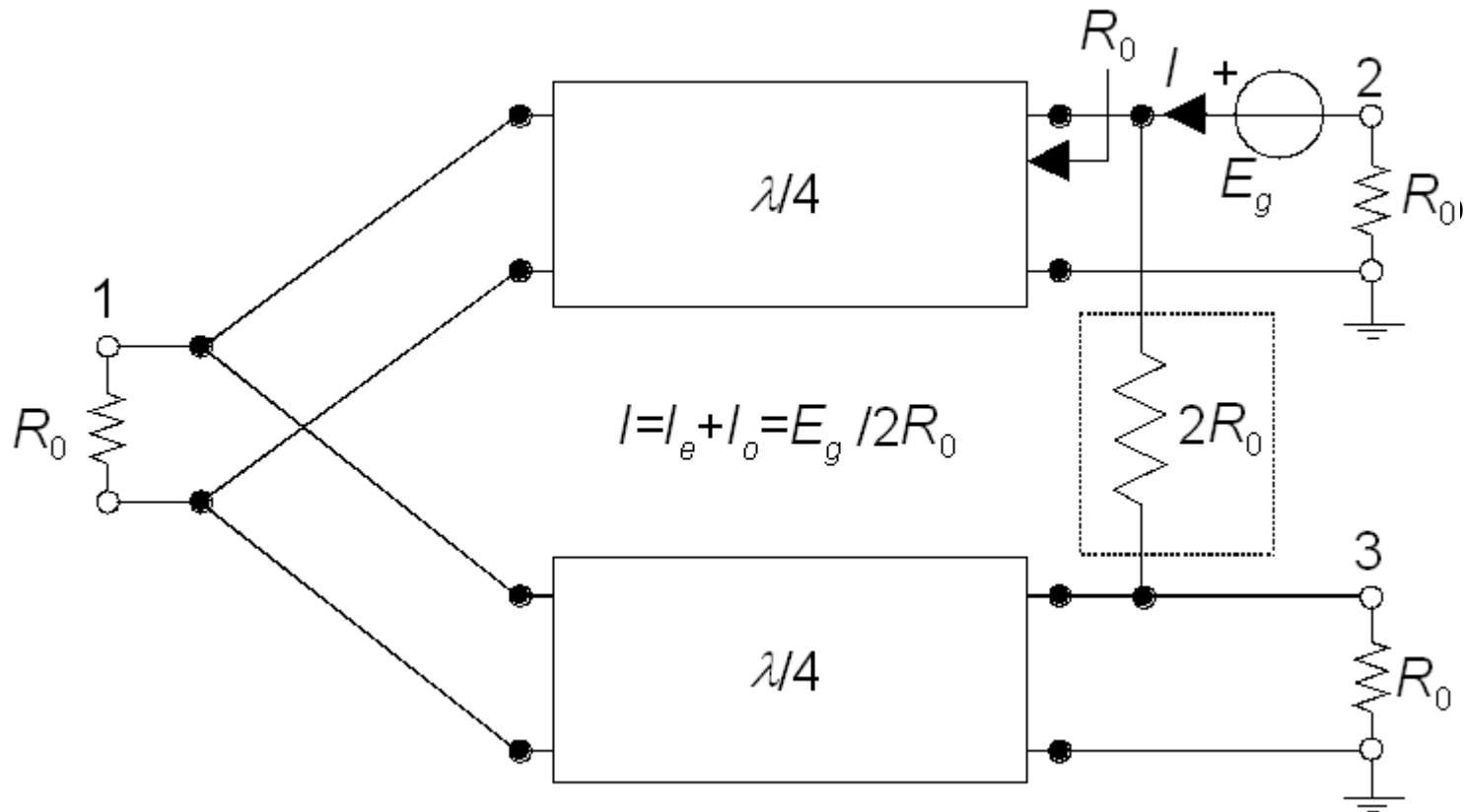
# Even-odd proof of $R = 2Z_0$ - IV




- Summing the even and odd mode currents we find  $I = E_g / 2R_0 \rightarrow$  the input resistance is  $R_0$  at port 2 (same at port 3)



# N-branch Wilkinson divider/combiner

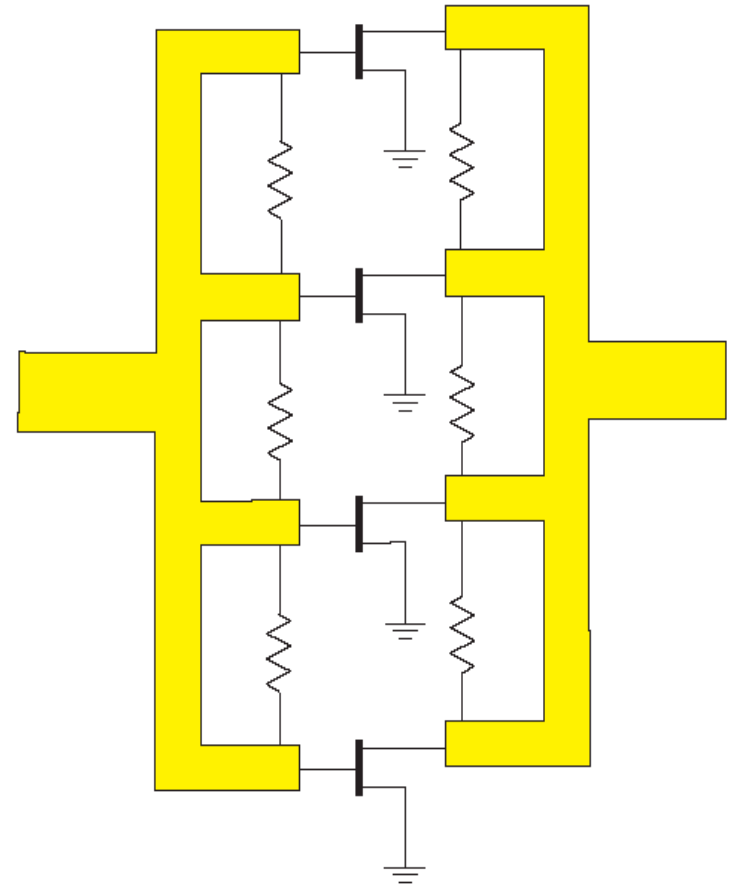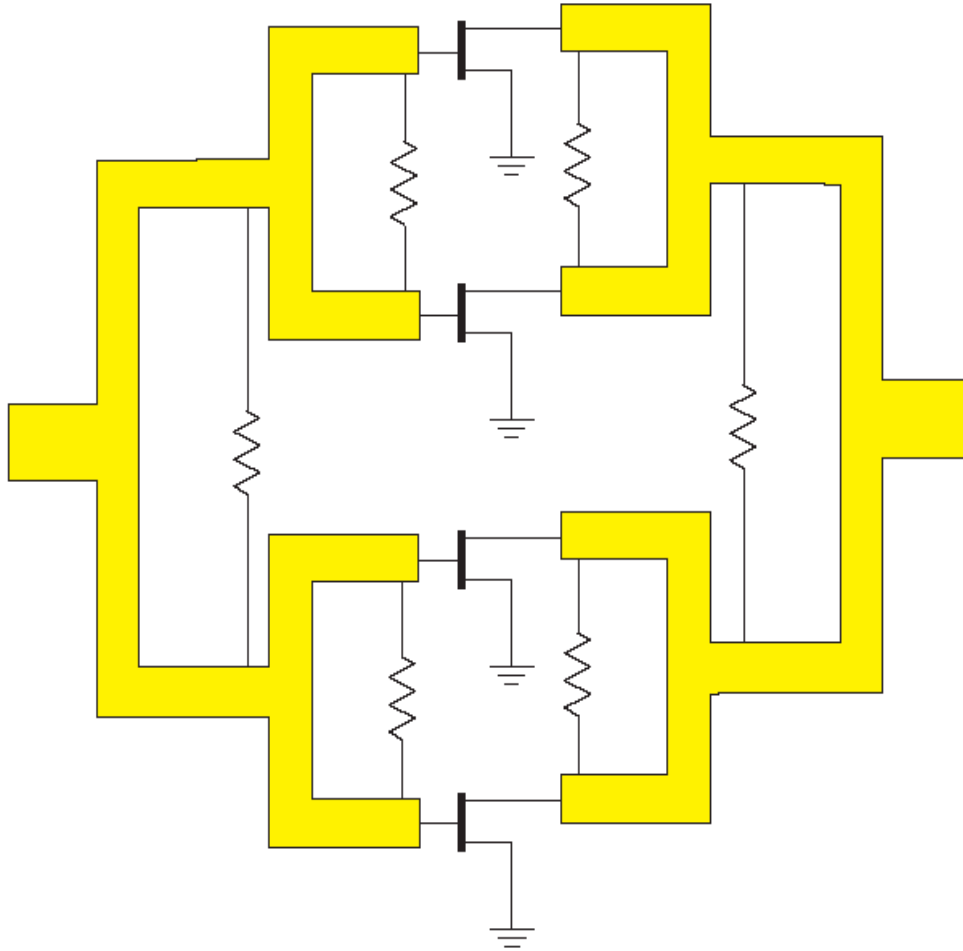

# Example of n-branch combiner

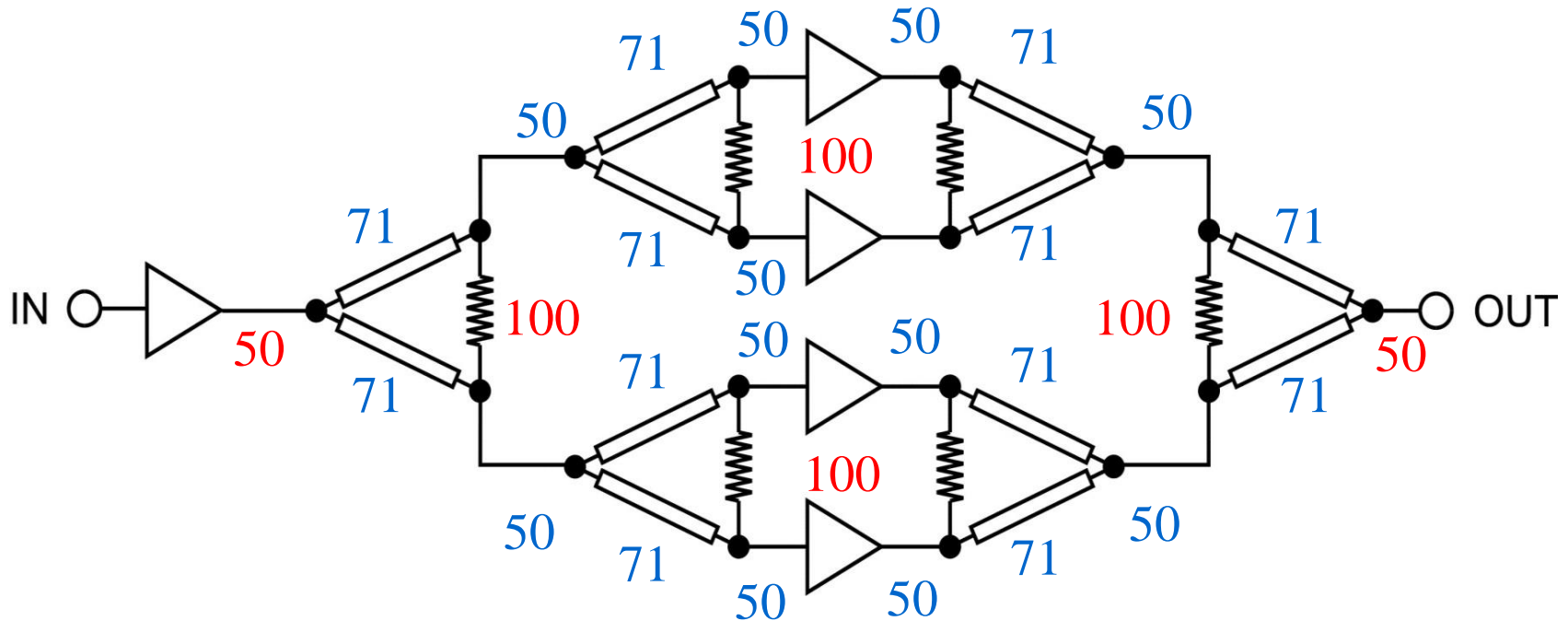


- Combining more modules is straightforward but combiner loss will increase

# Lumped parameter Wilkinson



lumped  
 $\lambda/4$  line

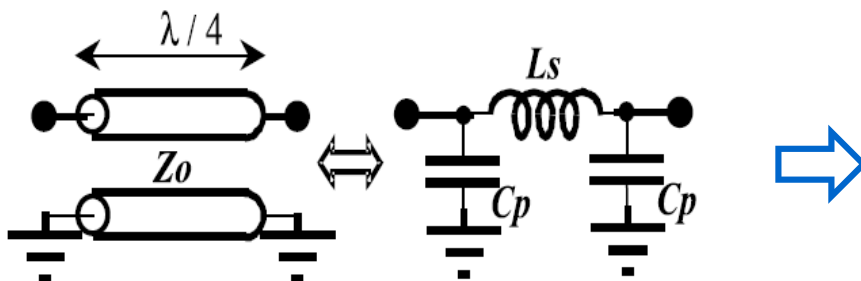

lumped  
Wilkinson

