

Linear amplifiers

Microwave Electronics

Giovanni Ghione, Marco Pirola

Politecnico di Torino, DET



RF amplifier choices




- **Purpose:** max. gain \leftrightarrow LNA \leftrightarrow PA
- **Topology:** single stage \leftrightarrow multistage, open loop \leftrightarrow feedback
- **Technology:** hybrid \leftrightarrow integrated
- **Bandwidth:** Narrowband ($<10\%$) \leftrightarrow wideband ($<40\%$) \leftrightarrow ultrawideband
- **Significant examples:**
 - open-loop, narrowband amplifier, reactively matched
 - wideband balanced amplifier
 - wideband parallel feedback amplifier
 - ultrawideband distributed amplifier
 - narrowband LNA with inductive series feedback

An RF evergreen: open loop, narrowband, maximum gain amplifier design



- Narrowband ($< 10\% f_0$) design can be carried out virtually as single frequency design + some further optimization
- The design flow can be summarized as follows:
 - *Choose the active device (e.g. cutoff frequency $> 2-4 \times f_0$)*
 - *Choose a suitable bias point and design the bias network*
 - *Make the active device unconditionally stable*
 - *Evaluate the optimum loads for maximum gain*
 - *Design matching networks*
 - *Generate the circuit schematic and layout*
- Broadbanding is possible, but up to a certain point (see later)!



Amplifier “typical” bias points

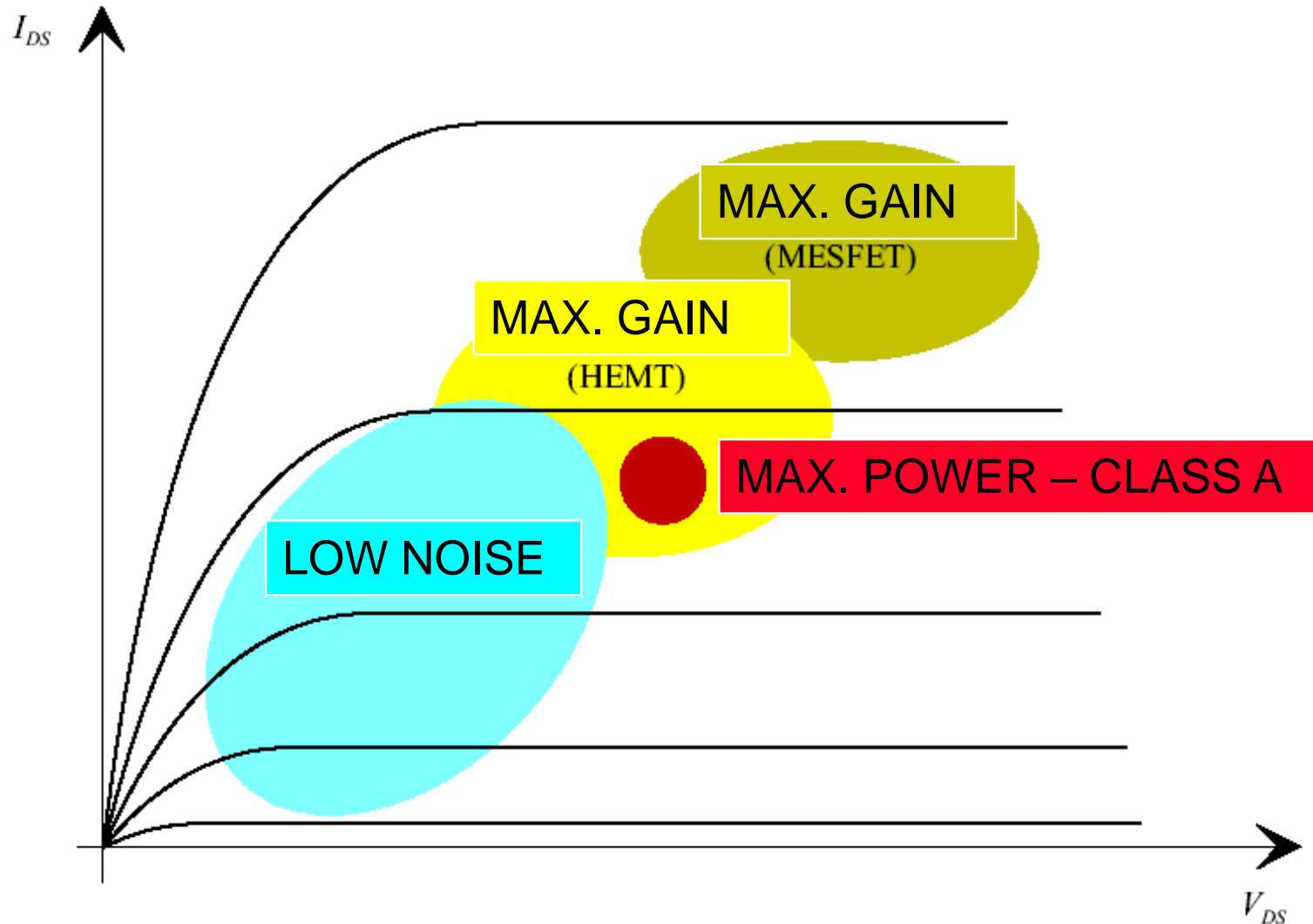

Device biasing: active device bias Ts




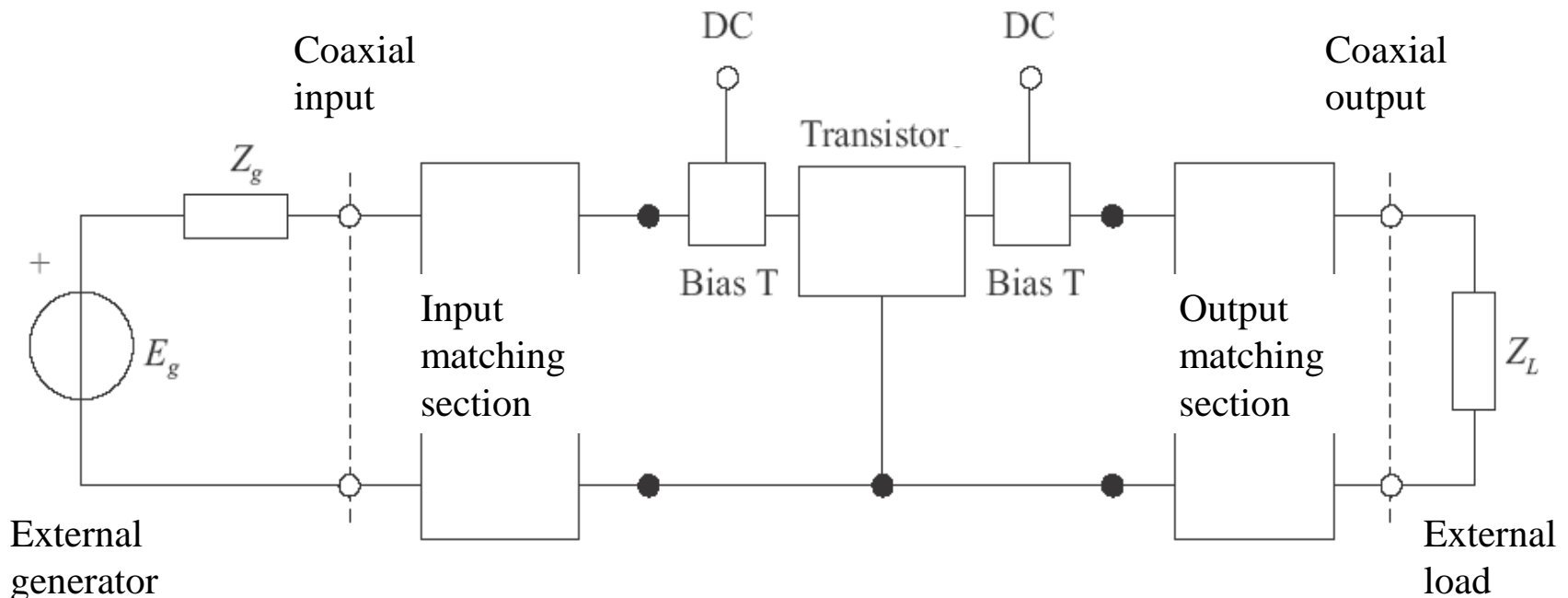
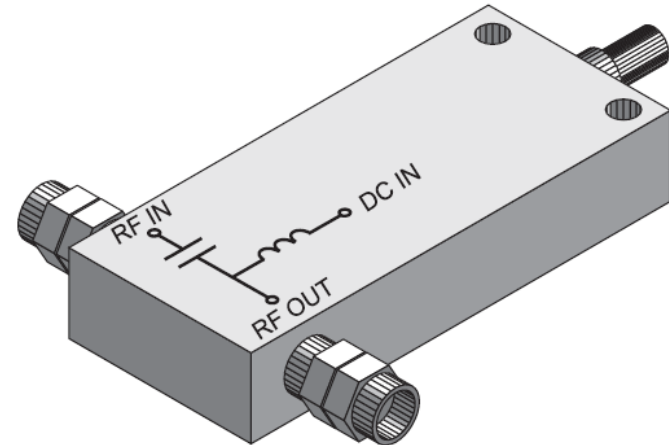
- The bias network has to be decoupled from the RF circuit through proper components, called *Bias Tees* (*Bias Ts*).
- Bias T wideband design (e.g. for instrumentation) critical



Lumped Bias T



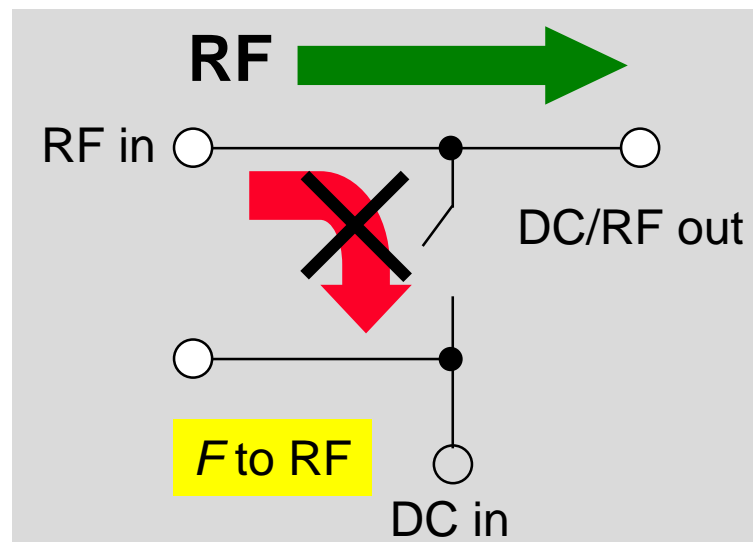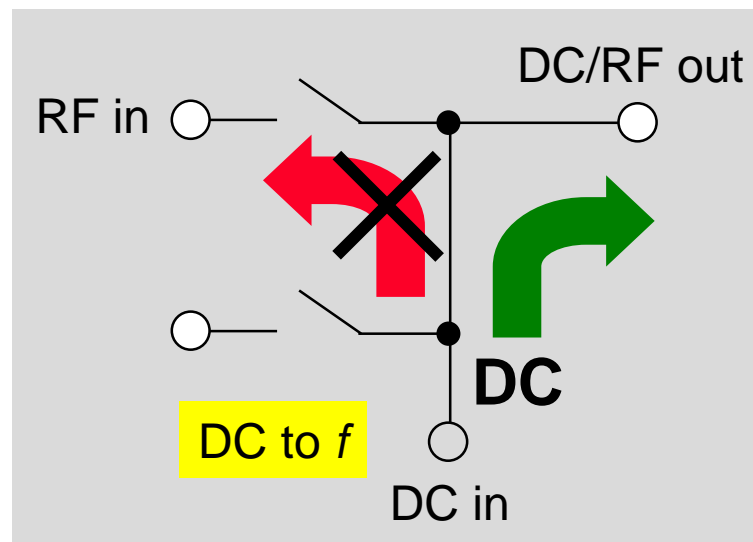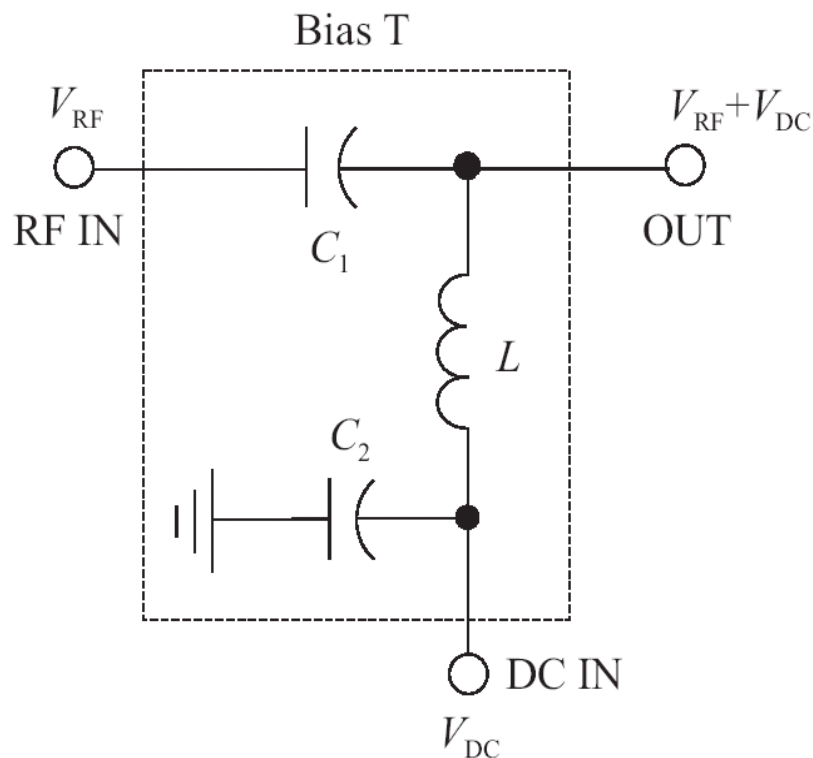- A tripole with two inputs (RF IN, DC IN) and one output (RF+DC OUT).
- In practice $DC \rightarrow$ from 0 to f , $RF \rightarrow$ from F to infinity; if f and F are low the design requires very high C and L values



Making active devices unconditionally stable








- RF transistors have a decreasing gain with frequency → they are potentially unstable at least at low frequency, if not in the design bandwidth.
- Stabilization from DC to the design bandwidth is **mandatory** since there is no control on the loads
- **In-band stabilization** can be avoided by *proper load and generator design* but is usually **strongly advised** for easier design, above all in microwave monolithic ICs
- Above the design bandwidth the device becomes asymptotically stable.
- Since the amount of stabilization needed decreases with frequency, proper resistive network with reactive bypasses or blocks have to be used.

Stabilizing active devices



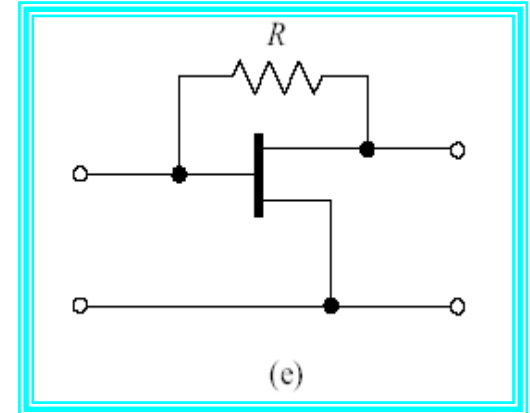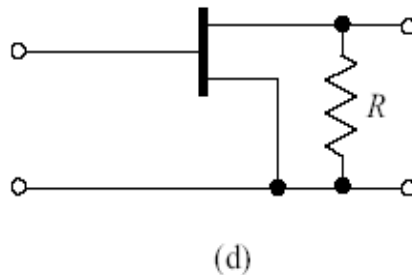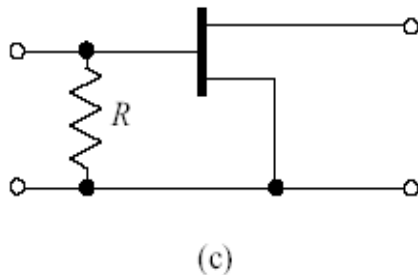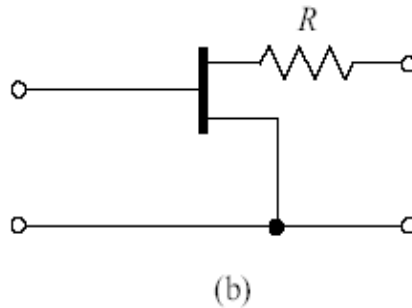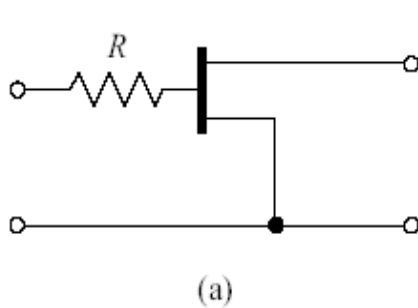- Stabilization can be obtained through
 - series/parallel input resistors [not for LNA \rightarrow noise at input!]
 - series/parallel output resistors
 - feedback resistors [non convenient, unless for feedback amplifiers]
- **Mandatory at low frequency**, optional in band




Inconvenient in open loop design

Stabilizing through dissipative elements



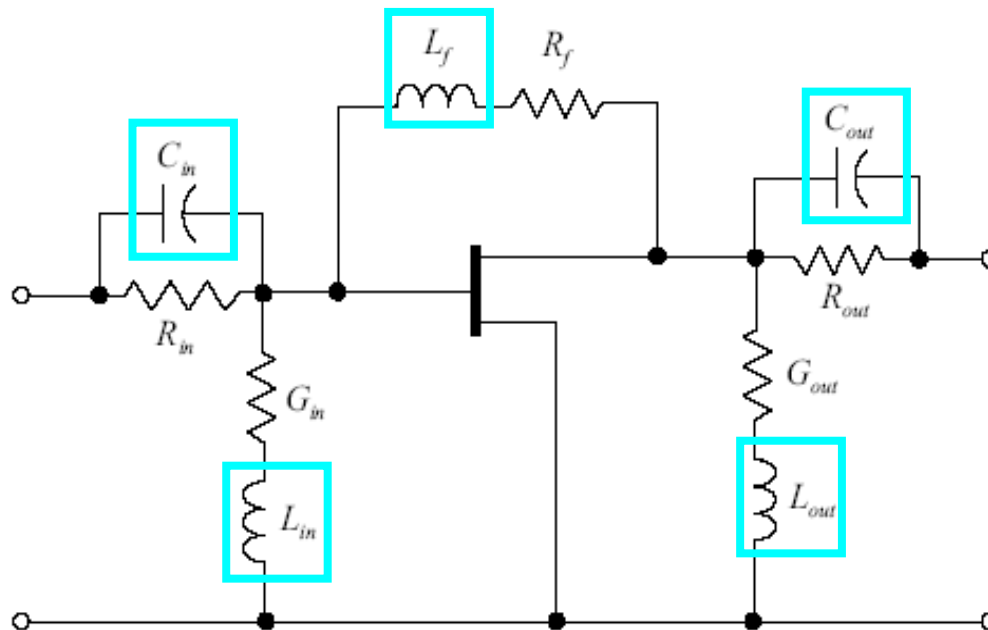- A combination of reactive and resistive elements can be exploited to obtain the required degree of stabilization at low frequency (strong) and at high frequency (light)
- This can be obtained through numerical optimization of K ; too strong in-band stabilization compromises gain
- Often just *one* resistor + reactive element is enough (C preferred)




- Sometimes the stabilization networks can be integrated with the Bias Ts
- In the feedback loop also a DC block is needed!

Matching networks



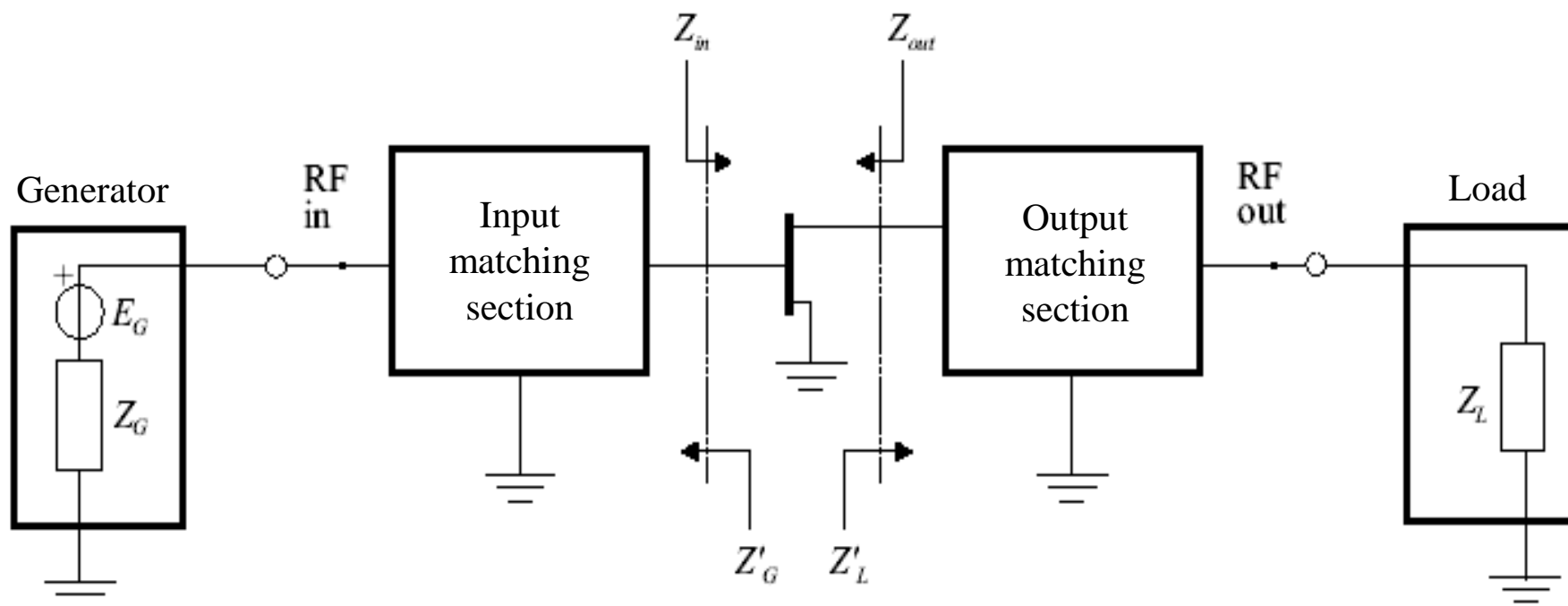
- Needed to transform the load and generator impedances (e.g. $50\ \Omega$) in the device optimum load
- **Reactive match**: narrowband (why?)
- **Resistive or lossy match**: more wideband but noisy



Multistage interstage matching



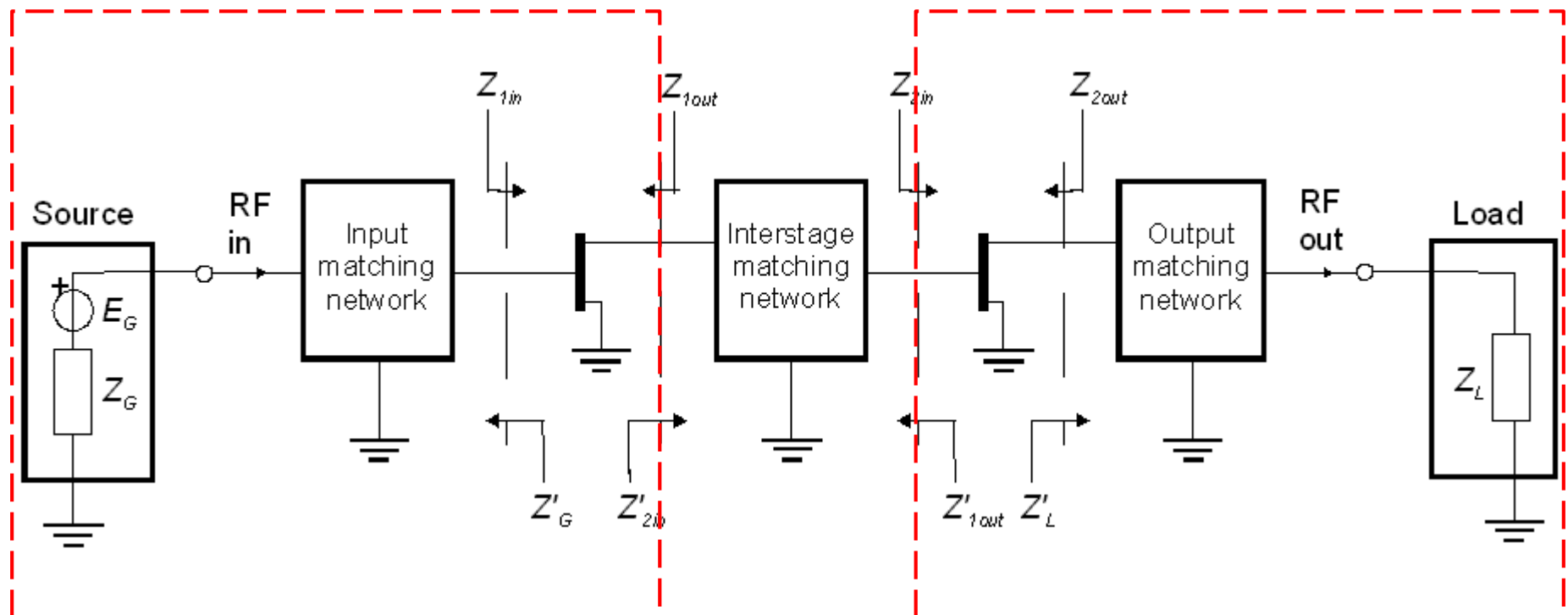- The interstage matching section transforms into each other the complex impedances allowing for conjugate matching of the e.g. first and second stage
- Typically optimization required!




Two-stage design recipe




- The optimum load of the two stage is known at a given frequency starting from the S-parameters
- The output stage matching section transforms $Z_L \rightarrow Z'_L$
- The input stage matching section transforms $Z_G \rightarrow Z'_G$
- Since conjugate matching holds in the chain we have:
$$Z_{2in} = Z'^*_{1out}$$
- The inter-stage matching stage transforms the complex impedances $Z_{2in} \rightarrow Z'_{2in} = Z^*_{1out}$
- Difficulty: the input and output matching sections design amount to transform a real into a complex impedance, the interstage two complex impedances into each other (see next slides).
- The design can also be carried out by optimization.

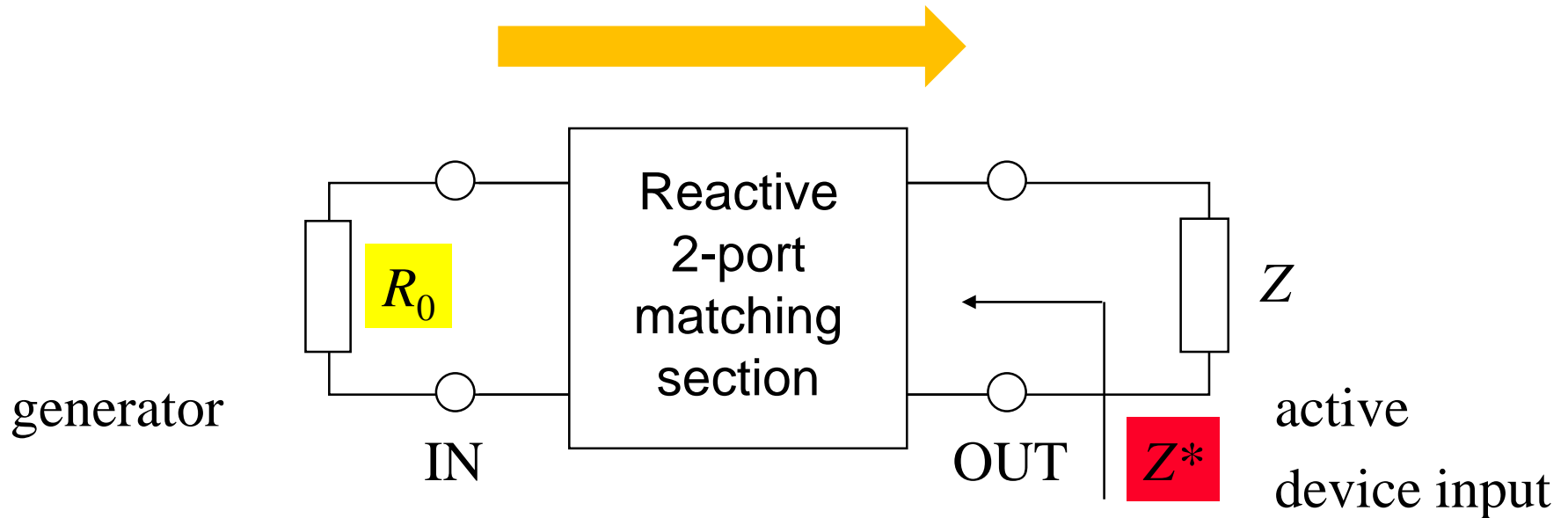Design of lossless (reactive) matching networks




- Lumped- or distributed-parameter implementation

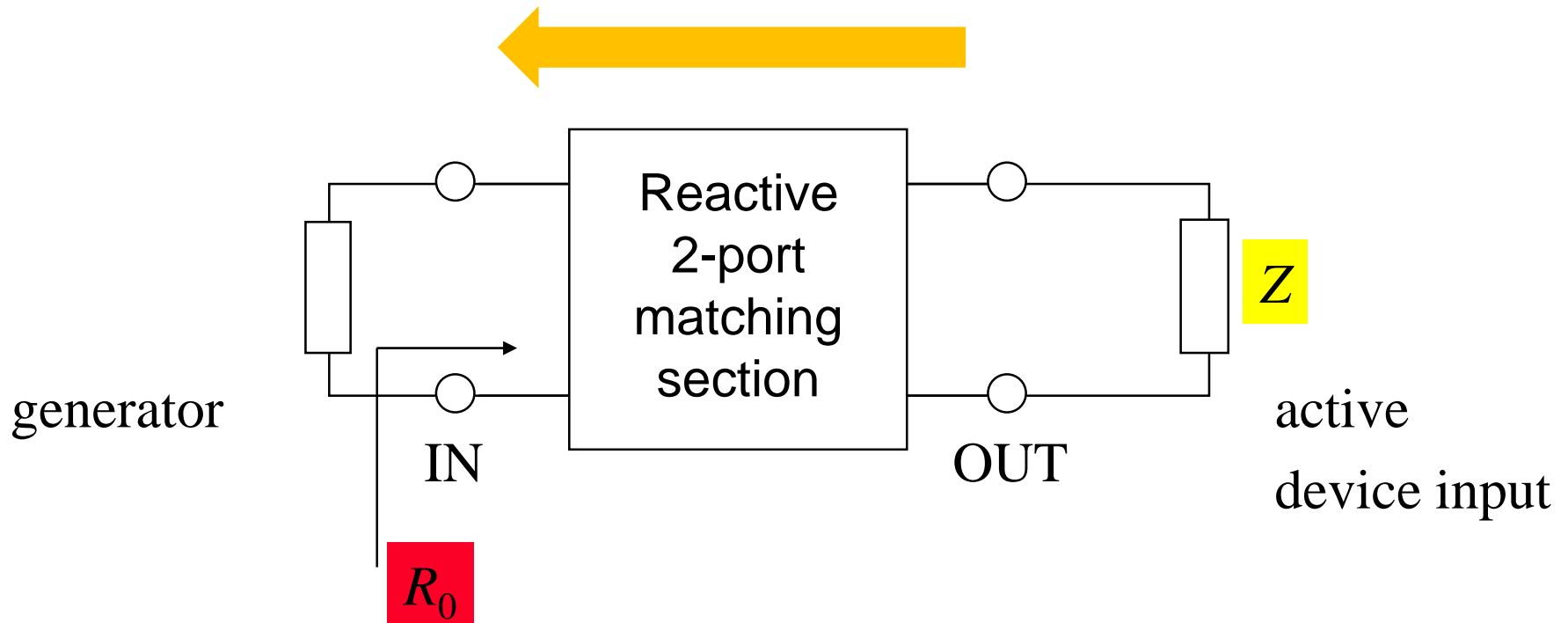Design of lossless (reactive) matching networks




- Lumped- or distributed-parameter implementation

In general...

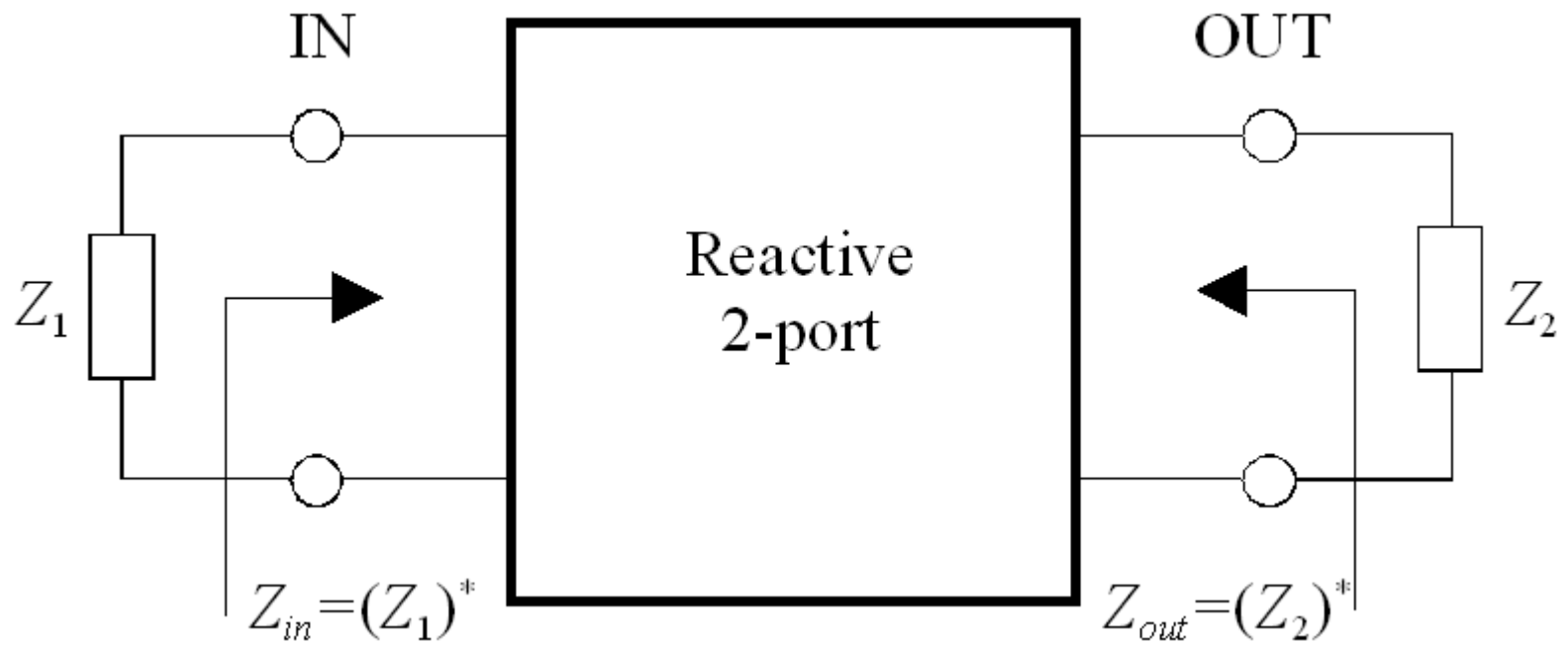

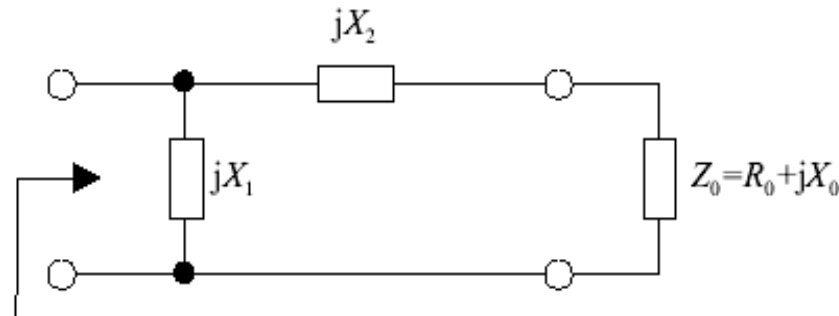Example of lumped reactive matching sections



$$G_M = 1/50, B_M = 0$$

(a)


$$X_1 = \left(-B_M \mp \sqrt{\frac{G_M}{R_0}(1 - G_M R_0)} \right)^{-1}$$

$$X_2 = -X_0 \pm \sqrt{\frac{R_0}{G_M}(1 - G_M R_0)}.$$

A

$$G_M R_0 < 1$$

in practice $R_0 < 50\Omega$

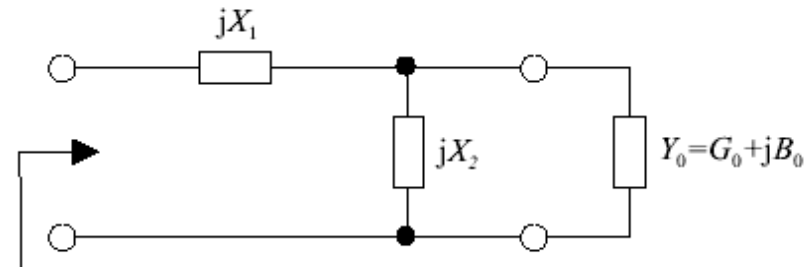

$$R_M = 50, X_M = 0$$

(b)

$$X_1 = X_M \pm \sqrt{\frac{R_M}{G_0}(1 - R_M G_0)}$$

$$X_2 = \left(B_0 \mp \sqrt{\frac{G_0}{R_M}(1 - R_M G_0)} \right)^{-1}$$

B



$$R_M G_0 \leq 1$$

in practice $G_0 < 1/50S$

Solutions A and B on the Smith chart



Smith chart Z_0 , norm. res. $1/G_M$

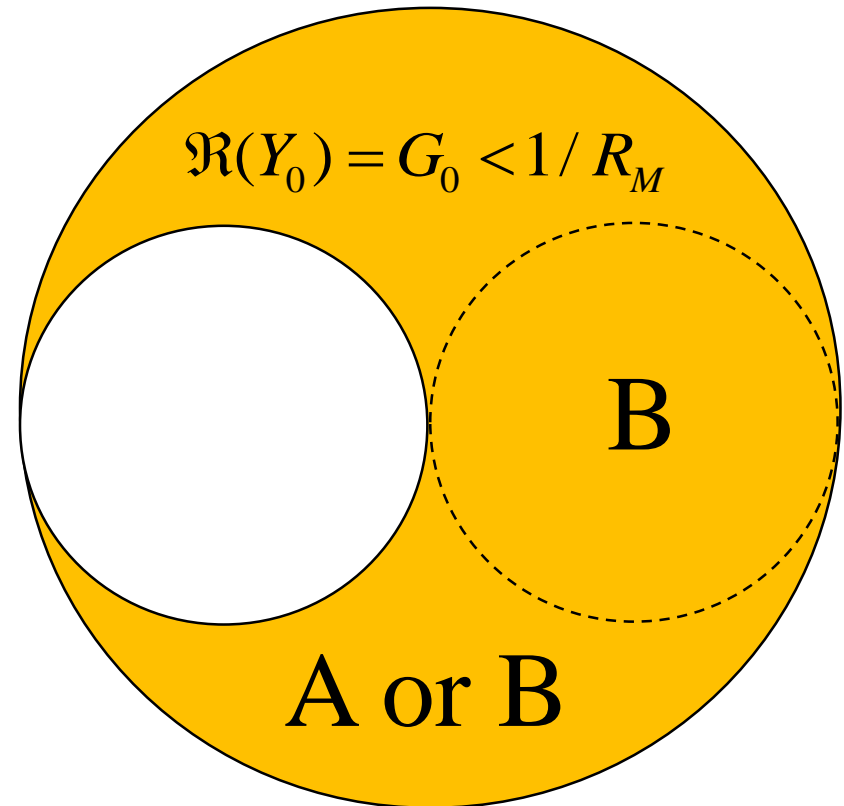
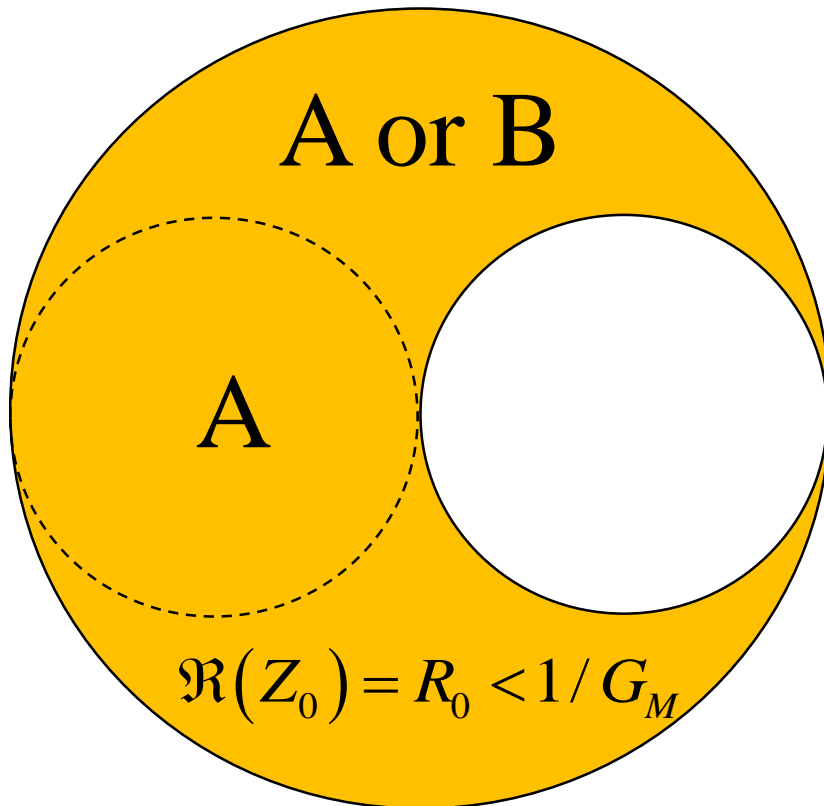


Smith chart Z_0 , norm. res. R_M

Line + stub matching network



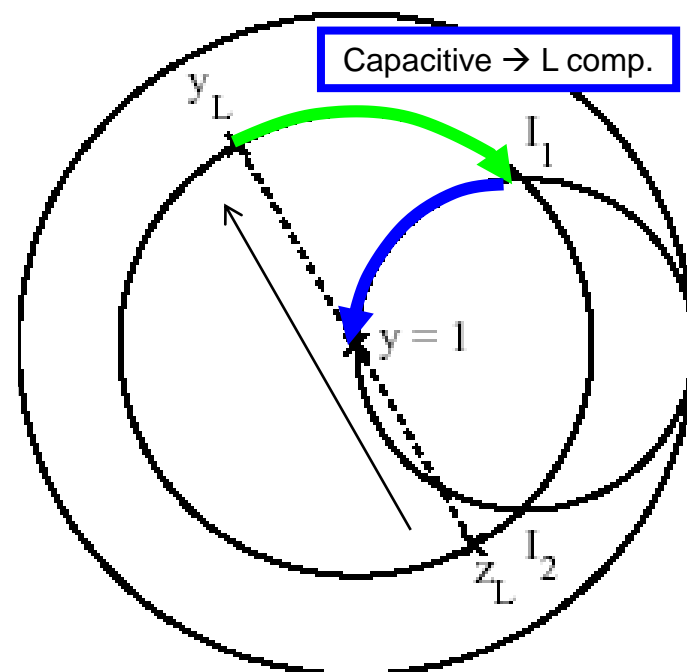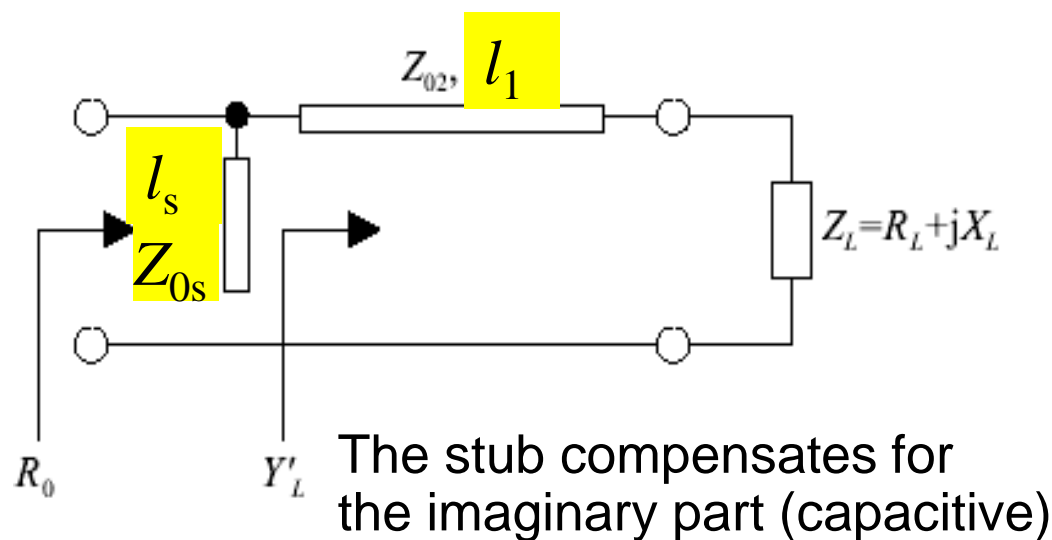Typically the characteristic line impedance is given and only the line and stub length should be designed




Shorted stub

$$Z_{in}(z) = jZ_{0s} \tan(\beta z)$$

Line + stub matching network



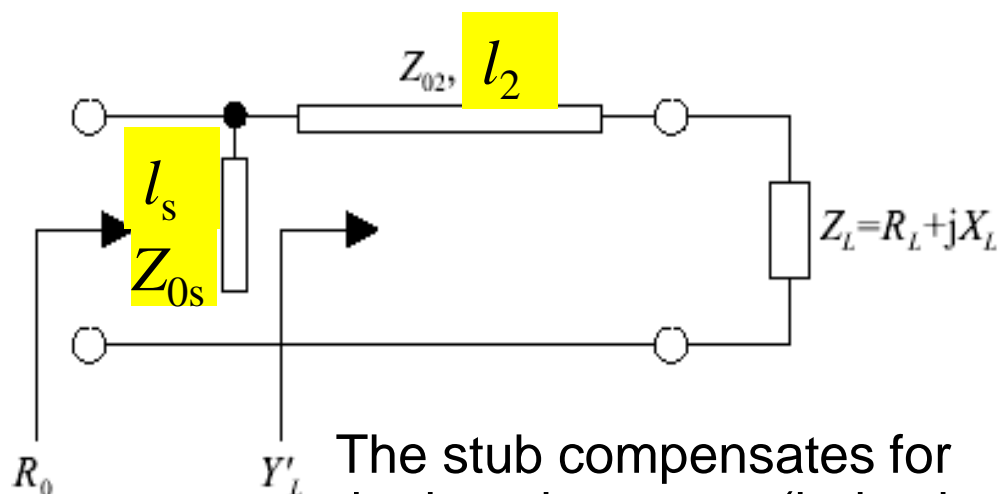
Typically the characteristic line impedance is given and only the line and stub length should be designed



The stub compensates for the imaginary part (inductive)

Open stub
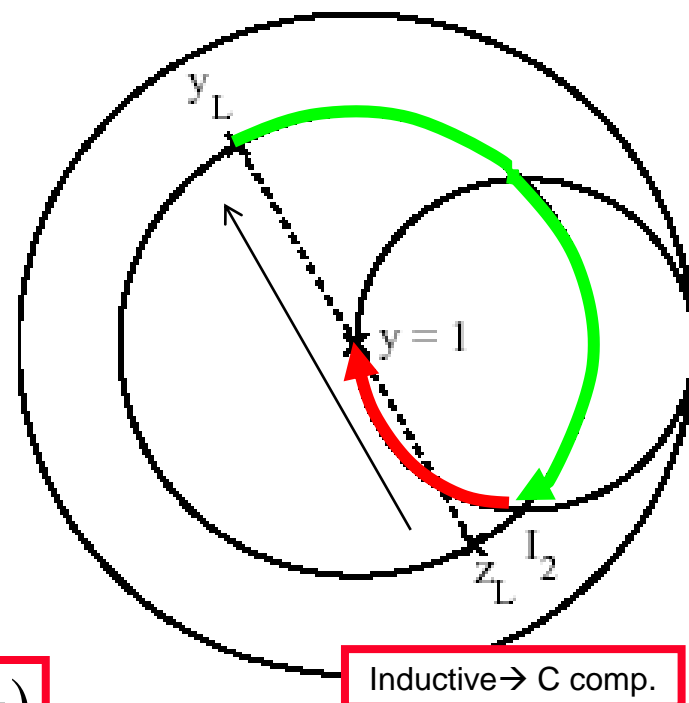
$$Z_{in}(z) = -jZ_{\infty} \cot(\beta z)$$






Wideband reactive matching sections for wideband amplifiers




- Transistor inputs (outputs) are **RC networks** (series or parallel)
- It can be theoretically shown that a lumped or distributed **lossless matching section** allows for ideal matching in a **discrete set of frequencies**; however (*Fano's limit*) the average matching *decreases exponentially with bandwidth*, independent of the complexity of the matching stages
- **Moreover, the device MAG decreases with $f \rightarrow$ to have wideband flat gain we need to mismatch the transistor (usually at input)**
- If the input network is reactive **mismatch at low frequency** is **not compatible** with **low input reflection coefficient**, unless some dissipative elements are introduced directly or indirectly in the input matching network

Wideband open-loop amplifiers

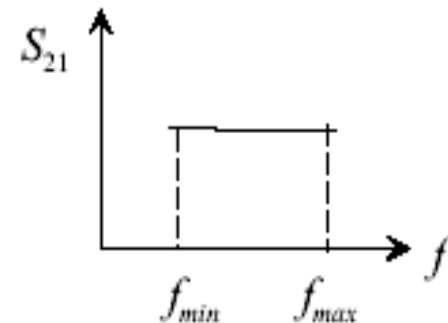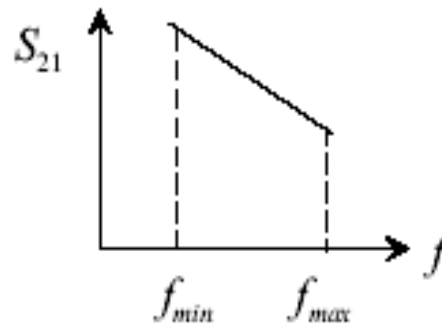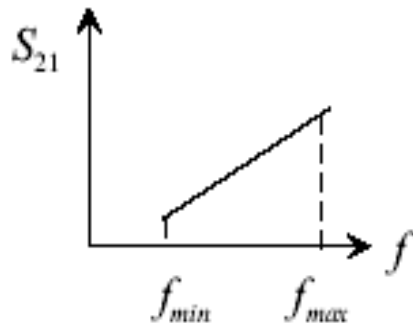


The balanced amplifier

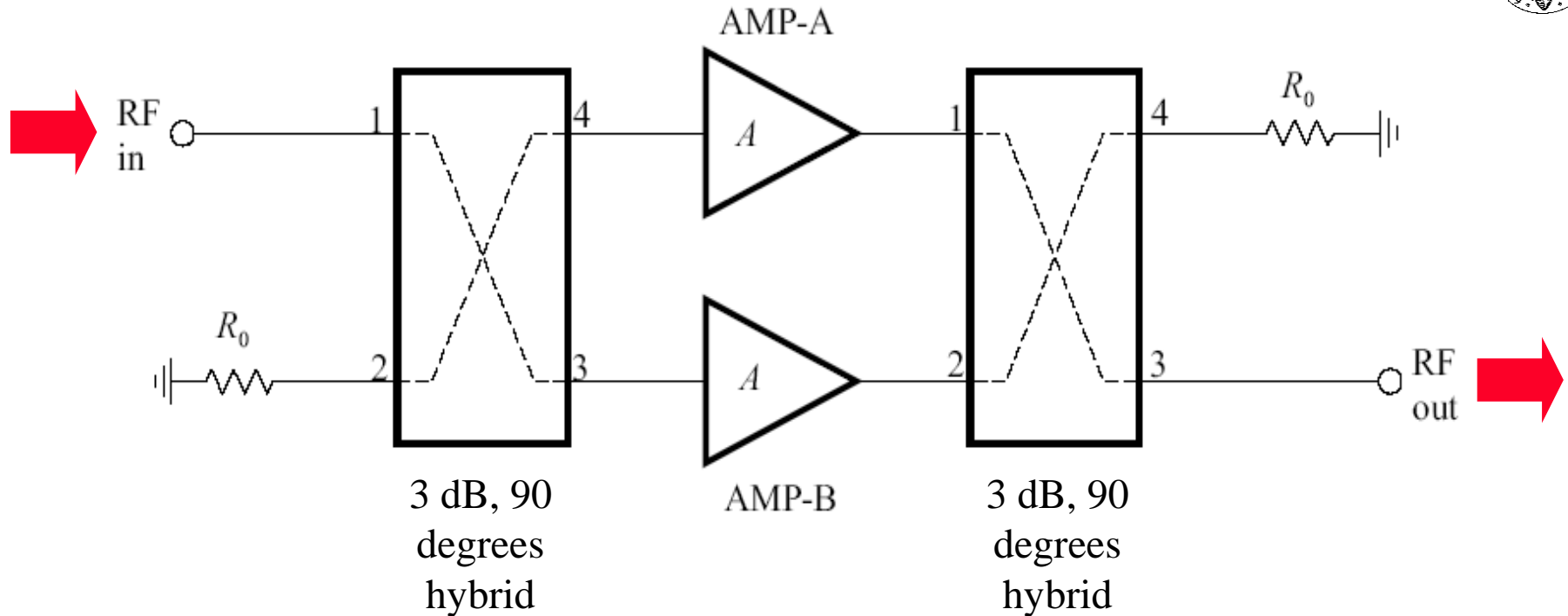

- The BA allows for
 - IN/OUT matching in the coupler bandwidth (1 octave approx.)
 - Gain equal to the single amplifier $|S_{21}|$
 - Saturation power twice as the single amplifier P_{sat}

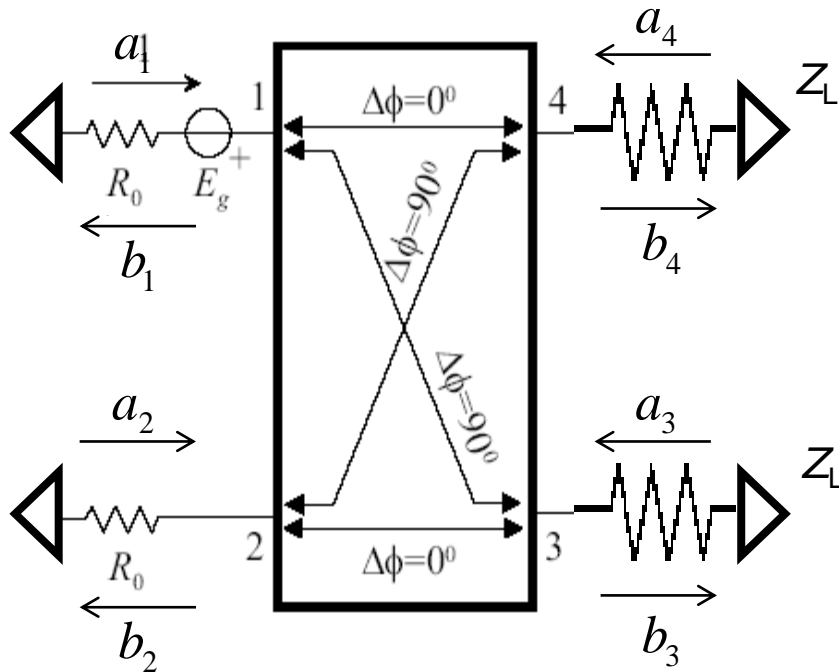Balanced amplifier: **input power match** (center band)




Port 3 and 4 are loaded
by the same impedance
different from norm. Z

S matrix at centerband

$$\mathbf{b} = \mathbf{S}\mathbf{a}$$

$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{bmatrix} = \begin{bmatrix} 0 & 0 & -j/\sqrt{2} & 1/\sqrt{2} \\ 0 & 0 & 1/\sqrt{2} & -j/\sqrt{2} \\ -j/\sqrt{2} & 1/\sqrt{2} & 0 & 0 \\ 1/\sqrt{2} & -j/\sqrt{2} & 0 & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \\ a_4 \end{bmatrix}$$

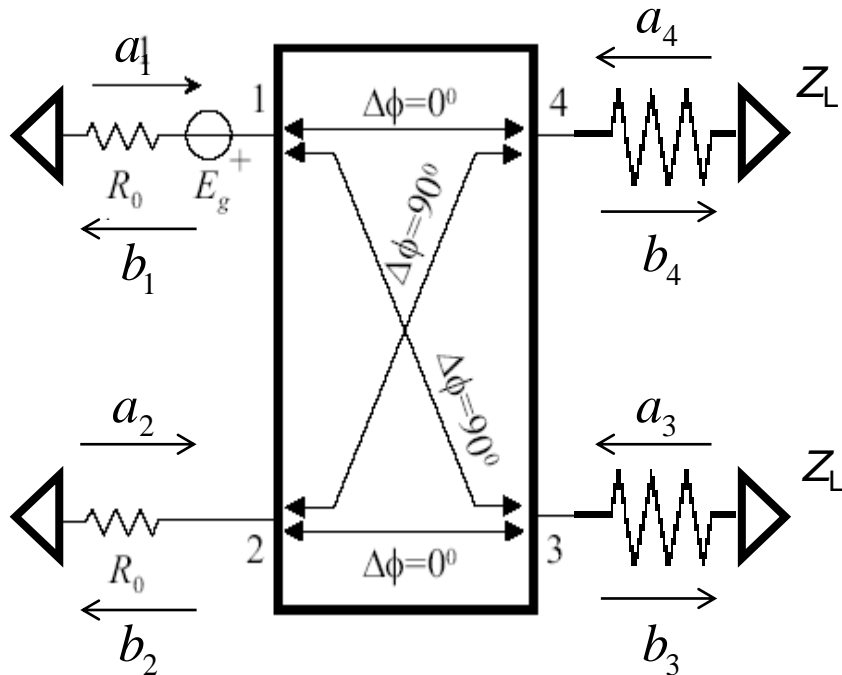Balanced amplifier: **input power match** (center band)



Port 1 is matched if
the two amplifiers have
the same input impedance
The reflected power is
dissipated in the resistor
at port 2

$$b_1 = \frac{-j}{\sqrt{2}} a_3 + \frac{1}{\sqrt{2}} a_4$$

$$b_2 = \frac{1}{\sqrt{2}} a_3 + \frac{-j}{\sqrt{2}} a_4$$

$$a_2 = 0 \text{ (port loaded on } R_0) \rightarrow$$


$$b_3 = \frac{-j}{\sqrt{2}} a_1, \quad b_4 = \frac{1}{\sqrt{2}} a_1$$

$$a_3 = \Gamma_L b_3 = \frac{-j\Gamma_L}{\sqrt{2}} a_1, \quad a_4 = \Gamma_L b_4 = \frac{\Gamma_L}{\sqrt{2}} a_1$$

$$b_1 = \frac{-j}{\sqrt{2}} \frac{-j\Gamma_L}{\sqrt{2}} a_1 + \frac{1}{\sqrt{2}} \frac{\Gamma_L}{\sqrt{2}} a_1 = 0$$


$$b_2 = \frac{1}{\sqrt{2}} \frac{-j\Gamma_L}{\sqrt{2}} a_1 + \frac{-j}{\sqrt{2}} \frac{\Gamma_L}{\sqrt{2}} a_1 = -j\Gamma_L a_1$$

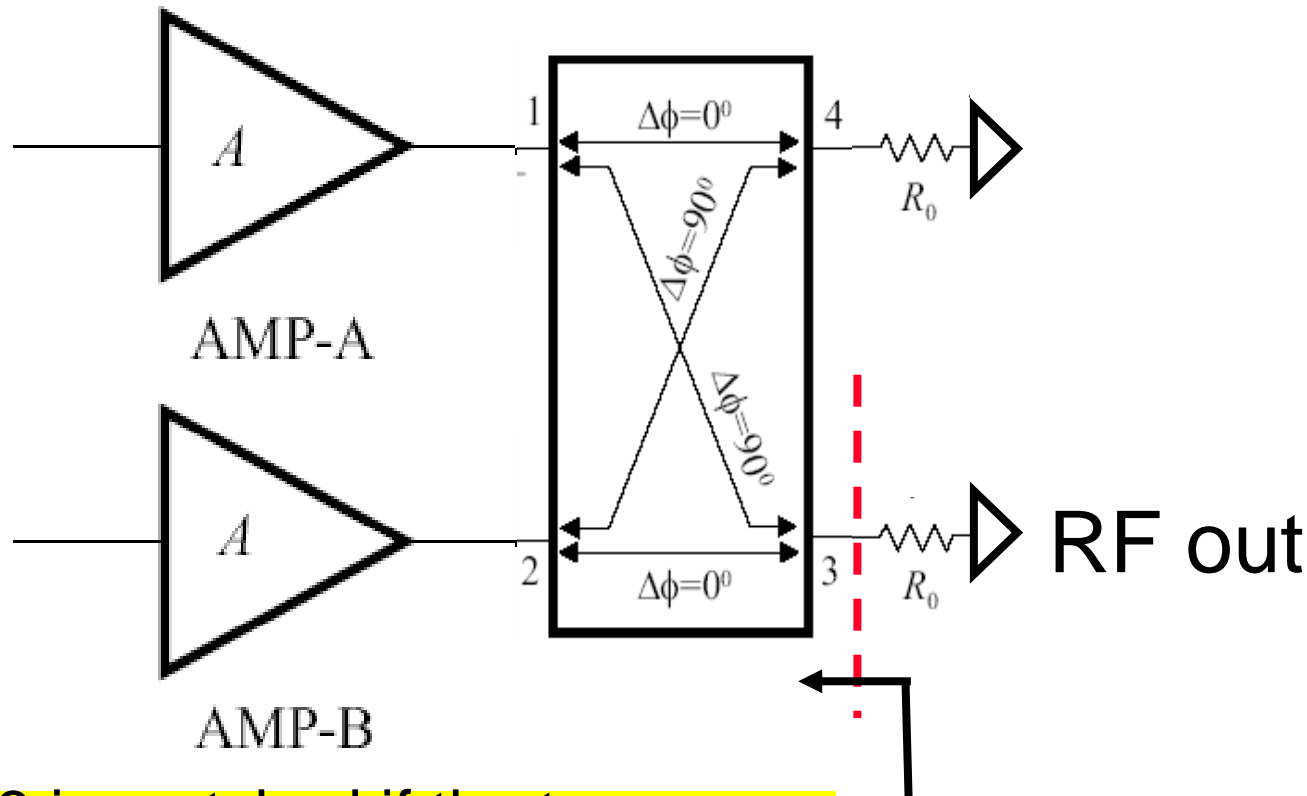Balanced amplifier: **output power match** (center band)




Port 3 is matched if the two amplifiers have the same output impedance
The reflected power is dissipated in the resistor at port 4

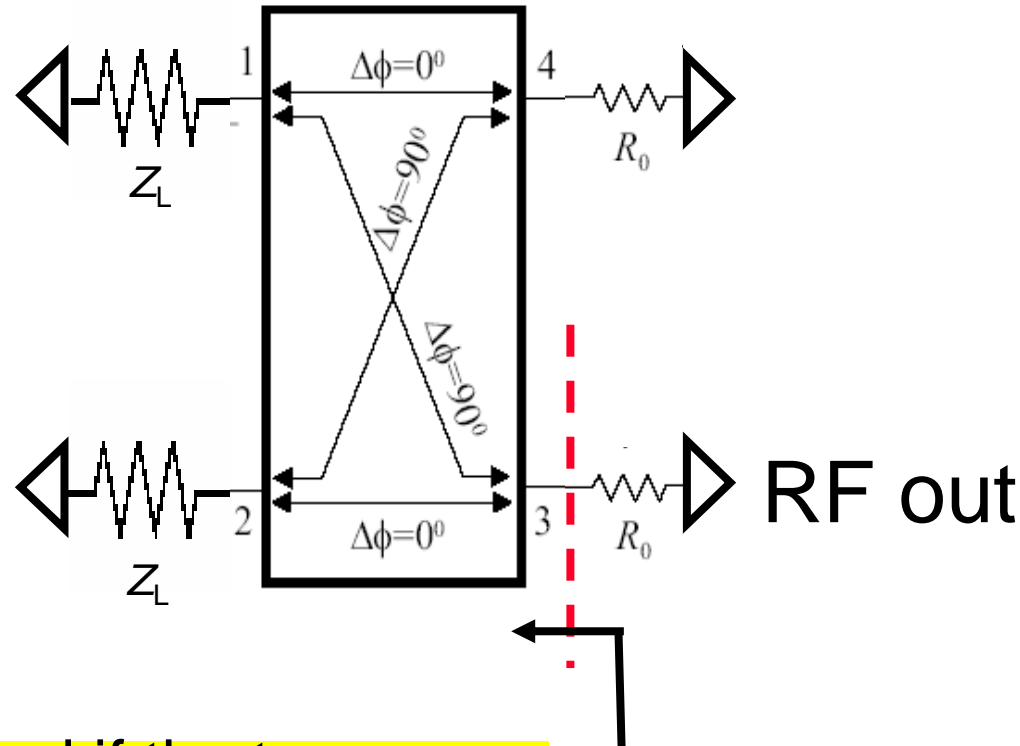Balanced amplifier: **output power match** (center band)



Port 3 is matched if the two amplifiers have the same output impedance
The reflected power is dissipated in the resistor at port 4

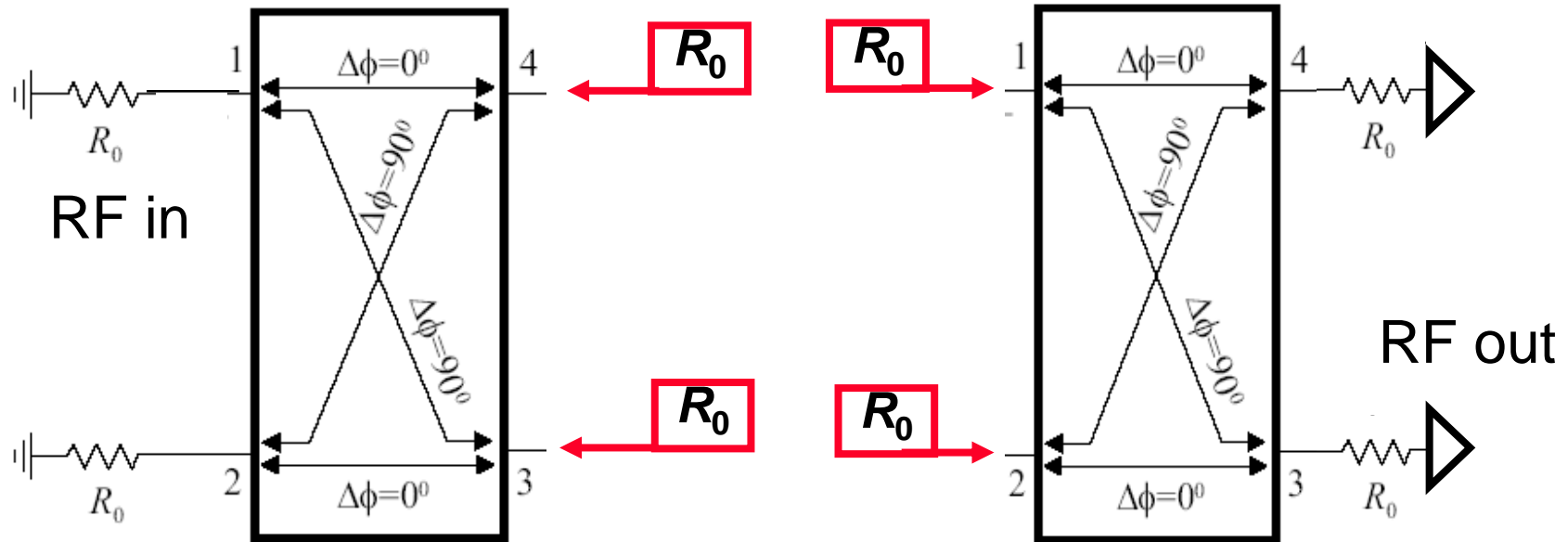Balanced amplifier: device input and output matching



Ports 1 and 2 are matched, $a_1 = a_2 = 0$

$$b_3 = \frac{-j}{\sqrt{2}} a_1 + \frac{1}{\sqrt{2}} a_2 = 0$$


$$b_4 = \frac{1}{\sqrt{2}} a_1 - \frac{j}{\sqrt{2}} a_2 = 0$$

also ports 3 and 4 have $Z_{in} = R_0$

At the input and output ports the two AMPS A B are closed on the normalization resistance

The AMPS A B is described by the S parameters on R_0

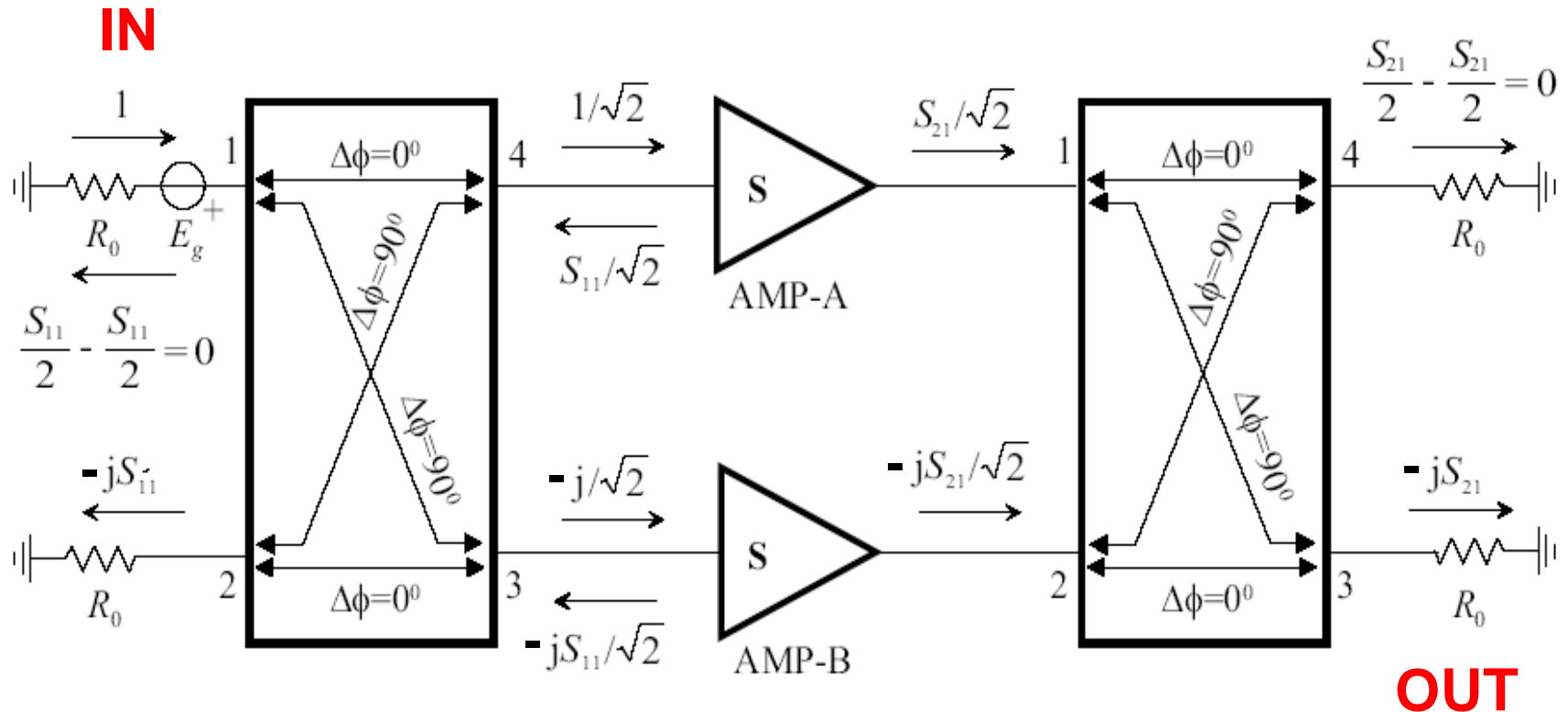Balanced amplifier operation (centerband)




Amplification $\rightarrow |S_{21}|$, gain $|S_{21}|^2$

Balanced amplifier operation (out of centerband)




IN

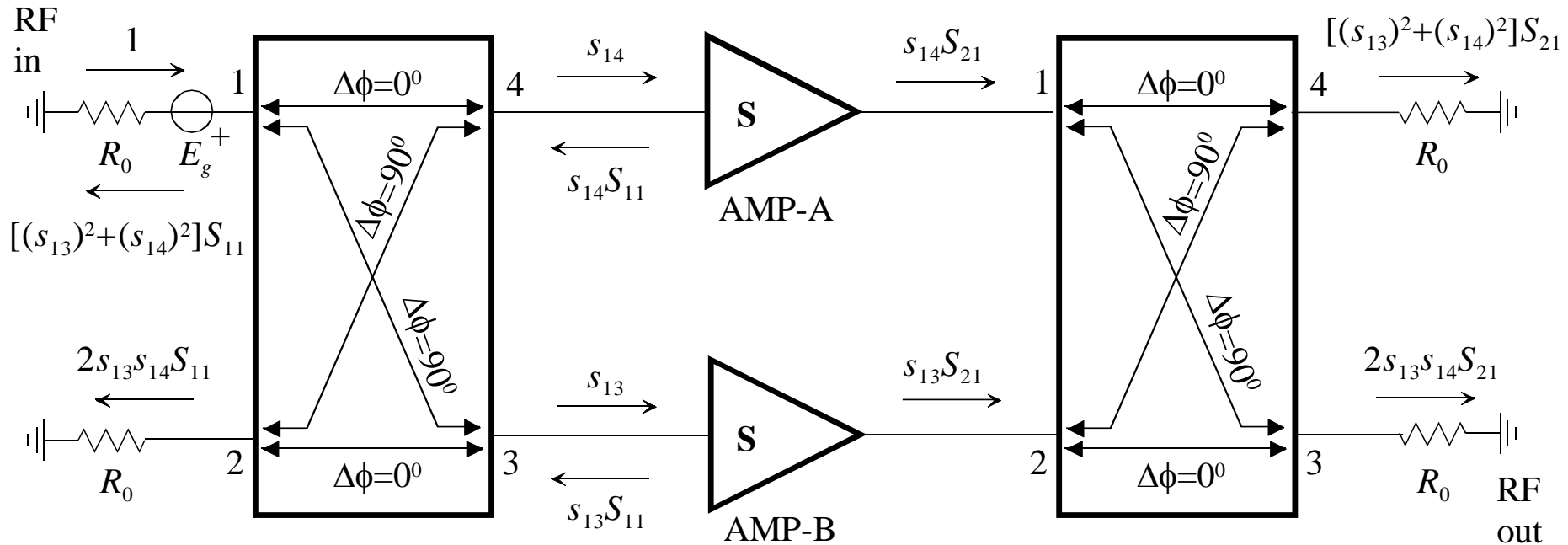


Amplification $\rightarrow |2s_{13}s_{14}S_{21}|$, gain $|2s_{13}s_{14}S_{21}|^2$

OUT

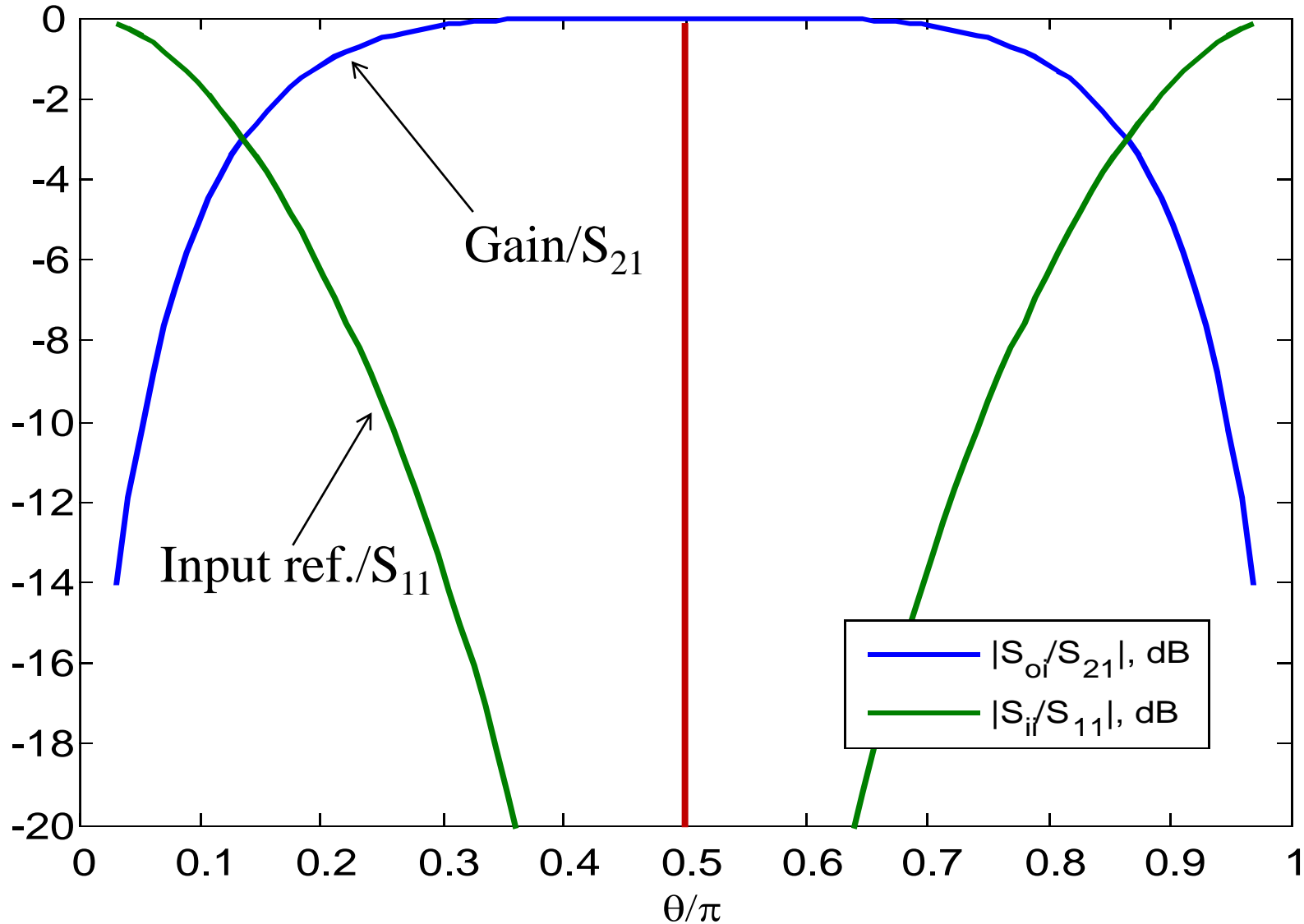Balanced amplifier operation (out of centerband)



Mm-wave MMIC balanced amplifier

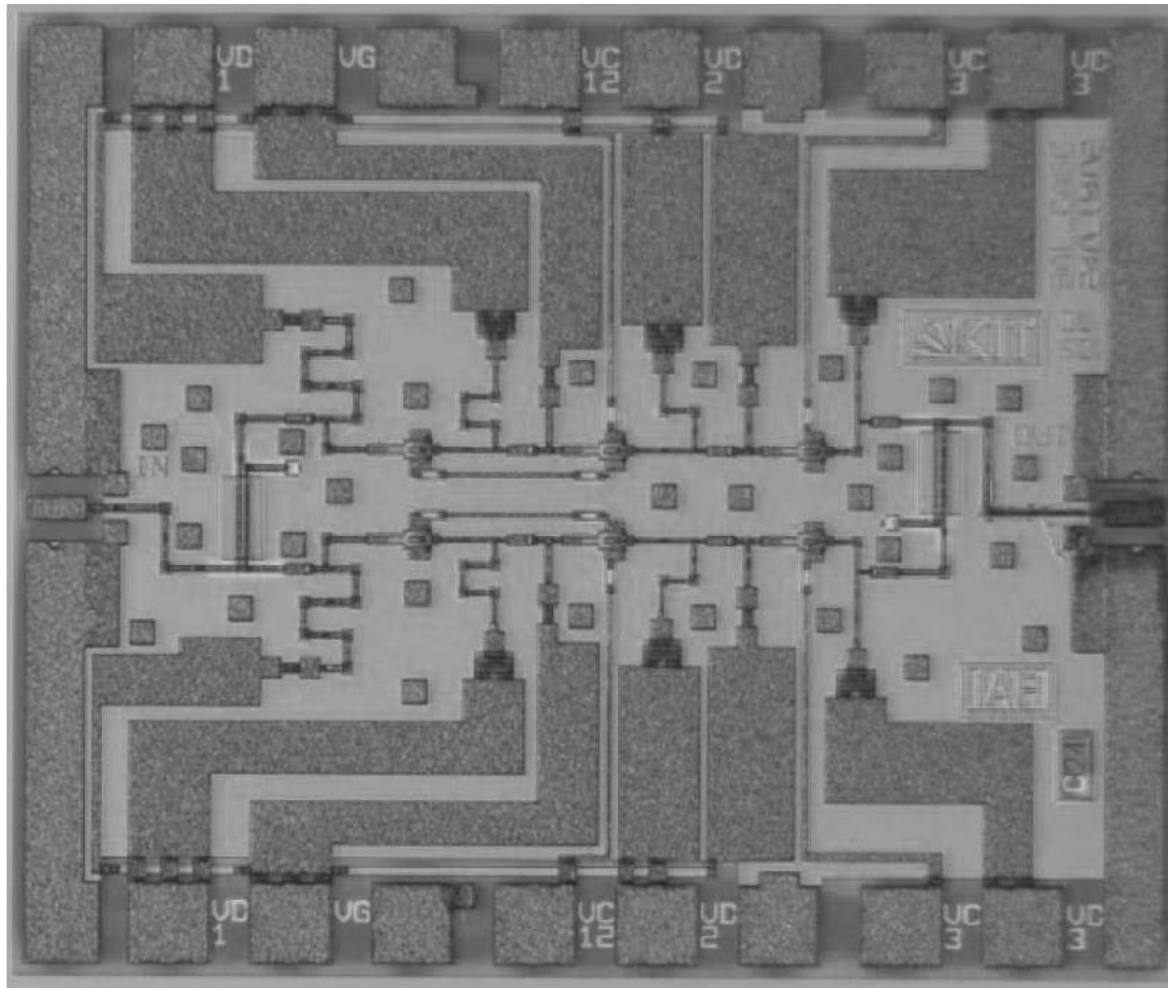


Copyright 2013 IEEE. All rights reserved. Reprinted, with permission, from J. Laengst et al., "Balanced medium power amplifier MMICs from 200 to 270 GHz," in 2013 38th International Conference on Infrared, Millimeter, and Terahertz Waves (IRMMW-THz), Sep. 2013, pp. 1–3.

RF parallel feedback amplifiers



- As at low frequency, resistive parallel feedback is used to obtain **flat gain from low frequency up to a high-frequency cutoff**, however feedback also **improves input and output matching**
- Parallel feedback requires high (enough) open-loop gain vs. gain with feedback
- In the example we consider in the low-frequency limit a device with *mixed resistive series-parallel feedback*; **reactive elements** are added to the feedback path to increase the gain flatness (“**inductive peaking**”)
- Feedback common also in narrowband MMIC design → gain stabilization vs. active element fluctuations.

RF feedback amplifier design

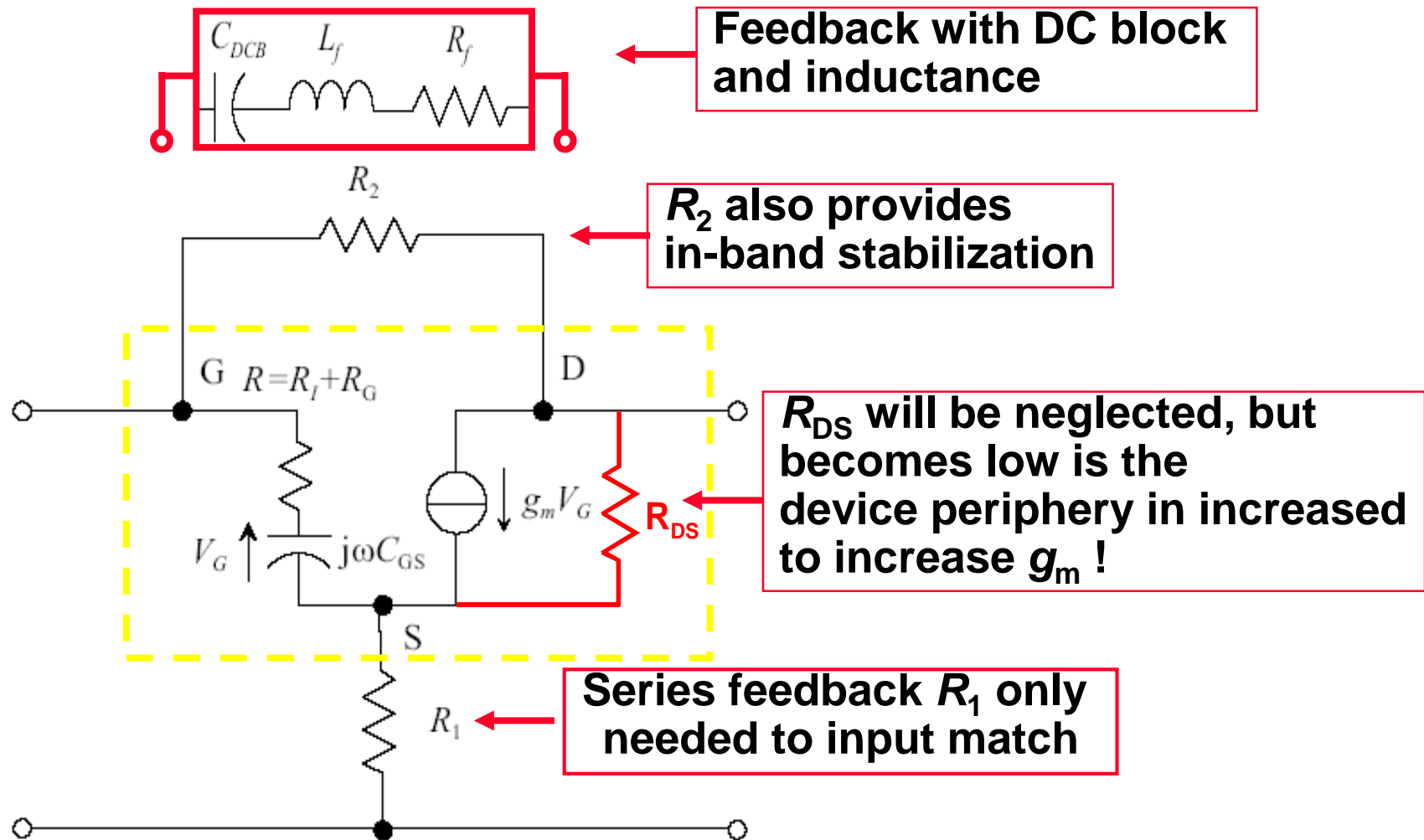

Low-frequency analysis



- The scattering parameters of the feedback amplifier can be shown to be:

$$S_{11}(0) = \frac{(R_2 R_1 - R_0^2) g_m + R_2}{(2R_0 R_1 + R_2 R_1 + R_0^2) g_m + 2R_0 + R_2}$$

$$S_{12}(0) = 2R_0 \frac{1 + R_1 g_m}{(2R_0 R_1 + R_2 R_1 + R_0^2) g_m + 2R_0 + R_2}$$

$$S_{21}(0) = -2R_0 \frac{(R_2 - R_1) g_m - 1}{(2R_0 R_1 + R_2 R_1 + R_0^2) g_m + 2R_0 + R_2}$$

$$S_{22}(0) = \frac{(R_2 R_1 - R_0^2) g_m + R_2}{(2R_0 R_1 + R_2 R_1 + R_0^2) g_m + 2R_0 + R_2}.$$

- Input and output matching can be simultaneously obtained by proper dimensioning of the feedback resistances!

Matching condition and minimum open-loop gain



- Matching implies:

$$R_1 = \frac{R_0^2}{R_2} - \frac{1}{g_m}$$



$$S_{11f} = S_{22f} = 0$$

$$S_{12f} = \frac{R_0}{R_0 + R_2}$$

$$S_{21f} = \frac{R_0 - R_2}{R_0}$$

- The parallel feedback resistance is obtained from feedback gain:

$$R_2 = R_0 \left(1 + |S_{21f}(0)| \right)$$

- A minimum g_m is needed:





$$g_m \geq R_2 / R_0^2$$

- corresponding to a condition on open-loop gain:

$$|S_{21}| \geq 2 \left(1 + |S_{21f}(0)| \right)$$

- The transconductance can be increased by scaling but with a decrease of $R_{DS} \dots$
- In MMIC design the minimum g_m is used to avoid series feedback

S parameters with & without feedback

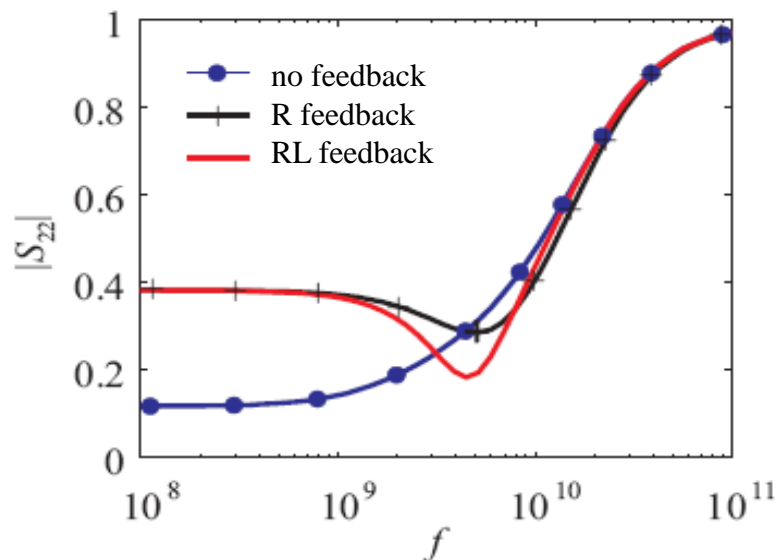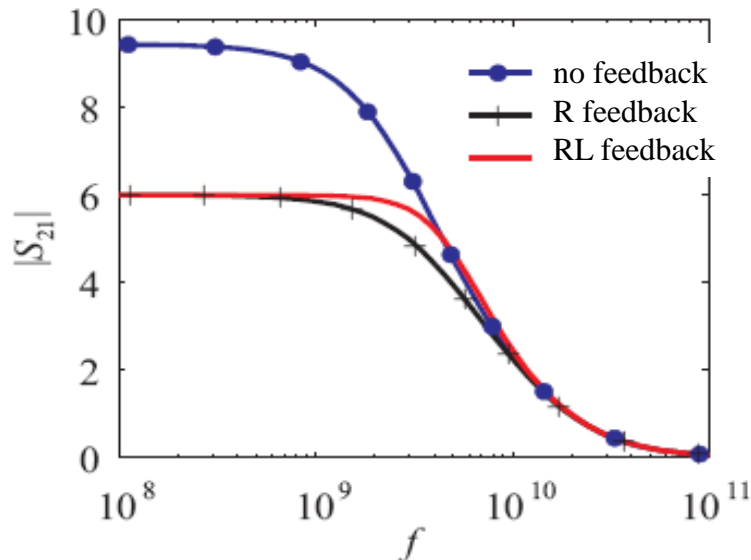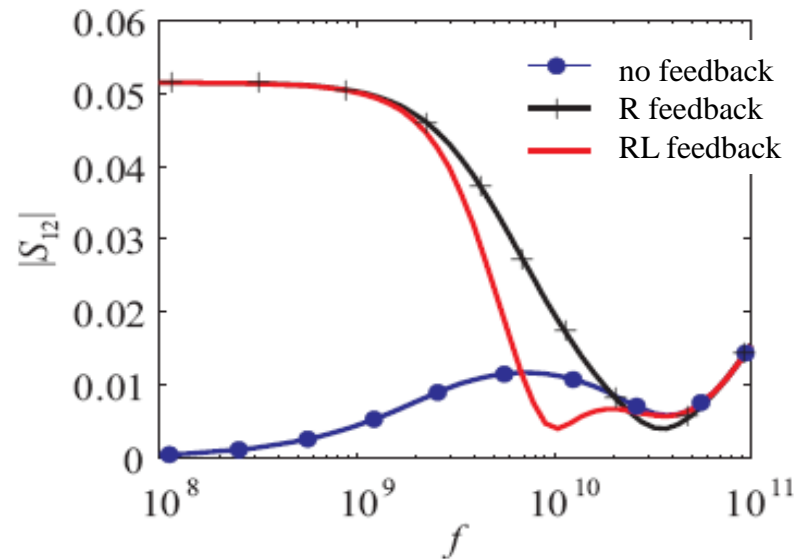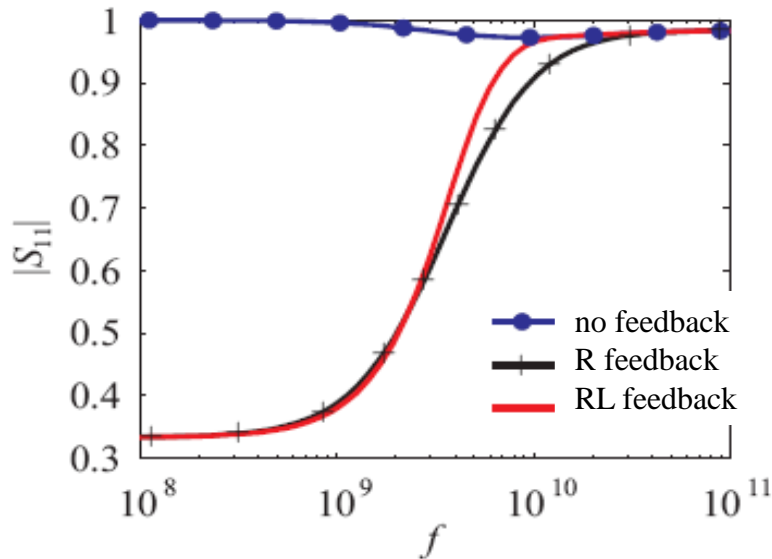



Ultrawideband distributed amplifiers (DAMPs)




- DAMPs allow to (theoretically) increase the gain-bandwidth product (GBP) of conventional amplifiers through a distributed structure made of two transmission lines having the same phase velocity:

$$f_T = A_V(0) f_\beta = \frac{g_m}{2\pi C_{GS}} \quad (\text{why?})$$

Low-frequency gain   3dB bandwidth

- In practice the bandwidth is limited by velocity mismatch and by losses; transmission lines are implemented through a discrete-cell approach
- Practical DAMPS have 5-10 cells with low gain (10-15 dB) but spectacular bandwidths (e.g. 100 KHz - 60 GHz)

Gain Bandwidth Product

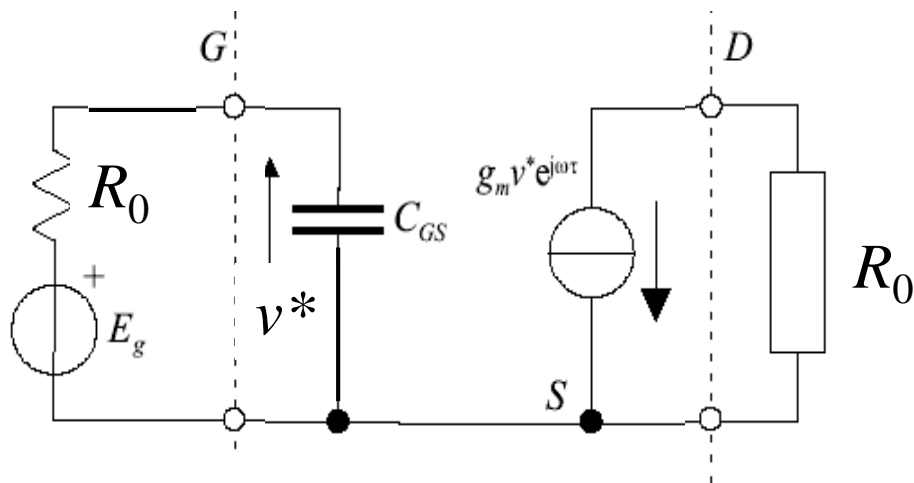

- Same generator and load resistance

$$v^* = \frac{E_g}{1 + j\omega C_{GS} R_0}$$

$$V_L = -g_m v^* R_0 = -\frac{g_m R_0 E_g}{1 + j\omega C_{GS} R_0}$$

$$\frac{V_L}{E_g} = A_V(f) = -\frac{R_0 g_m}{1 + j\omega C_{GS} R_0}$$


$$|A_V(0)| = R_0 g_m, \quad f_\beta = \frac{1}{2\pi C_{GS} R_0}$$

$$|A_V(0)| f_\beta = \frac{g_m}{2\pi C_{GS}} = f_T$$


The DAMP concept



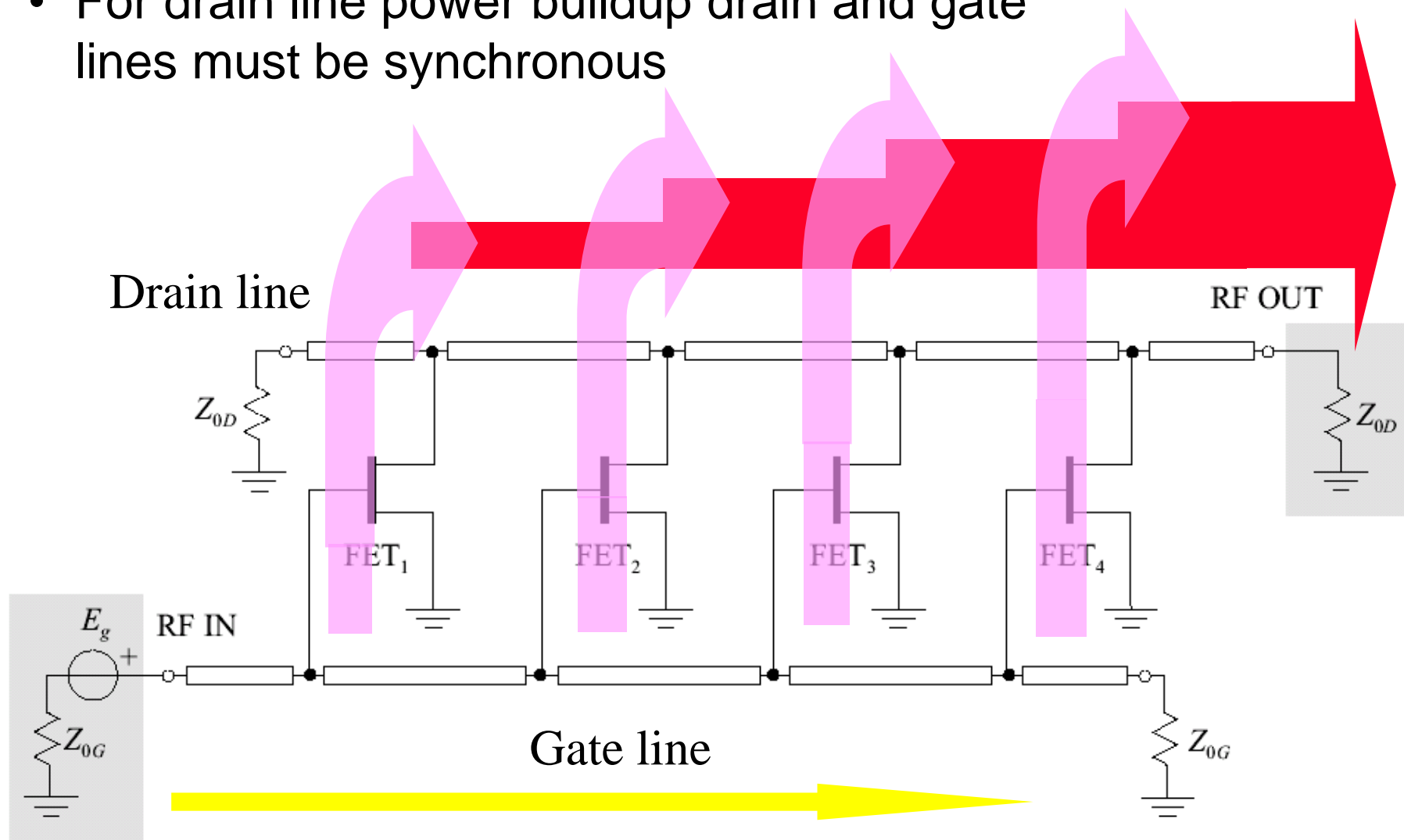
- For drain line power buildup drain and gate lines must be synchronous



The continuous DAMP concept

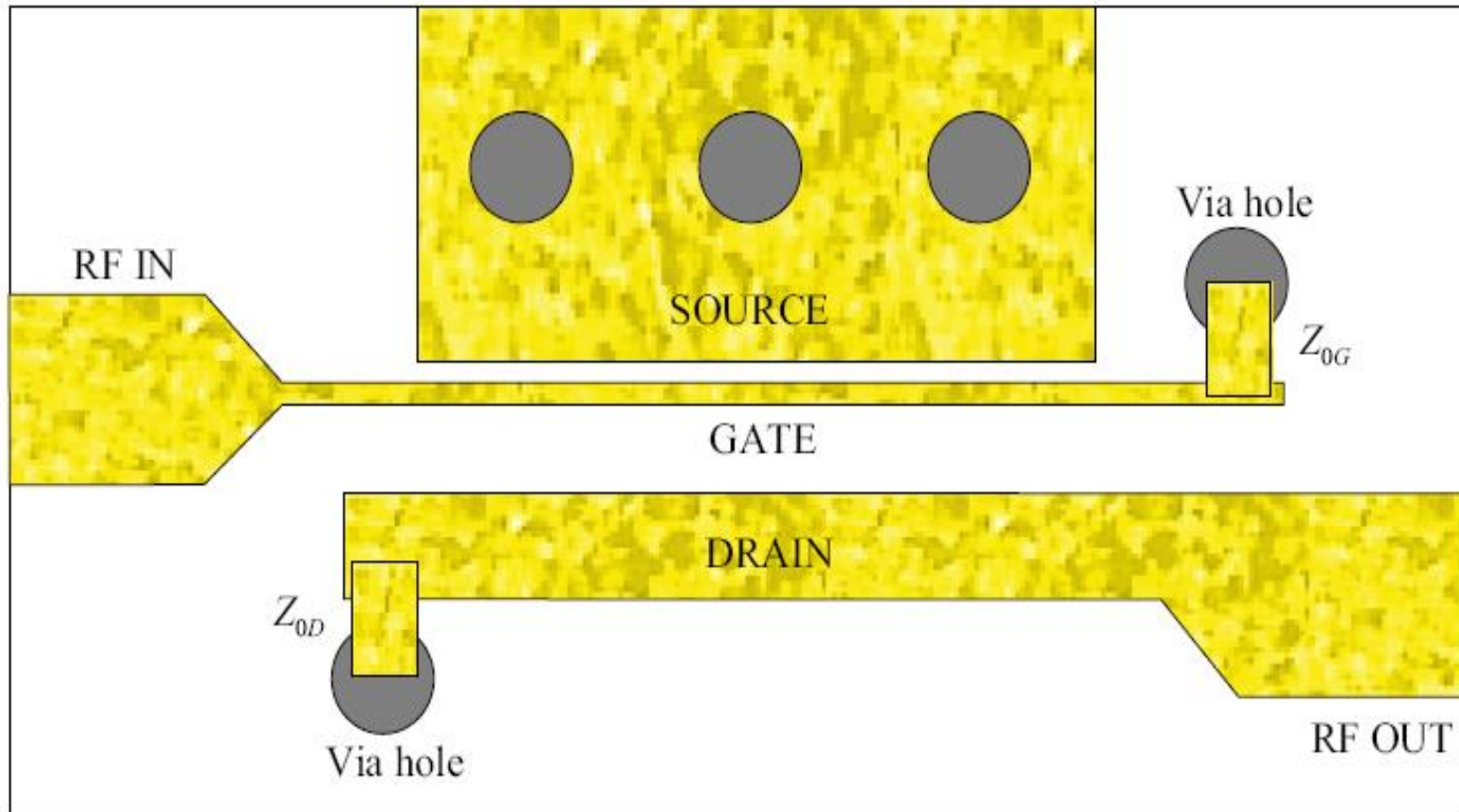

The continuous DAMP model

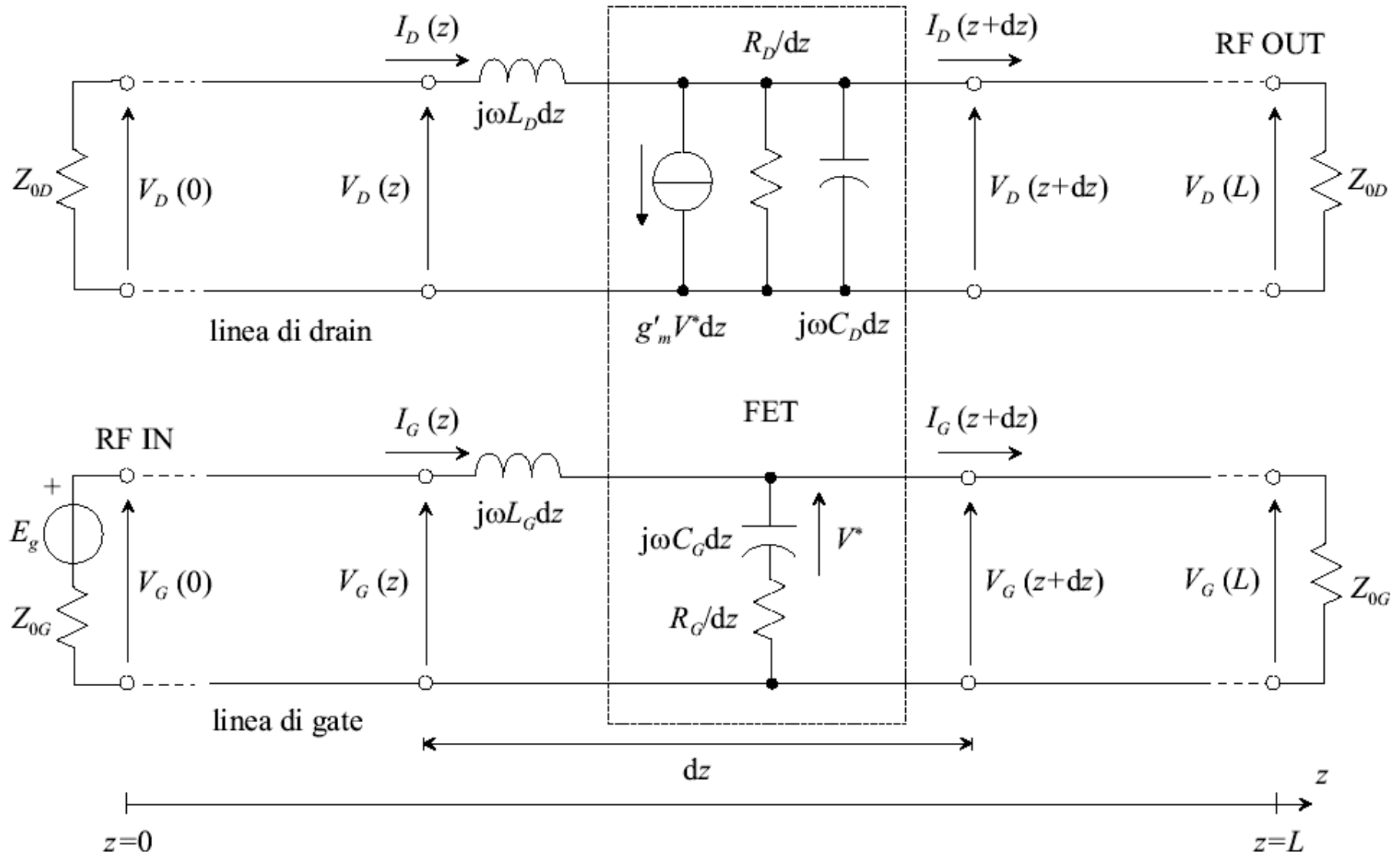

Gate and drain lines



- In general those are dispersive, however a frequency range exists where they behave as lossy nondispersive lines:

$$Z_{0G} \approx \sqrt{\frac{L_G}{C_G}}$$

$$Z_{0D} \approx \sqrt{\frac{L_D}{C_D}}$$

$$\gamma_G \approx \frac{\omega^2 R_G C_G \sqrt{L_G C_G}}{2} + j\omega \sqrt{L_G C_G} = \alpha_G + j\beta_G$$

$$\gamma_D \approx \frac{1}{2} \frac{\sqrt{L_D C_D}}{R_D C_D} + j\omega \sqrt{L_D C_D} = \alpha_D + j\beta_D$$

DAMP frequency response



- The frequency response is of a sinc type:

$$A_V = -\frac{g_m Z_{0D}}{2(1 + j\omega\tau_G)} e^{-\left(\frac{\gamma_D + \gamma_G}{2}\right)L} \frac{\sinh\left[\left(\frac{\gamma_D - \gamma_G}{2}\right)L\right]}{\left(\frac{\gamma_D - \gamma_G}{2}\right)L}$$

- Neglecting losses, infinite bandwidth for synchronous gate and drain lines:**

$$|A_V| = \frac{g_m Z_{0D}}{2} \frac{\sin\left[\left(\frac{\beta_D - \beta_G}{2}\right)L\right]}{\left(\frac{\beta_D - \beta_G}{2}\right)L} \quad \Rightarrow \quad |A_V| = \frac{Z_{0D} g_m}{2}$$

$L_D C_D = L_G C_G$

...too good to be true...




- In practice the frequency response is limited by velocity mismatch and losses:


$$L_{opt} = \frac{\log(\alpha_D / \alpha_G)}{\alpha_D - \alpha_G}$$

- Moreover the continuous amplifier is unfeasible from a technological standpoint → losses are huge, the discrete-cell structure allows an easier velocity matching through lumped or distributed elements
- Bandwidth is limited by losses and by the bandwidth of the delay elements (“artificial lines”).

The discrete DAMP

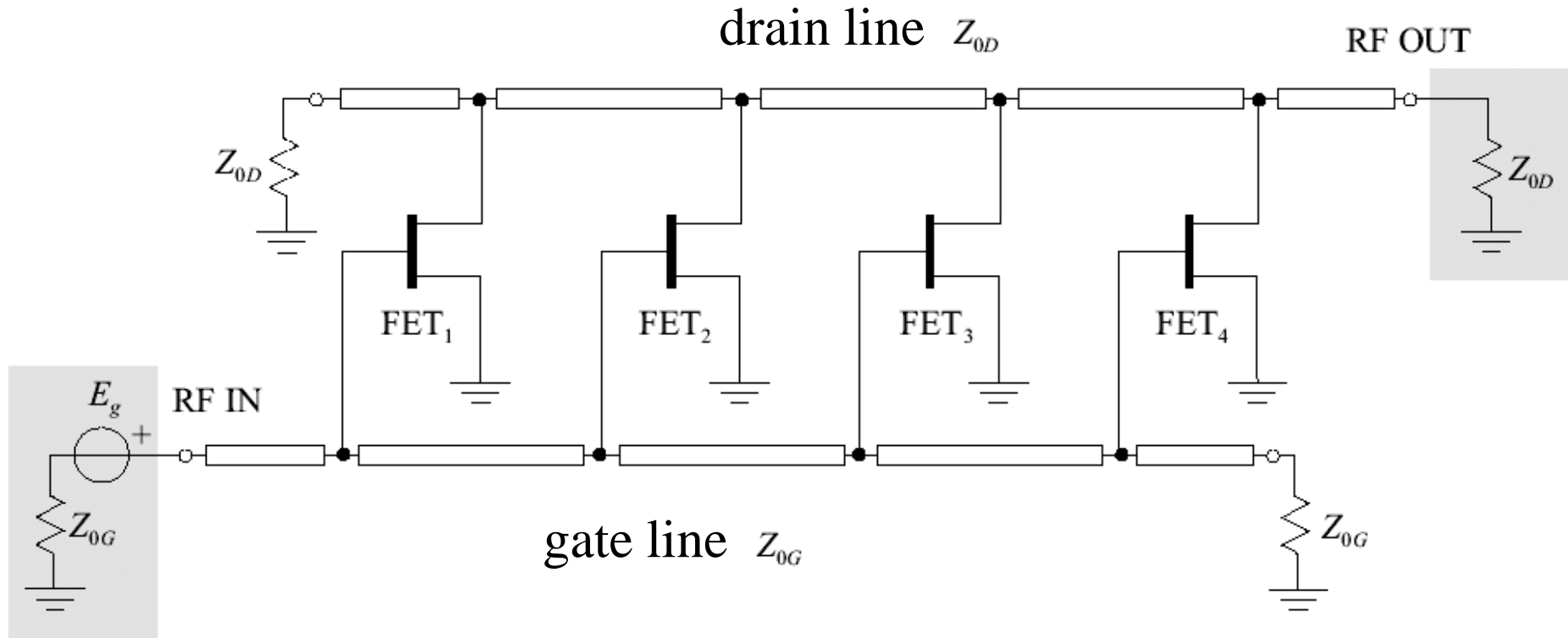

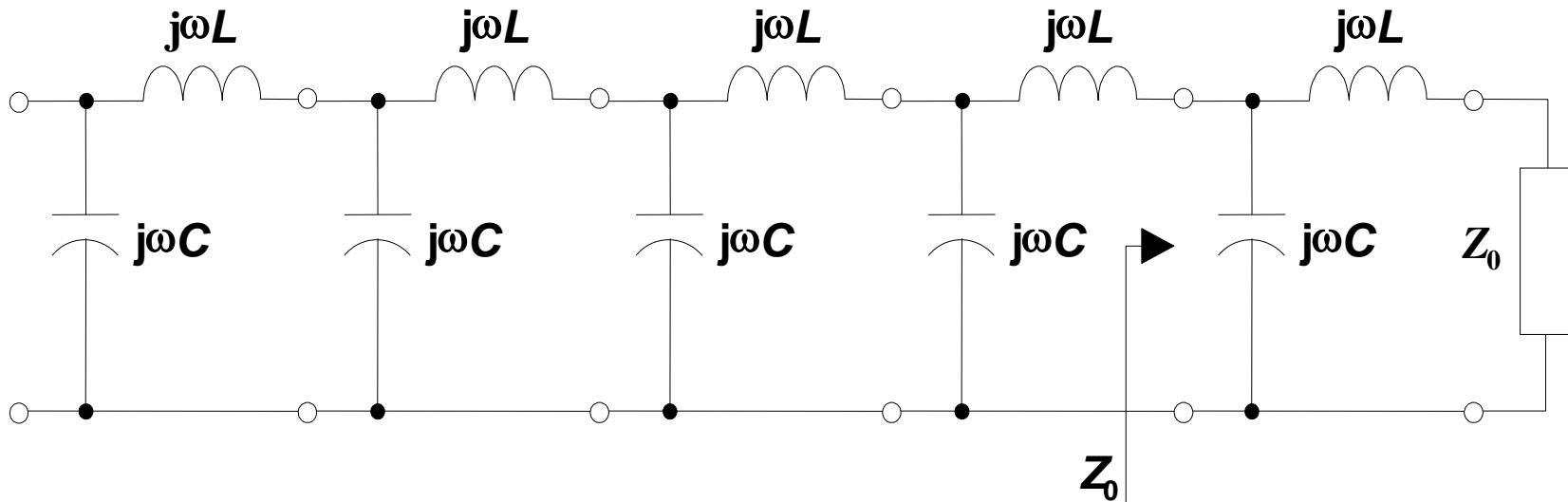Artificial lines (Z_0 iterative impedance)



$$Z_0 = \frac{1}{j\omega C + \frac{1}{j\omega L + Z_0}}$$

$$Z_0^2 + j\omega LZ_0 - \frac{L}{C} = 0$$


$$Z_0 = -j\omega \frac{L}{2} + \sqrt{\frac{-\omega^2 L^2}{4} + \frac{L}{C}}$$

$$f_c = \frac{1}{\pi Z_0(0)C}$$

$$A_V(0) = \frac{Z_0(0)}{2} n g_m$$

$$f_T = \frac{n g_m}{2\pi C}$$

Discrete cell DAMP model

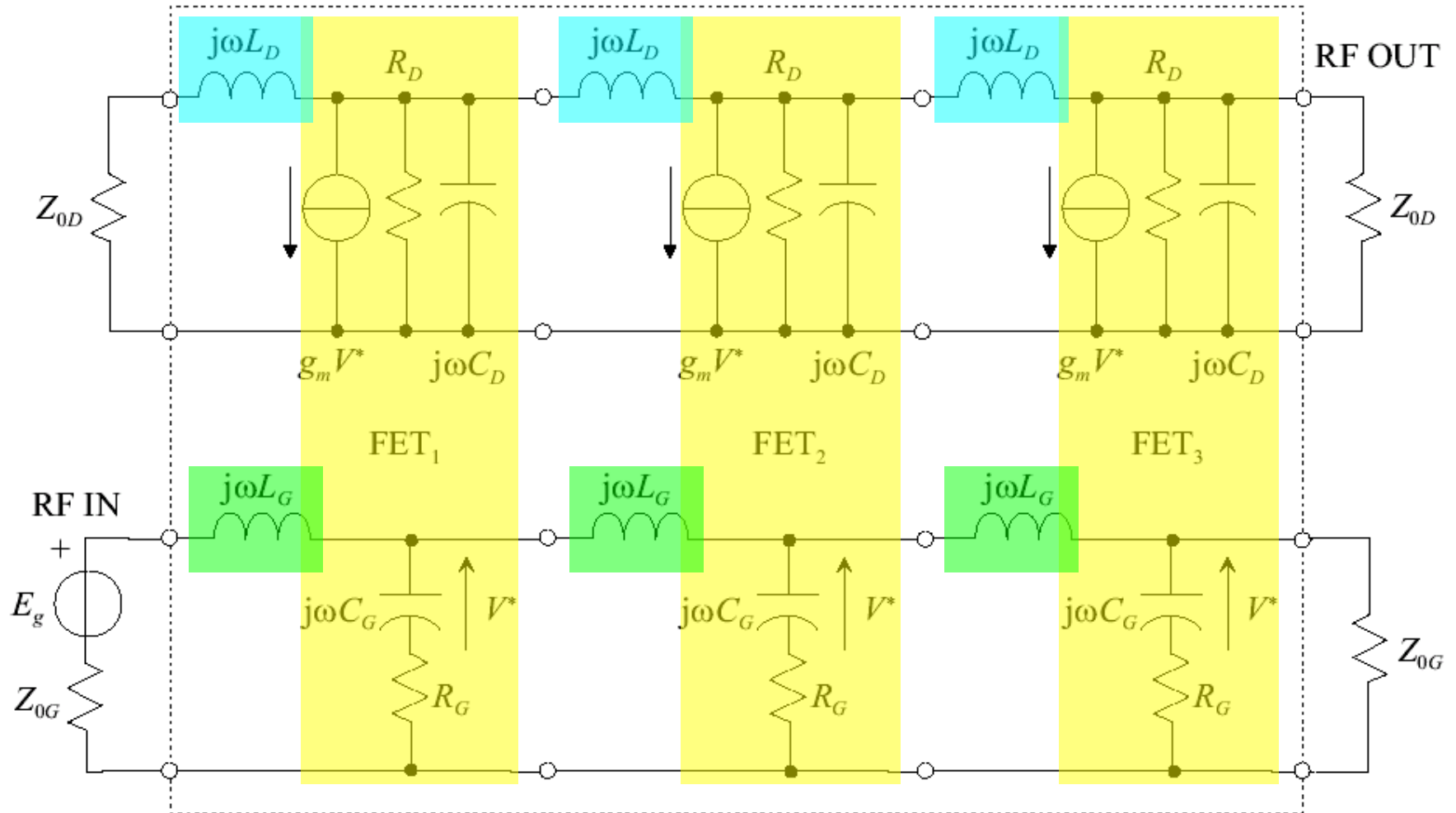

Discrete cell DAMP



- In a discrete cell DAMP the ideal frequency response suggest that the gain bandwidth product is:


PBG (f_T) of n cells $\sim n \times$ PBG (f_T) of one cell

- Optimum cell number \rightarrow losses \rightarrow typically 10-15 max in integrated implementations

$$n_{ott} = \frac{\log(A_D/A_G)}{A_D - A_G}$$



- A_D and A_G are the total attenuations of the gate and drain lines.

Example of integrated DAMP

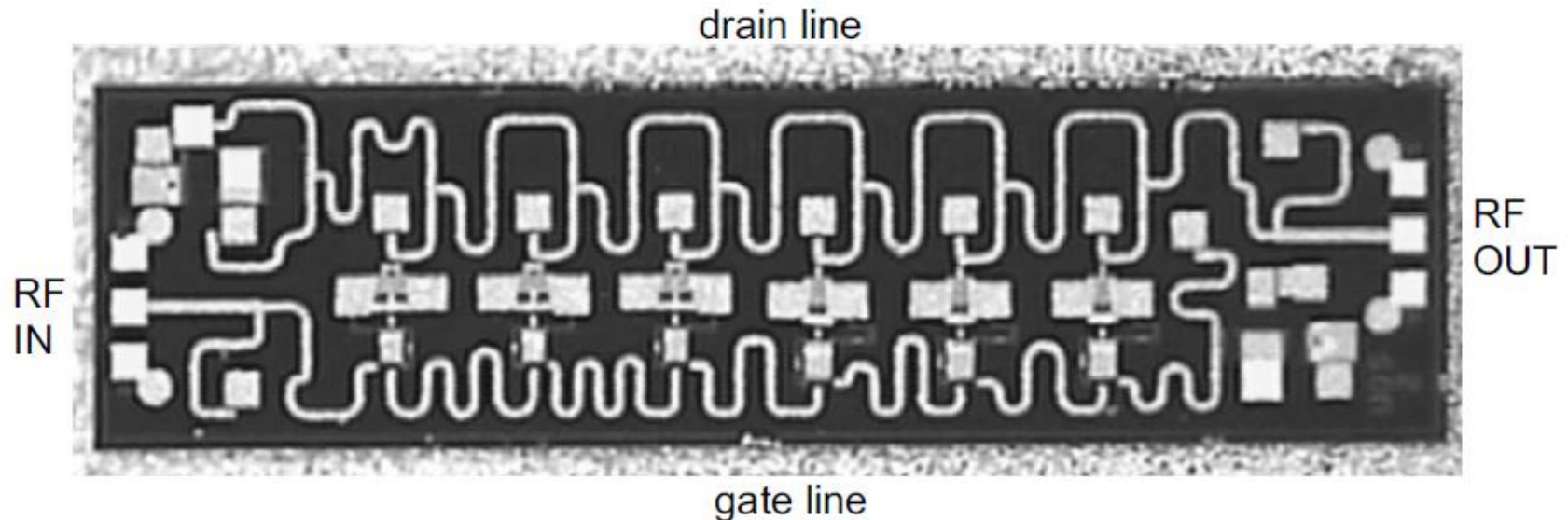



The amplifier has 6 stages and includes drain and gate delay lines having different length to achieve synchronous coupling. The chip technology is power PHEMT and the chip size is $3.75 \times 1 \text{ mm}^2$. The average gain is 7 dB up to around 15 GHz and the DAMP was designed as a 10 Gbps electro-optic modulator driver. Copyright 2005 GAAS Association. All rights reserved. Reprinted, with permission, from J. Shohat, I. D. Robertson, and S. J. Nightingale, "High efficiency 10 Gb/s optical modulator driver amplifier using a power pHEMT technology," in European Gallium Arsenide and Other Semiconductor Application Symposium, GAAS 2005, Oct. 2005, pp. 129–132.

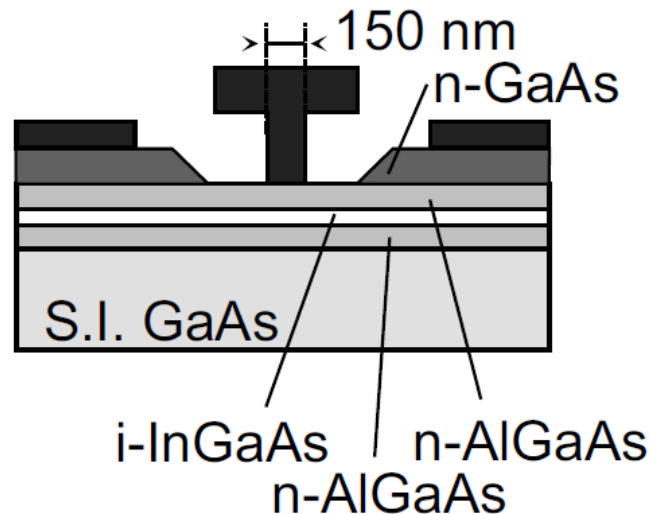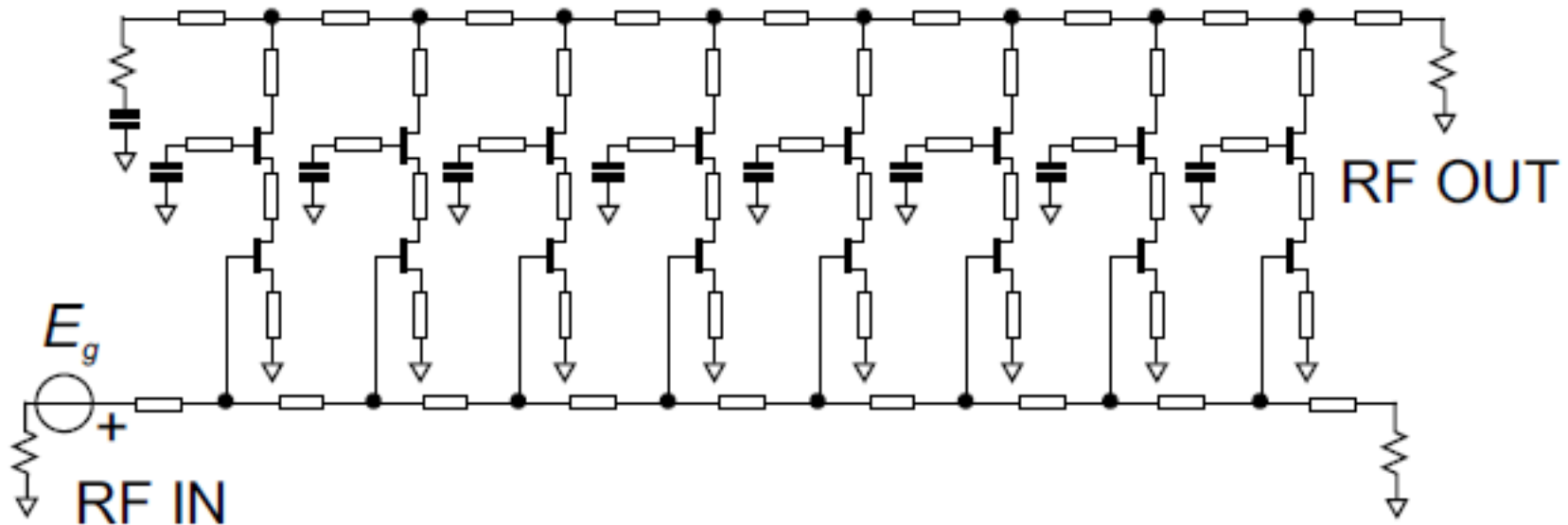Fujitsu cascode DAMP for optical communication systems - I



- PHEMT
InGaAs/GaAs
Fujitsu
- 40 Gbps, 6 Vpp

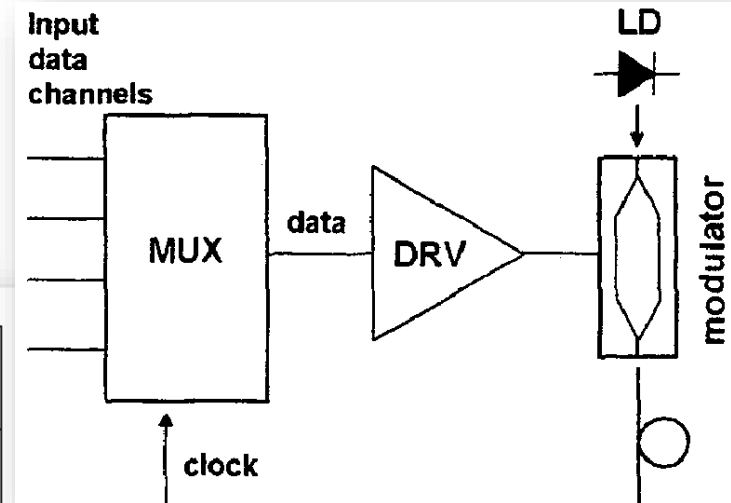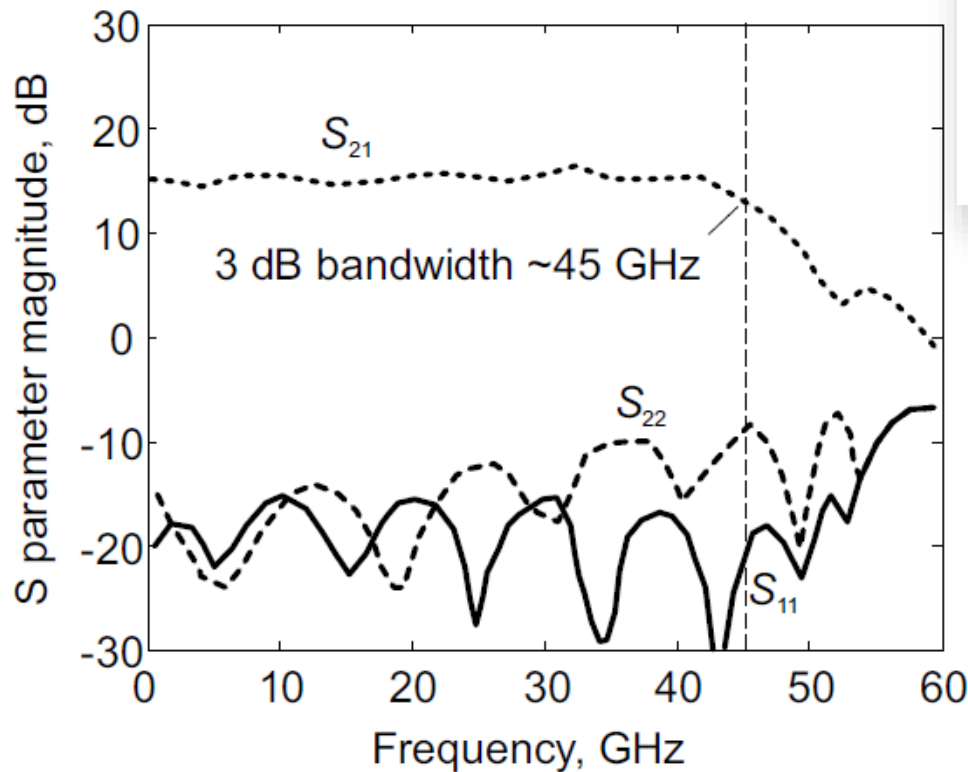Fujitsu cascode DAMP for optical communication systems - II



H. Shigematsu, M. Sato, T. Hirose, and Y. Watanabe, "A 54-GHz distributed amplifier with 6-VPP output for a 40-Gb/s LiNbO₃ modulator driver," IEEE Journal of Solid-State Circuits, vol. 37, no. 9, pp. 1100–1105, Sep. 2002. Copyright 2002 IEEE, with permission.