

# Gains in a loaded two-port

***Microwave Electronics***

**Giovanni Ghione, Marco Pirola**



**Politecnico di Torino, DET**


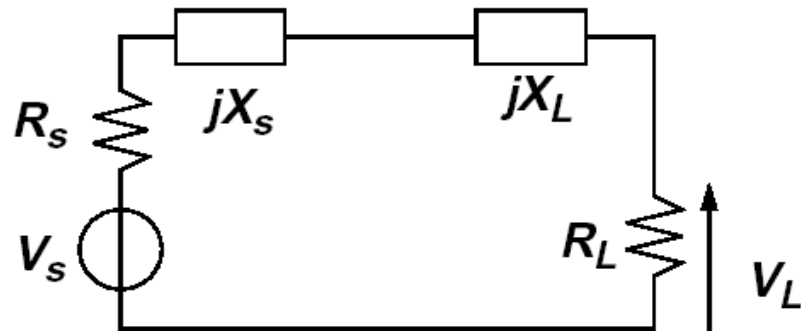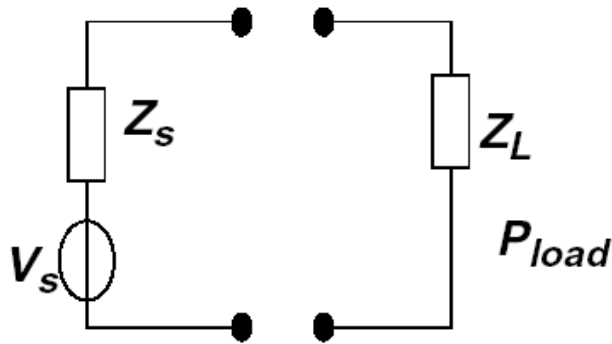
# Power (conjugate) match $\rightarrow$ max. power transfer – usual approach



Consider a source with the complex impedance  $Z_s$




$$P_L = \frac{|V_L|^2}{R_L}, \quad V_L = V_s \frac{R_L}{(R_L + R_s) + j(X_L + X_s)}$$

$$P_L = \frac{|V_s|^2 R_L}{(R_L + R_s)^2 + (X_L + X_s)^2} \text{ max. vs. } X_L \rightarrow X_L = -X_s$$


$$P_L = \frac{|V_s|^2 R_L}{(R_L + R_s)^2} \text{ max. vs. } R_L \rightarrow \frac{dP_L}{dR_L} = |V_s|^2 \left[ \frac{R_s - R_L}{(R_L + R_s)^3} \right] = 0 \rightarrow R_L = R_s$$

$$\text{Finally } Z_L = Z_s^* \text{ (conjugate or power match) } P_{L\max} = P_{Sav} = \frac{|V_s|^2}{4R_s}$$

# Forward and backward wave generators

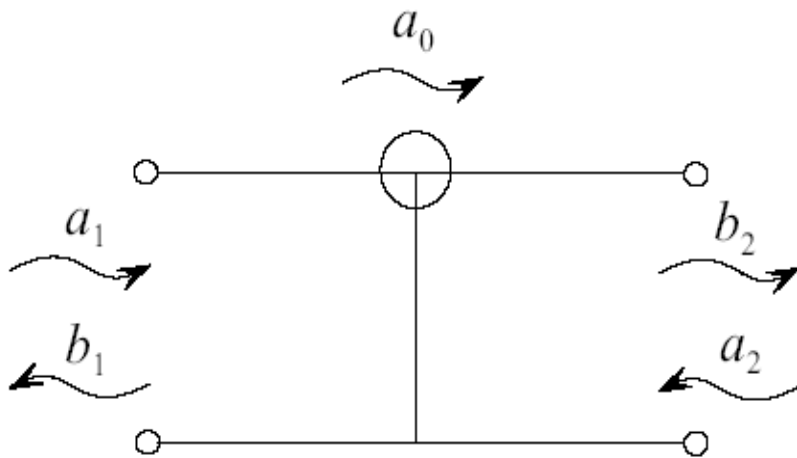

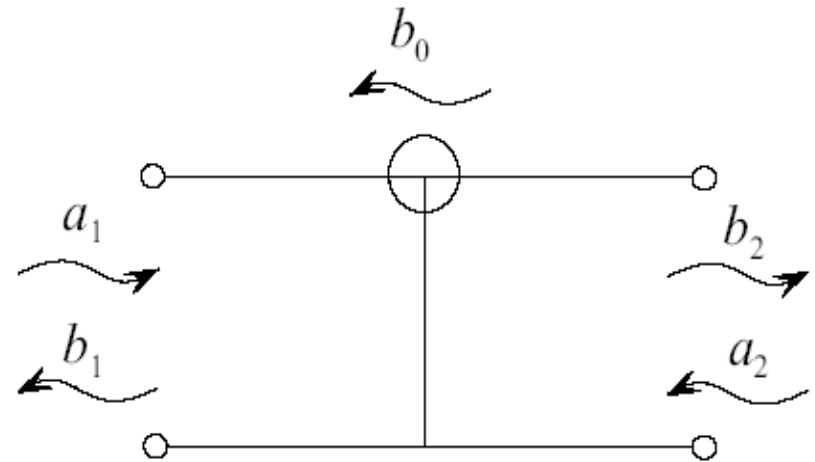
$$\begin{cases} b_1 = a_2 \\ b_2 = a_0 + a_1 \end{cases}$$



$$\begin{cases} b_1 = a_2 + b_0 \\ b_2 = a_1 \end{cases}$$

# Power transfer in a loaded one-port

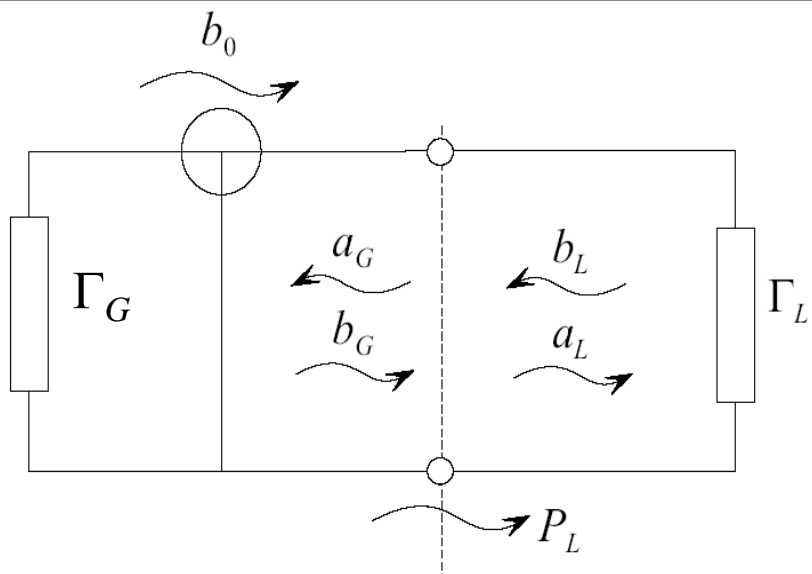

$$\left\{ \begin{array}{l} a_L = b_G \\ a_G = b_L \\ b_G = b_0 + \Gamma_G a_G \\ b_L = \Gamma_L a_L \end{array} \right. \quad \left\{ \begin{array}{l} a_L = \frac{b_0}{1 - \Gamma_G \Gamma_L} \\ b_L = \frac{b_0 \Gamma_L}{1 - \Gamma_G \Gamma_L} \end{array} \right.$$

$$P_L = |a_L|^2 - |b_L|^2 = |a_L|^2(1 - |\Gamma_L|^2) = |b_0|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_G \Gamma_L|^2}$$

$$Z_L = Z_G^* \Rightarrow \Gamma_L = \Gamma_G^* \quad R_0 \in \mathbb{R}$$


Power matching (maximum power transfer,  $Z_L = Z_G^* \rightarrow \Gamma_L = \Gamma_G^*$ )

power to load  $\rightarrow$  generator available power

$$P_L = P_{av} \frac{(1 - |\Gamma_G|^2)(1 - |\Gamma_L|^2)}{|1 - \Gamma_G \Gamma_L|^2}$$

$$\begin{aligned} P_{av} &= \frac{|b_0|^2 (1 - |\Gamma_G^*|^2)}{|1 - \Gamma_G \Gamma_G^*|^2} = \frac{|b_0|^2 (1 - |\Gamma_G|^2)}{|1 - |\Gamma_G|^2|^2} = \frac{|b_0|^2 (1 - |\Gamma_G|^2)}{(1 - |\Gamma_G|^2)^2} = \\ &= \frac{|b_0|^2}{1 - |\Gamma_G|^2} = |V_0|^2 \frac{R_0}{|Z_G + R_0|^2} \frac{|Z_G + R_0|^2}{|Z_G + R_0|^2 - |Z_G - R_0|^2} = \frac{|V_0|^2}{4R_G} \end{aligned}$$

# Analysis of loaded two-port

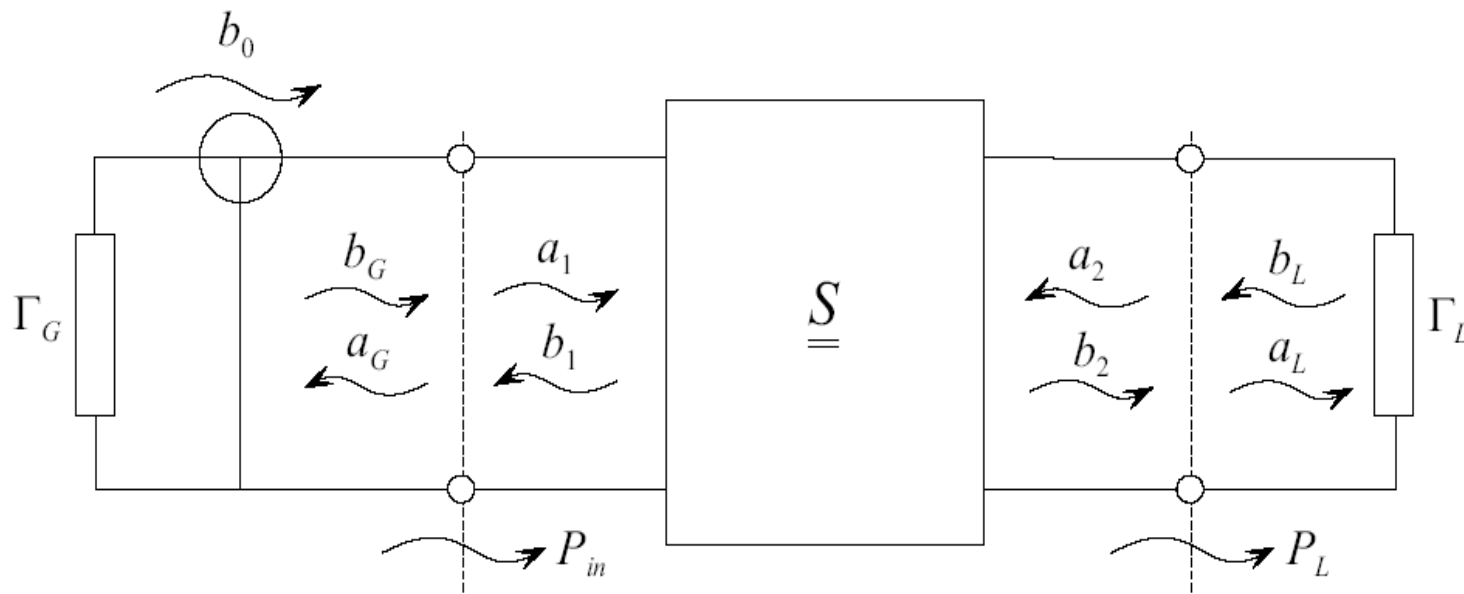

$$\begin{aligned}
 b_G &= b_0 + \Gamma_G a_G & a_1 &= b_G \\
 b_1 &= S_{11}a_1 + S_{12}a_2 & b_1 &= a_G \\
 b_2 &= S_{21}a_1 + S_{22}a_2 & b_2 &= a_L \\
 b_L &= \Gamma_L a_L & a_2 &= b_L
 \end{aligned}
 \quad \longrightarrow \quad
 \begin{pmatrix} 1 & -\Gamma_G & 0 & 0 \\ -S_{11} & 1 & -S_{12} & 0 \\ -S_{21} & 0 & -S_{22} & 1 \\ 0 & 0 & 1 & -\Gamma_L \end{pmatrix}
 \begin{pmatrix} a_1 \\ b_1 \\ a_2 \\ b_2 \end{pmatrix}
 = b_0
 \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

# Solution in terms of power waves



- Solving the system one has:

$$\longrightarrow a_1 = b_G = b_0 \frac{1 - S_{22}\Gamma_L}{(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L}$$

$$\begin{aligned} \longrightarrow b_1 = a_G &= b_0 \frac{S_{12}S_{21}\Gamma_L + S_{11}(1 - S_{22}\Gamma_L)}{(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L} = \\ &= b_0 \frac{S_{11} - \Delta_S\Gamma_L}{(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L} \end{aligned}$$

$$\longrightarrow a_2 = b_L = b_0 \frac{\Gamma_L S_{21}}{(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L}$$

$$\longrightarrow b_2 = a_L = b_0 \frac{S_{21}}{(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L}$$

$\Delta_S$  is the determinant of the S matrix

$$\Delta_S = S_{11}S_{22} - S_{12}S_{21}$$

# Some input port parameters



- Input reflection coefficient:

$$\Gamma_{in} = \frac{b_1}{a_1} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = \frac{S_{11} - \Delta_S\Gamma_L}{1 - S_{22}\Gamma_L}.$$

- Input power:

$$P_{in} = |a_1|^2 - |b_1|^2 = |b_0|^2 \frac{|1 - S_{22}\Gamma_L|^2 - |S_{11} - \Delta_S\Gamma_L|^2}{|(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L|^2},$$

alternatively:

$$P_{in} = |a_1|^2(1 - |\Gamma_{in}|^2) = |b_0|^2 \frac{1 - |\Gamma_{in}|^2}{|1 - \Gamma_G\Gamma_{in}|^2}.$$

# Input reflection coefficient - proof



$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$

$$a_2 = \Gamma_L b_2 \Rightarrow$$

$$b_1 = S_{11}a_1 + S_{12}\Gamma_L b_2$$

$$b_2 = S_{21}a_1 + S_{22}\Gamma_L b_2$$

$$\Rightarrow b_2 = \frac{S_{21}a_1}{1 - S_{22}\Gamma_L}$$

$$\Rightarrow b_1 = S_{11}a_1 + \frac{S_{12}S_{21}\Gamma_L a_1}{1 - S_{22}\Gamma_L} \Rightarrow$$


$$\frac{b_1}{a_1} = \Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = \frac{S_{11} - S_{11}S_{22}\Gamma_L + S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = \frac{S_{11} - \Delta_S \Gamma_L}{1 - S_{22}\Gamma_L}$$


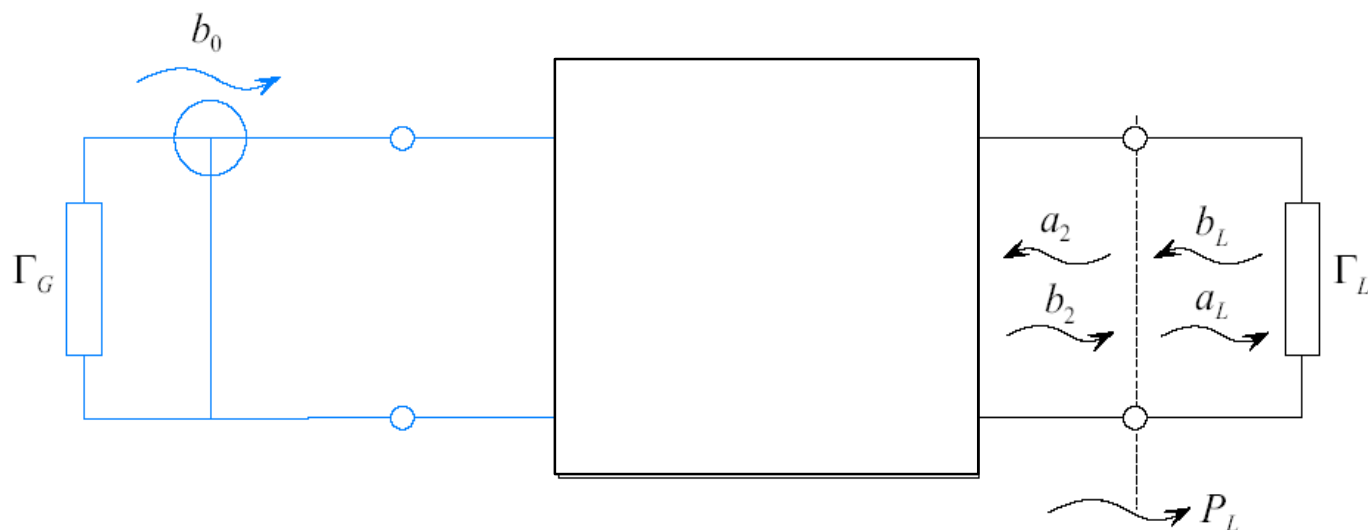
# Output equivalent circuit



- It is useful to evaluate the equivalent circuit of the two-port as seen from the output port:




$$b_2 = \bar{b}_0 + \Gamma_{out} a_2.$$

$$\bar{b}_0 = b_0 \frac{S_{21}}{1 - S_{11}\Gamma_G}, \quad \Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_G}{1 - S_{11}\Gamma_G} = \frac{S_{22} - \Delta_S \Gamma_G}{1 - S_{11}\Gamma_G}$$
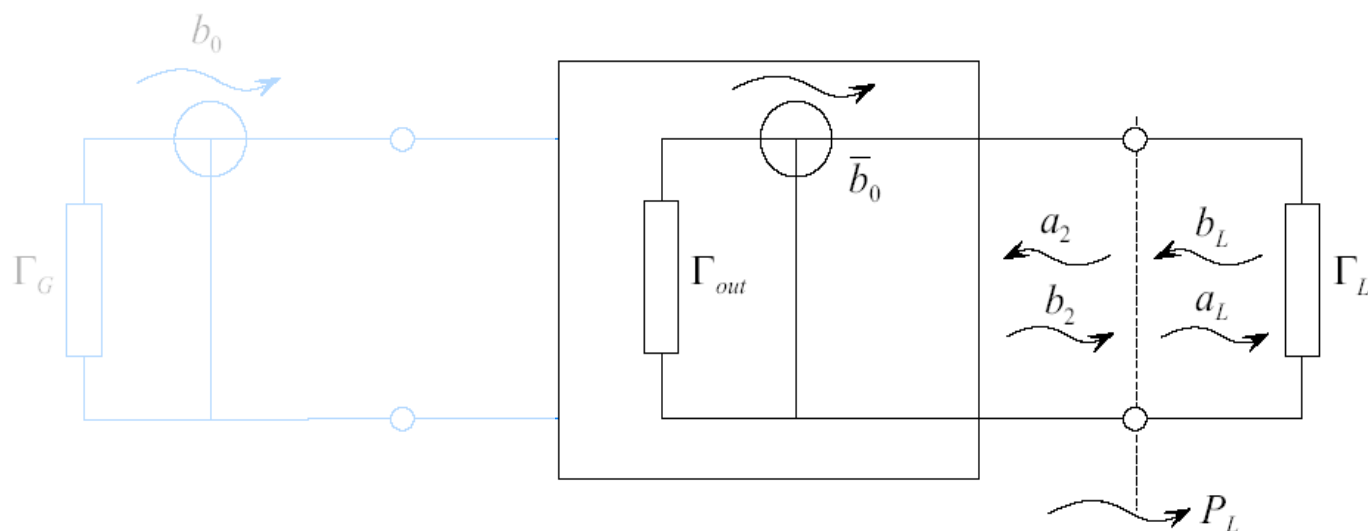
# Output equivalent circuit



- It is useful to evaluate the equivalent circuit of the two-port as seen from the output port:



$$b_2 = \bar{b}_0 + \Gamma_{out} a_2.$$

$$\bar{b}_0 = b_0 \frac{S_{21}}{1 - S_{11}\Gamma_G}, \quad \Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_G}{1 - S_{11}\Gamma_G} = \frac{S_{22} - \Delta_S \Gamma_G}{1 - S_{11}\Gamma_G}$$

# Proof



- Load the output with the normalization resistance, the input gamma will be by definition  $S_{11}$  thus:

$$\Gamma_L = 0 \Rightarrow a_2 = 0 \Rightarrow b_2 = \bar{b}_0 = S_{21}a_1$$

$$\text{since } b_2 = \bar{b}_0 + \Gamma_{out}a_2 = \bar{b} \text{ with } a_2 = 0$$

$$a_1 = \frac{b_0}{1 - S_{11}\Gamma_G} \text{ from the input port circuit}$$

$$\bar{b}_0 = \frac{S_{21}b_0}{1 - S_{11}\Gamma_G}$$

- The output gamma is obtained by superposition setting  $b_0 = 0$  and using the input gamma result.

# Power on the load



- Equivalent expressions:

$$P_L = |a_L|^2 - |b_L|^2 = |b_0|^2 \frac{|S_{21}|^2(1 - |\Gamma_L|^2)}{|(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L|^2}$$

$$P_L = |\bar{b}_0|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_{out}\Gamma_L|^2} = |b_0|^2 \frac{|S_{21}|^2(1 - |\Gamma_L|^2)}{|1 - \Gamma_L \Gamma_{out}|^2 |1 - S_{11}\Gamma_G|^2} .$$

# Two-port gains



- Having defined:
  - The **input power** at port 1  $P_{in}$
  - The **generator (input) available power**  $P_{av,in}$
  - The **power on the load**  $P_L$
  - The **load (output) available power**  $P_{av,L}$

we define the following power ratios:

- **Operational gain** →  $G_{op} = \frac{P_L}{P_{in}}$
- **Available power gain** →  $G_{av} = \frac{P_{av,L}}{P_{av,in}}$
- **Transducer gain** →  $G_t = \frac{P_L}{P_{av,in}}$

# A note on gain measurements

---




- The **transducer gain** is easy to measure because it only requires a power measurement on the load → the input available power is derived from the generator setup (e.g. I set 100 mW available power on a 50 Ohm generator)
- The measurement of the **available power gain** further requires to match the output load (a so-called load-pull measurement)
- The **operational power gain** requires input and output power measurement → setup similar to the S-matrix measurement, a network analyzer is required (also scalar, only magnitudes of power waves, not phases)
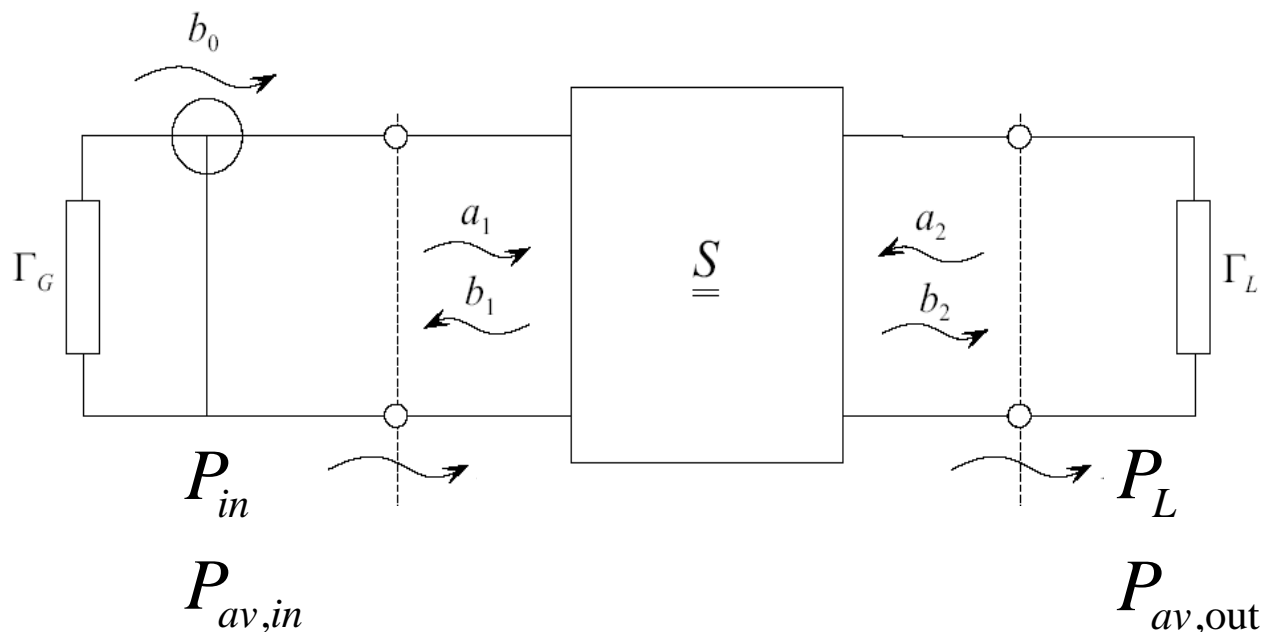
# What do gains depend on?



- Apart from the S parameters, gains depend on the load and generator reflection coefficients as follows:
  - **Operational gain**  $\rightarrow$  on  $\Gamma_L$
  - **Available power gain**  $\rightarrow \Gamma_G$
  - **Transducer gain**  $\rightarrow$  on  $\Gamma_L$  and  $\Gamma_G$ .
- Why?



# Why?

---



- Operational gain  $\rightarrow$  on  $\Gamma_L$ 
  - In fact if the *generator* impedance is changed, this changes the input matching and the input power, but the power on the load changes of the same amount
- Available power gain  $\rightarrow$  on  $\Gamma_G$ 
  - By definition the available power at the output is the power on the load when power transfer on the load is maximum (conjugate matching), thus the load impedance **is related to the generator impedance**
- Transducer gain  $\rightarrow$  on  $\Gamma_L$  and  $\Gamma_G$ 
  - In this case the input available power changes with generator gamma while the power on the load changes with the generator and load gamma (both independently)



# Maximum gain and maximum power transfer: same thing?

---




- The **maximum power transfer** occurs when the generator yields the maximum power, i.e.
  - the input power is the generator (input) available power
  - the power on the load is the output available power
- The maximum power transfer implies power impedance matching **simultaneously** at the input and output (*if this is possible*)
- The maximum power transfer implies maximum gain (for all gains!), but *maximum gain alone* implies *maximum power transfer* only for transducer gain, see later.

# Power transfer and gains - I



$$P_{in} = P_{av,in} \frac{(1 - |\Gamma_G|^2)(1 - |\Gamma_{in}(\Gamma_L)|^2)}{|1 - \Gamma_G \Gamma_{in}(\Gamma_L)|^2}$$

$$P_L = P_{av,out} \frac{(1 - |\Gamma_{out}(\Gamma_G)|^2)(1 - |\Gamma_L|^2)}{|1 - \Gamma_{out}(\Gamma_G)\Gamma_L|^2}$$

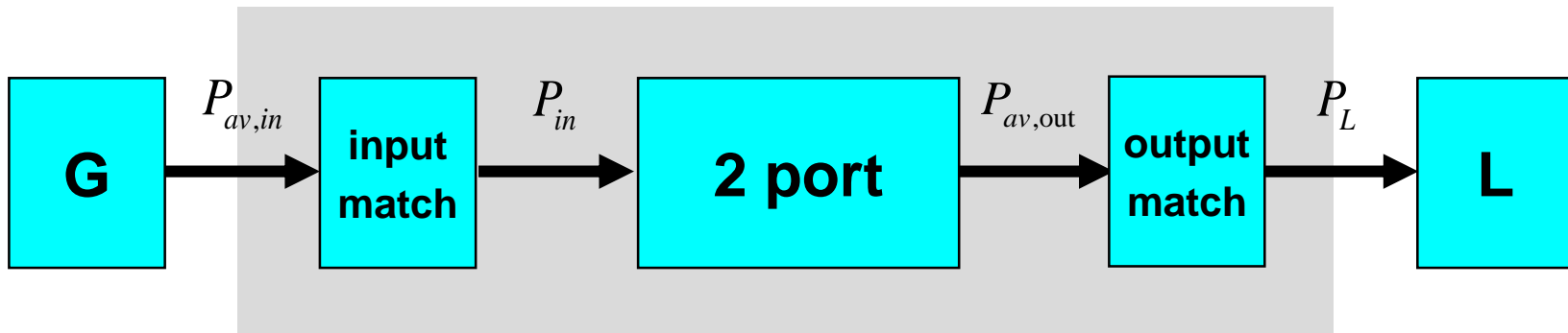

$$G_t(\Gamma_G, \Gamma_L) = \frac{P_L}{P_{av,in}} \Rightarrow \text{max. transducer gain implies max power transfer}$$

# Power transfer and gains - II



$$P_{in} = P_{av,in} \frac{(1 - |\Gamma_G|^2)(1 - |\Gamma_{in}(\Gamma_L)|^2)}{|1 - \Gamma_G \Gamma_{in}(\Gamma_L)|^2}$$

$$G_{op}(\Gamma_L) = \frac{P_L}{P_{in}} \Rightarrow \text{max. operational gain implies max. power transfer only if input power matching is also achieved}$$

# Power transfer and gains – III



$$P_L = P_{av,out} \frac{(1 - |\Gamma_{out}(\Gamma_G)|^2)(1 - |\Gamma_L|^2)}{|1 - \Gamma_{out}(\Gamma_G)\Gamma_L|^2}$$

$$G_{av}(\Gamma_G) = \frac{P_{av,out}}{P_{av,in}} \Rightarrow \text{max. av. power gain} \rightarrow \text{max. power transfer only with output power matching}$$

# Operational gain



- We start with operational gain – easier to optimize since it only depends on the (complex) load gamma [We could have started from available power gain as well]
- Doing all the math we obtain:

$$G_{op} = \frac{P_L}{P_{in}} = |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2 - |S_{11} - \Delta_S\Gamma_L|^2}$$

- or:

$$G_{op} = |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{1 - |S_{11}|^2 + |\Gamma_L|^2(|S_{22}|^2 - |\Delta_S|^2) + 2\Re(\Gamma_L(S_{11}^*\Delta_S - S_{22}))} .$$

- The operational gain is a real function of the complex variable “gamma of the load” which is in turn defined in the Smith chart → let us have a look at **constant gain curves**

# Operational gain - proof




$$P_{in} = |b_0|^2 \frac{|1 - S_{22}\Gamma_L|^2 - |S_{11} - \Delta_S \Gamma_L|^2}{|(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L|^2}$$

$$P_L = |b_0|^2 \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{|(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L|^2}$$

$$G_{op} = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2 - |S_{11} - \Delta_S \Gamma_L|^2}$$

Notice that the input and load power depend on the generator gamma **in the same way** → their ratio is **independent on the generator gamma**

# Constant operational gain circles

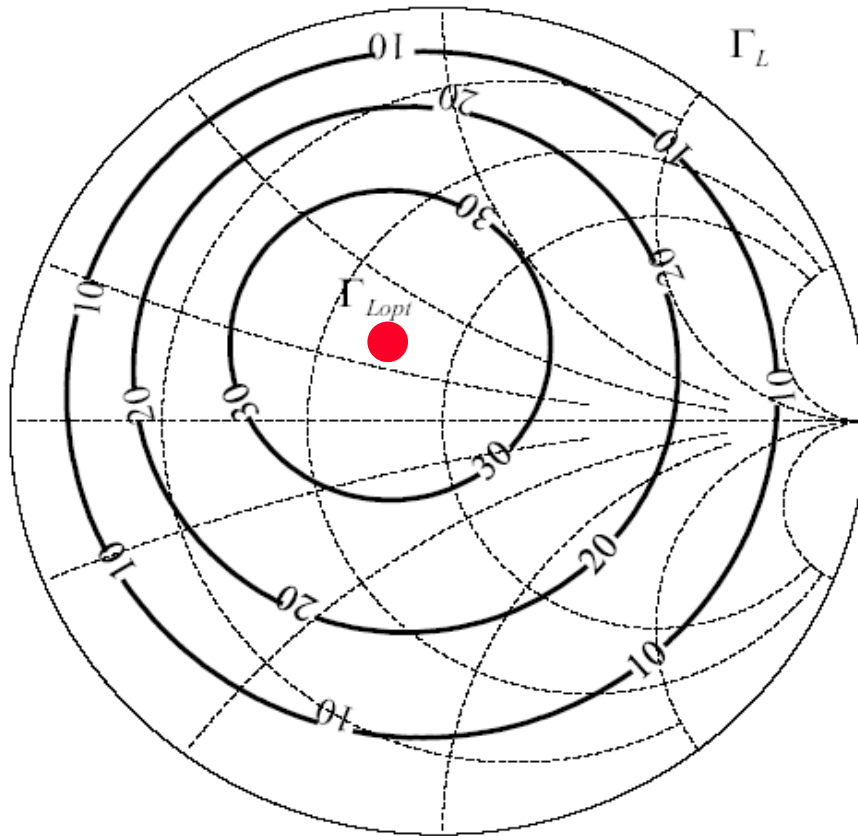

- The constant level curves of the operational gain in the complex plane  $\Gamma_L$  are *circles*
- The gain is maximum in a point  $\rightarrow$  optimum  $\Gamma_L$ ; the maximum gain is:

$$G_{op_{MAX}} = \left| \frac{S_{21}}{S_{12}} \right| (K - \sqrt{K^2 - 1})$$

- However this maximum exists only if  $K \geq 1$  where:

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta_S|^2}{2|S_{21}||S_{12}|}$$

**Linville (Rollet)  
stability factor**



# The Unilateral Case ( $S_{12}=0$ )



- Simple if considered as a particular case

$$\Gamma_{in}=S_{11}, \Gamma_{out}=S_{22}, P_L=|S_{21}|^2 \frac{1-|\Gamma_L|^2}{|1-S_{22}\Gamma_L|^2} |a_1|^2, P_{in}=\left(1-|S_{11}|^2\right) |a_1|^2$$

$$\rightarrow G_{OP} = \frac{P_L}{P_{in}} = |S_{21}|^2 \frac{1-|\Gamma_L|^2}{|1-S_{22}\Gamma_L|^2 \left(1-|S_{11}|^2\right)} \rightarrow G_{OPMAX} = G_{OP}|_{\Gamma_L=S_{22}^*} = \frac{|S_{21}|^2}{\left(1-|S_{22}|^2\right) \left(1-|S_{11}|^2\right)}$$

- To be dealt with care if derived from the general previous seen expressions since  $K \rightarrow \infty$  when  $S_{12} \rightarrow 0$  .....



# The Unilateral case from the general approach 1



From the Rollet formula

$$2K|S_{12}| = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |S_{11}|^2|S_{22}|^2}{|S_{21}|} = \frac{(1 - |S_{11}|^2)(1 - |S_{22}|^2)}{|S_{21}|}$$

From the max op gain formula

$$G_{OPMAX} |S_{12}| = |S_{21}| \left( K - \sqrt{K^2 - 1} \right)$$

When  $K \rightarrow \infty$  (K real!)

$$G_{OPMAX} = \left| \frac{S_{21}}{S_{12}} \right| \left( K - |K| \sqrt{1 - \frac{1}{K^2}} \right) \approx \left| \frac{S_{21}}{S_{12}} \right| \left[ K - |K| \left( 1 - \frac{1}{2K^2} \right) \right] = \left| \frac{S_{21}}{S_{12}} \right| \left( K - |K| + \frac{1}{2|K|} \right)$$

Hence, when  $S_{12} \rightarrow 0$   $K \rightarrow +\infty$

$$G_{OPMAX} \rightarrow \frac{|S_{21}|}{2|K||S_{12}|} = \frac{|S_{21}|}{2K|S_{12}|} \quad \text{and from top page expr} \quad G_{OPMAX} \rightarrow \frac{|S_{21}|^2}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)}$$

# The Unilateral case from the general approach 2



$$G_{OPMAX} = \left| \frac{S_{21}}{S_{12}} \right| \left( K - |K| \sqrt{1 - \frac{1}{K^2}} \right) \approx \left| \frac{S_{21}}{S_{12}} \right| \left[ K - |K| \left( 1 - \frac{1}{2K^2} \right) \right] = \left| \frac{S_{21}}{S_{12}} \right| \left( K - |K| + \frac{1}{2|K|} \right)$$

Instead, when  $S_{12} \rightarrow 0$  but  $K \rightarrow -\infty$   $G_{OPMAX}$  is going to  $-\infty$  too.

**That means instability!**

The negative sign of  $G_{OPMAX}$  means also that one of the two ports has the power flowing in reverted direction.

From the expression  $K|S_{12}| = \frac{(1 - |S_{11}|^2)(1 - |S_{22}|^2)}{2|S_{21}|}$

We can see that in a unilateral device condition  $K \rightarrow +\infty$  is verified when  $|S_{11}| < 1$  and  $|S_{22}| < 1$  while  $K \rightarrow -\infty$  if  $|S_{11}| > 1$  or  $|S_{22}| > 1$

[In the case  $|S_{11}| > 1$  and  $|S_{22}| > 1$  both port powers have reverted sign so that the power flow is not going from generator to load, but in the opposite direction, and virtually the gain is positive.]

# Max. operational gain & max. power transfer

---



- If  $K \geq 1$  the operational gain has a maximum; the condition on  $K$  corresponds to an *unconditionally stable* two-port  $\rightarrow$  i.e. a two port stable for any choice of load and generator impedances
- When the operational gain is maximum (condition on optimum load  $\gamma$ ) the **maximum power transfer** between generator and load **occurs when the generator is power matched to the two-port input** (condition on optimum generator  $\gamma$ )
- The set of two optimum load and generator  $\gamma$ s corresponds to **simultaneous power matching** at the two ports (for analytic expressions of optimum  $\gamma$ s see text)

# Available power gain



- One has:

$$G_{av} = \frac{P_{av,out}}{P_{av,in}} = \frac{|S_{21}|^2 (1 - |\Gamma_G|^2)}{|1 - S_{11}\Gamma_G|^2 - |S_{22} - \Delta_S \Gamma_G|^2}$$

or:

$$G_{av} = |S_{21}|^2 \frac{1 - |\Gamma_G|^2}{1 - |S_{22}|^2 + |\Gamma_G|^2(|S_{11}|^2 - |\Delta_S|^2) + 2\Re(\Gamma_G(S_{22}^* \Delta_S - S_{11}))} .$$

- The available power gain is defined by its constant level curves in the complex plane  $\Gamma_G$  (*circles* again!). The gain is zero on the Smith chart unit circle (reactive source impedance  $\rightarrow$  *infinite input available power*)  $\rightarrow$  dual situation vs. operational gain

# Available power gain - proof



$$P_{in} = |b_0|^2 \frac{1 - |\Gamma_{in}|^2}{|1 - \Gamma_G \Gamma_{in}|^2} \Rightarrow P_{av,in} \underset{\Gamma_{in} = \Gamma_G^*}{=} \frac{|b_0|^2}{1 - |\Gamma_G|^2}$$

$$P_L = \frac{|b_0|^2 |S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - \Gamma_L \Gamma_{out}|^2 |1 - S_{11} \Gamma_G|^2} \Rightarrow P_{av,out} \underset{\Gamma_L = \Gamma_{out}^*}{=} \frac{|b_0|^2 |S_{21}|^2}{(1 - |\Gamma_{out}|^2) |1 - S_{11} \Gamma_G|^2}$$

$$G_{av} = \frac{P_{av,out}}{P_{av,in}} = \frac{|b_0|^2 |S_{21}|^2}{(1 - |\Gamma_{out}|^2) |1 - S_{11} \Gamma_G|^2} \frac{1 - |\Gamma_G|^2}{|b_0|^2} =$$

$$\underset{\Gamma_{out} = \frac{S_{22} - \Delta_S \Gamma_G}{1 - S_{11} \Gamma_G}}{=} \frac{|S_{21}|^2 (1 - |\Gamma_G|^2)}{|1 - S_{11} \Gamma_G|^2 - |S_{22} - \Delta_S \Gamma_G|^2}$$

The input and output available power **do not depend** on the load gamma  
 → their ratio is **independent on the load gamma**

# $G_{op} - G_{av}$ duality and maximum values



- Taking into account that the two following formulae are obtained by exchanging  $1 \rightarrow 2$ ,  $L \rightarrow G$  (the determinant and  $K$  are invariant with respect to this change):

$$\frac{G_{av}}{|S_{21}|^2} = \frac{1 - |\Gamma_G|^2}{|1 - S_{11}\Gamma_G|^2 - |S_{22} - \Delta_S \Gamma_G|^2} \quad \frac{G_{op}}{|S_{21}|^2} = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2 - |S_{11} - \Delta_S \Gamma_L|^2}$$

- we immediately get the two maxima:

$$\left( \frac{G_{op}}{|S_{21}|^2} \right)_{\max} = \frac{1}{|S_{12}S_{21}|} \left( K - \sqrt{K^2 - 1} \right) \Rightarrow \left( \frac{G_{av}}{|S_{21}|^2} \right)_{\max} = \frac{1}{|S_{21}S_{12}|} \left( K - \sqrt{K^2 - 1} \right)$$

- i.e.:

$$\left( G_{op} \right)_{\max} = \left( G_{av} \right)_{\max}$$

# Maximum available gain (MAG)

---



- MAG coincides with maximum operational gain, but again a maximum exists only for  $K \geq 1$  (unconditionally stable two-port)
- MAG corresponds to an optimum choice of generator gamma, to achieve *maximum power transfer* we also have to power match the load to the two-port output (optimum load gamma)
- We obtain again that maximum power transfer corresponds to conjugate matching at the two ports simultaneously → **same condition** already discussed

# Transducer gain



- One has the following expression, depending on both generator and load gammas:

$$G_t = \frac{P_L}{P_{av,in}} = |S_{21}|^2 \frac{(1 - |\Gamma_L|^2)(1 - |\Gamma_G|^2)}{|(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_L\Gamma_G|^2}$$

the optimum condition directly corresponds to maximum power transfer, i.e. again to simultaneous conjugate matching at ports 1 and 2:

$$\begin{cases} \Gamma_G &= \Gamma_{in}^*(\Gamma_L) \\ \Gamma_L &= \Gamma_{out}^*(\Gamma_G) \end{cases}$$

- The optimum transducer gain (obviously) is **the same** as MAG and maximum operational gain.



# Transducer gain - proof



$$P_{in} = |b_0|^2 \frac{1 - |\Gamma_{in}|^2}{|1 - \Gamma_G \Gamma_{in}|^2} \Rightarrow P_{av,in} \underset{\Gamma_{in} = \Gamma_G^*}{=} \frac{|b_0|^2}{1 - |\Gamma_G|^2} \text{ depends on } \Gamma_G$$

$$P_L = \frac{|b_0|^2 |S_{21}|^2 (1 - |\Gamma_L|^2)}{|(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_L\Gamma_G|^2} \text{ depends on } \Gamma_G, \Gamma_L$$

$$G_t = \frac{P_L}{P_{av,in}} = \frac{|b_0|^2 |S_{21}|^2 (1 - |\Gamma_L|^2)}{|(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_L\Gamma_G|^2} \frac{1 - |\Gamma_G|^2}{|b_0|^2} =$$

$$= \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)(1 - |\Gamma_G|^2)}{|(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_L\Gamma_G|^2} \text{ depends on } \Gamma_G, \Gamma_L$$

# Unilateral transducer gain



- Transducer gain of a *unilateral device* where  $S_{12}=0$  (is that meaningful and why? “always” unconditionally stable):

$$G_u = G_t|_{S_{12}=0} = |S_{21}|^2 \frac{(1 - |\Gamma_L|^2)(1 - |\Gamma_G|^2)}{|1 - \Gamma_L S_{22}|^2 |1 - \Gamma_G S_{11}|^2}$$

the **maximum unilateral gain (MUG)** is obtained when the two ports are power matched, a condition which can now be obtained separately at port 1 and 2:

$$\begin{cases} \Gamma_G &= S_{11}^* \\ \Gamma_L &= S_{22}^* \end{cases} \quad \longrightarrow \quad G_{u_{max}} = \frac{|S_{21}|^2}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)}$$

# Summary and MSG (Maximum Stable Gain)



$$G_{op} = \frac{P_L}{P_{in}} = |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{1 - |S_{11}|^2 + |\Gamma_L|^2(|S_{22}|^2 - |\Delta_S|^2) + 2\Re(\Gamma_L(S_{11}^* \Delta_S - S_{22}))}$$

$$G_{av} = \frac{P_{av,out}}{P_{av,in}} = |S_{21}|^2 \frac{1 - |\Gamma_G|^2}{1 - |S_{22}|^2 + |\Gamma_G|^2(|S_{11}|^2 - |\Delta_S|^2) + 2\Re(\Gamma_G(S_{22}^* \Delta_S - S_{11}))}$$

$$G_t = \frac{P_L}{P_{av,in}} = |S_{21}|^2 \frac{(1 - |\Gamma_L|^2)(1 - |\Gamma_G|^2)}{|(1 - \Gamma_L S_{22})(1 - \Gamma_G S_{11}) - S_{12} S_{21} \Gamma_G \Gamma_L|^2}$$

$$\text{MAG} = \frac{|S_{21}|}{|S_{12}|} \left( K - \sqrt{K^2 - 1} \right) \xrightarrow{K=1} \text{MSG} = \frac{|S_{21}|}{|S_{12}|} \quad \text{MSG=MAG for } K=1 \rightarrow \text{figure of merit if } K \leq 1$$

$$\text{MUG} = \frac{|S_{21}|^2}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)}$$

# Conclusion on simultaneous power matching

---



- **Simultaneous power matching** leads to **maximum gain(s)** and **maximum power transfer** → basic design of maximum gain amplifier
- Can be implemented only if the stability factor is equal to or larger than one → this happens if the device is *unconditionally stable* (unconditional stability implies  $K \geq 1$ )
- Names to be remembered:
  - **MAG** (Maximum Available Gain, the maximum gain);
  - **MSG** (Maximum Stable Gain, often used as a figure of merit as a function of frequency if the device is potentially unstable);
  - **MUG** (Maximum Unilateral Gain, less important)