

# Digital Logic Design: a rigorous approach ©

## Chapter 13: Decoders and Encoders

Guy Even   Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

January 24, 2013

Book Homepage:

<http://www.eng.tau.ac.il/~guy/Even-Medina>

## Example

an adder and a register (a memory device). The output of the adder should be stored by the register. Different name to each bit?!

## Definition

A *bus* is a set of wires that are connected to the same modules. The *width* of a bus is the number of wires in the bus.

## Example

PCI bus is used to connect hardware devices (e.g., network cards, sound cards, USB adapters) to the main memory.

In our settings, we consider wires instead of nets.

# Indexing conventions

- 1 Connection of terminals is done by assignment statements:  
The statement  $b[0 : 3] \leftarrow a[0 : 3]$  means connect  $a[i]$  to  $b[i]$ .
- 2 “Reversing” of indexes does not take place unless explicitly stated:  $b[i : j] \leftarrow a[i : j]$  and  $b[i : j] \leftarrow a[j : i]$ , have the same meaning, i.e.,  $b[i] \leftarrow a[i], \dots, b[j] \leftarrow a[j]$ .
- 3 “Shifting” is done by default:  $a[0 : 3] \leftarrow b[4 : 7]$ , meaning that  $a[0] \leftarrow b[4], a[1] \leftarrow b[5]$ , etc. We refer to such an implied re-assignment of indexes as **hardwired shifting**.

# Example - 1


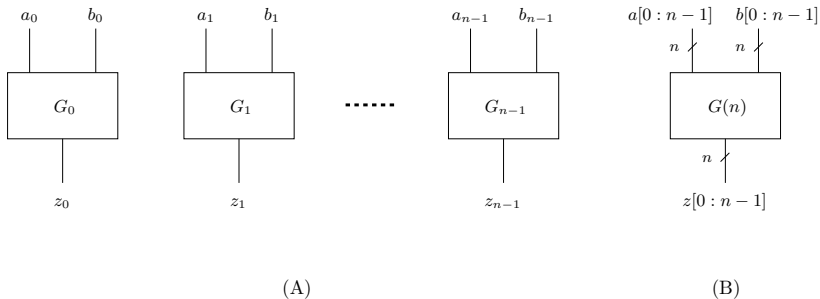


Figure: Vector notation: multiple instances of the same gate.

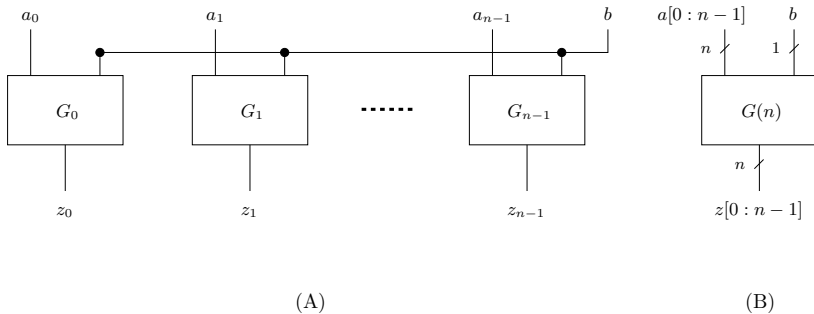

**Figure:** Vector notation:  $b$  feeds all the gates.

# Reminder: Binary Representation

Recall that  $\langle a[n-1 : 0] \rangle_n$  denotes the binary number represented by an  $n$ -bit vector  $\vec{a}$ .

$$\langle a[n-1 : 0] \rangle_n \triangleq \sum_{i=0}^{n-1} a_i \cdot 2^i.$$

## Definition

*Binary representation* using  $n$ -bits is a function  $bin_n : \{0, 1, \dots, 2^n - 1\} \rightarrow \{0, 1\}^n$  that is the inverse function of  $\langle \cdot \rangle$ . Namely, for every  $a[n-1 : 0] \in \{0, 1\}^n$ ,

$$bin_n(\langle a[n-1 : 0] \rangle_n) = a[n-1 : 0].$$

# Division in Binary Representation

$$r = (a \bmod b):$$

$$a = q \cdot b + r, \text{ where } 0 \leq r < b.$$

## Claim

Let  $s = \langle x[n-1:0] \rangle_n$ , and  $0 \leq k \leq n-1$ . Let  $q$  and  $r$  denote the quotient and remainder obtained by dividing  $s$  by  $2^k$ . Define the binary strings  $x_R[k-1:0]$  and  $x_L[n-1:n-k-1]$  as follows.

$$x_R[k-1:0] \triangleq x[k-1:0]$$

$$x_L[n-k-1:0] \triangleq x[n-1:k].$$

Then,

$$q = \langle x_L[n-k-1:0] \rangle$$

$$r = \langle x_R[k-1:0] \rangle.$$

# Definition of Decoder

## Definition

A **decoder with input length  $n$**  is a combinational circuit specified as follows:

**Input:**  $x[n-1:0] \in \{0,1\}^n$ .

**Output:**  $y[2^n-1:0] \in \{0,1\}^{2^n}$

**Functionality:**

$$y[i] \triangleq \begin{cases} 1 & \text{if } \langle \vec{x} \rangle = i \\ 0 & \text{otherwise.} \end{cases}$$

We denote a decoder with input length  $n$  by  $\text{DECODER}(n)$ .



# Definition of Decoder

## Definition

A **decoder with input length  $n$** :

**Input:**  $x[n-1:0] \in \{0,1\}^n$ .

**Output:**  $y[2^n-1:0] \in \{0,1\}^{2^n}$

**Functionality:**

$$y[i] \triangleq \begin{cases} 1 & \text{if } \langle \vec{x} \rangle = i \\ 0 & \text{otherwise.} \end{cases}$$

Number of outputs of a decoder is exponential in the number of inputs. Note also that exactly one bit of the output  $\vec{y}$  is set to one. Such a representation of a number is often termed **one-hot encoding** or **1-out-of- $k$  encoding**.

## Example

Consider a decoder `DECODER(3)`. On input  $x = 101$ , the output  $y$  equals 00100000.

An example of how a decoder is used is in decoding of controller instructions. Suppose that each instruction is coded by an 4-bit string. Our goal is to determine what instruction is to be executed. For this purpose, we feed the 4 bits to a `DECODER(4)`. There are 16 outputs, exactly one of which will equal 1. This output will activate a module that should be activated in this instruction.

# Brute force design

- simplest way: build a separate circuit for every output bit  $y[i]$ .
- The circuit for  $y[i]$  is simply a product of  $n$  literals.
- Let  $v \triangleq \text{bin}_n(i)$ , i.e.,  $v$  is the binary representation of the index  $i$ .
- define the minterm  $p_v$  to be  $p_v \triangleq (\ell_1^v \cdot \ell_2^v \cdots \ell_n^v)$ , where:

$$\ell_j^v \triangleq \begin{cases} x_j & \text{if } v_j = 1 \\ \bar{x}_j & \text{if } v_j = 0. \end{cases}$$

## Claim

$$y[i] = p_v.$$

The brute force decoder circuit consists of:

- $n$  inverters used to compute  $\text{INV}(\vec{x})$ , and
- a separate  $\text{AND}(n)$ -tree for every output  $y[i]$ .
- The delay of the brute force design is
$$t_{pd}(\text{INV}) + t_{pd}(\text{AND}(n)\text{-tree}) = O(\log_2 n).$$
- The cost of the brute force design is  $\Theta(n \cdot 2^n)$ , since we have an  $\text{AND}(n)$ -tree for each of the  $2^n$  outputs.

Wasteful because, if the binary representation of  $i$  and  $j$  differ in a single bit, then the  $\text{AND}$ -trees of  $y[i]$  and  $y[j]$  share all but a single input. Hence the product of  $n - 1$  bits is computed twice.

We present a systematic way to share hardware between different outputs.

# An asymptotically optimal decoder design

## Base case $\text{DECODER}(1)$ :

The circuit  $\text{DECODER}(1)$  is simply one inverter where:

$y[0] \leftarrow \text{INV}(x[0])$  and  $y[1] \leftarrow x[0]$ .

## Reduction rule $\text{DECODER}(n)$ :

We assume that we know how to design decoders with input length less than  $n$ , and design a decoder with input length  $n$ .

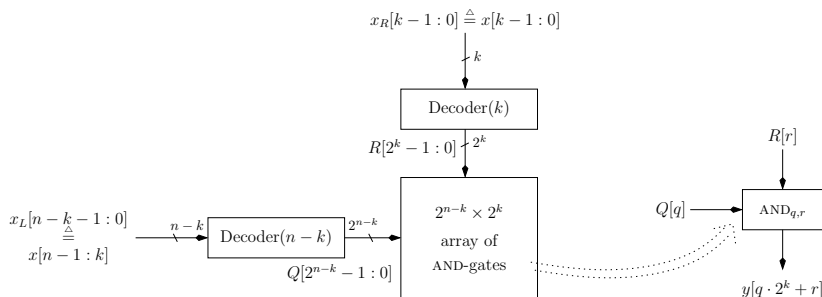


Figure: A recursive implementation of  $\text{DECODER}(n)$ .

### Claim (Correctness)

$$y[i] = 1 \iff \langle x[n-1:0] \rangle = i.$$

# Cost analysis

We denote the cost and delay of  $\text{DECODER}(n)$  by  $c(n)$  and  $d(n)$ , respectively. The cost  $c(n)$  satisfies the following recurrence equation:

$$c(n) = \begin{cases} c(\text{INV}) & \text{if } n=1 \\ c(k) + c(n-k) + 2^n \cdot c(\text{AND}) & \text{otherwise.} \end{cases}$$

It follows that, up to constant factors

$$c(n) = \begin{cases} 1. & \text{if } n = 1 \\ c(k) + c(n-k) + 2^n & \text{if } n > 1. \end{cases} \quad (1)$$

Obviously,  $c(n) = \Omega(2^n)$  (regardless of the value of  $k$ ).

## Claim

$c(n) = O(2^n)$  if  $k = \lceil n/2 \rceil$ .

# Delay analysis.

The delay of  $\text{DECODER}(n)$  satisfies the following recurrence equation:

$$d(n) = \begin{cases} d(\text{INV}) & \text{if } n=1 \\ \max\{d(k), d(n-k)\} + d(\text{AND}) & \text{otherwise.} \end{cases}$$

Set  $k = n/2$ . It follows that  $d(n) = \Theta(\log n)$ .



## Theorem

*For every decoder  $G$  of input length  $n$ :*

$$d(G) = \Omega(\log n)$$

$$c(G) = \Omega(2^n).$$

## Proof.

- ① lower bound on delay : use log delay lower bound theorem.
- ② lower bound on cost? The proof is based on the following observations:
  - Computing each output bit requires at least one nontrivial gate.
  - No two output bits are identical.



- An encoder implements the inverse Boolean function implemented by a decoder.
- the Boolean function implemented by a decoder is not surjective.
- the range of the Boolean function implemented by a decoder is the set of binary vectors in which exactly one bit equals 1.
- It follows that an encoder implements a partial Boolean function (i.e., a function that is not defined for every binary string).

# Hamming Distance and Weight

## Definition

The **Hamming distance** between two binary strings  $u, v \in \{0, 1\}^n$  is defined by

$$\text{dist}(u, v) \triangleq |\{i \mid u_i \neq v_i\}|.$$

## Definition

The **Hamming weight** of a binary string  $u \in \{0, 1\}^n$  equals  $\text{dist}(u, 0^n)$ . Namely, the number of non-zero symbols in the string.

We denote the Hamming weight of a binary string  $\vec{a}$  by  $\text{wt}(\vec{a})$ , namely,

$$\text{wt}(a[n-1:0]) \triangleq |\{i : a[i] \neq 0\}|.$$

# Concatenation of strings

Recall that the concatenation of the strings  $a$  and  $b$  is denoted by  $a \circ b$ .

## Definition

The binary string obtained by  $i$  concatenations of the string  $a$  is denoted by  $a^i$ .

Consider the following examples of string concatenation:

- If  $a = 01$  and  $b = 10$ , then  $a \circ b = 0110$ .
- If  $a = 1$  and  $i = 5$ , then  $a^i = 11111$ .
- If  $a = 01$  and  $i = 3$ , then  $a^i = 010101$ .
- We denote the zeros string of length  $n$  by  $0^n$  (beware of confusion between exponentiation and concatenation of the binary string 0).

# Definition of Encoder function

We define the encoder partial function as follows.

## Definition

The function  $\text{ENCODER}_n : \{\vec{y} \in \{0, 1\}^{2^n} : \text{wt}(\vec{y}) = 1\} \rightarrow \{0, 1\}^n$  is defined as follows:  $\langle \text{ENCODER}_n(\vec{y}) \rangle$  equals the index of the bit of  $y[2^n - 1 : 0]$  that equals one. Formally,

$$\text{wt}(y) = 1 \implies y[\langle \text{ENCODER}_n(\vec{y}) \rangle] = 1.$$

Examples:

- ①  $\text{ENCODER}_3(0001) = 00$ ,  $\text{ENCODER}_3(0010) = 01$ ,  
 $\text{ENCODER}_3(0100) = 10$ ,  $\text{ENCODER}_3(1000) = 11$ .
- ②  $\text{ENCODER}_n(0^{2^n-k-1} \circ 1 \circ 0^k) = \text{bin}_n(k)$ .

# Encoder circuit - definition

## Definition

An **encoder** with input length  $2^n$  and output length  $n$  is a combinational circuit that implements the Boolean function  $\text{ENCODER}_n$ .

We denote an encoder with input length  $2^n$  and output length  $n$  by  $\text{ENCODER}(n)$ . An  $\text{ENCODER}(n)$  can be also specified as follows:

**Input:**  $y[2^n - 1 : 0] \in \{0, 1\}^{2^n}$ .

**Output:**  $x[n - 1 : 0] \in \{0, 1\}^n$ .

**Functionality:** If  $\text{wt}(\vec{y}) = 1$ , let  $i$  denote the index such that  $y[i] = 1$ . In this case  $\vec{x}$  should satisfy  $\langle \vec{x} \rangle = i$ .  
Formally:

$$\text{wt}(\vec{y}) = 1 \implies y[\langle \vec{x} \rangle] = 1.$$

- functionality is not specified for all inputs  $\vec{y}$ .
- functionality is only specified for inputs whose Hamming weight equals one.
- Since an encoder is a combinational circuit, it implements a Boolean function. This means that it outputs a digital value even if  $wt(y) \neq 1$ . Thus, two encoders must agree only with respect to inputs whose Hamming weight equals one.
- If  $\vec{y}$  is output by a decoder, then  $wt(\vec{y}) = 1$ , and hence an encoder implements the inverse function of a decoder.

# Brute Force Implementation

Recall that  $\text{bin}_n(i)[j]$  denotes the  $j$ th bit in the binary representation of  $i$ . Let  $A_j$  denote the set

$$A_j \triangleq \{i \in [0 : 2^n - 1] \mid \text{bin}_n(i)[j] = 1\}.$$

## Claim

If  $\text{wt}(y) = 1$ , then  $x[j] = \bigvee_{i \in A_j} y[i]$ .



## Claim

*If  $\text{wt}(y) = 1$ , then  $x[j] = \bigvee_{i \in A_j} y[i]$ .*

Implementing an  $\text{ENCODER}(n)$ :

- For each output  $x_j$ , use a separate OR-tree whose inputs are  $\{y[i] \mid i \in A_j\}$ .
- Each such OR-tree has at most  $2^n$  inputs.
- the cost of each OR-tree is  $O(2^n)$ .
- total cost is  $O(n \cdot 2^n)$ .
- The delay of each OR-tree is  $O(\log 2^n) = O(n)$ .

# Can we do better?

- We will prove that the cone of the first output is  $\Omega(2^n)$ .
- So for every encoder  $C$ :  $c(C) = \Omega(2^n)$  and  $d(C) = \Omega(n)$ .
- The brute force design is not that bad. Can we reduce the cost?
- Let's try...

## ENCODER'(n) - a recursive design

For  $n = 1$ , is simply  $x[0] \leftarrow y[1]$ .

**Reduction step:**

$$y_L[2^{n-1} - 1 : 0] = y[2^n - 1 : 2^{n-1}]$$

$$y_R[2^{n-1} - 1 : 0] = y[2^{n-1} - 1 : 0].$$

Use two ENCODER'(n - 1) with inputs  $\vec{y}_L$  and  $\vec{y}_R$ . But,

$$wt(\vec{y}) = 1 \Rightarrow (wt(\vec{y}_L) = 0) \vee (wt(\vec{y}_R) = 0).$$


What does an encoder output when input all-zeros?

Augment the definition of the  $\text{ENCODER}_n$  function so that its domain also includes the all-zeros string  $0^{2^n}$ . We define

$$\text{ENCODER}_n(0^{2^n}) \triangleq 0^n.$$


Note that  $\text{ENCODER}'(1)$  (i.e.,  $x[0] \leftarrow y[1]$ ) also meets this new condition, so the induction basis of the correctness proof holds.
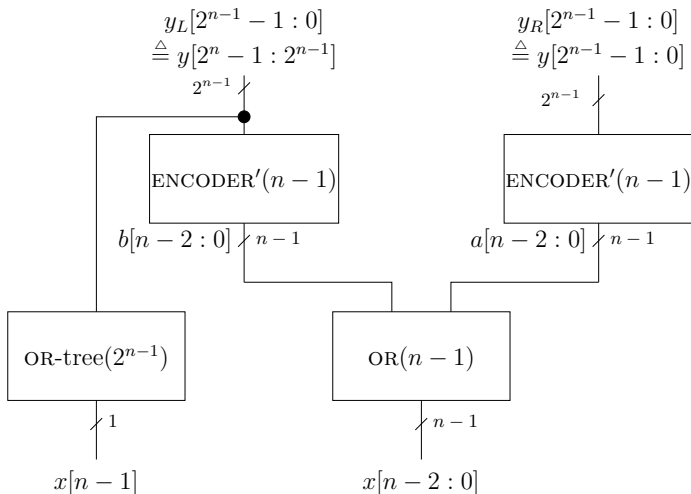
# Reduction step for $\text{ENCODER}'(n)$


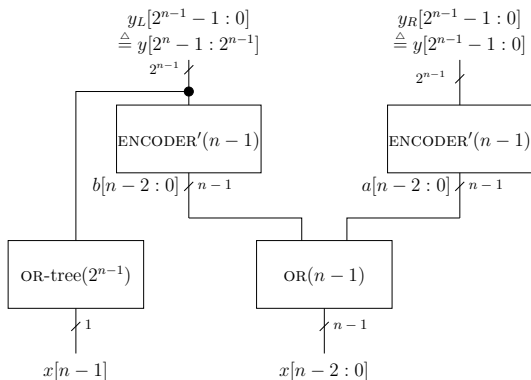
## Claim

*The circuit  $\text{ENCODER}'(n)$  implements the Boolean function  $\text{ENCODER}_n$ .*



$$c(\text{ENCODER}'(n)) = \begin{cases} 0 & \text{if } n = 1 \\ 2 \cdot c(\text{ENCODER}'(n-1)) \\ \quad + c(\text{OR-tree}(2^{n-1})) \\ \quad + (n-1) \cdot c(\text{OR}) & \text{if } n > 1. \end{cases}$$

Let  $c(n) \triangleq c(\text{ENCODER}'(n))/c(\text{OR})$ .

$$c(n) = \begin{cases} 0 & \text{if } n = 1 \\ 2 \cdot c(n-1) + (2^{n-1} - 1 + n - 1) & \text{if } n > 1. \end{cases} \quad (2)$$

## Claim

$$c(n) = \Theta(n \cdot 2^n).$$


So  $c(\text{ENCODER}'(n))$  (asymptotically) equals the cost of the brute force design...
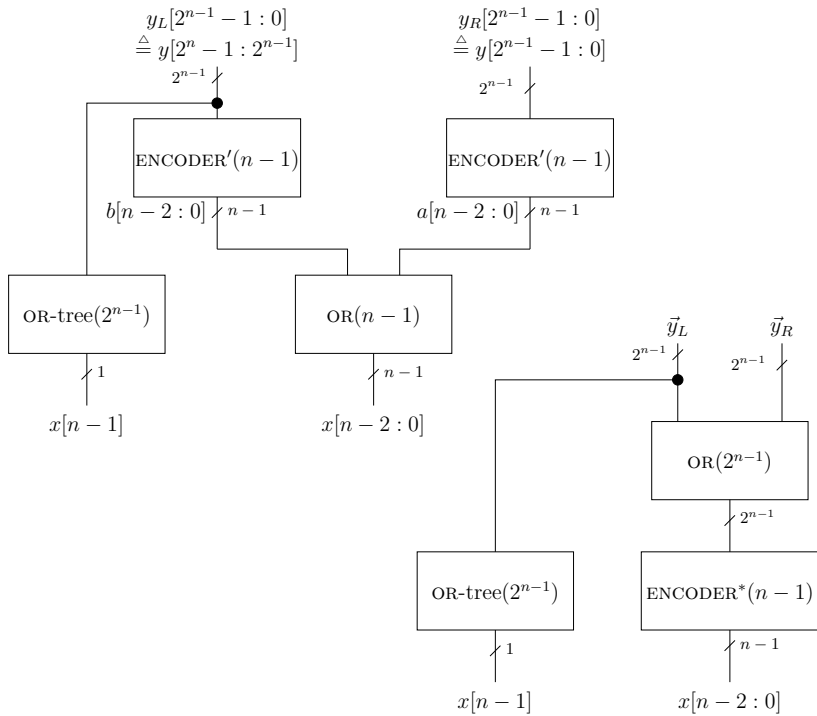
## Claim


*If  $\text{wt}(y[2^n - 1 : 0]) \leq 1$ , then*

$$\begin{aligned}\text{ENCODER}_{n-1}(\text{OR}(\vec{y}_L, \vec{y}_R)) \\ = \text{OR}(\text{ENCODER}_{n-1}(\vec{y}_L), \text{ENCODER}_{n-1}(\vec{y}_R)).\end{aligned}$$





# Correctness?

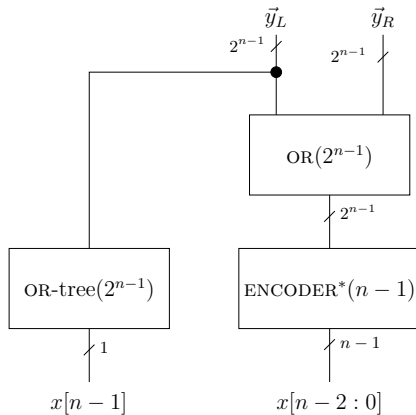

## Definition

Two combinational circuits are **functionally equivalent** if they implement the same Boolean function.

## Claim

*If  $\text{wt}(y[2^n - 1 : 0]) \leq 1$ , then*

$$\text{ENCODER}_{n-1}(\text{OR}(\vec{y}_L, \vec{y}_R)) = \text{OR}(\text{ENCODER}_{n-1}(\vec{y}_L), \text{ENCODER}_{n-1}(\vec{y}_R)).$$

## Claim

*$\text{ENCODER}'(n)$  and  $\text{ENCODER}^*(n)$  are functionally equivalent.*

## Corollary

*$\text{ENCODER}^*(n)$  implements the  $\text{ENCODER}_n$  function.*

# Cost analysis

The cost of  $\text{ENCODER}^*(n)$  satisfies the following recurrence equation:

$$c(\text{ENCODER}^*(n)) = \begin{cases} 0 & \text{if } n=1 \\ c(\text{ENCODER}^*(n-1)) + (2^n - 1) \cdot c(\text{OR}) & \text{otherwise} \end{cases}$$

$C(2^k) \triangleq c(\text{ENCODER}^*(k))/c(\text{OR})$ . Then,

$$C(2^k) = \begin{cases} 0 & \text{if } k=0 \\ C(2^{k-1}) + (2^k - 1) \cdot c(\text{OR}) & \text{otherwise.} \end{cases}$$

we conclude that  $C(2^k) = \Theta(2^k)$ .

## Claim

$$c(\text{ENCODER}^*(n)) = \Theta(2^n) \cdot c(\text{OR}).$$

The delay of  $\text{ENCODER}^*(n)$  satisfies the following recurrence equation:

$$d(\text{ENCODER}^*(n)) = \begin{cases} 0 & \text{if } n=1 \\ \max\{d(\text{OR-tree}(2^{n-1})), \\ \quad d(\text{ENCODER}^*(n-1) + d(\text{OR}))\} & \text{otherwise.} \end{cases}$$

Since  $d(\text{OR-tree}(2^{n-1})) = (n-1) \cdot d(\text{OR})$ , it follows that

$$d(\text{ENCODER}^*(n)) = n \cdot d(\text{OR}).$$

# Asymptotic Optimality

Our goal is to prove that the encoder design we presented is optimal.

## Theorem

*For every encoder  $G$  of input length  $n$ :*

$$d(G) = \Omega(n)$$

$$c(G) = \Omega(2^n).$$

## Proof.

Let  $f_0 : \{0, 1\}^{2^n} \rightarrow \{0, 1\}$  denote the Boolean function implemented by the output  $x[0]$ . We claim that

$$\{2i + 1 \mid 0 \leq i \leq 2^n - 1\} \subseteq \text{cone}(f_0).$$

Indeed, consider  $y = 0^{2^n}$  and  $z \triangleq \text{flip}_{2i+1}(y)$ .



We discussed:

- buses
- decoders
- encoders

Three main techniques were used in this chapter.

- Divide & Conquer - a recursive design methodology.
- Extend specification to make problem easier. Adding restrictions to the specification made the task easier since we were able to add assumptions in our recursive designs.
- Evolution. Naive, correct, costly design. Improved while preserving functionality to obtain a cheaper design.