

# Digital Logic Design: a rigorous approach ©

## Chapter 14: Selectors

Guy Even   Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

April 10, 2012

Book Homepage:

<http://www.eng.tau.ac.il/~guy/Even-Medina>

# Preliminary questions:

- ❶ Which types of shifts are you familiar with in your favorite programming language? What is the differences between these shifts? Why do we need different types of shifts?
- ❷ How are these shifts executed in a microprocessor?
- ❸ Should shifters be considered to be combinational circuits? After all, they simply “move bits around” and do not compute “new bits”.

# Multiplexer (MUX)

## Definition

A MUX-gate is a combinational gate that has three inputs  $D[0]$ ,  $D[1]$ ,  $S$  and one output  $Y$ . The functionality is defined by

$$Y = \begin{cases} D[0] & \text{if } S = 0 \\ D[1] & \text{if } S = 1. \end{cases}$$

Note that we could have used the shorter expression  $Y = D[S]$  to define the functionality of a MUX-gate.

## Definition

An  $(n:1)$ -MUX is a combinational circuit defined as follows:

**Input:** **data input**  $D[n-1:0]$  and **select input**  $S[k-1:0]$   
where  $k = \lceil \log_2 n \rceil$ .

**Output:**  $Y \in \{0, 1\}$ .

**Functionality:**

$$Y = D[\langle \vec{S} \rangle].$$

To simplify the discussion, we will assume in this chapter that  $n$  is a power of 2, namely,  $n = 2^k$ .


## Example

Let  $n = 4$  and  $D[3:0] = 0101$ . If  $S[1:0] = 00$ , then  $Y = D[0] = 1$ . If  $S[1:0] = 01$ , then  $Y = D[1] = 0$ .

We describe two implementations of  $(n:1)$ -MUX.

- translate the number  $\langle \vec{S} \rangle$  to 1-out-of- $n$  representation (using a decoder).
- tree based.


# decoder based $(n:1)$ -MUX

 

## Claim

*The  $(n:1)$ -MUX design is correct.*


# decoder based $(n:1)$ -MUX - cost

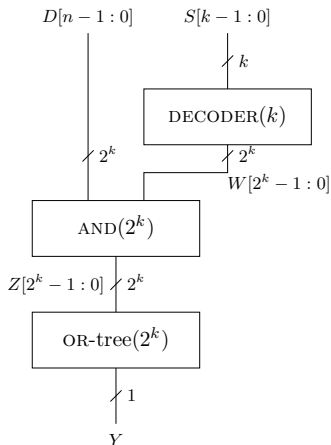

## Claim

*The cost of the  $(n:1)$ -MUX design is  $\Theta(n)$ .*

# decoder based $(n:1)$ -MUX - delay

 

## Claim

*The delay of the  $(n:1)$ -MUX design is  $\Theta(\log n)$ .*



## $(n:1)$ -MUX - lower bounds

### Claim

*The cone of the Boolean function implemented by a  $(n : 1)$ -MUX circuit contains at least  $n$  elements.*

Consider combinational circuits with at most two input terminals per gate (or any constant).


### Corollary

*The cost of the  $(n:1)$ -MUX design is asymptotically optimal.*

### Corollary

*The delay of the  $(n:1)$ -MUX design is asymptotically optimal.*


# tree based $(n:1)$ -MUX

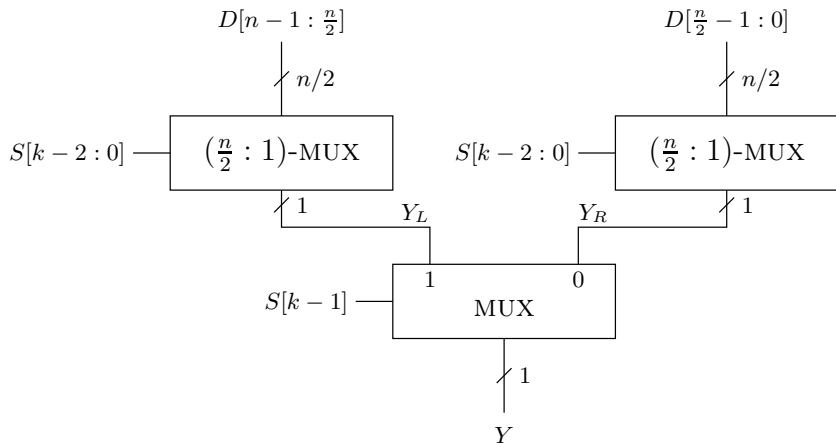

## Claim

*The  $(n:1)$ -MUX design is correct.*


## tree based $(n:1)$ -MUX - cost

 

### Claim

*The cost of the  $(n:1)$ -MUX design is  $\Theta(n)$ .*

## tree based $(n:1)$ -MUX - delay

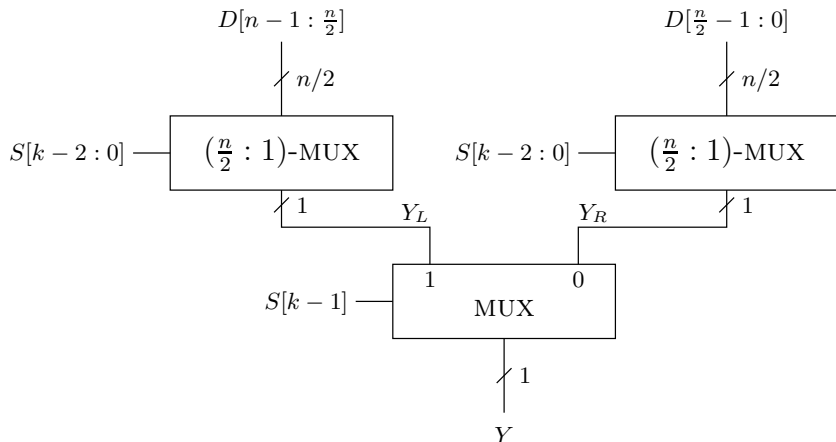

### Claim

*The delay of the  $(n:1)$ -MUX design is  $\Theta(\log n)$ .*

- Both implementations are asymptotically optimal with respect to cost and delay.
- The cost/delay table suggests that the tree-like implementation is cheaper and faster.
- Fast and cheap implementations of MUX-gates in CMOS technology do not restore the signals well. This means that long paths consisting only of MUX-gates are not allowed.
- What about physical layout? Which design has a smaller “drawing”?
- Conclusion: our simplified model cannot be used to deduce conclusively which multiplexer design is better.