

## WS 20.1 Power converters

© 2018 Richard G Carter

This Mathcad 14 worksheet is designed to accompany the author's book "Microwave and RF Vacuum Electronic Power Sources", Cambridge University Press (2018). The section, equation, and figure numbers refer to the corresponding sections, equations, and figures in the book. Data input fields are highlighted in yellow and output fields are highlighted in green.

This resource is provided free of charge by Cambridge University Press with permission of the author, but is subject to copyright. You are permitted to view, print and download this resource for your own personal use only, provided any copyright lines are not removed or altered in any way. Any other use, including but not limited to, distribution of the resource in modified form, or via electronic or other media, is strictly prohibited unless you have permission from the author and provided you give appropriate acknowledgement of the source.

The contents of this sheet are provided for educational purposes only and no warranty is expressed or implied that they are suitable for use as professional design tools.

This sheet can be used to explore the properties of different types of simple power converter. For further information see Mohan, N., T. M. Undeland, et al. (2003). *Power Electronics: Converters, Applications and Design*. Hoboken, NJ, Wiley & Sons Inc.

Peak AC source voltage

$$V_{pk} := 1$$

Load resistance

$$R := 1$$

DC source voltage

$$V_0 := 1$$

Series inductance

$$L := 1$$

Frequency

$$f := 1$$

Time constant

$$\tau := \frac{L}{R}$$

$$\tau = 1$$


Period

$$T := \frac{1}{f}$$


$$T = 1$$

**Circuits**


Circuit A

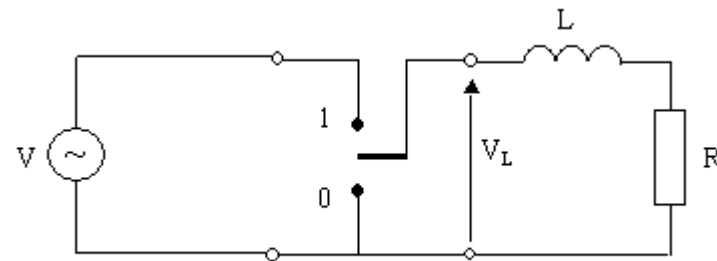

Circuit B

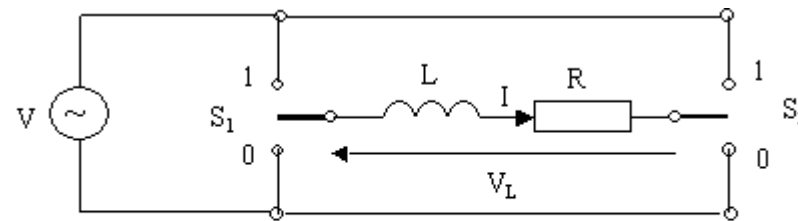

Circuit C

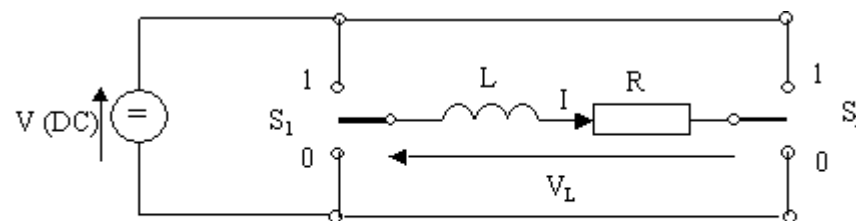

## AC to DC Converters (Rectifiers)

### 1. Half-wave uncontrolled rectifier (Circuit A)

Source EMF  $V(t) := V_{pk} \cdot \sin(2 \cdot \pi \cdot f \cdot t)$




Switch position

$$S(t) := \begin{cases} 1 & \text{if } (\sin(2 \cdot \pi \cdot f \cdot t) > 0) \\ 0 & \text{otherwise} \end{cases}$$

Output voltage  $V_L(t) := S(t) \cdot V(t)$

DC load voltage  $V_{av} = \frac{V_{pk}}{2 \cdot \pi} \cdot \int_0^\pi \sin(\theta) d\theta$   $V_{av} := \frac{V_{pk}}{\pi}$

$$V_{av} = 0.318$$

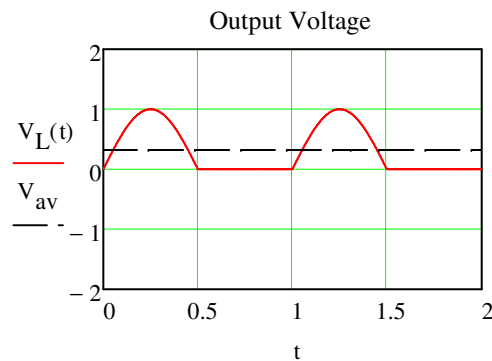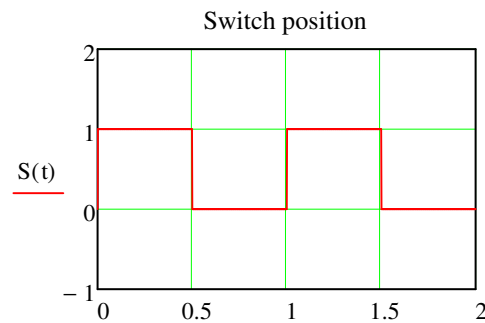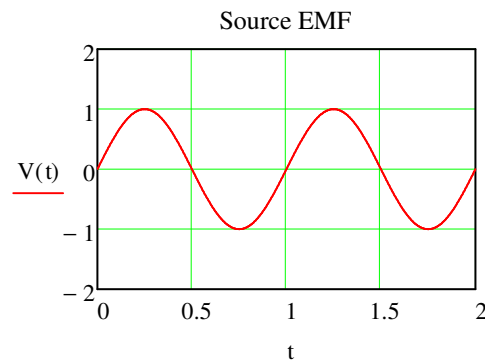


Solve equation for I(t)

$$D(t, I) := \frac{(V_L(t) - R \cdot I)}{L}$$

$$\tau = 1$$
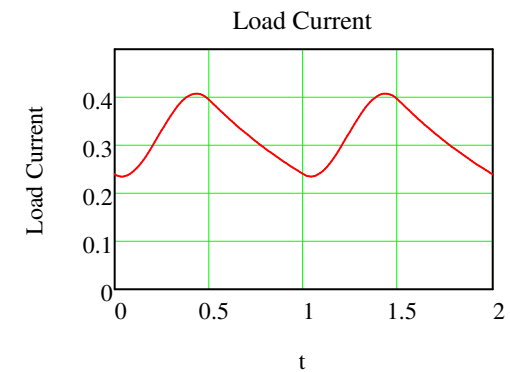
$$I_0 := \frac{V_{av}}{R} \quad Z := \text{rkfixed}(I, -10, 2, 1000, D)$$



## 2. Half-wave controlled rectifier (Circuit A)

Source EMF

$$V(t) := V_{pk} \cdot \sin(2 \cdot \pi \cdot t)$$

Define the **firing angle**  $\alpha$   
(Usually expressed in degrees)

$$\alpha := 60\text{-deg}$$

Switch position

$$S(t) := \begin{cases} 1 & \text{if } (\sin(2 \cdot \pi \cdot t) > 0) \wedge (\sin(2 \cdot \pi \cdot t - \alpha) > 0) \\ 0 & \text{otherwise} \end{cases}$$

Output voltage



$$V_L(t) := S(t) \cdot V(t)$$

DC load voltage

$$V_{av} = \frac{V_{pk}}{2\pi} \int_{\alpha}^{\pi} \sin(\theta) d\theta$$

$$V_{av} := \frac{1}{2} \cdot \frac{V_{pk}}{\pi} \cdot (1 + \cos(\alpha))$$

$$V_{av} = 0.239$$

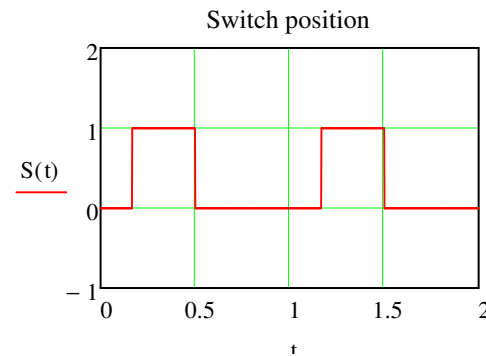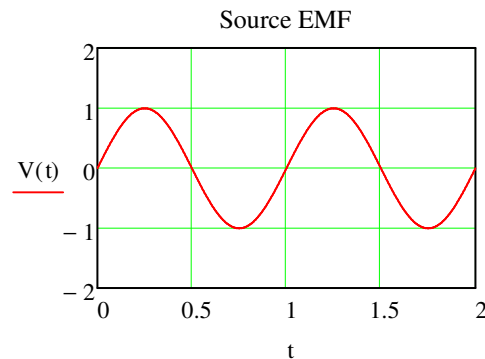



Solve equation for  $I(t)$

$$D(t, I) := \frac{(V_L(t) - R \cdot I)}{L}$$

$$\tau = 1$$

$$I_0 := 0$$
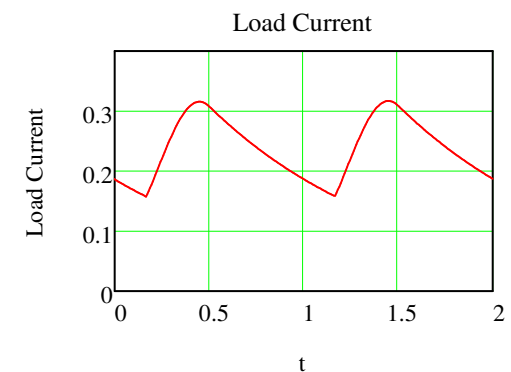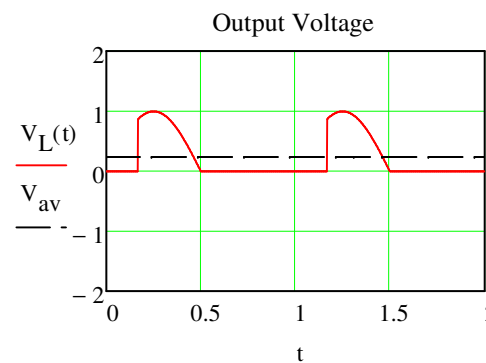
$$Z := \text{rkfixed}(I, -5 \cdot \tau, 2, 1000, D)$$



### 3. Full-wave uncontrolled rectifier (Circuit B)

Source EMF  $V(t) := V_{pk} \cdot \sin(2 \cdot \pi \cdot t)$





Switch 1 position  $S_1(t) := \begin{cases} 1 & \text{if } (\sin(2 \cdot \pi \cdot t) > 0) \\ 0 & \text{otherwise} \end{cases}$

Switch 2 position  $S_2(t) := \begin{cases} 1 & \text{if } (\sin(2 \cdot \pi \cdot t) < 0) \\ 0 & \text{otherwise} \end{cases}$

DC load voltage  $V_{av} = \frac{V_{pk}}{\pi} \cdot \int_0^\pi \sin(\theta) d\theta$   $V_{av} := \frac{2 \cdot V_{pk}}{\pi}$

Output voltage  $V_L(t) := (S_1(t) - S_2(t)) \cdot V(t)$

$V_{av} = 0.637$

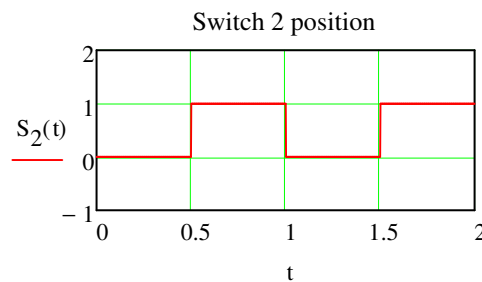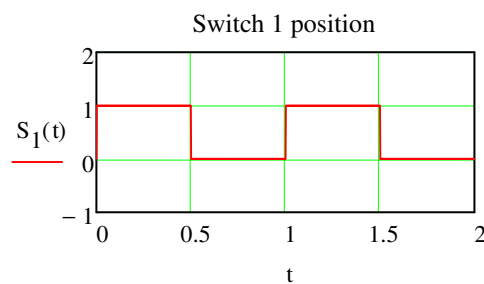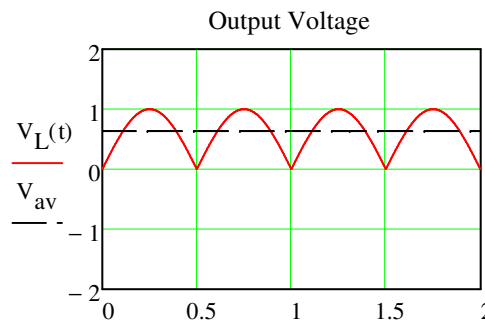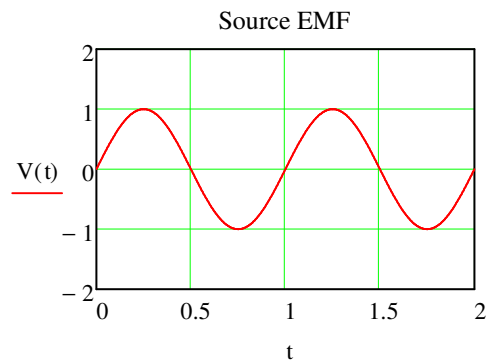


Solve equation for I(t)

$D(t, I) := \frac{(V_L(t) - R \cdot I)}{L}$

$\tau = 1$

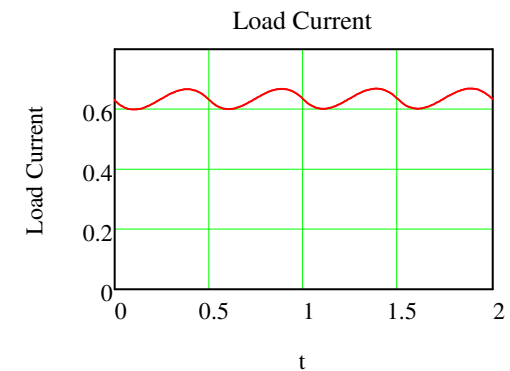$I_0 := 0$   $Z := \text{rkfixed}(I, -5 \cdot \tau, 2, 1000, D)$



#### 4. Full-wave half-controlled rectifier (Circuit B)

Source EMF

$$V(t) := V_{pk} \cdot \sin(2 \cdot \pi \cdot t)$$

$$\alpha := 60 \cdot \text{deg}$$

Switch 1 position

$$S_1(t) := \begin{cases} 1 & \text{if } (\sin(2 \cdot \pi \cdot t) > 0) \wedge \sin(2 \cdot \pi \cdot t - \alpha) > 0 \\ 0 & \text{otherwise} \end{cases}$$

Switch 2 position

$$S_2(t) := \begin{cases} 1 & \text{if } (\sin(2 \cdot \pi \cdot t) < 0) \wedge \sin(2 \cdot \pi \cdot t - \alpha) < 0 \\ 0 & \text{otherwise} \end{cases}$$



Output voltage

$$V_L(t) := (S_1(t) - S_2(t)) \cdot V(t)$$

DC load voltage

$$V_{av} = \frac{V_{pk}}{\pi} \cdot \int_{\alpha}^{\pi} \sin(\theta) d\theta \quad V_{av} := \frac{V_{pk}}{\pi} \cdot (1 + \cos(\alpha))$$

$$V_{av} = 0.477$$

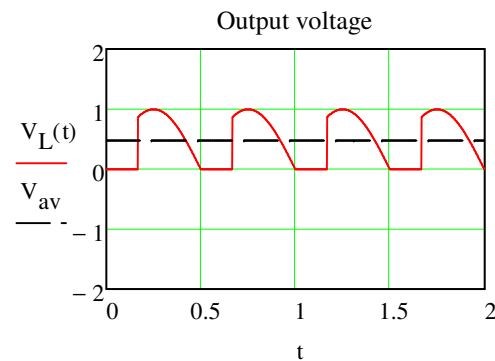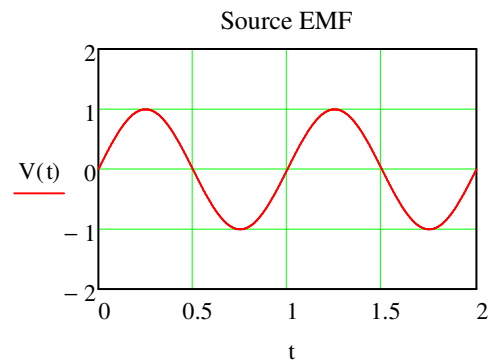




Solve equation for I(t)

$$D(t, I) := \frac{(V_L(t) - R \cdot I)}{L}$$

$$\tau = 1$$

$$I_0 := 0$$
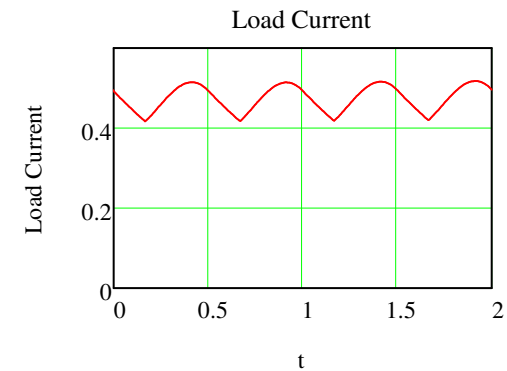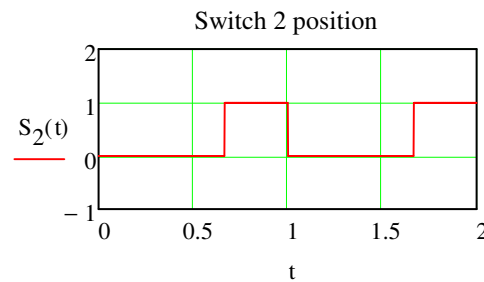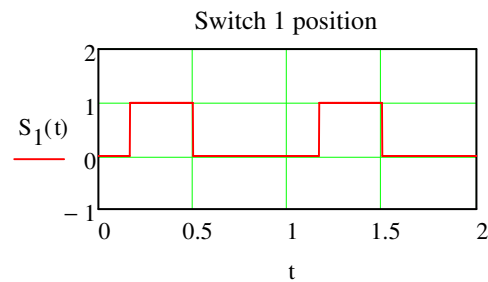
$$Z := \text{rkfixed}(I, -5 \cdot \tau, 2, 1000, D)$$



# 5. Full-wave fully-controlled rectifier (Circuit B)

Source EMF

$$V(t) := V_{pk} \cdot \sin(2 \cdot \pi \cdot t)$$

$$\alpha := 60 \cdot \text{deg}$$

Switch 1 position

$$S_1(t) := \begin{cases} 1 & \text{if } \sin(2 \cdot \pi \cdot t - \alpha) > 0 \\ 0 & \text{otherwise} \end{cases}$$

Note: If  $\alpha > 90$  degrees  $V_{av}$  is negative.

Switch 2 position

$$S_2(t) := \begin{cases} 1 & \text{if } S_1(t) = 0 \\ 0 & \text{otherwise} \end{cases}$$

Output voltage



$$V_L(t) := (S_1(t) - S_2(t)) \cdot V(t)$$

DC load voltage

$$V_{av} = \frac{V_{pk}}{\pi} \cdot \int_{\alpha}^{\pi+\alpha} \sin(\theta) d\theta$$

$$V_{av} := \frac{2 \cdot V_{pk}}{\pi} \cdot \cos(\alpha)$$

$$V_{av} = 0.318$$

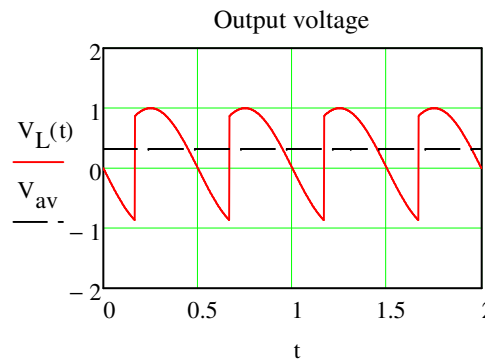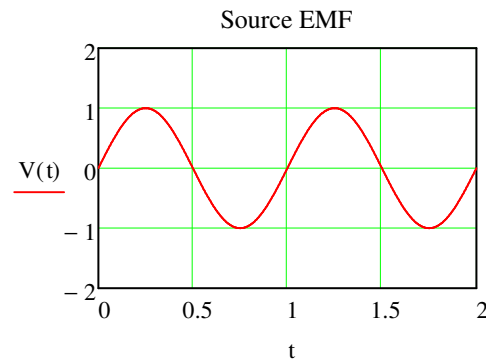




Solve equation for I(t)

$$D(t, I) := \frac{(V_L(t) - R \cdot I)}{L}$$

$$\tau = 1$$

$$I_0 := 0$$
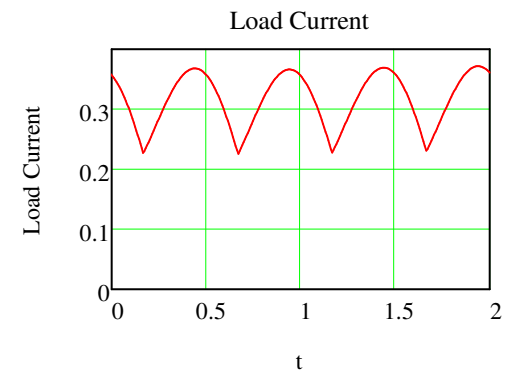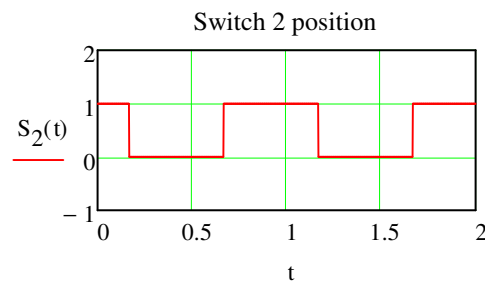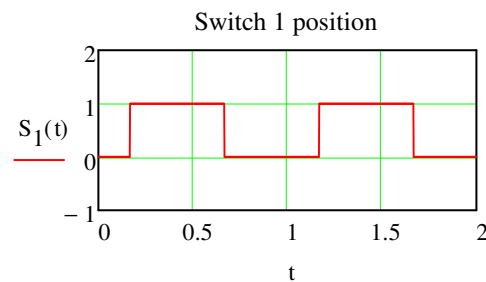
$$Z := \text{rkfixed}(I, -5 \cdot \tau, 2, 1000, D)$$



## DC to AC converters (Inverters)

### 6. Square Wave Inverter (Circuit C)

Switch 1 position  $S_1(t) := \begin{cases} 1 & \text{if } (\sin(2 \cdot \pi \cdot t) > 0) \\ 0 & \text{otherwise} \end{cases}$

Switch 2 position  $S_2(t) := \begin{cases} 1 & \text{if } (\sin(2 \cdot \pi \cdot t) < 0) \\ 0 & \text{otherwise} \end{cases}$

Output voltage  $V_L(t) := (S_1(t) - S_2(t)) \cdot V_0$





Solve equation for I(t)

$$D(t, I) := \frac{(V_L(t) - R \cdot I)}{L}$$

$$\tau = 1$$

$$I_0 := 0$$
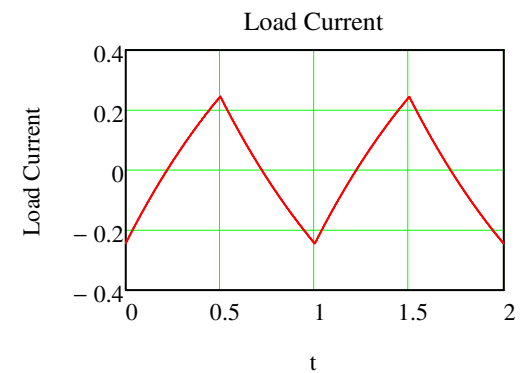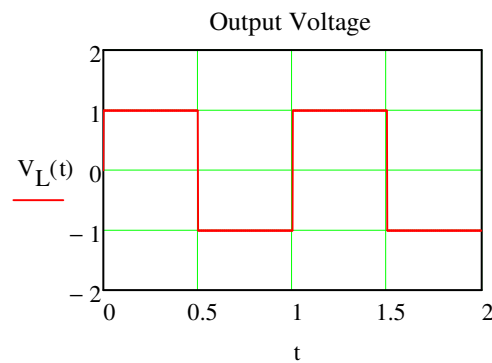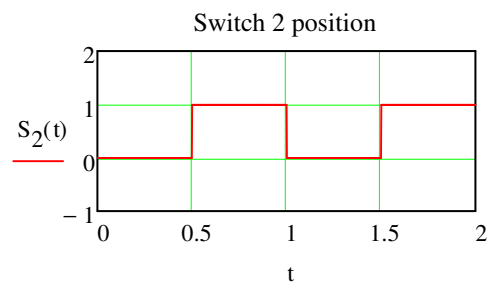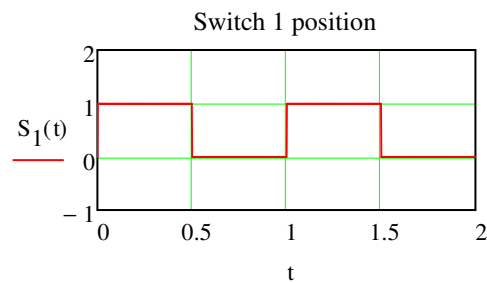
$$Z := \text{rkfixed}(I, -5 \cdot \tau, 2, 5000, D)$$








## 7. Quasi-Square Wave Inverter (Circuit C)

$$\beta := 30 \cdot \text{deg}$$

Switch 1 position  $S_1(t) := \begin{cases} 1 & \text{if } (\sin(2 \cdot \pi \cdot t) > \sin(\beta)) \\ 0 & \text{otherwise} \end{cases}$

Switch 2 position  $S_2(t) := \begin{cases} 1 & \text{if } (\sin(2 \cdot \pi \cdot t) < -\sin(\beta)) \\ 0 & \text{otherwise} \end{cases}$

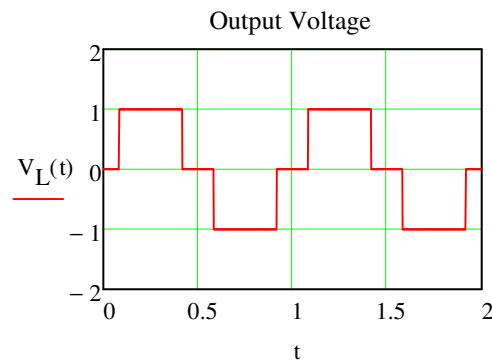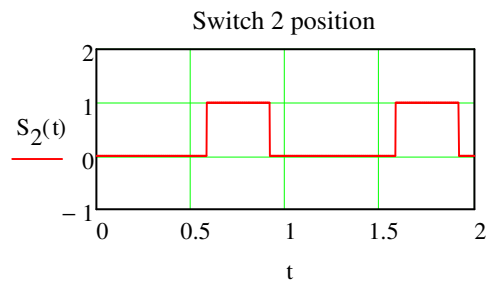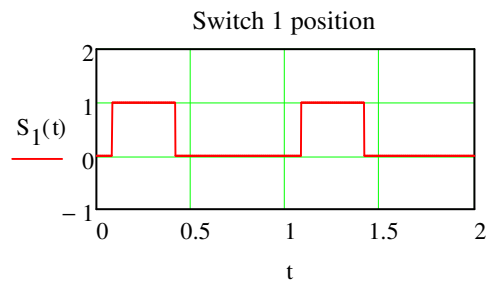
Output voltage  $V_L(t) := (S_1(t) - S_2(t)) \cdot V_0$



Solve equation for  $I(t)$

$$I_0 := 0 \quad D(t, I) := \frac{(V_L(t) - R \cdot I)}{L}$$
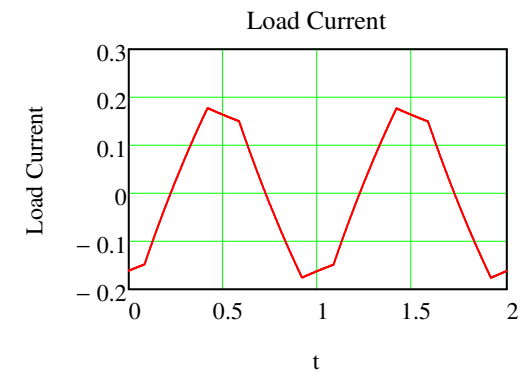
$$Z := \text{rkfixed}(I, -5 \cdot \tau, 2, 5000, D)$$



### 8. Pulse Width Modulated (PWM) Inverter (Alternate Switching, Circuit C)

Define a triangular wave  $f(t)$  with a frequency much higher than the waveform to be generated  $g(t)$

$$f(t) := \text{asin}(\cos(40 \cdot \pi \cdot t))$$

$$g(t) := \sin(2 \cdot \pi \cdot t)$$

Switch 1 position


$$S_1(t) := \begin{cases} 1 & \text{if } (\sin(2 \cdot \pi \cdot t) > f(t)) \\ 0 & \text{otherwise} \end{cases}$$

Switch 2 position


$$S_2(t) := \begin{cases} 0 & \text{if } S_1(t) = 1 \\ 1 & \text{otherwise} \end{cases}$$

Output voltage

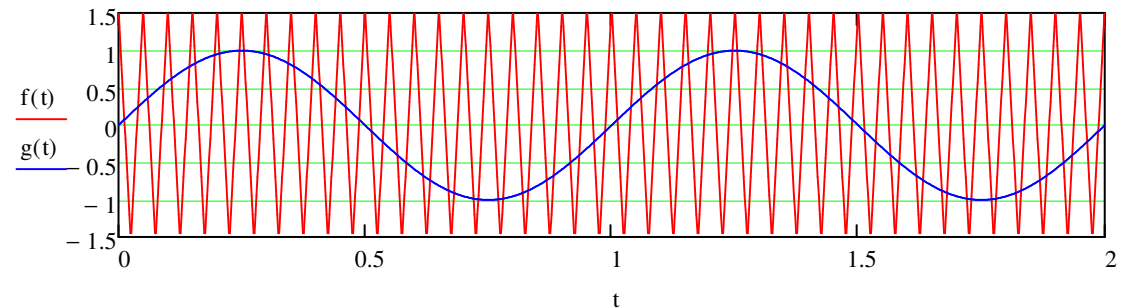
$$V_L(t) := (S_1(t) - S_2(t)) \cdot V_0$$



Switch 1 position

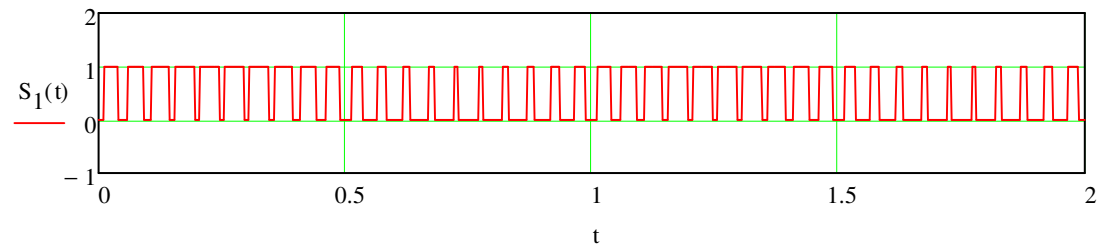



Switch 2 position

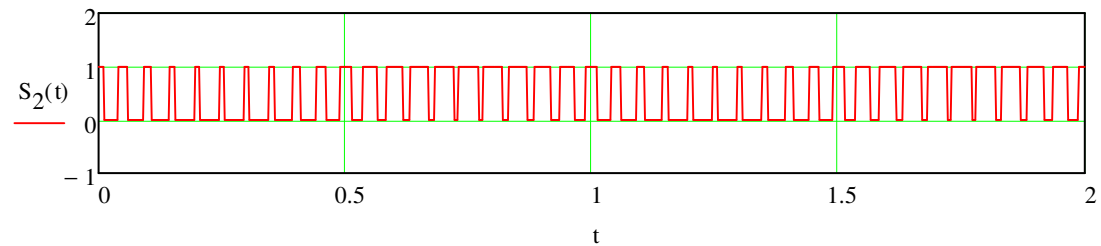

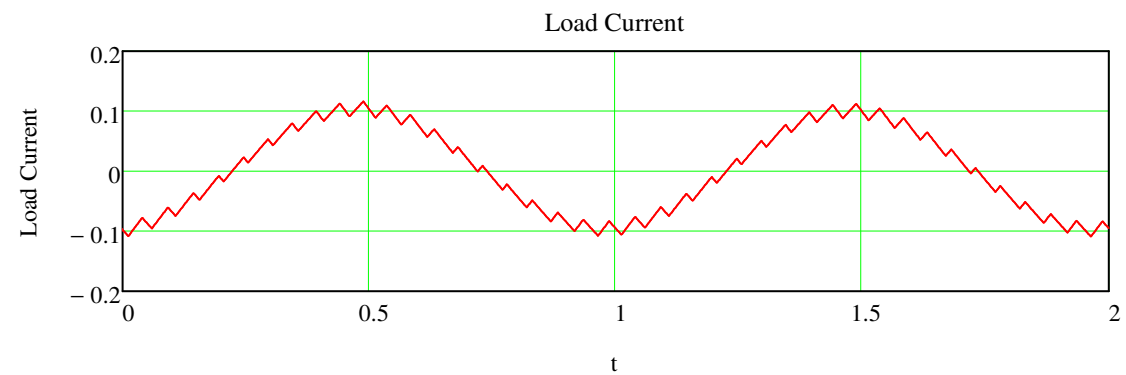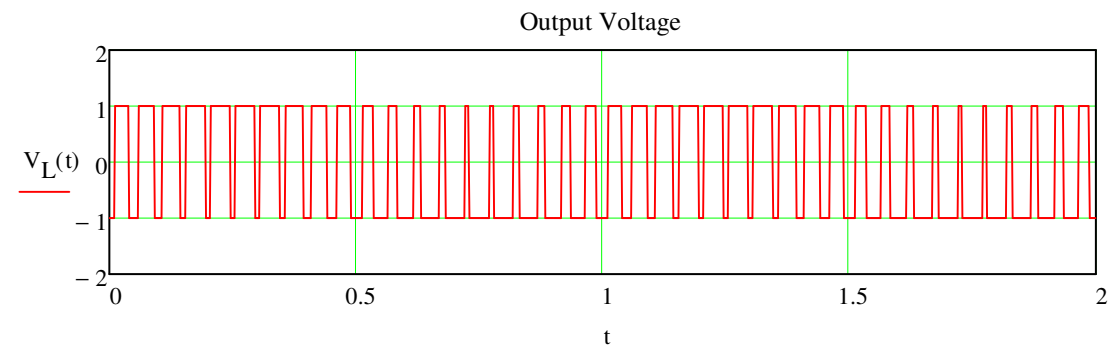**Solve equation for  $I(t)$**

$$I_0 := 0 \quad \underline{\underline{D}}(t, I) := \frac{(V_L(t) - R \cdot I)}{L}$$

$$\underline{\underline{Z}} := \text{rkfixed}(I, -5 \cdot \tau, 2, 5000, D)$$



### 9. Pulse Width Modulated (PWM) Inverter (Sequential Switching, Circuit C)

$$f(t) := \frac{2}{\pi} \arcsin(\cos(40 \cdot \pi \cdot t)) + 1$$

$$g(t) := \sin(2 \cdot \pi \cdot t)$$

Switch 1 position


$$S_1(t) := \begin{cases} 1 & \text{if } (g(t) > f(t)) \wedge g(t) > 0 \\ 0 & \text{otherwise} \end{cases}$$

Switch 2 position


$$S_2(t) := \begin{cases} 1 & \text{if } -g(t) > f(t) \wedge g(t) < 0 \\ 0 & \text{otherwise} \end{cases}$$

Output voltage

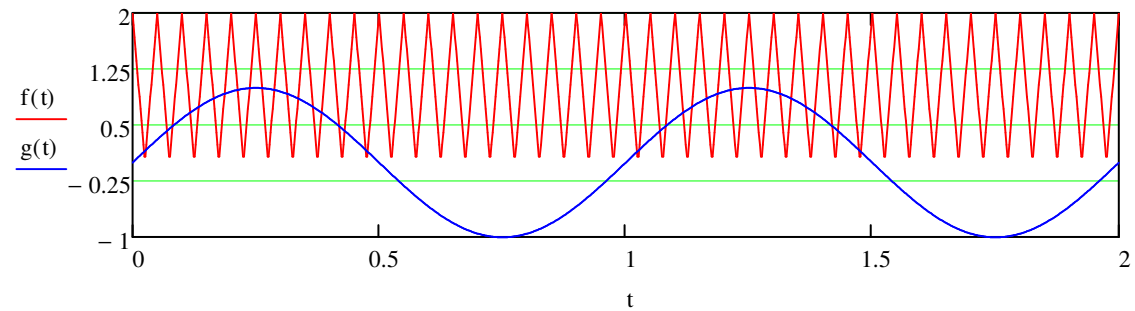
$$V_L(t) := (S_1(t) - S_2(t)) \cdot V_0$$



Switch 1 position

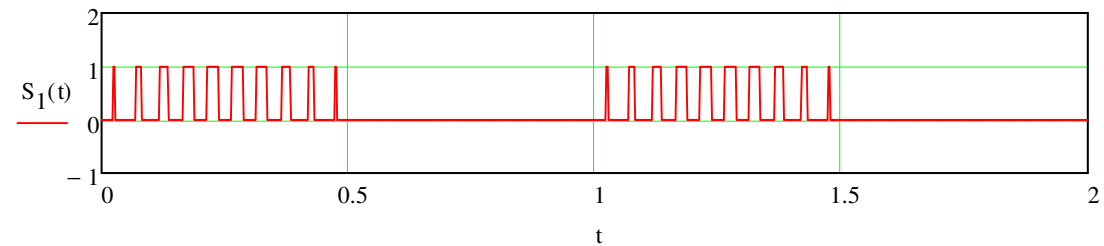

Switch 2 position

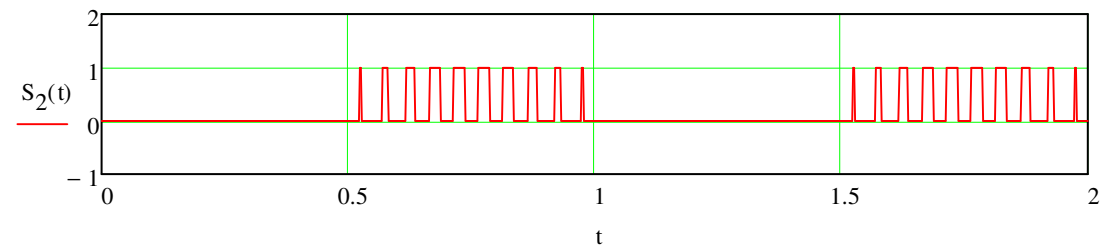

Solve equation for  $I(t)$

$$I_0 := -0.01 \quad \underline{\underline{D}}(t, I) := \frac{(V_L(t) - R \cdot I)}{L}$$

$$\underline{\underline{Z}} := \text{rkfixed}(I, -5 \cdot \tau, 2, 5000, D)$$

