



Fundamentals of High-Frequency CMOS Analog Integrated Circuits

Duran Leblebici
Yusuf Leblebici

Chapter 4

Frequency-Selective RF Circuits (Tuned Amplifiers)

a) Common source tuned amplifier:

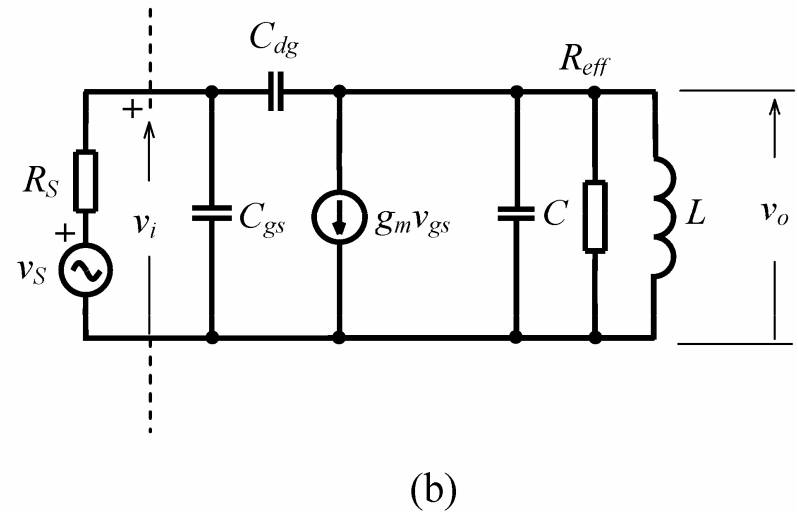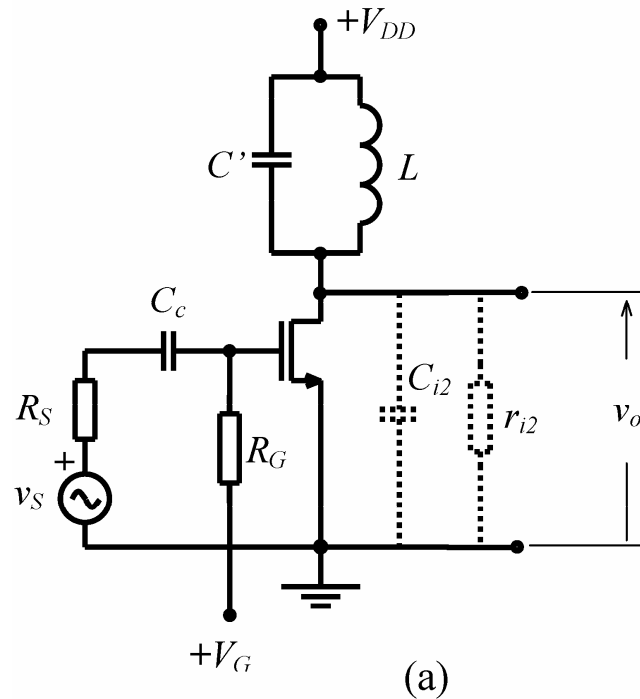

$$A_v = -\frac{g_m - sC_{dg}}{Y_o} \rightarrow A_v = -\frac{g_m - sC_{dg}}{sC + \frac{1}{sL} + G_{eff}}$$

There are two ways to investigate the frequency characteristics:

a) Calculate the magnitude and the phase of the gain as functions of the frequency.

b) Use the pole-zero diagram of the gain function.

(useful to investigate multi-stage, stagger-tuned and double-tuned circuits)

$$A_v = \frac{C_{dg}}{C} \frac{s - \frac{g_m}{C_{dg}}}{s^2 + s \frac{G_{eff}}{C} + \frac{1}{LC}} = \frac{C_{dg}}{C} \frac{s(s - s_0)}{(s - s_{p1})(s - s_{p2})}$$


$$s_0 = +\frac{g_m}{C_{dg}} \quad , \quad s_{p1,p2} = -\frac{G_{eff}}{2C} \mp j \sqrt{\frac{1}{LC} - \left(\frac{G_{eff}}{2C}\right)^2}$$

$$\text{with } \omega_0^2 = \frac{1}{LC} \quad , \quad \sigma = -\frac{G_{eff}}{2C} = -\frac{\omega_0}{2Q_{eff}}$$


$$s_0 = +\frac{g_m}{C_{dg}} \quad , \quad s_{p1,p2} = \sigma \mp j \sqrt{\omega_0^2 - \sigma^2}$$

$$|A| = \frac{C_{dg}}{C} \frac{|s| |s - s_0|}{|s - s_{p1}| |s - s_{p2}|}$$
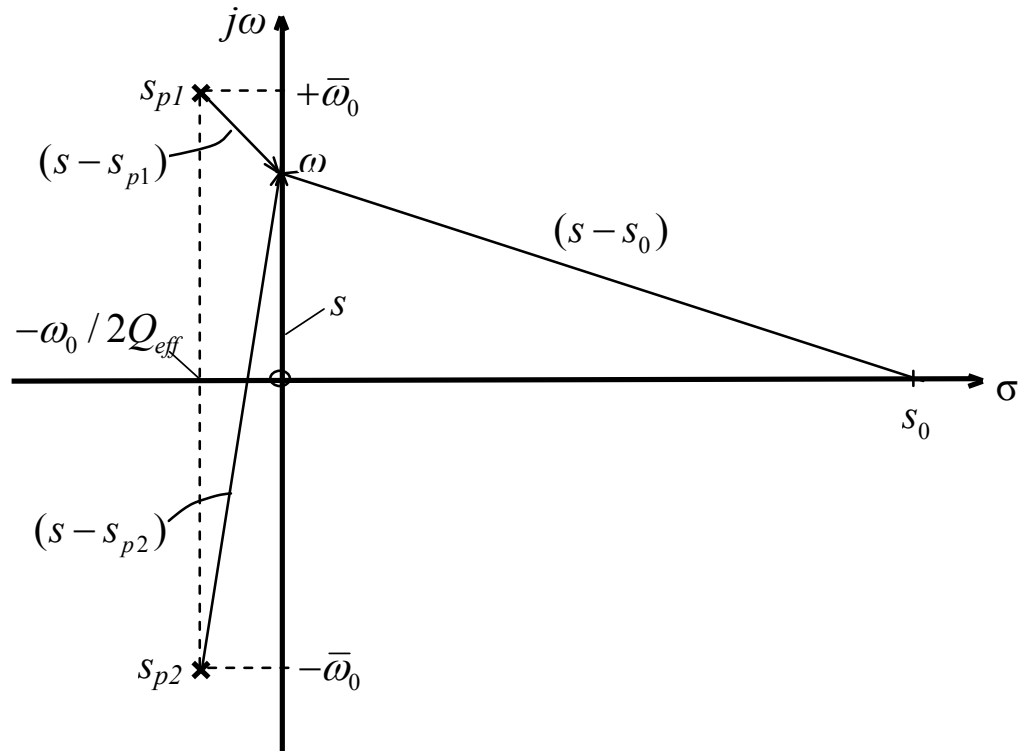
$$\Phi = \Phi_s + \Phi_{(s-s_0)} - \Phi_{(s-s_{p1})} - \Phi_{(s-s_{p2})}$$



For $|s_0| \ll \omega_0$ and $\omega_0 \ll \sigma$ in the vicinity of ω_0 ;

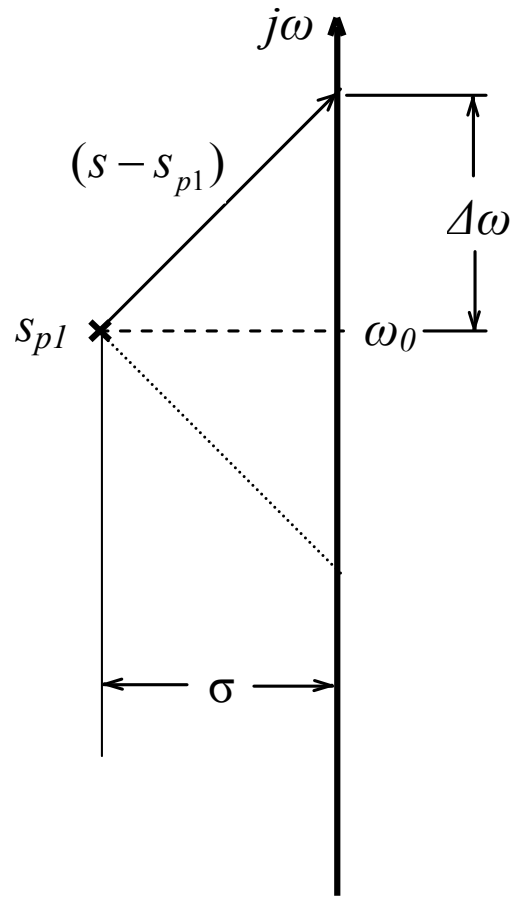

$$|A| \cong \frac{C_{dg}}{C} \frac{|\omega||s_0|}{|s - s_{p1}|2\omega_0} = \frac{g_m}{2C|s - s_{p1}|}$$

$$\Phi \cong \frac{\pi}{2} + \pi - \Phi_{(s-s_{p1})} - \frac{\pi}{2} = \pi - \Phi_{(s-s_{p1})}$$

$$\Delta\omega = \sigma = \frac{\omega_0}{2Q_{ff}} \rightarrow \Delta f = \frac{f_0}{2Q_{eff}}$$

$$f_{(-3dB)} = f_0 \pm \Delta f = f_0 \pm \frac{f_0}{2Q_{eff}}$$

$$B = 2\Delta f = \frac{f_0}{Q_{eff}}$$

Gain at resonance frequency:

$$\text{With } |s - s_{p1}| = \sigma = \omega_0 / 2Q_{eff} ;$$

$$|A(\omega_0)| = g_m \frac{Q_{eff}}{\omega_0 C} = g_m R_{eff} , \quad \Phi(\omega_0) = \pi$$

Band width:

$$B = 2\Delta f = \frac{f_0}{Q_{eff}}$$

The Miller effect on the input admittance

$$y_i = s(C_{gs} + C_{dg}) + y_{mi} = s(C_{gs} + C_{dg}) + s C_{dg} \frac{g_m - s C_{dg}}{Y_o}$$


$$y_{mi}(\omega) = j\omega C_{dg} \frac{g_m - j\omega C_{dg}}{G + j\omega C + \frac{1}{j\omega L}} = \omega^2 L C_{dg} \frac{-g_m + j\omega C_{dg}}{(1 - \omega^2 LC) + j\omega LG}$$

$$\text{Re}\{y_{mi}\} = \frac{(\omega / \omega_0)^2 \frac{C_{dg}}{C}}{\left[1 - (\omega / \omega_0)^2\right]^2 + \omega^2 L^2 G^2} \left(-g_m \left[1 - (\omega / \omega_0)^2\right] + (\omega / \omega_0)^2 \frac{C_{dg}}{C} G \right)$$

$$\text{Im}\{y_{mi}\} = \frac{(\omega / \omega_0)^2 \frac{C_{dg}}{C}}{\left[1 - (\omega / \omega_0)^2\right]^2 + \omega^2 L^2 G^2} \omega \left\{ C_{dg} \left[1 - (\omega / \omega_0)^2\right] + LG g_m \right\}$$


- The input conductance at resonance: $\text{Re}\{y_{mi}(\omega_0)\} = \frac{\omega_0^2 C_{dg}^2}{G}$
- The input conductance above resonance is always positive.
- Below the resonance frequency, the input conductance has a frequency dependent **negative** component.
- The input susceptance is capacitive and frequency dependent.
- If the amplifier is driven by another tuned amplifier;
 - Its frequency characteristic skews (becomes asymmetric).
 - There is a risk of oscillation due to the negative conductance.

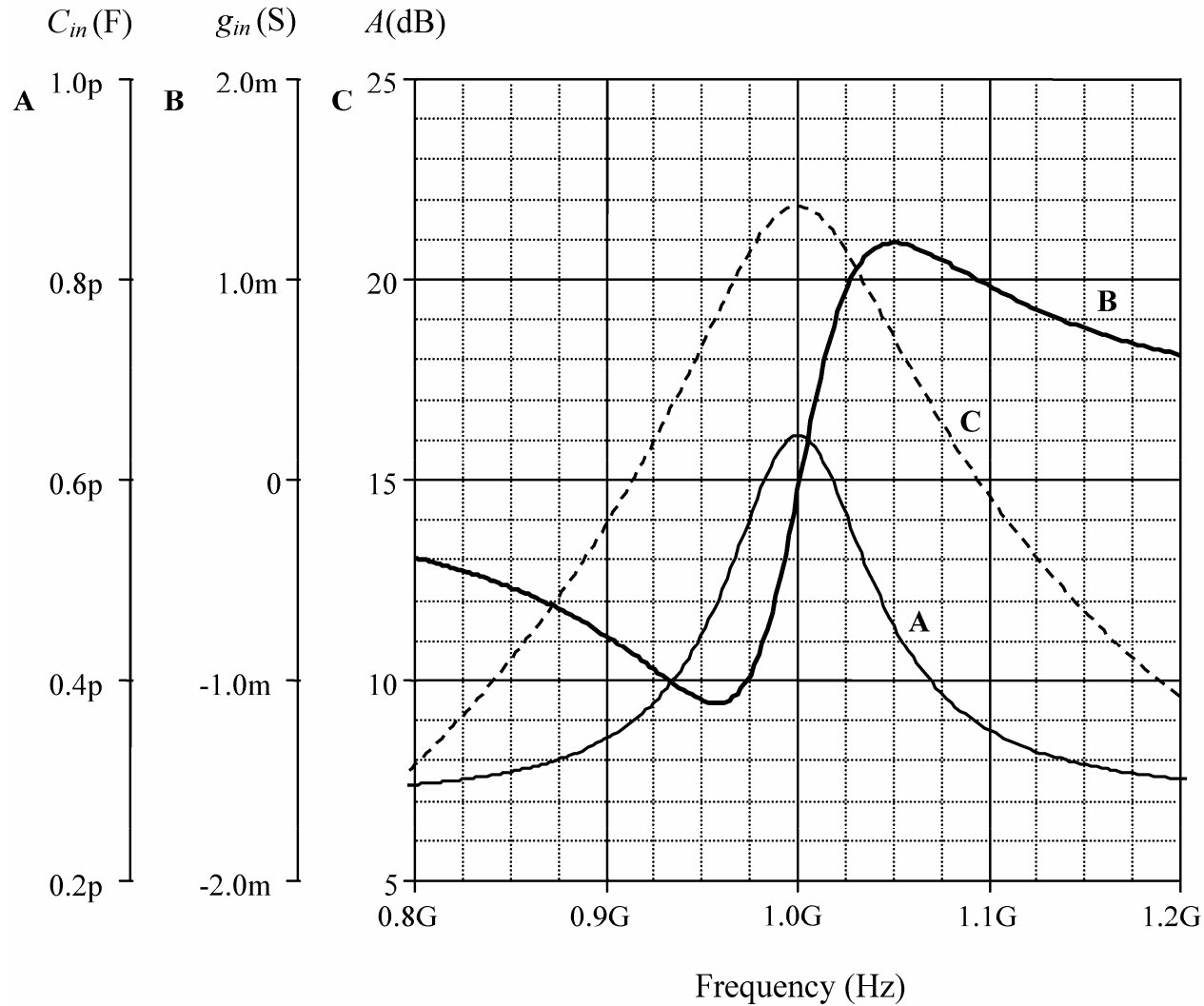Example: AMS 035, 200/0.35, $V_{DD} = 3V$, $V_{GS} = 0.8V$, $L = 10 \text{ nH}$, $C = 2.34 \text{ pF}$, $Q_{eff} = 15.9$





(A) Input capacitance, (B) Input conductance, (C) Voltage gain.

The cascode tuned amplifier

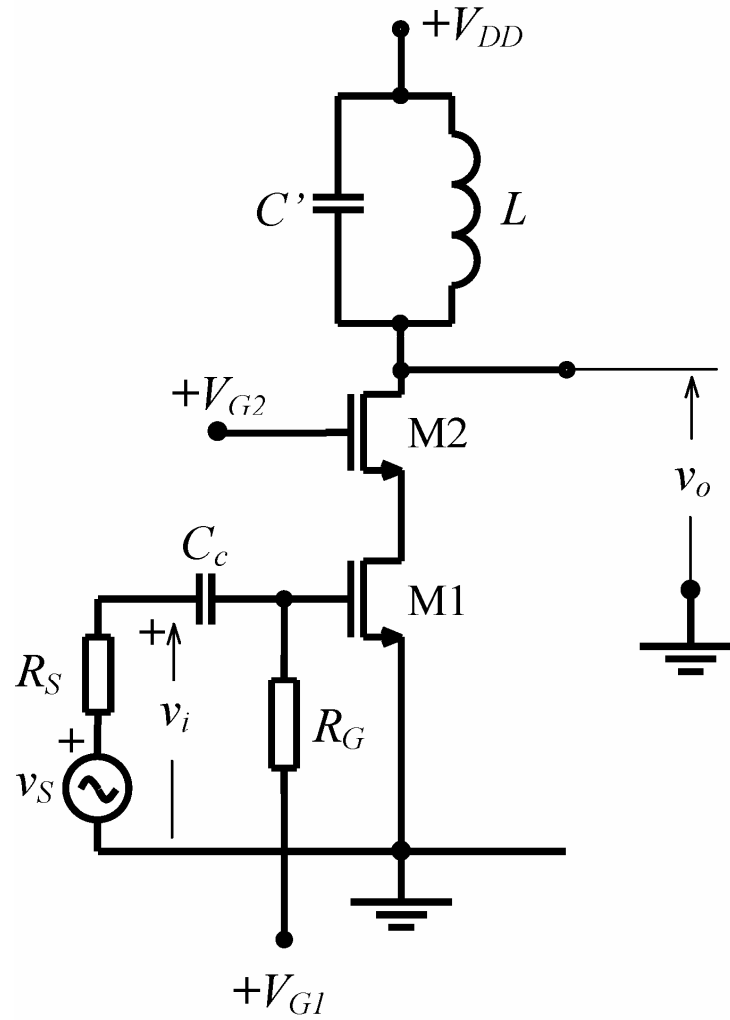

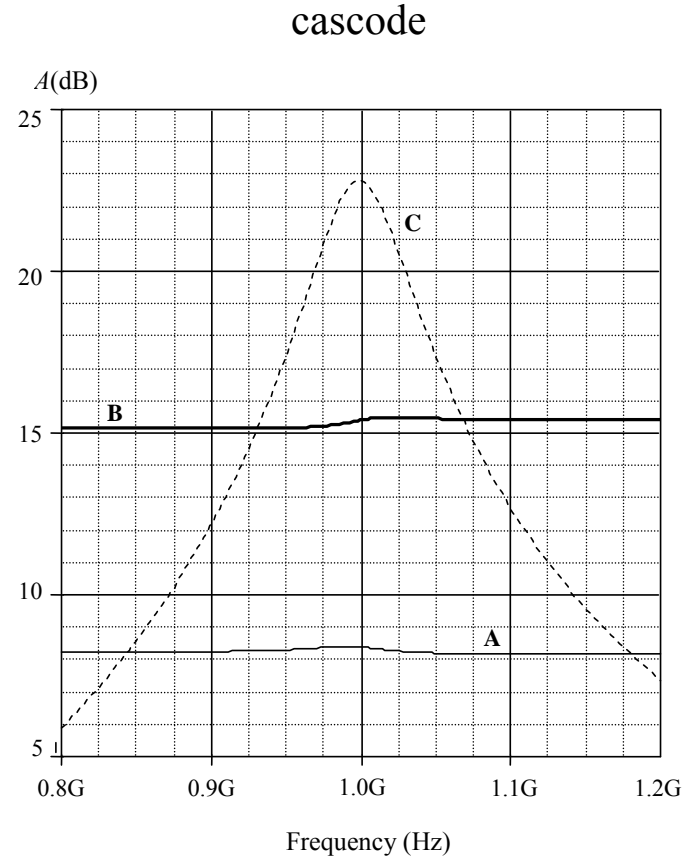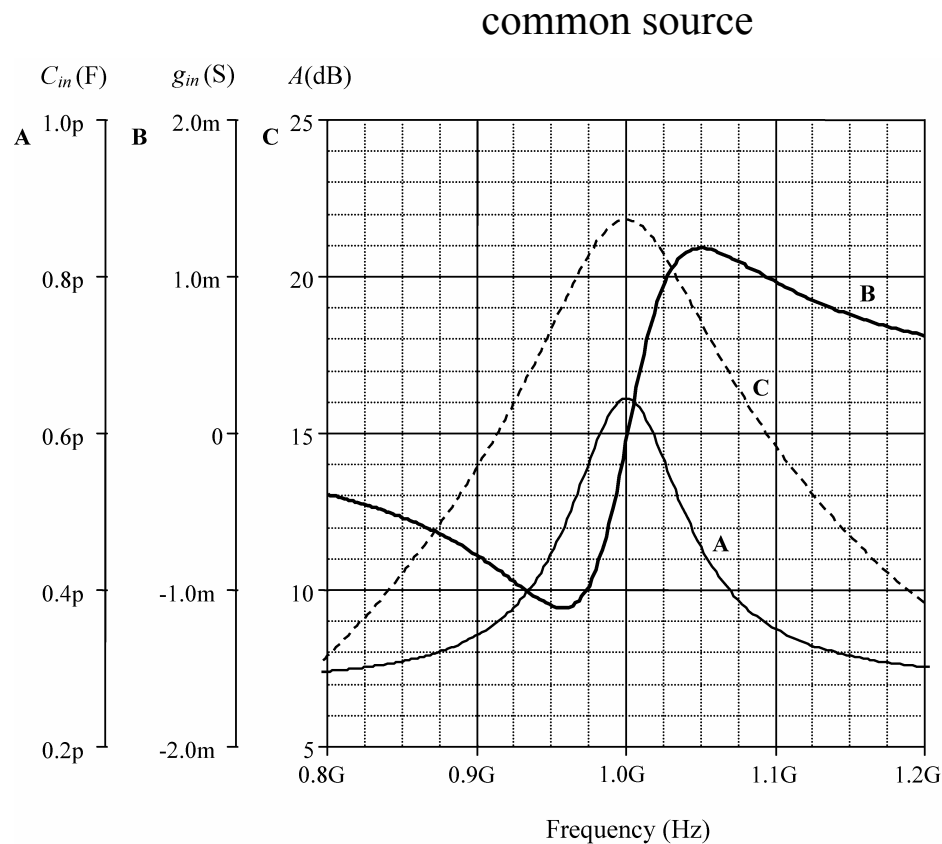The comparison of the common source and the cascode amplifiers:



(A) Input capacitance, (B) Input conductance, (C) Voltage gain.

The obvious advantages of the cascode circuit:

- The input capacitance is almost constant in the entire frequency band.
- The input conductance is positive and almost constant.
(no adverse effect on the load resonance circuit of the previous stage)
- The bandwidth is smaller (the selectivity is better)
thanks to the higher output resistance, consequently higher Q_{eff} .
- Higher voltage gain due to the higher Q_{eff} .

Cascaded tuned stages and staggered tuning

$$A_v = \frac{C_{dg}}{C} \frac{s(s - s_0)}{(s - s_{p1})(s - s_{p2})} \cong -\frac{C_{dg}}{2C} \frac{s_0}{(s - s_{p1})}$$

$$A_v(\omega_0) = -g_m R_{eff} \quad , \quad Q_{eff} = \omega_0 C R_{eff}$$

$$A_v \cong A_v(\omega_0) \frac{\omega_0}{2Q_{eff}} \frac{1}{(s - s_{p1})} = A_v(\omega_{p1}) \frac{\omega_{p1}}{2Q_{eff}} \frac{1}{(s - s_{p1})}$$


Gain of the cascaded n identical stages:

$$A_{vT} \cong [A_v(\omega_{p1})]^n \left(\frac{\omega_0}{2Q_{eff}} \right)^n \frac{1}{(s - s_{p1})^n}$$

Band-width of the cascaded n identical stages:

$$B_T = B \sqrt{2^{1/n} - 1}$$

Normalized gain (dB)

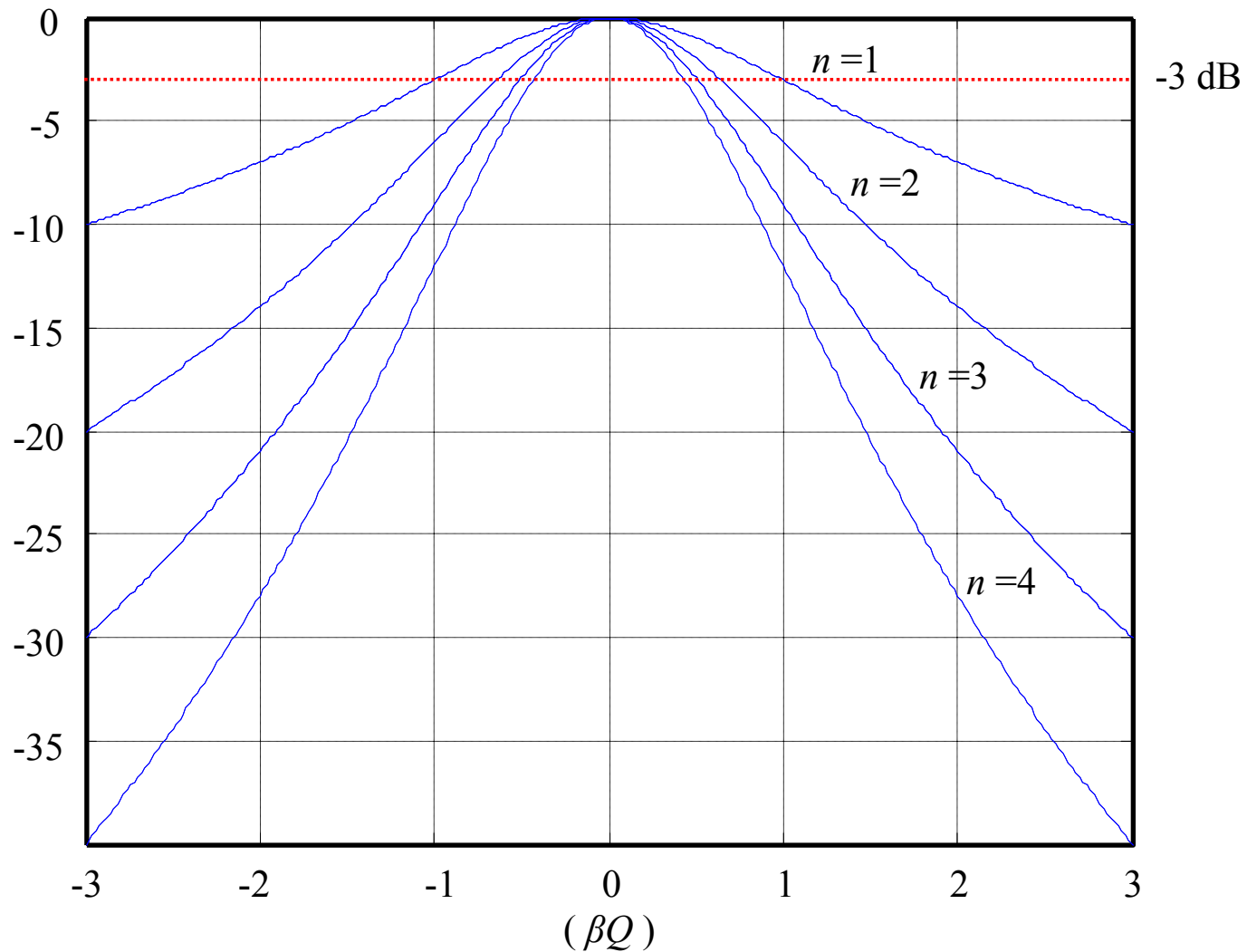

Frequency characteristics of n cascaded identical stages

(Normalized to the gain at resonance frequency)

Gain for cascaded n **non-identical** stages


$$A_{vT} \cong A_{v1}(\omega_{p1}) \cdots A_{vn}(\omega_{pn}) \frac{\omega_{p1}}{2Q_{eff1}} \cdots \frac{\omega_{pn}}{2Q_{effn}} \frac{1}{(s - s_{p1}) \cdots (s - s_{pn})}$$

Important typical pole distributions:


- a) Butterworth type pole positioning for
maximally flat frequency response.
- b) Chebyshev type pole positioning for
equi-ripple response with steeper side-walls

Typical Butterworth and Chebyshev type characteristics having the same relative bandwidth


Magnitude (dB)

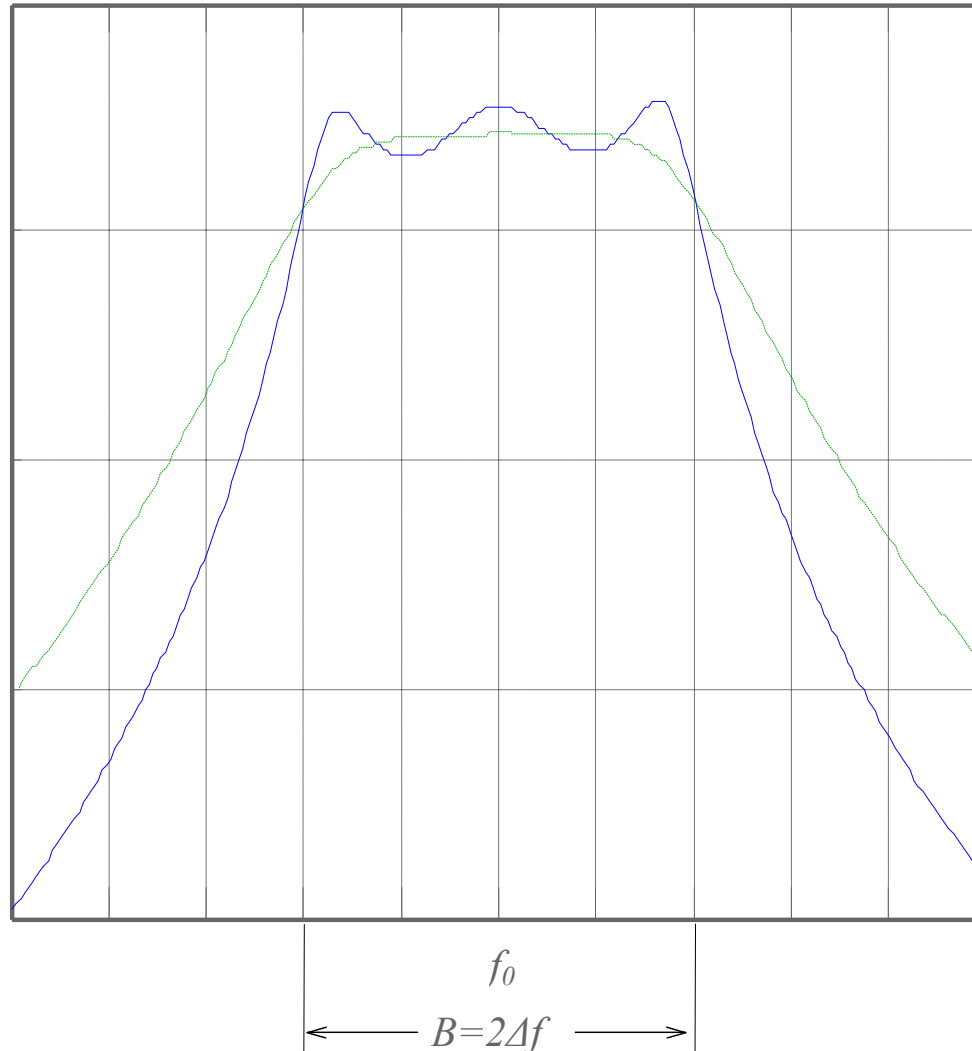

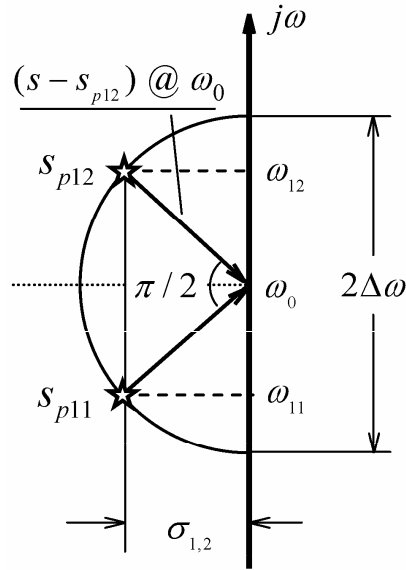
2, 3 and 4 pole Butterworth type pole distributions:



(a)

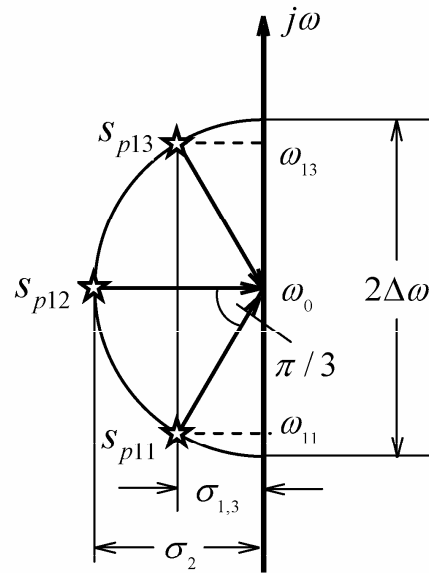

(b)

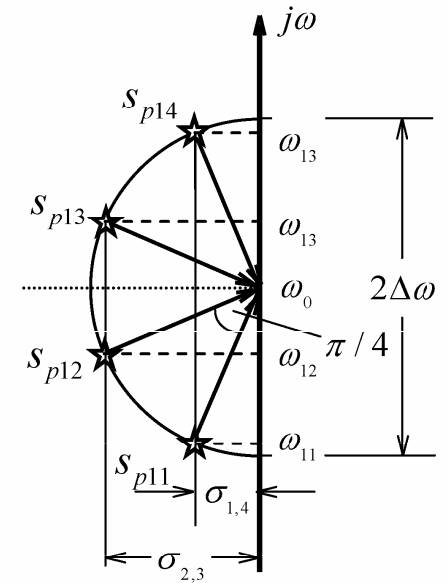

(c)

$$\sigma_{1,2} = -\frac{\omega_{11}}{2Q_1} = -\frac{\omega_{12}}{2Q_2}$$

$$\sigma_2 = -\frac{\omega_0}{2Q_2}$$

$$\sigma_{1,3} = -\frac{\omega_{11}}{2Q_1} = -\frac{\omega_{13}}{2Q_3}$$

$$\sigma_{1,4} = -\frac{\omega_{11}}{2Q_1} = -\frac{\omega_{14}}{2Q_4}$$

$$\sigma_{2,3} = -\frac{\omega_{12}}{2Q_2} = -\frac{\omega_{13}}{2Q_3}$$


Approximate expressions for $2\Delta\omega \ll \omega_0$:

$$\sigma_{1,2} \cong -\frac{\omega_0}{2Q_1} = -\frac{\omega_0}{2Q_2} \Rightarrow Q_1 \cong Q_2$$

$$\sigma_{1,3} \cong -\frac{\omega_0}{2Q_1} = -\frac{\omega_0}{2Q_3} \Rightarrow Q_1 \cong Q_3$$

$$\sigma_{1,4} \cong -\frac{\omega_0}{2Q_1} = -\frac{\omega_0}{2Q_4} , \quad \sigma_{2,3} \cong -\frac{\omega_0}{2Q_2} = -\frac{\omega_0}{2Q_3} \Rightarrow Q_1 \cong Q_4 , \quad Q_2 \cong Q_3$$

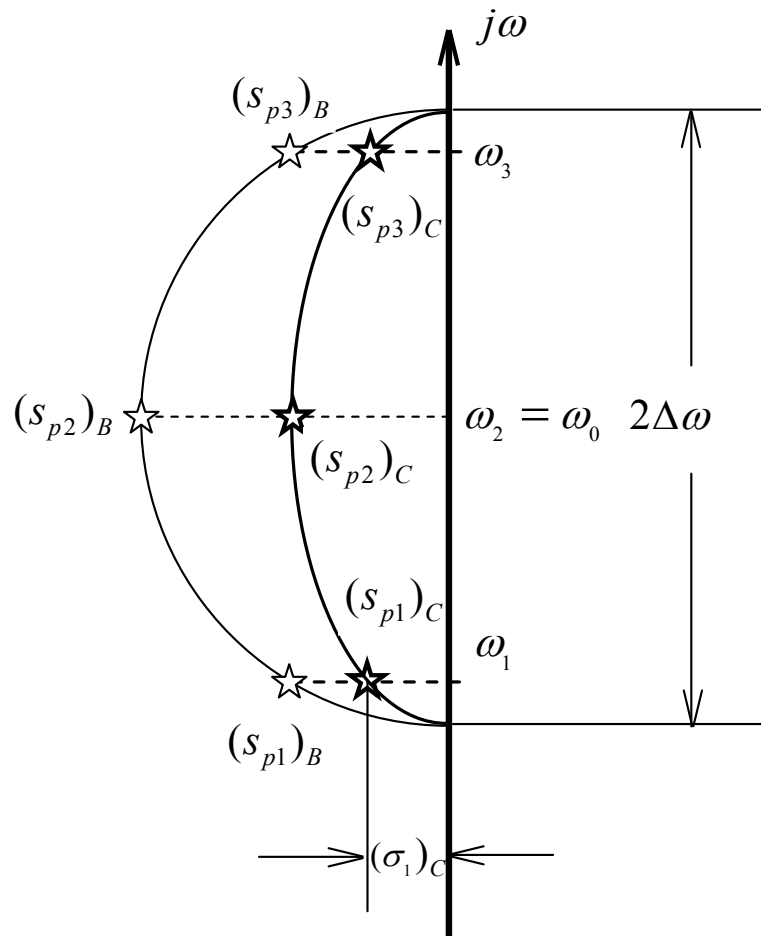Converting Butterworth poles to Chebyshev poles



$$(\sigma_i)_C = \tanh \alpha \times (\sigma_i)_B$$

$$\alpha = \frac{1}{n} \sinh^{-1} \frac{1}{\sqrt{\varepsilon}},$$

$$\varepsilon = \log^{-1} \frac{r(\text{dB})}{10} - 1$$

$(\tanh \alpha)$ for $n = 2, 3, 4$
and various ripple values

<u>r (dB)</u>	<u>$n = 2$</u>	<u>$n = 3$</u>	<u>$n = 4$</u>
0.05	0.898	0.750	0.623
0.1	0.859	0.696	0.567
0.2	0.806	0.631	0.505
0.3	0.767	0.588	0.467
0.4	0.736	0.556	0.439
0.5	0.709	0.524	0.416


Example: Two-stage stagger-tuned amplifier

Voltage gain: ≈ 40 dB

Center frequency: $f_0 = 900$ MHz

Band width: $B = 120$ MHz

Response: Butterworth type

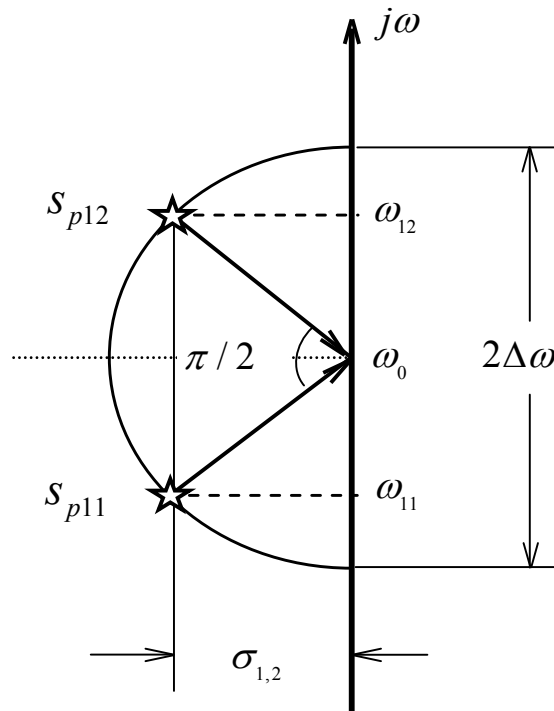

$$f_0 = 900 \text{ MHz}$$


$$\Delta f = 60 \text{ MHz}$$

$$f_1 = 900 - \frac{60}{\sqrt{2}} = 857.6 \text{ MHz}$$

$$f_2 = 900 + \frac{60}{\sqrt{2}} = 942.4 \text{ MHz}$$

$$\sigma_1 = \sigma_2 = \frac{\omega_1}{2Q_1} = \frac{\omega_2}{2Q_2} = \frac{\Delta\omega}{\sqrt{2}}$$

One of the stages

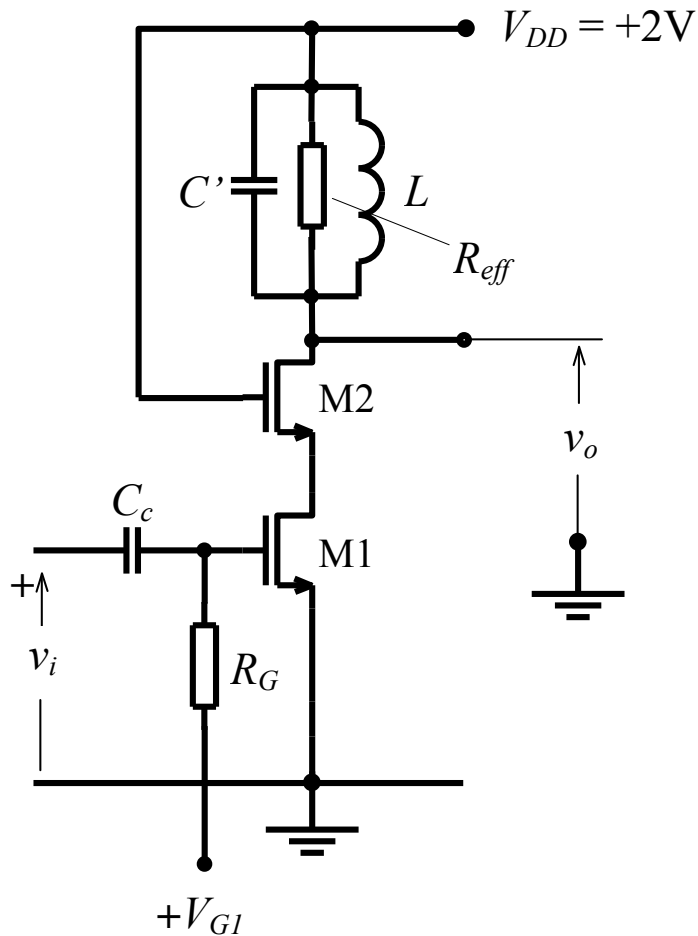

$$L = 10 \text{ nH}, Q_L = 10$$

$$Q_C = 40$$

$$R_L = 100 \text{ k ohm}$$

Technology: UMC018

$$P_{tot} \leq 10 \text{ mW}$$

$$Q_{1(eff)} = \frac{\sqrt{2} \cdot \omega_1}{2\Delta\omega} = \frac{1}{\sqrt{2}} \frac{f_1}{\Delta f}$$

$$Q_{1(eff)} = \frac{1}{\sqrt{2}} \frac{857.6}{60} = 10.1$$

$$Q_{2(eff)} = \frac{1}{\sqrt{2}} \frac{942.4}{60} = 11.1$$

Q enhancement is necessary for both!

$$\frac{1}{Q_{1(eff)}} = \frac{1}{Q_L} + \frac{1}{Q_C} + \frac{1}{Q_{N1}} \rightarrow \frac{1}{Q_{N1}} = \frac{1}{10.1} - \frac{1}{10} - \frac{1}{40} \rightarrow Q_{N1} = -38.5$$

$$R_{N1} = Q_{N1} \cdot \omega_0 L = -2154.5 \text{ ohm}$$

Similarly; $R_{N2} = -1617.3 \text{ ohm}$

Voltage gain per stage: $|A_v|=10$

$$A_{v1} = -g_{m1} \cdot R_{L1(\text{eff})}$$

$$R_{L1(\text{eff})} = Q_{1(\text{eff})} \cdot L\omega_0 = 10.1 \times (10 \times 10^{-9}) \times (2\pi \times 900 \times 10^9) = 571 \text{ ohm}$$

$$g_{m1} = \frac{10}{571} = 17.5 \text{ mS}$$

Similarly;

$$R_{L2(\text{eff})} = 627.7 \text{ ohm} \rightarrow g_{m2} = 16 \text{ mS}$$

1st Stage:

$$g_{m1} = 17.5 \text{ mS}$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} (W / L) I_D} \rightarrow W \cdot I_D = \frac{g_{m1}^2 L}{2\mu_n C_{ox}}$$

$$C_{ox} = 8.2 \times 10^{-7} \text{ F/cm}^2$$

$$\mu_{n0} = 326 \text{ cm}^2/\text{V.s} \rightarrow \mu_n = 196 \text{ cm}^2/\text{V.s} \text{ for } V_{GS} = 1 \text{ V}$$

↓

$$W \cdot I_D = 1.71 \times 10^{-5} : \quad I_D = 1 \text{ mA}; \quad W = 171 \text{ } \mu\text{m} \text{ (excessive parasitics)}$$


$$I_D = 2 \text{ mA}; \quad W = 85.7 \text{ } \mu\text{m} \text{ (preferred)}$$

V_{GS} for $I_D = 2 \text{ mA}$:


$$(V_{GS} - V_T)^2 = \frac{2 \times (2 \times 10^{-3})}{196 \times (8.2 \times 10^{-7}) \times (85.7 / 0.18)} = 0.052 \rightarrow V_{GS} = 0.55 \text{ V}$$

With DC sweep:

$$V_{GS} = 0.62 \text{ V}$$

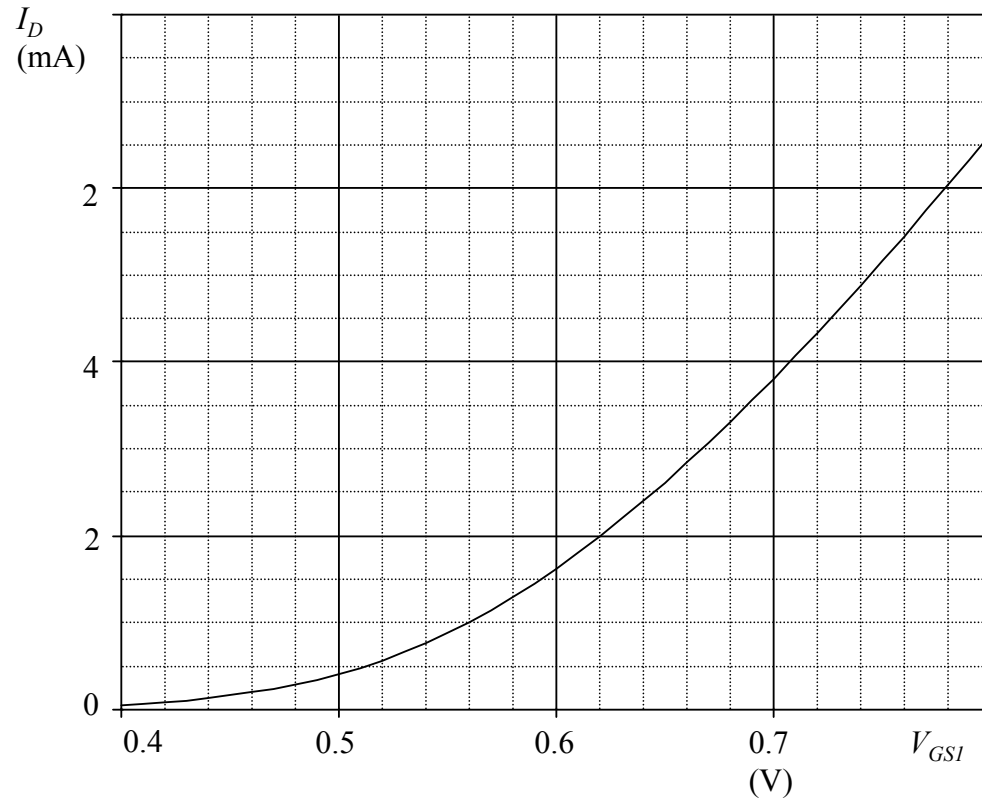

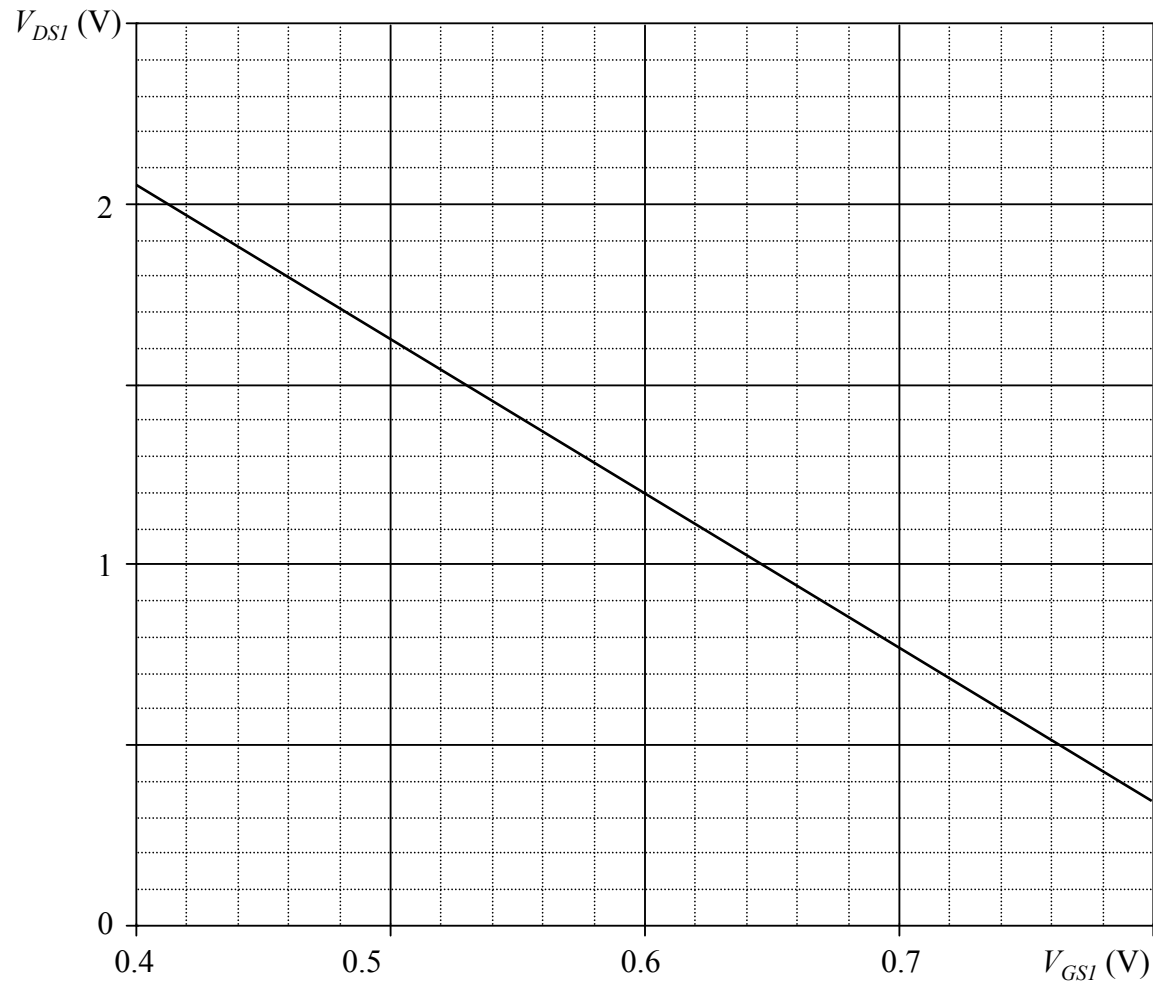Check the DC operating point (the saturation control) for M1 with $W_2 = W_1$



Capacitors:

- Resonance capacitance of the first stage:

(Parasitics and the load cap. included)

$$C_{1T} = \frac{1}{\omega_1^2 L} = \frac{1}{(2\pi \times 857.6 \times 10^6)^2 \times (10 \times 10^{-9})} = 3.44 \text{ pF}$$

- Resonance capacitance of the second stage:

(Parasitics and the load cap. included)

$$C_{2T} = \frac{1}{\omega_2^2 L} = \frac{1}{(2\pi \times 942.4 \times 10^6)^2 \times (10 \times 10^{-9})} = 2.85 \text{ pF}$$


- Coupling capacitor for $\leq 1\%$ signal loss:

$$C_c \geq 100 \times C_{in1}$$


$$C_c \geq 100 \times [(W_1 \times L \times C_{ox}) + CGSO \times W_1] = 2.66 \text{ pF}$$

pSpice Simulation results

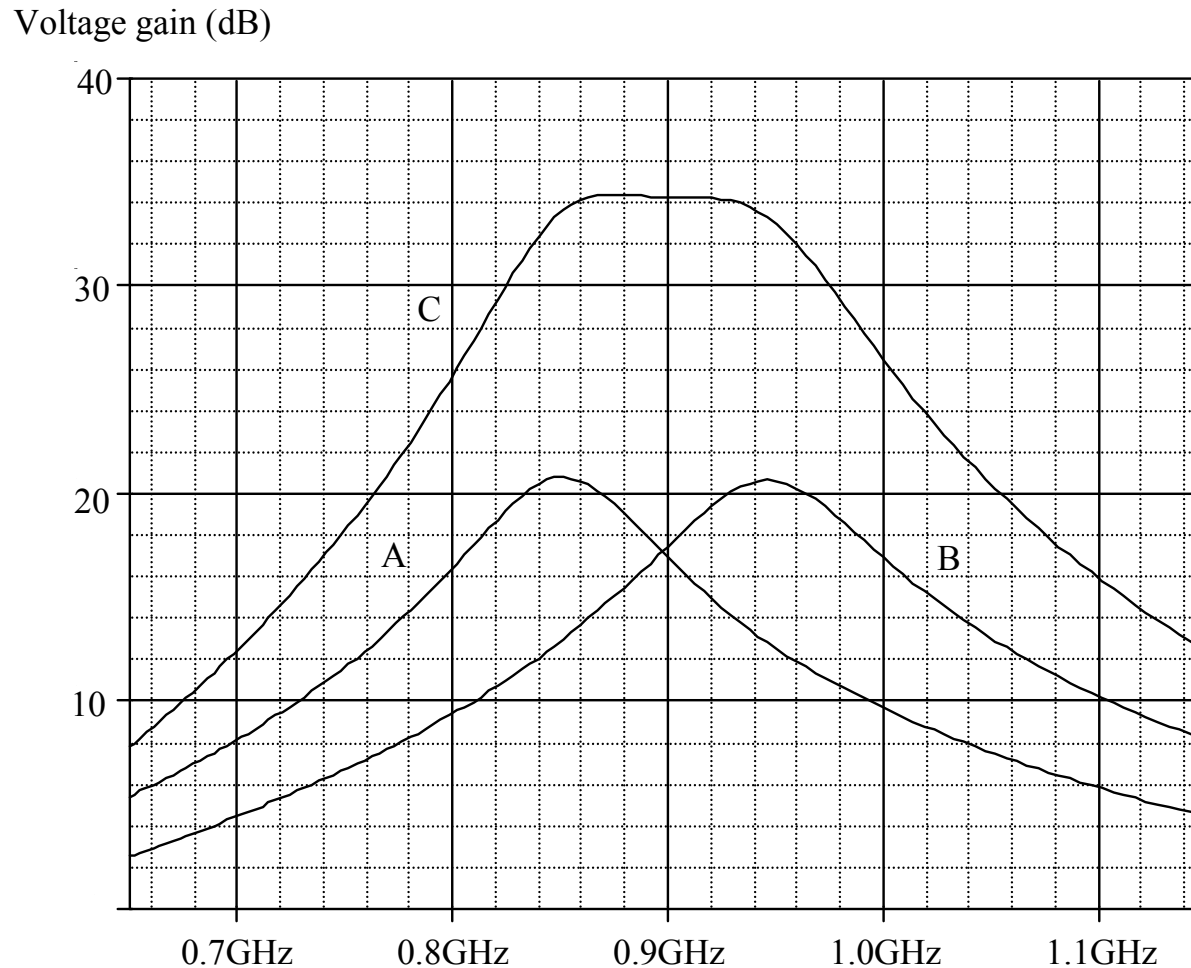Frequency characteristics: (A) First stage, (B) Second stage, (C) Total



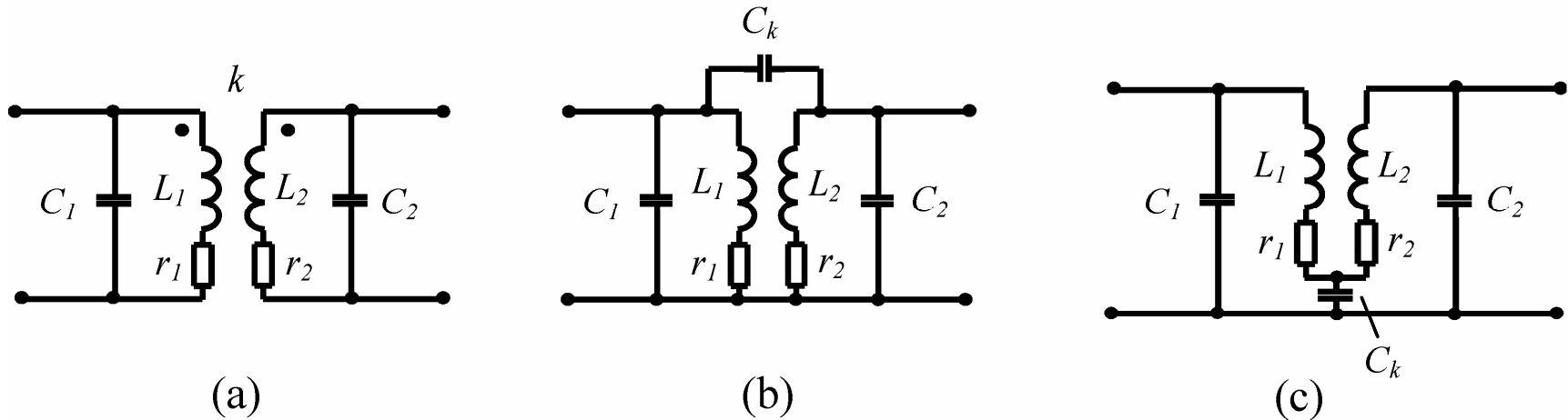The classical solution for 2nd order
Butterworth or Chebyshev characteristics:
Use of coupled, double tuned circuits.



- (a) Magnetic coupling.
- (b) Capacitive voltage coupling.
- (c) Capacitive current coupling.

Transfer impedance of a magnetic coupled double tuned circuit:

$$\frac{V_2}{I_1} = \frac{sM}{(1 + sr_1C_1 + s^2L_1C_1)(1 + sr_2C_2 + s^2L_2C_2) - s^4M^2C_1C_2}$$

$$\omega_0^2 = \frac{1}{L_1C_1} = \frac{1}{L_2C_2} , \quad Q_1 = \frac{1}{\omega_0C_1r_1} , \quad Q_2 = \frac{1}{\omega_0C_2r_2}$$

$$\frac{V_2}{I_1} = \frac{sM\omega_0^4Q_1Q_2}{(s^2Q_1 + s\omega_0 + \omega_0^2Q_1)(s^2Q_2 + s\omega_0 + \omega_0^2Q_2) - s^4k^2Q_1Q_2}$$

Denominator polynome with $s^4 Q_1 Q_2 (1 - k^2) = s^4 Q_1 Q_2 (1 - k)(1 + k)$:

$$\left[(s^2 Q_1 (1 - k) + s\omega_0 + \omega_0^2 Q_1) \right] \left[(s^2 Q_2 (1 + k) + s\omega_0 + \omega_0^2 Q_2) \right]$$

Poles:

$$s_1, s_1' = -\frac{\omega_0}{2Q_1(1-k)} \mp j \frac{\omega_0}{Q_1(1-k)} \sqrt{4Q_1^2(1-k) - 1}$$

$$s_2, s_2' = -\frac{\omega_0}{2Q_2(1+k)} \mp j \frac{\omega_0}{Q_2(1+k)} \sqrt{4Q_2^2(1+k) - 1}$$

For small k values; $4Q_1^2(1-k) \approx 1$, $4Q_2^2(1+k) \approx 1$



$$s_1, s_1' \cong -\frac{\omega_0}{2Q_1(1-k)} \mp j \frac{\omega_0}{\sqrt{1-k}}$$

$$s_2, s_2' \cong -\frac{\omega_0}{2Q_2(1+k)} \mp j \frac{\omega_0}{\sqrt{1+k}}$$

With $(1-k) \cong 1$, $(1+k) \cong 1$ and $1/\sqrt{1-k} \cong 1+(k/2)$, $1/\sqrt{1+k} \cong 1-(k/2)$;

$$s_1, s_1' \cong -\frac{\omega_0}{2Q_1(1-k)} \mp j\omega_0 \left(1 + \frac{k}{2}\right)$$

$$s_2, s_2' \cong -\frac{\omega_0}{2Q_2(1+k)} \mp j\omega_0 \left(1 - \frac{k}{2}\right)$$

For a Butterworth or Chebyshev response
the real parts of the poles must be equal:


$$\sigma = -\frac{\omega_0}{2Q_1(1-k)} = -\frac{\omega_0}{2Q_2(1+k)}$$

$$k \ll 1$$



$$\sigma \cong -\frac{\omega_0}{2Q_1} \cong -\frac{\omega_0}{2Q_2} \cong -\frac{\omega_0}{2Q}$$

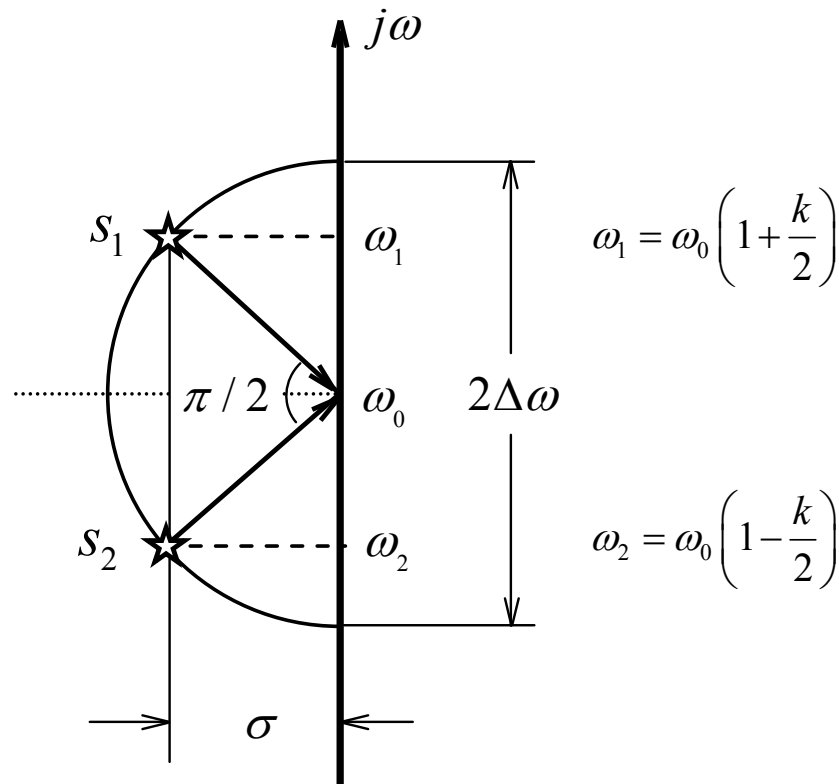
Positions of the poles for a Butterworth characteristic:



$$|\sigma| = \frac{\omega_0}{2Q} = \omega_0 \frac{k}{2} \Rightarrow k = \frac{1}{Q}$$

$$2\Delta\omega = 2 \times \left(\sqrt{2} |\sigma| \right) = \sqrt{2} \frac{\omega_0}{Q} \Rightarrow B = 2\Delta f = \sqrt{2} \frac{f_0}{Q}$$

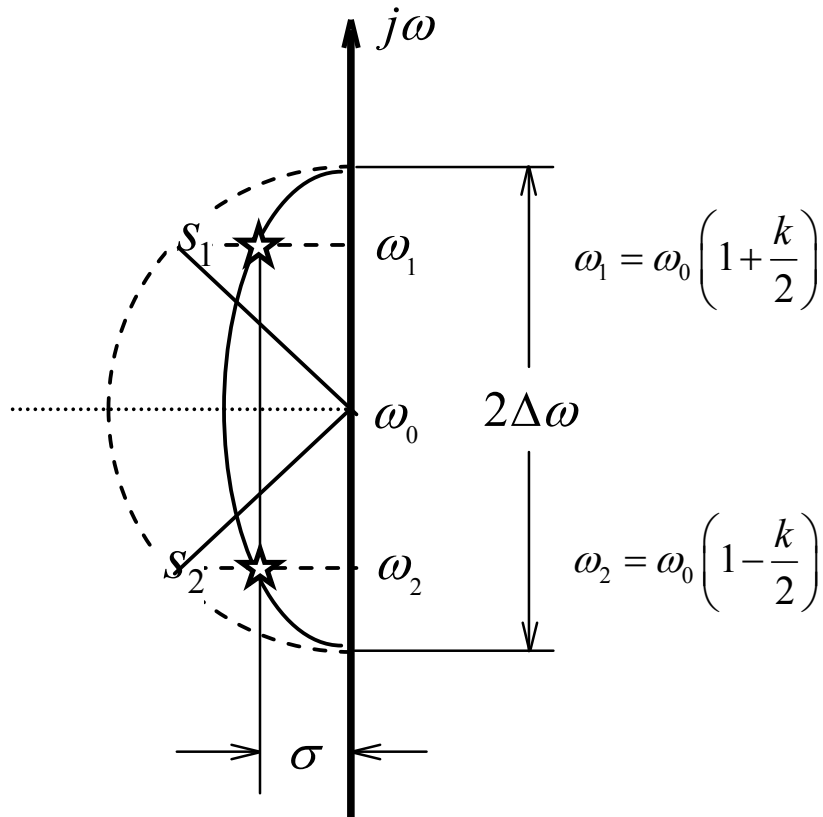Positions of the poles for a Chebyshev characteristic:



(b)

$$(\sigma)_C = \frac{\omega_0}{2Q} = \tanh \alpha \times \omega_0 \frac{k}{2}$$



$$k = \frac{1}{\tanh \alpha} \frac{1}{Q}$$

$$\begin{aligned} 2\Delta\omega &= 2 \times \sqrt{2} \times \omega_0 \frac{k}{2} \\ &= \sqrt{2} \times \omega_0 \frac{1}{\tanh \alpha} \frac{1}{Q} \end{aligned}$$




$$2\Delta f = B = \sqrt{2} \times f \frac{1}{\tanh \alpha} \frac{1}{Q}$$

Example: $r = 0.5 \text{ dB} \rightarrow \tanh \alpha = 0.709 \cong \frac{1}{\sqrt{2}}$


$$k = \frac{1}{Q \times \tanh \alpha} \cong \frac{\sqrt{2}}{Q} \rightarrow kQ = \sqrt{2}$$

$$B = \sqrt{2} \times f_0 \frac{1}{\tanh \alpha} \frac{1}{Q} \cong 2 \frac{f_0}{Q}$$

Problem 4-6 (Simulation result)

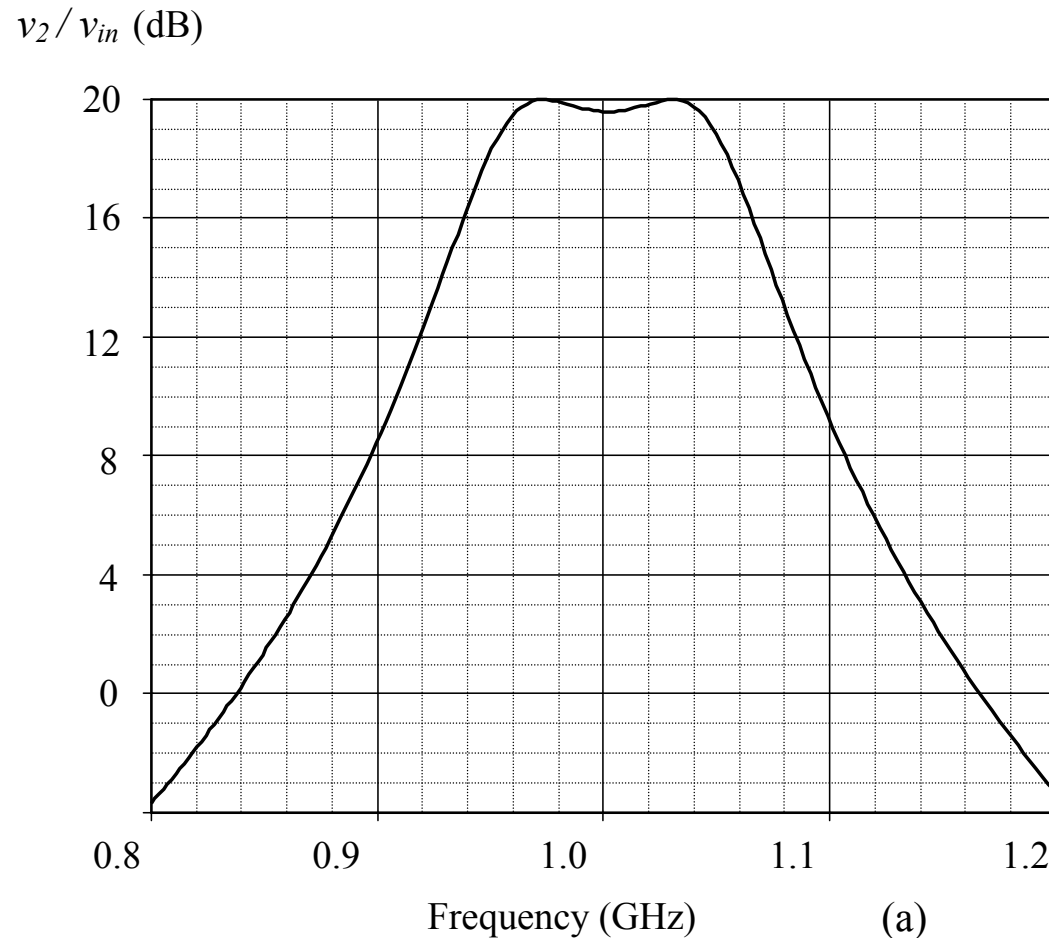

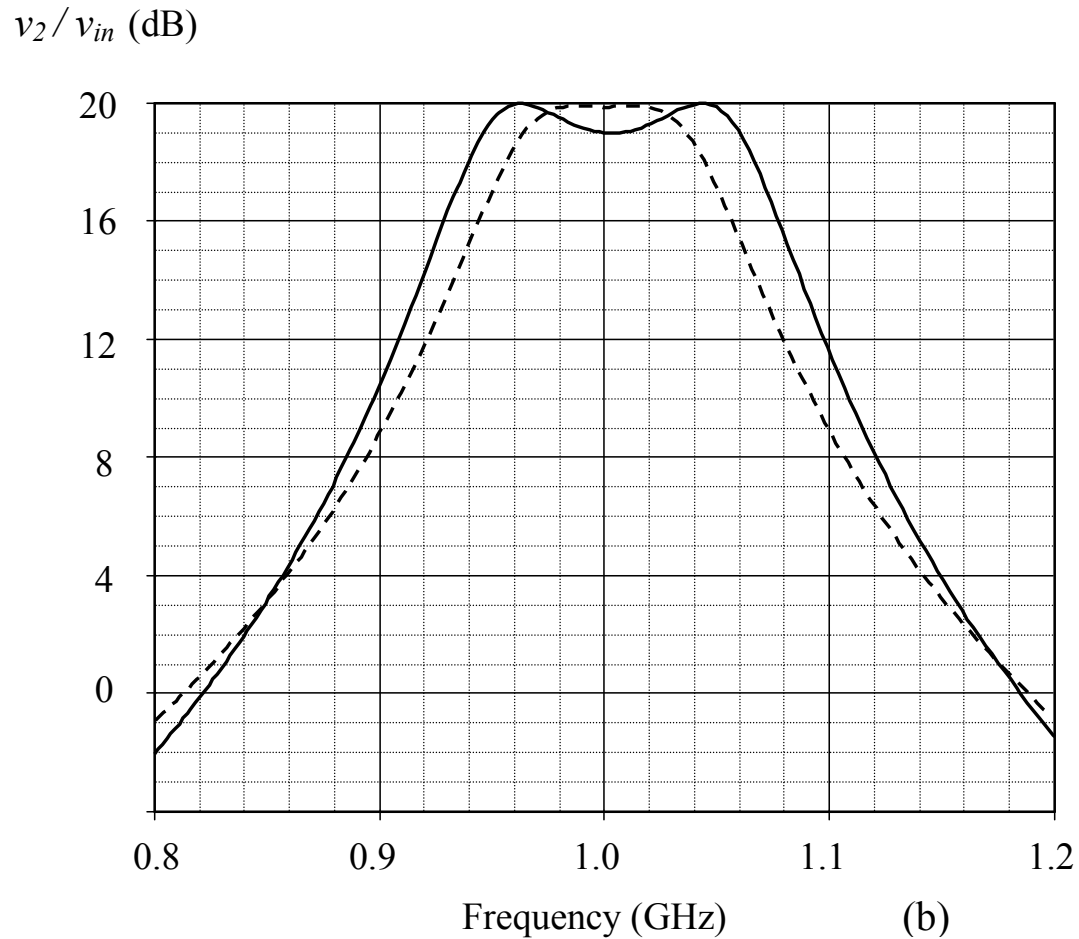Problem 4-6. (Simulation results for $\pm 20\%$ tolerance of k)



Transformation formula to apply the expressions derived for magnetic coupling to capacitive coupled circuits:

a) For capacitive voltage coupling:

$$C_k = -\frac{k}{\omega_0^2 \sqrt{L_1 L_2}}$$

b) For capacitive current coupling:

$$C_k = -\frac{1}{k \omega_0^2 \sqrt{L_1 L_2}}$$