

Fundamentals of High-Frequency CMOS Analog Integrated Circuits

Duran Leblebici
Yusuf Leblebici

Chapter 4

Frequency-Selective RF Circuits (Noise)

- All signal components at the output of an amplifier, not related to the input signal are called as "noise".
- Noise types that can be eliminated or reduced by necessary precautions are mostly originated from external sources.
- The noise generated in the components of the amplifier, originating from the random movements of the carriers due to the thermal agitation is called as the "thermal noise".
- The major part of the noise originating from thermal agitation of charge carriers exhibits a flat power density spectrum and is called as the "white noise".
- The another type of noise, mostly related to the material imperfections and is higher at low frequencies, is called as the "pink noise" or " $1/f$ noise".

The metrics to characterize the noise of an amplifier: The "Noise Factor" and the "Noise Figure"

The noise factor:
$$F = \frac{(S / N)_{input}}{(S / N)_{output}}$$

$$F = \frac{S_{in}}{S_{out}} \frac{N_{out}}{N_{in}} = \frac{S_{in}}{A_p \times S_{in}} \frac{(A_p \times N_{in}) + N_{amp}}{N_{in}}$$

Where;

□ A_p is the power gain of the amplifier,

□ N_{amp} is the noise power at the output,

originating from amplifier itself.



The "Noise Factor": $F = 1 + \frac{N_{amp}}{A_p \times N_{in}}$

The "Noise Figure": $NF(dB) = 10 \times \log F$

The thermal noise generated in a conductor:

- Observed and measured by J. B. Johnson in 1928.
- Theoretically derived expression by H. Nyquist (1928):

$$P_n = 4kTB$$

P_n : The noise power

k : The Boltzmann constant (1.36×10^{-23} joules / K)

T : The temperature in K

B : The bandwidth for which P_n is calculated or measured.

$$P_n = 4kTB$$

Indicates that the noise power generated in a conductor due to the random movements of the charge carriers:

- Depends only on the temperature of the conductor and the interested bandwidth, **regardless of the position of this bandwidth on the frequency axis.**
- **Is independent of the material and the shape of the conductor.**


- The noise power in terms of the mean-square voltage

of the random noise: $P_n = \overline{v_n^2} \times \frac{1}{R}$



- Root-mean square noise voltage: $\overline{v_n} = \sqrt{4kTB \times R}$

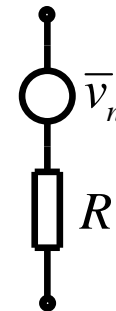- The noise voltage equivalent of a resistor:




$$\overline{v_n} = \sqrt{4kTB \times R}$$

- The noise power in terms of the mean-square current of the random noise: $P_n = \overline{i_n^2} \times R$



- Root-mean square noise current: $\overline{i_n} = \sqrt{4kTB \frac{1}{R}}$

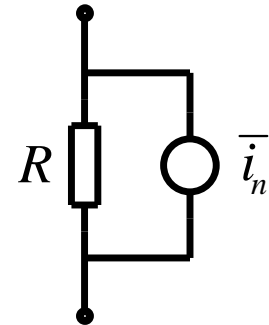- The noise current equivalent of a resistor:



$$\overline{i_n} = \sqrt{4kTB / R}$$

The spectral density; noise for 1 Hz band-width:

- Spectral density of the noise power:

$$S_p = P_n \Big|_{B=1\text{Hz}} = 4kT$$

- Spectral density of the mean square noise voltage:

$$S_v = \overline{v_n^2} \Big|_{B=1\text{Hz}} = 4kT \times R$$

- Spectral density of the mean square noise current:


$$S_i = \overline{i_n^2} \Big|_{B=1\text{Hz}} = \frac{4kT}{R}$$

Noise of a MOS Transistor


(First investigated by A. Van der Ziel, 1986)

Noise generating resistors in a MOS transistor:

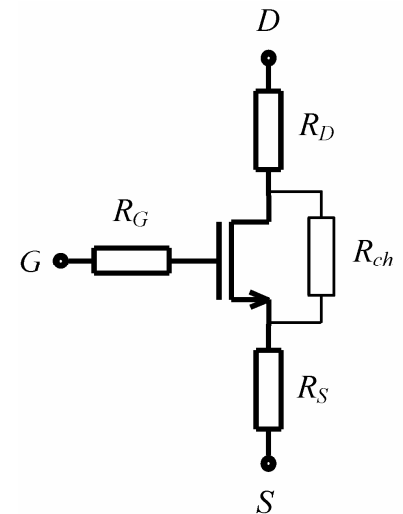- Parasitic series resistances (R_S , R_D , R_G)
- The resistance of the channel:
 - (a) The resistance of the non velocity saturated (pre-pinch off) part of the channel (the **dominating** noise source).
 - (b) The resistance of the pinched-off part of the channel.



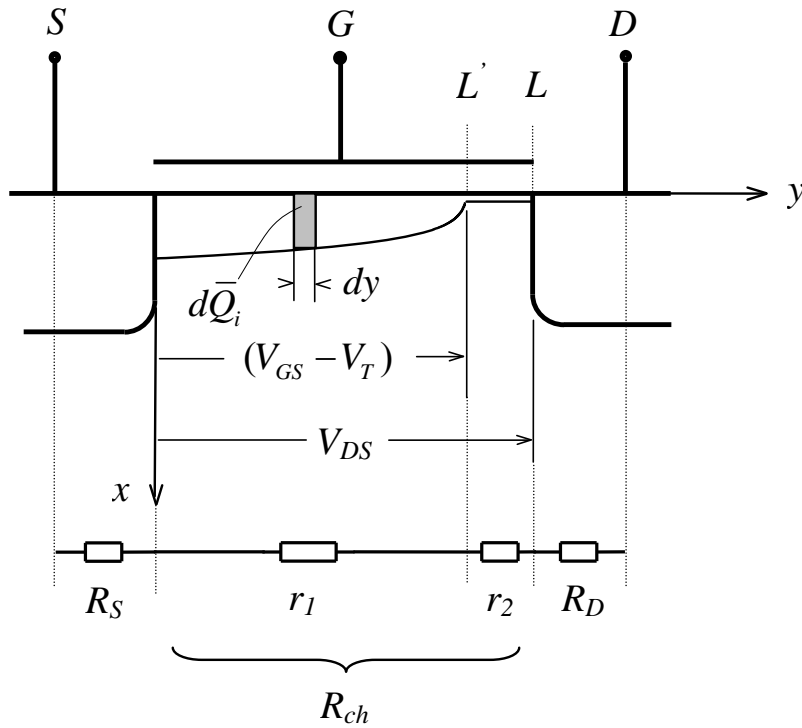The value of the inversion channel resistance:



$$dr(y) = \frac{dV_c}{I_D}$$

$$I_D = \frac{d\bar{Q}_i(y)}{dt}$$

$$d\bar{Q}_i(y) = -C_{ox}W(V_{GS} - V_T)\sqrt{1 - \frac{y}{L'}} \cdot dy$$

$$dt = \frac{dy}{v} = \frac{dy}{\mu E(y)} = \frac{dy}{-\mu(dV_c / dy)}$$

$$dr(y) = \frac{dy}{\mu C_{ox} W (V_{GS} - V_T) \sqrt{1 - \frac{y}{L'}}$$

$$R_{ch} = \int_0^{L'} dr(y) = \frac{2}{\mu C_{ox} \frac{W}{L'} (V_{GS} - V_T)}$$

$$R_{ch} = \frac{(V_{GS} - V_T)}{I_D} \quad (\text{as expected!})$$

From basic $I_D = f(V_{DS})$ relation:

$$R_{ch} = \sqrt{\frac{2}{I_D \mu C_{ox} \frac{W}{L}}} \Rightarrow R_{ch} = \frac{2}{g_m}$$

The mean-square noise current of the inversion channel resistance:

$$\overline{i_{nd}^2} = \frac{4kTB}{R_{ch}} = 2kTB \times g_m = 4kTB \sqrt{\frac{1}{2} \mu C_{ox} \frac{W}{L} I_D}$$


- Increases with g_m .
- Increases with the drain DC current.
- Increases with (W / L) .
- Is higher for small geometries, due to the higher C_{ox} values.
- Is smaller for PMOS transistors, related to mobility.

The spectral density of the mean square channel noise:

$$S_{ich} = \overline{i_{nd}^2} \Big|_{B=1\text{Hz}} = \frac{4kT}{R_{ch}} = 2kTg_m \quad [\text{A}^2 / \text{Hz}]$$


Simulation result for a 35 μ / 0.35 μ AMS NMOS transistor

S_{ich} (A²/Hz)

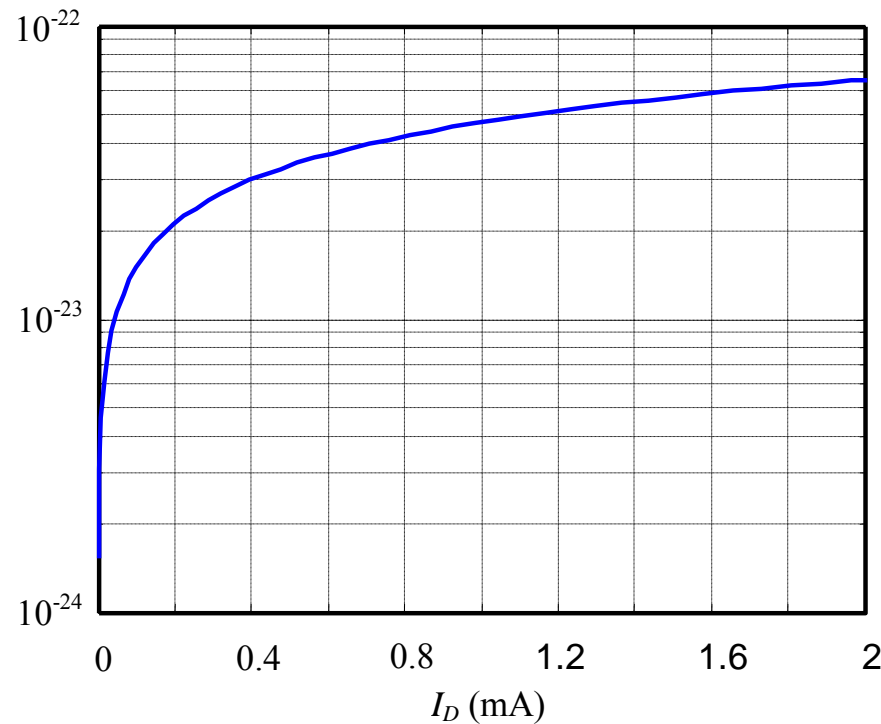


The contribution of the source series resistance on noise

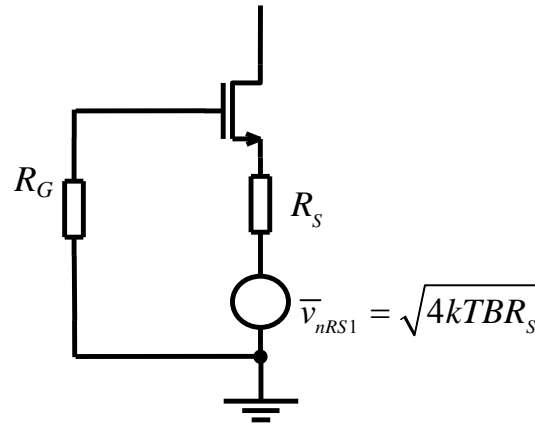
(a) The contribution of the noise generated in R_S itself:



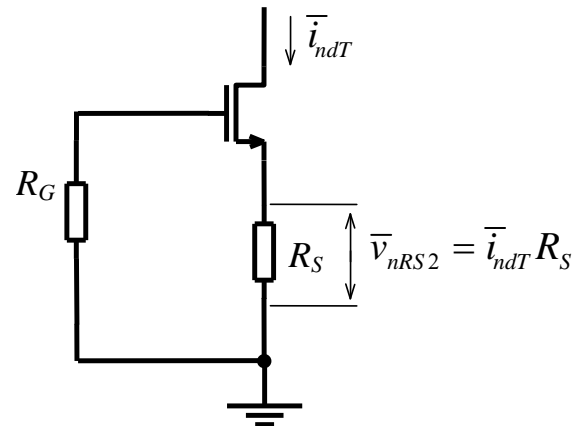(b) The contribution of the noise voltage drop on R_S due to the channel noise current:



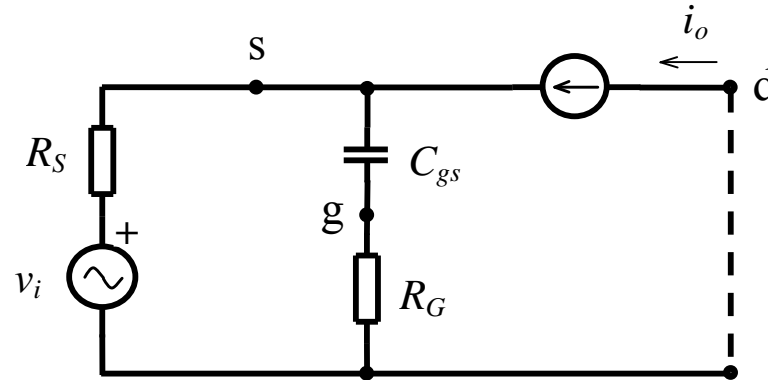To investigate the contribution (a), it is necessary to calculate the transconductance from \bar{v}_{nRS1} to \bar{i}_{ndT} :



$$g_{mSD(eff)} = - \frac{g_m}{R_S(g_m + j\omega C_{gs}) + (1 + j\omega C_{gs}R_G)}$$

$$|g_{mSD(eff)}| = \frac{g_m}{\sqrt{(1 + g_m R_S)^2 + \omega^2 C_{gs}^2 (R_S + R_G)^2}}$$

$$\bar{i}_{ndS1} = |g_{mSD(eff)}| \bar{v}_{nRS1}$$

Similarly, to investigate the contribution (b),
the transconductance from \bar{v}_{nRS2} to \bar{i}_{ndT} ,
that corresponds to $R_S = 0$, must be calculated :


$$g'_{mSD(eff)} = -\frac{g_m}{(1 + j\omega C_{gs} R_G)}$$

$$\left| g'_{mSD(eff)} \right| = \frac{g_m}{\sqrt{1 + (\omega C_{gs} R_G)^2}}$$

$$\bar{i}_{ndS2} = \left| g'_{mSD(eff)} \right| \bar{i}_{ndT} R_S$$

The contribution of the gate series resistance on noise

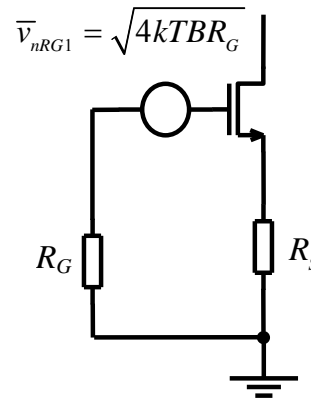
(a) The contribution of the noise generated in R_G :



$$\overline{v}_{nRG1} = \sqrt{4kTBR_G}$$

$$\overline{i}_{ndG1} = |g_{m(eff)}| \overline{v}_{nRG}$$

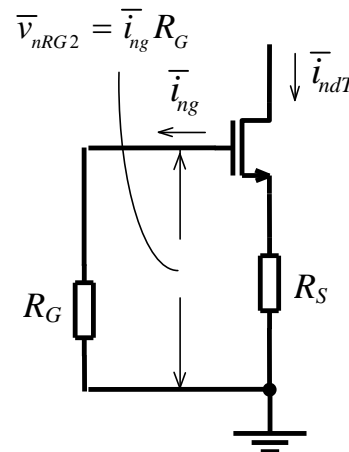
(b) The contribution of the noise current flowing over C_{dg} at high frequencies:



$$\overline{v}_{nRG2} = \overline{i}_{ng} R_G$$

$$\overline{i}_{ndG2} = |g_{m(eff)}| \overline{v}_{nRG2}$$

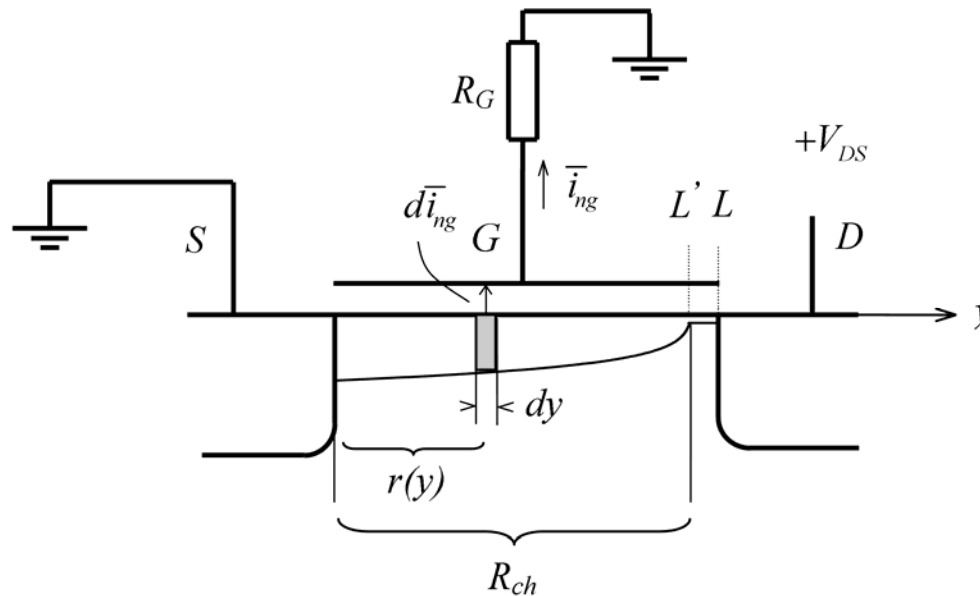Calculation of the non-white gate noise current, \bar{i}_{ng} :



$$dC_g = C_{ox} W dy$$

$$r(y) = \frac{2}{\mu C_{ox} \frac{W}{L'} (V_{GS} - V_T)} \left(1 - \sqrt{1 - \frac{y}{L'}} \right)$$

$$\bar{v}_n(y) = \bar{i}_{nd} \cdot r(y)$$

$$d\bar{i}_{ng} = j\omega(dC_g) \times \bar{v}_n(y) = j\omega(C_{ox}Wdy) \times r(y)\bar{i}_{nd}$$

$$\bar{i}_{ng} = j\omega C_{ox}W \frac{2}{\mu C_{ox} \frac{W}{L'} (V_{GS} - V_T)} \int_0^{L'} \left(1 - \sqrt{1 - \frac{y}{L'}} \right) dy \times \bar{i}_{nd}$$

For $L \cong L'$; $\left| \bar{i}_{ng} \right| \cong \frac{\omega C_{gs}}{g_m} \bar{i}_{nd} = \omega \frac{1}{A} \sqrt{\frac{W}{I_D}} \times \bar{i}_{nd}$

where $A = \sqrt{\frac{2\mu}{C_{ox}L^3k_{ol}^2}}$

Total noise of a MOS transistor

(a) Uncorrelated (independent) components of the channel noise:

$$\overline{i_{ndU}^2} = \overline{i_{nd}^2} + \overline{i_{ndS1}^2} + \overline{i_{ndG1}^2}$$

$$\overline{i_{nd}^2} = \frac{4kTB}{R_{ch}} = 2kTBg_m$$

$$\overline{i_{ndS1}^2} = \left| g_{mSD(eff)} \right|^2 \overline{v_{nR_S}^2} = \left| g_{mSD(eff)} \right|^2 4kTB R_S$$

$$\overline{i_{ndG1}^2} = \left(\left| g_{m(eff)} \right| \overline{v_{nR_G}} \right)^2 = \left| g_{m(eff)} \right|^2 4kTB R_G$$

(b) Noise components related to the total channel noise:

$$\overline{i}_{ndS2}^2 = \left| g'_{mSD(eff)} \right|^2 R_S^2 \cdot \overline{i}_{ndT}^2 = \alpha_1 \cdot \overline{i}_{ndT}^2 ,$$

$$\text{Where } \alpha_1 = \left| g'_{mSD(eff)} \right|^2 R_S^2$$

$$\begin{aligned} \overline{i}_{ndG2}^2 &= \left(\left| g_{m(eff)} \right| \overline{v}_{nRG2} \right)^2 = \left| g_{m(eff)} \right|^2 R_G^2 \cdot \overline{i}_{ng}^2 \\ &= \left| g_{m(eff)} \right|^2 \left(\omega \frac{1}{A} \sqrt{\frac{W}{I_D}} \right)^2 R_G^2 \cdot \overline{i}_{ndT}^2 = \alpha_2 \cdot \overline{i}_{ndT}^2 \end{aligned}$$

$$\text{Where } \alpha_2 = \left| g_{m(eff)} \right|^2 \left(\omega \frac{1}{A} \sqrt{\frac{W}{I_D}} \right)^2 R_G^2$$

The total channel noise:


$$\begin{aligned}\overline{i_{ndT}^2} &= \overline{i_{ndTU}^2} + \overline{i_{ndS2}^2} + \overline{i_{ndG2}^2} \\ &= \overline{i_{ndTU}^2} + \alpha_1 \cdot \overline{i_{ndT}^2} + \alpha_2 \cdot \overline{i_{ndT}^2}\end{aligned}$$

⇓

$$\overline{i_{ndT}^2} = \frac{\overline{i_{ndU}^2}}{[1 - (\alpha_1 + \alpha_2)]} = \frac{\overline{i_{nd}^2} + \overline{i_{ndS1}^2} + \overline{i_{ndG1}^2}}{[1 - (\alpha_1 + \alpha_2)]}$$

$$\overline{i_{ndT}^2} = 4kTB \frac{(g_m / 2) + |g_{mSD(eff)}|^2 R_S + |g_{m(eff)}|^2 R_G}{[1 - (\alpha_1 + \alpha_2)]}$$

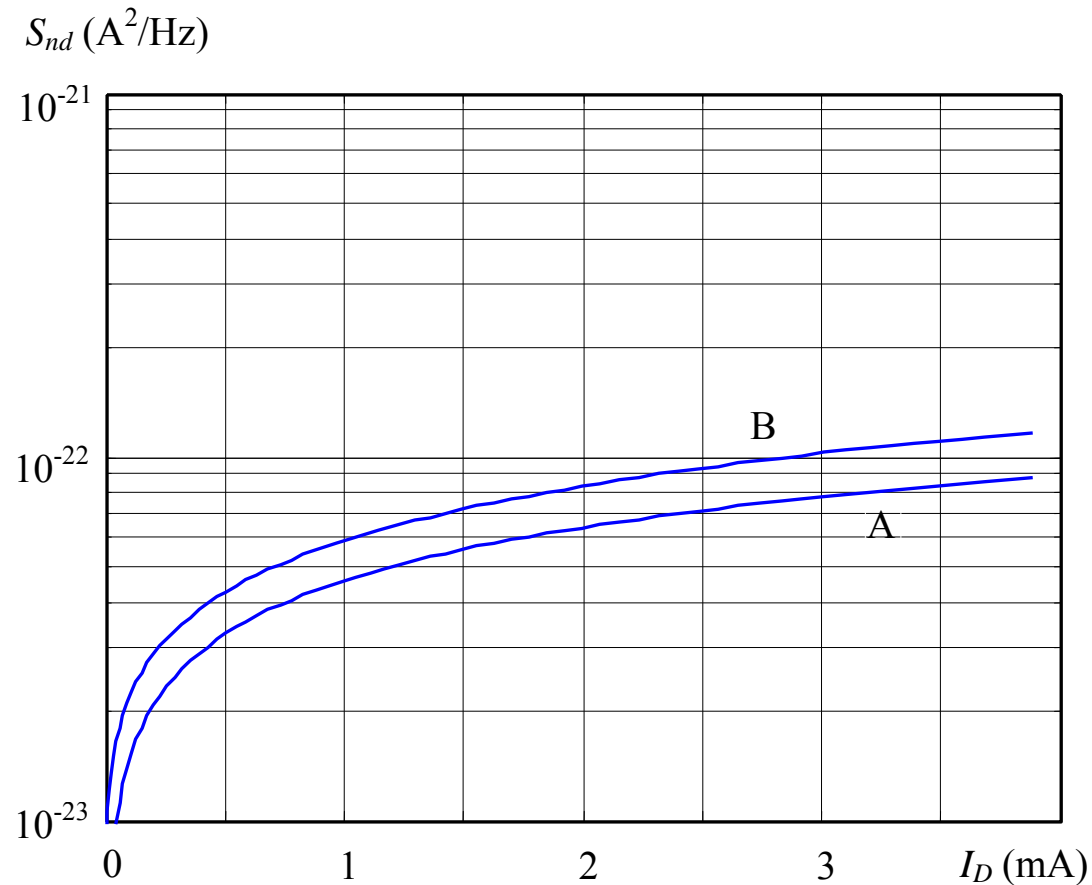Simulation to show the contributions of R_S and R_G




Transistor: $35\mu\text{m}$ ($7 \times 5\mu\text{m}$) / $0.35\mu\text{m}$ AMS NMOS.

$I_D = 2 \text{ mA}$, $V_{DS} = 3 \text{ V}$, $T = 300 \text{ K}$, $f = 3 \text{ GHz}$,

(A) The inversion resistance only,

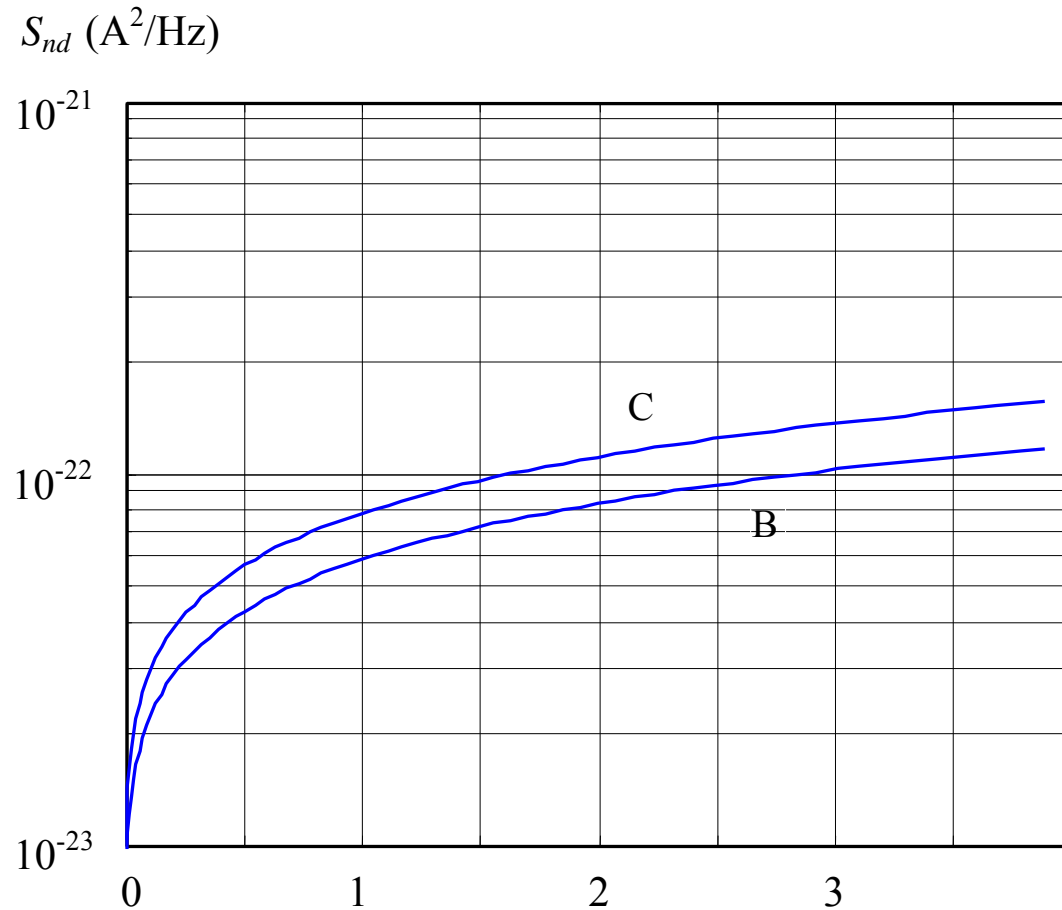(B) Contributions of R_S and R_G included.

Simulation to show the contribution of temperature




The total noise for the same transistor and the same operating conditions:

(B) 300K, (C) 400K


It must be noted that

the temperatures of the channels of various transistors on a chip
can be significantly different!

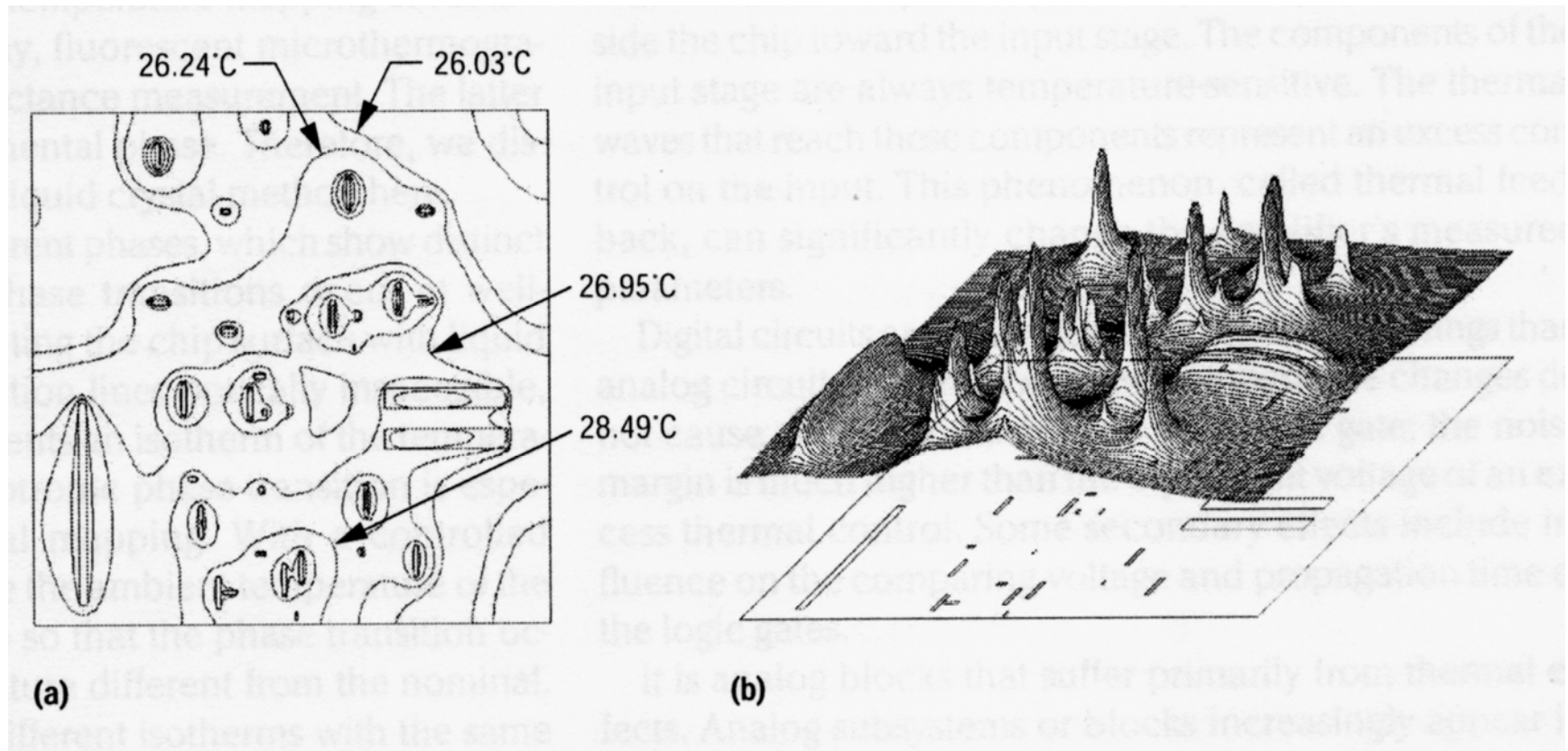Example (after V. Szekely and B. Courtois):



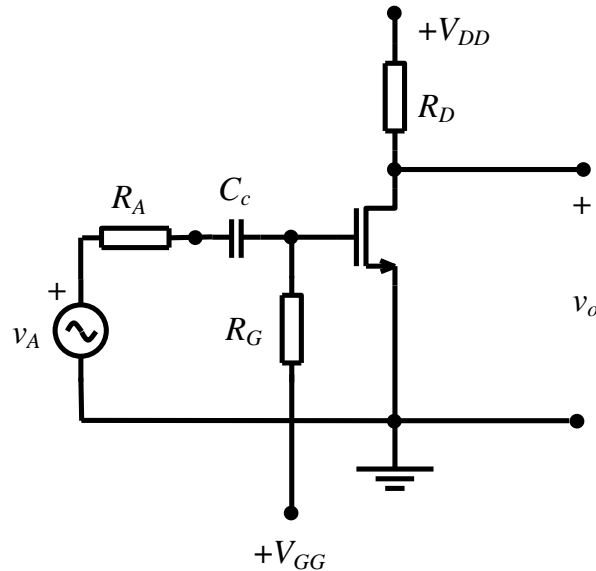Example: The noise figure of a CS amplifier:



$$g_m = 20 \text{ mS}$$

$$R_A = 50 \text{ ohm}$$

$$R_D = 200 \text{ ohm}$$

$$(a) R_G = 50 \text{ ohm}$$

$$(b) R_G = 1000 \text{ ohm}$$

Parasitics neglected

Spectral density of the channel noise:

$$\overline{i_{nd}^2} = 2kTB \times g_m$$

Spectral density of the noise current of R_D :

$$\overline{i_{nRD}^2} = 4kTB / R_D$$

Noise voltage generated on R_G :

$$\overline{v_{nRG}} = \sqrt{4kTB \times R_G}$$

Noise voltage generated on R_A :

$$\overline{v_{nRA}} = \sqrt{4kTB \times R_A}$$

Noise current at the output owing to \bar{v}_{nRA} : $\bar{i}_{noRA} = g_m \bar{v}_{nRA}$

Noise current at the output owing to \bar{v}_{nRG} : $\bar{i}_{noRG} = g_m \bar{v}_{nRG}$

Total output noise power

generated in the amplifier :

$$P_{no} = (\bar{i}_{nd}^2 + \bar{i}_{nRD}^2 + \bar{i}_{noRG}^2) R_D$$

$$P_{no} = 4kTB \left(\frac{1}{2} g_m + \frac{1}{R_D} + R_G g_m^2 \right) R_D$$

Noise power at the output owing to R_A : $P_{noRA} = \bar{i}_{noRA}^2 R_D = 4kTBR_A g_m^2 R_D$

The Noise factor: $F = 1 + \frac{P_{no}}{P_{noRA}} = 1 + \frac{(4kTB) \left(\frac{1}{2} g_m + \frac{1}{R_D} + R_G g_m^2 \right) R_D}{(4kTB) R_A g_m^2 R_D}$

$$F = 1 + \frac{\frac{1}{2} g_m + \frac{1}{R_D}}{R_A g_m^2} + \frac{R_G}{R_A}$$

(a) For $R_G = 50$ ohm:


$$F = 1 + \frac{\frac{1}{2}(20 \cdot 10^{-3}) + \frac{1}{200}}{50(20 \cdot 10^{-3})^2} + \frac{50}{50} = 2.75 \Rightarrow NF = 4.39 \text{ dB (high!)}$$

(b) For $R_G = 1000$ ohm:

$$F = 1 + \frac{\frac{1}{2}(20 \cdot 10^{-3}) + \frac{1}{200}}{50(20 \cdot 10^{-3})^2} + \frac{1000}{50} = 21.75 \Rightarrow NF = 13.37 \text{ dB (very high!)}$$

Note that the dominant component of the noise factor is related to R_G , a resistor parallel to the input of the amplifier!

A possible solution to eliminate R_G :

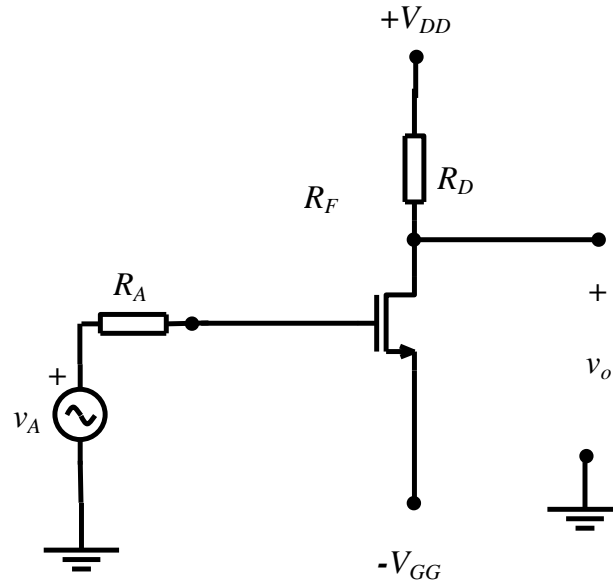

The noise figure without R_G :

$$F = 1 + \frac{\frac{1}{2}(20 \cdot 10^{-3}) + \frac{1}{200}}{50(20 \cdot 10^{-3})^2} = 1.75 \Rightarrow NF = 2.43 \text{ dB}$$