

Fundamentals of High-Frequency CMOS Analog Integrated Circuits


Duran Leblebici
Yusuf Leblebici

Chapter 4

Frequency-Selective RF Circuits (Resonance Circuits)

Resonance Circuits

a) Parallel resonance circuit:

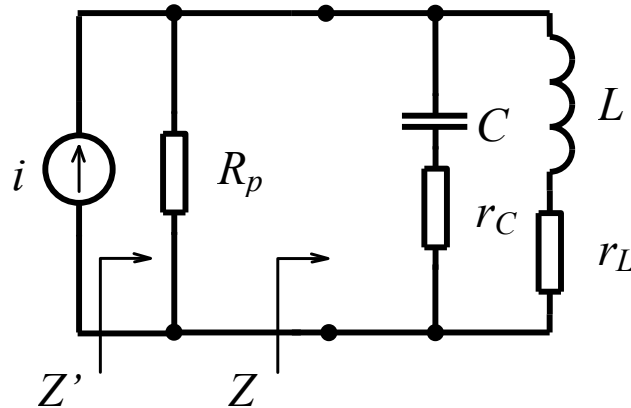


$$Z(\omega) = \frac{(r_L - \omega^2 L C r_C) + j\omega(L + C r_C r_L)}{(1 - \omega^2 L C) + j\omega C(r_C + r_L)}$$

$$\text{Re}\{Z\} = \frac{(r_L - \omega^2 L C r_C)(1 - \omega^2 L C) + \omega^2 C(r_L + r_C)(L + C r_L r_C)}{(1 - \omega^2 L C)^2 + \omega^2 C^2(r_L + r_C)^2}$$

$$\text{Im}\{Z\} = \frac{\omega(L + C r_L r_C)(1 - \omega^2 L C) - \omega C(r_L - \omega^2 L C r_C)(r_L + r_C)}{(1 - \omega^2 L C) + \omega^2 C^2(r_L + r_C)^2}$$

Locus of the impedance phasor:

(For $r_C \ll r_L$)

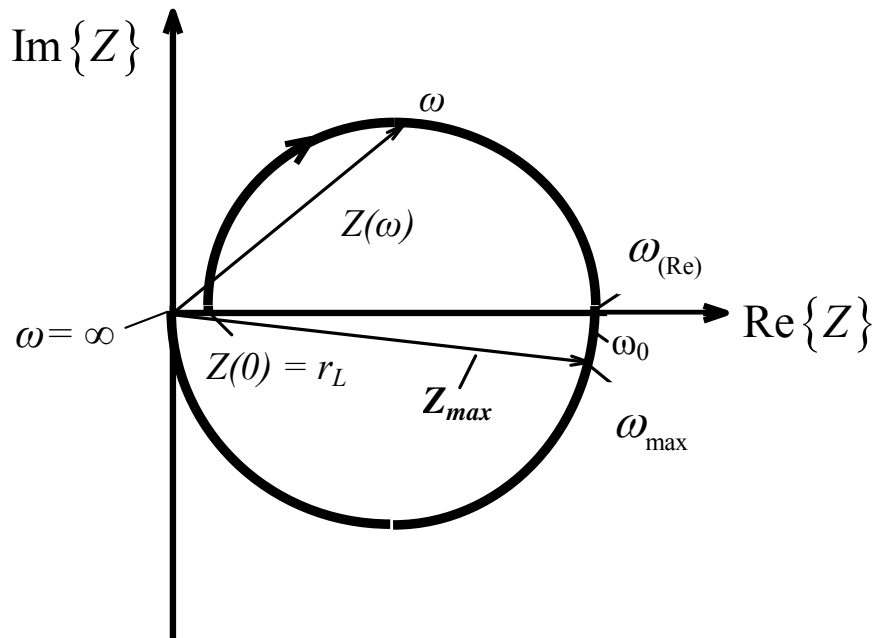


$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_{(\text{Re})}^2 = \frac{1}{LC} - \frac{r_L^2}{L^2}$$

$$\omega_{\text{max}}^2 = \frac{1}{LC} \sqrt{1 + 2r_L^2 \frac{C}{L}} - \frac{r_L^2}{L^2}$$


Locus of the impedance phasor:

(For $r_C = r_L$)

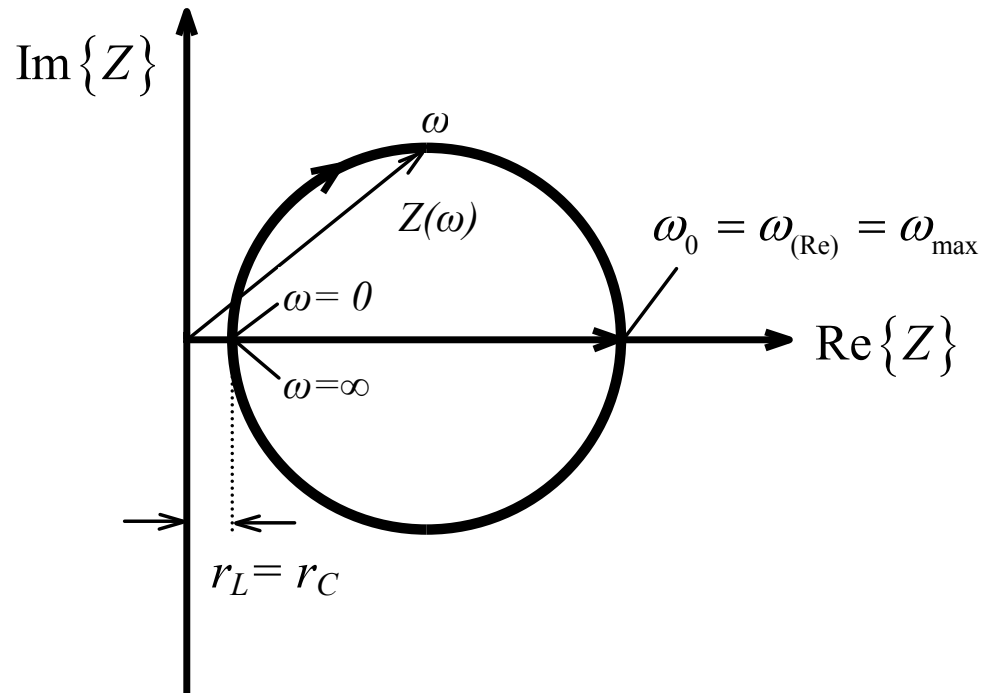


Variations of the magnitude and the phase of the impedance:

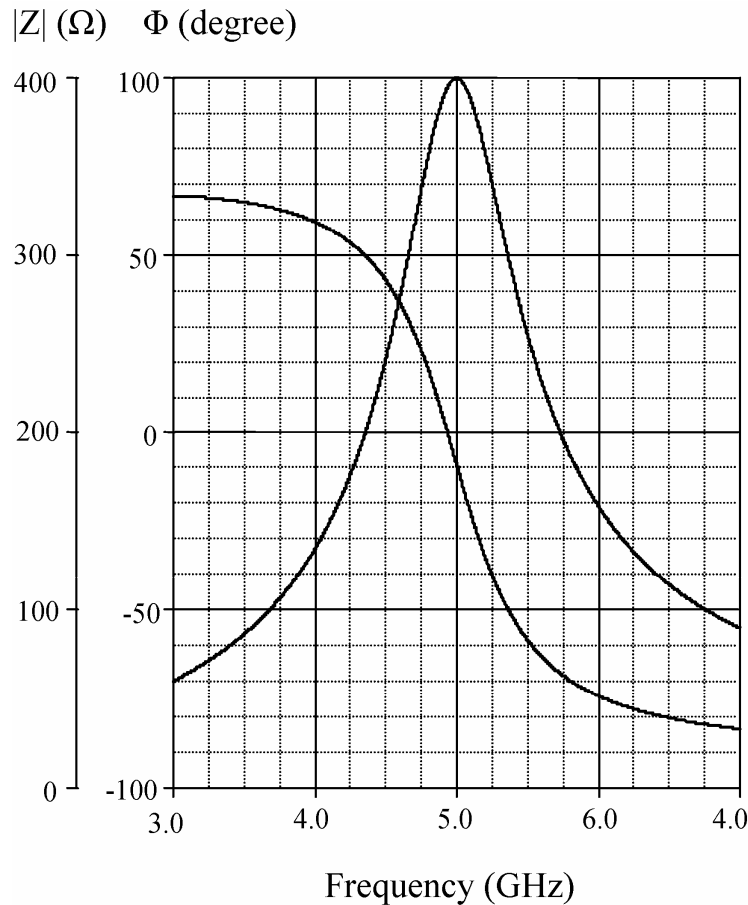(a) For $r_C \ll r_L$, (b) For $r_C = r_L$



(a)

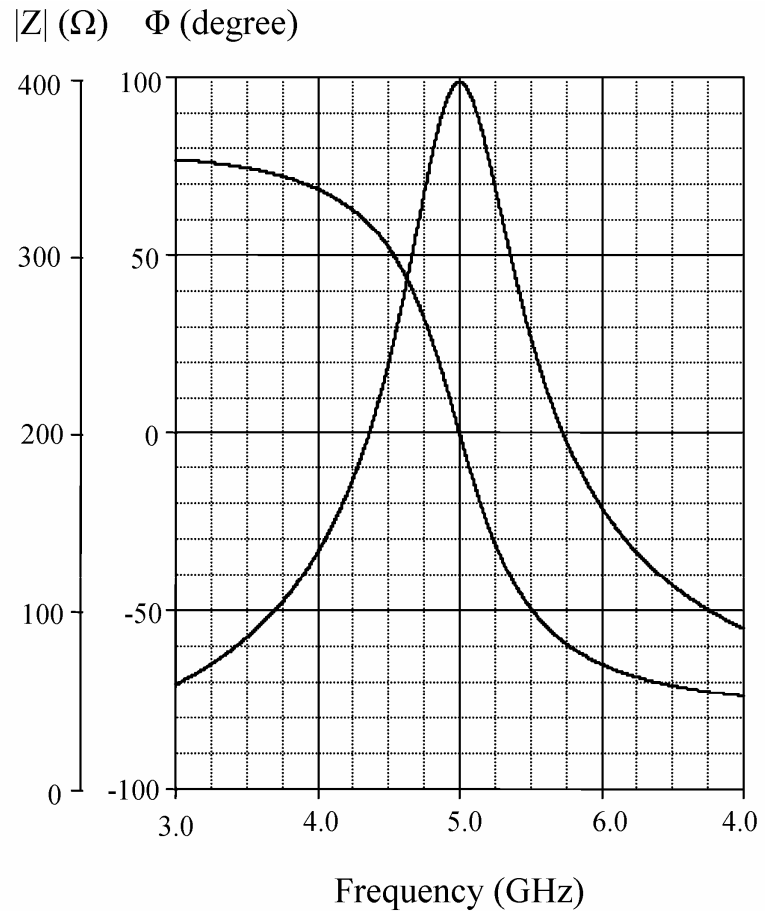

(b)


$f_0 = 5$ GHz, $L = 2$ nH, $r_L = 10$ ohm, $r_C = 0$

$f_0 = 5$ GHz, $L = 2$ nH, $r_L = 5$ ohm, $r_C = 5$ ohm

The quality factor of an oscillatory system

$$Q = 2\pi \frac{\text{The total energy of the system}}{\text{The energy lost in one period}}$$

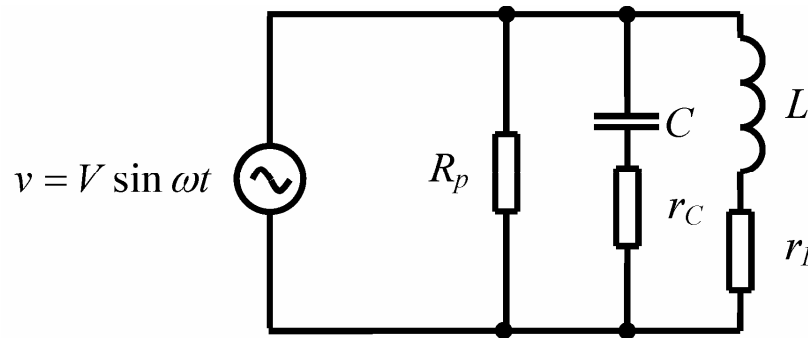Quality factor of a parallel resonance circuit:



Total (maximum) energy in the circuit: $E = \frac{1}{2} CV^2$

Energy consumed in one period in R_p : $E_p = T \times \frac{1}{2} \frac{V^2}{R_p} = \frac{1}{2f_0} \frac{V^2}{R_p}$

Energy consumed in one period in r_L : $E_L = \frac{1}{2f_0} V^2 \frac{r_L}{r_L^2 + \omega_0^2 L^2}$

Energy consumed in one period in r_C : $E_C = \frac{1}{2f_0} V^2 \frac{r_C}{r_C^2 + \frac{1}{\omega_0^2 C^2}}$

$$Q = 2\pi \frac{\frac{1}{2}V^2 C}{\frac{1}{2}V^2 \left[\frac{1}{f_0 R_p} + \frac{1}{f_0} \frac{r_L}{(r_L^2 + \omega_0^2 L^2)} + \frac{1}{f_0} \frac{r_C}{(r_C^2 + \frac{1}{\omega_0^2 C^2})} \right]}$$

This expression can be arranged as follows:

$$\frac{1}{Q_{eff}} = \frac{1}{Q_p} + \frac{1}{Q_L} + \frac{1}{Q_C}$$

where;

Q_{eff} is called as the "effective quality factor" of the circuit

$$Q_p = \omega_0 C R_p$$

(quality factor if R_p were the only lossy component)

$$Q_L = \frac{r_L^2 + \omega_0^2 L^2}{\omega_0 L r_L} \cong \frac{\omega_0 L}{r_L}$$

(quality factor if r_L were the only lossy component)

$$Q_C = \frac{\omega_0^2 C^2 r_C^2 + 1}{\omega_0 C r_C} \cong \frac{1}{\omega_0 C r_C}$$

(quality factor if r_C were the only lossy component)

Important Equivalencies

Parallel resistance R_{LP} equivalent to r_L :

$$Q_L = \frac{r_L^2 + \omega_0^2 L^2}{\omega_0 L r_L} \equiv \frac{R_{LP}}{\omega_0 L} \Rightarrow R_{LP} = r_L + \frac{\omega_0^2 L^2}{r_L} \cong r_L (1 + Q_L^2) \cong \frac{L}{r_L C}$$

Similarly, equivalent parallel resistance to r_C :

$$R_{Cp} = r_C + \frac{1}{\omega_0^2 C^2 r_C} \cong r_C (1 + Q_C^2) \cong \frac{L}{r_C C}$$

Note: These equivalencies are not valid for phase relations


The total parallel equivalent (effective) resistance:

$$R_{eff} = (R_{LP} // R_{Cp} // R_p), G_{eff} = G_{LP} + G_{Cp} + G_p$$

Effective quality factor in terms of R_{eff} and G_{eff} :

$$Q_{eff} = \frac{R_{eff}}{\omega_0 L} = \omega_0 C R_{eff}, Q_{eff} = \frac{1}{\omega_0 L G_{eff}} = \frac{\omega_0 C}{G_{eff}}$$

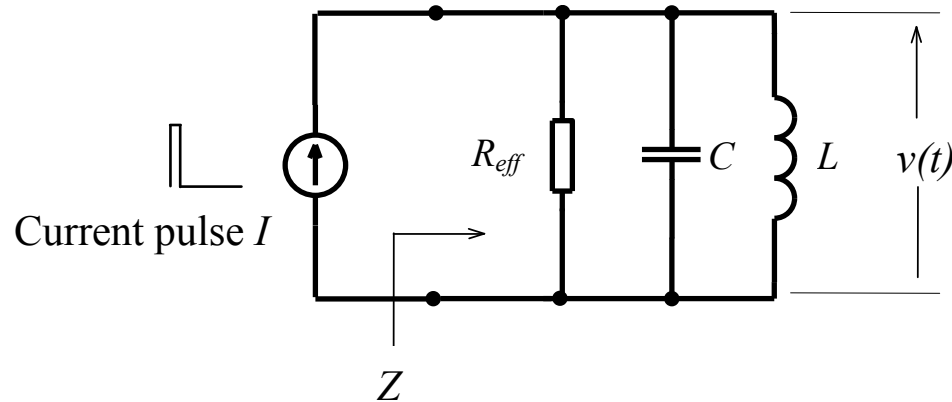Oscillation capability of a resonance circuit



$$Z = \frac{1}{C} \frac{s}{s^2 + s \frac{1}{R_{eff}C} + \frac{1}{LC}} = \frac{1}{C} \frac{s}{(s - s_{p1})(s - s_{p2})}$$

$$V = \left(\frac{I}{s} \right) \frac{1}{C} \frac{s}{(s - s_{p1})(s - s_{p2})}$$

$$v(t) = I \frac{1}{C} \frac{1}{(s_{p1} - s_{p2})} (e^{s_{p1}t} - e^{s_{p2}t})$$

$$s_{p1,p2} = -\frac{1}{2R_{eff}C} \mp \sqrt{\left(\frac{1}{2R_{eff}C}\right)^2 - \frac{1}{LC}}$$

$$s_{p1,p2} = \sigma \mp j\sqrt{\omega_0^2 - \sigma^2} = \sigma \mp j\bar{\omega}_0$$


where $\sigma = -\frac{1}{2R_{eff}C}$, $\omega_0 = \frac{1}{\sqrt{LC}}$ and $\bar{\omega}_0 = \sqrt{\omega_0^2 - \sigma^2}$

$$v(t) = I \frac{1}{C} \frac{1}{2j\bar{\omega}_0} e^{\sigma t} (e^{j\bar{\omega}_0 t} - e^{-j\bar{\omega}_0 t})$$

$$v(t) = I \frac{1}{C} \frac{1}{\bar{\omega}_0} e^{\sigma t} \sin \bar{\omega}_0 t$$


with $\sigma = -(\omega_0 / 2Q_{eff})$ and $\omega_0 \cong \bar{\omega}_0$;
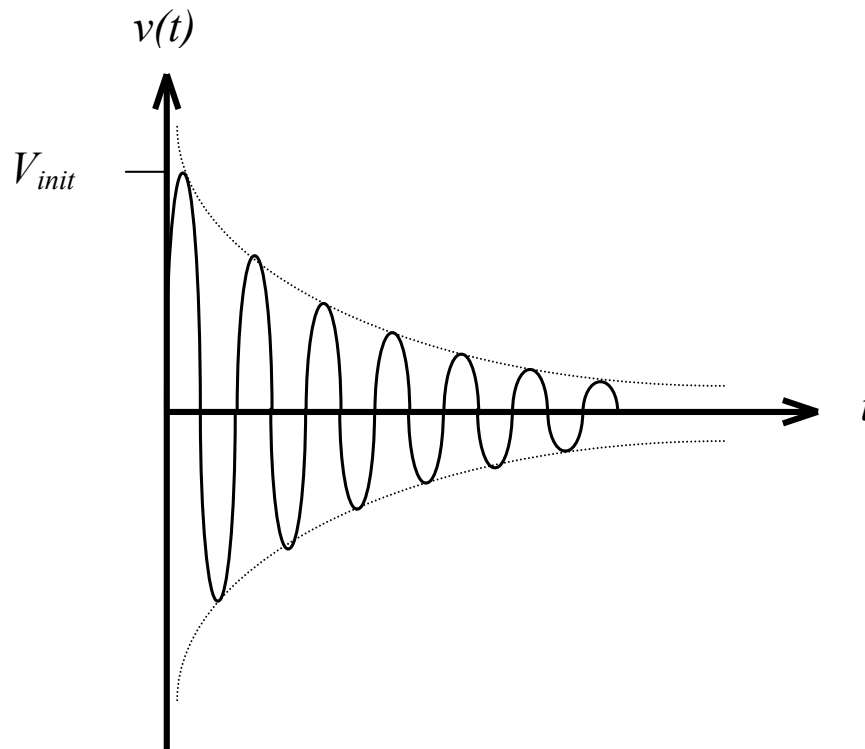
$$v(t) = V_{(init)} e^{-(\bar{\omega}_0 / 2Q_{eff})t} \sin \bar{\omega}_0 t$$





- At the end of $n = Q_{eff}$ periods, the amplitude drops to $V_{init} e^{-\pi}$.
- The number of periods corresponding to $\hat{v} = (1/e)V_{init}$ is (Q_{eff} / π) .

Q Enhancement

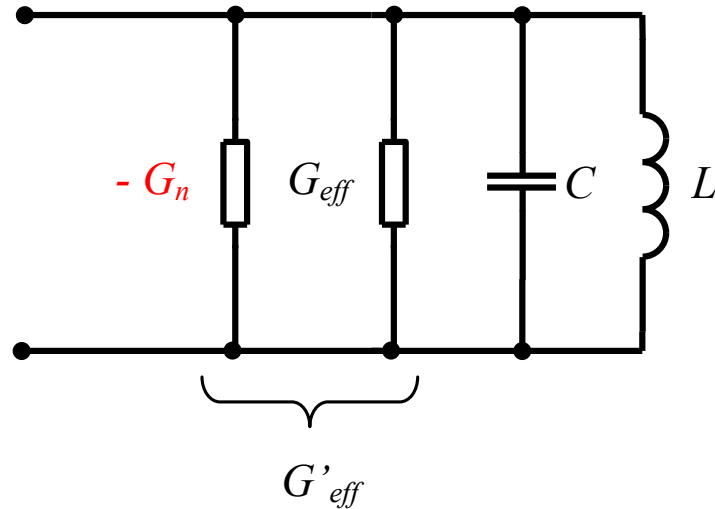


$$Q'_{eff} = \frac{1}{L\omega_0(G_{eff} - G_n)}$$

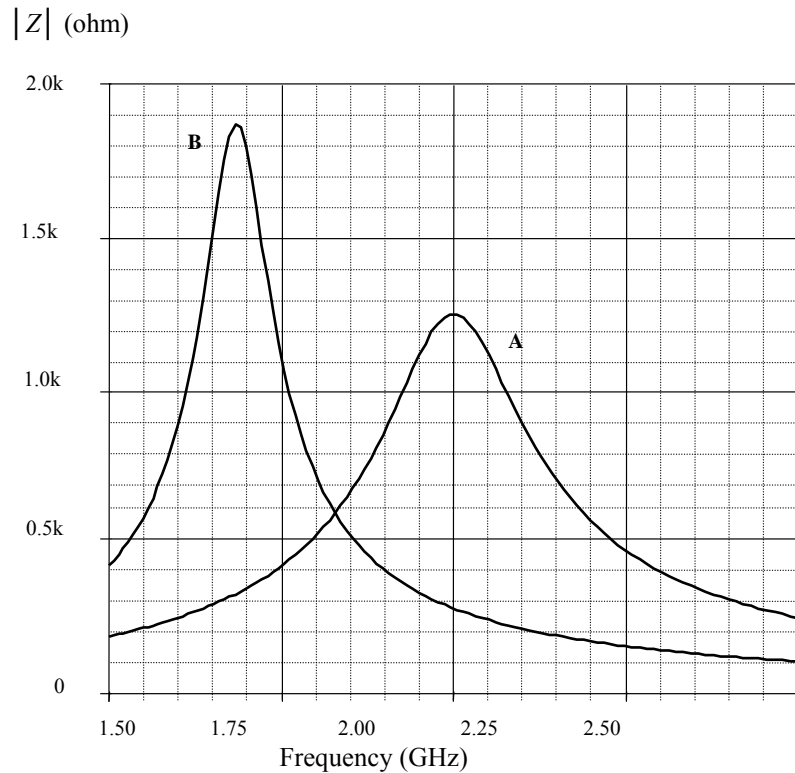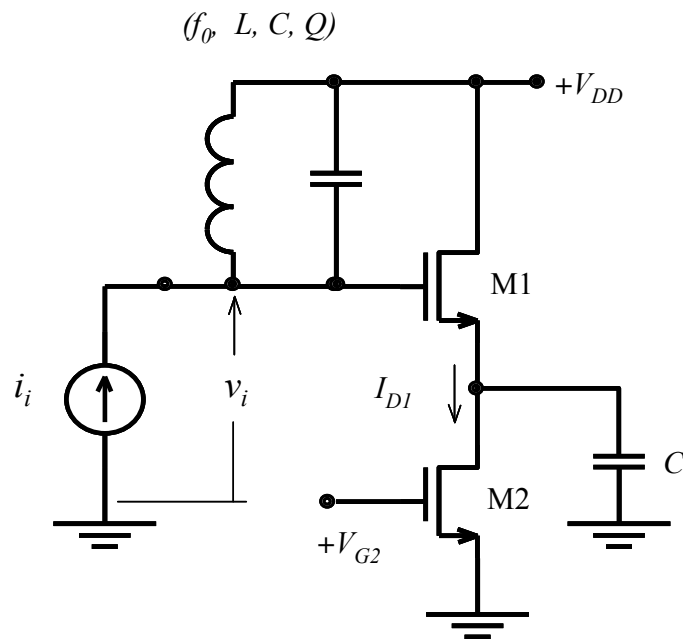Example: Q enhancement with a capacitive loaded source follower



(Shift of the resonance frequency is due to the input capacitance of M1)

$|Z|$ (ohm)

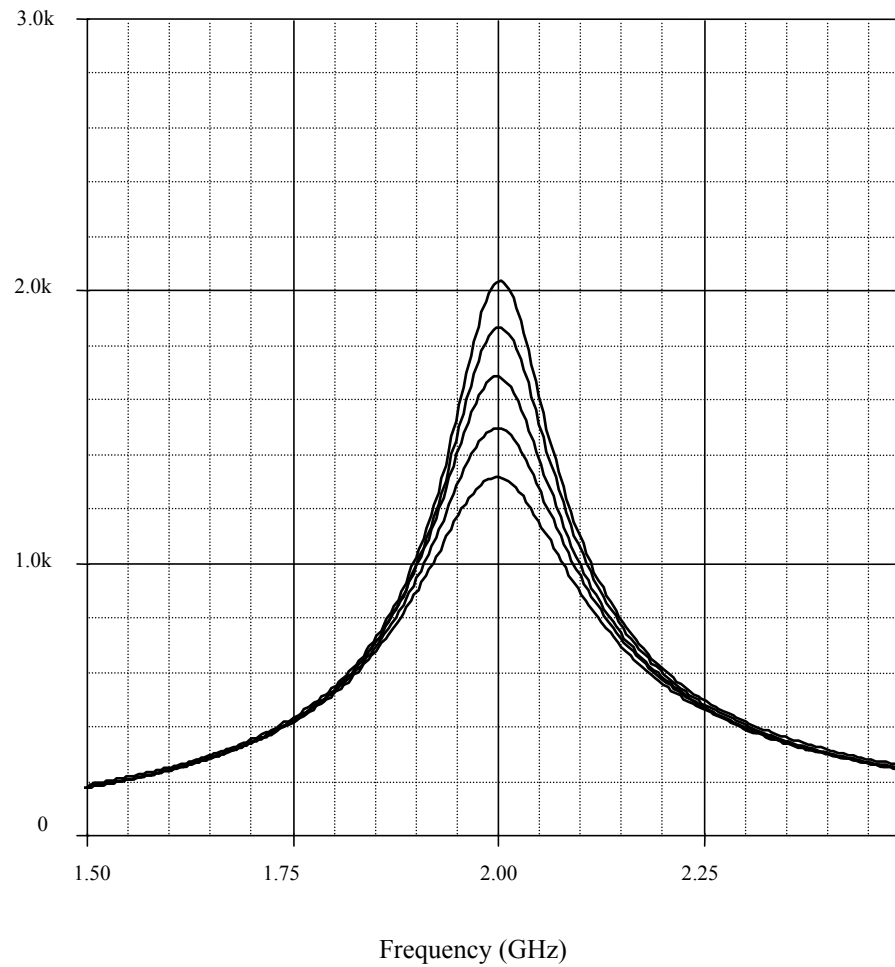

Parameter: The gate voltage of the current source transistor, T2
(Shift of the resonance frequency is compensated in the graph!)

The bandwidth of a parallel resonance circuit

$$Z = \frac{1}{C} \frac{s}{s^2 + s \frac{1}{R_{eff}C} + \frac{1}{LC}} \quad \rightarrow \quad Z(\omega) = R_{eff} \frac{1}{1 + j \frac{R_{eff}}{L\omega} (\omega^2 LC - 1)}$$



$$\text{with } LC = \frac{1}{\omega_0^2}, \quad Q_{eff} = \frac{R_{eff}}{L\omega_0};$$

$$Z = R_{eff} \frac{1}{1 + jQ_{eff} \frac{\omega_0}{\omega} \left(\frac{\omega^2}{\omega_0^2} - 1 \right)} = R_{eff} \frac{1}{1 + jQ_{eff} \frac{\omega_0}{\omega} \frac{(\omega + \omega_0)(\omega - \omega_0)}{\omega_0^2}}$$

$$Z \cong R_{eff} \frac{1}{1 + j\beta Q_{eff}}, \quad \text{where } \beta = \frac{2\Delta\omega}{\omega_0} = \frac{2\Delta f}{f_0}$$


$$|Z| = Z(\omega_0) \frac{1}{\sqrt{1 + (\beta Q_{eff})^2}}$$

$$\Phi = -\arctan(\beta Q_{eff})$$

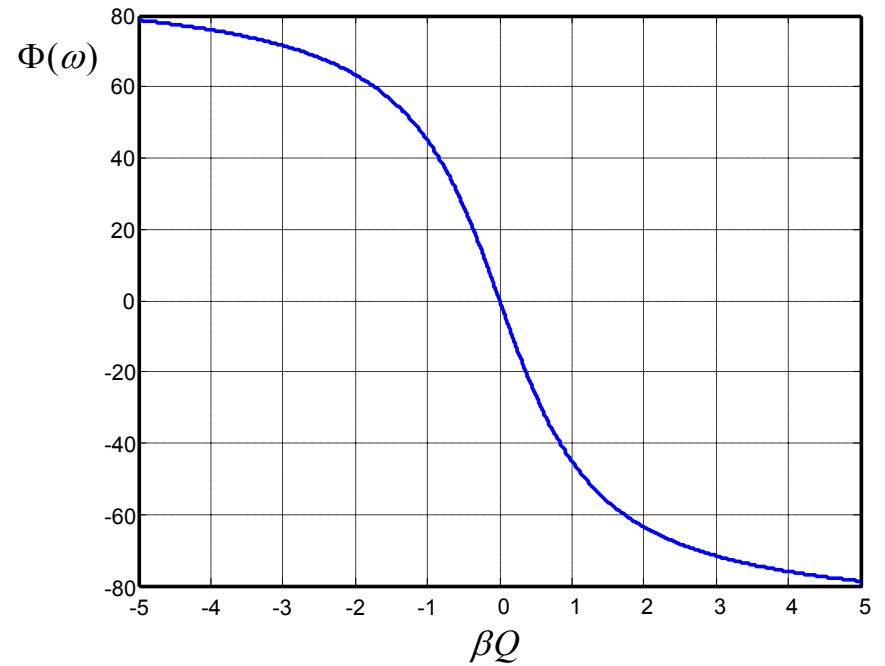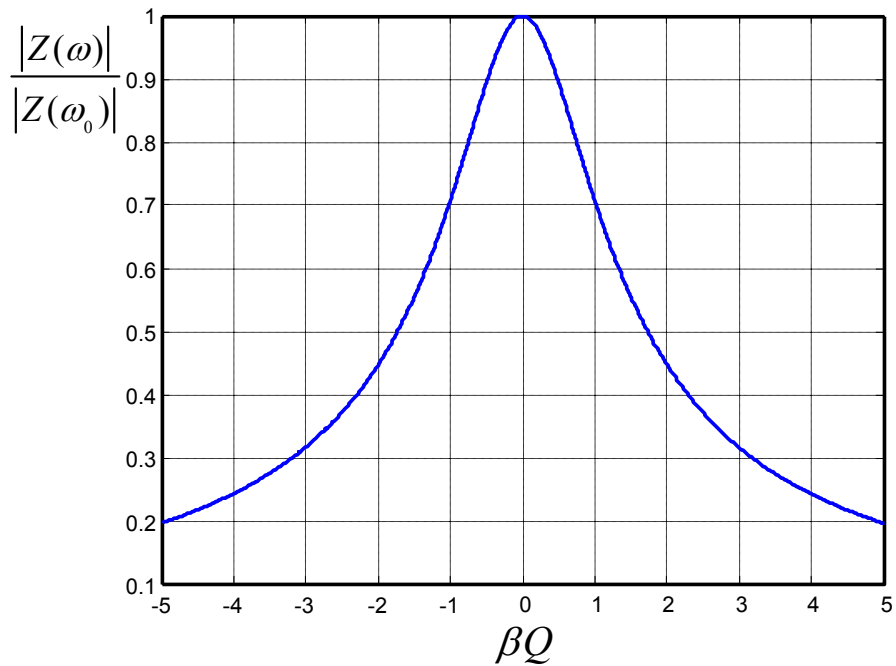

- At resonance; $Z(\omega_0) = R_{eff} = Q_{eff} L \omega_0$
- For $\beta Q_{eff} = \mp 1$; $|Z| = Z(\omega_0) / \sqrt{2}$
- $\Delta f = \frac{f_0}{2Q_{eff}} \Rightarrow f(-3 \text{ dB}) = f_0 \mp \frac{f_0}{2Q_{eff}}$, $B = \frac{f_0}{Q_{eff}}$
- $\Phi = 0$ at resonance.
- Impedance is
 - Inductive below the resonance frequency,
 - Capacitive above the resonance frequency.
- $\Phi = \mp \frac{\pi}{4}$ at -3 dB frequencies.

Branch currents at resonance:

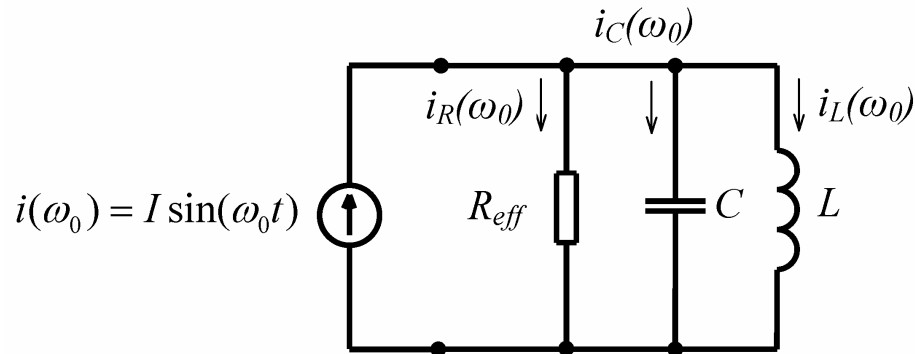

$$i_C(\omega_0) = v(\omega_0)(jC\omega_0) = i(\omega_0)R_{eff}(jC\omega_0)$$


$$i_C(\omega_0) = j [i(\omega_0) \times Q_{eff}]$$

$$i_L(\omega_0) = \frac{v(\omega_0)}{jL\omega_0} = \frac{i(\omega_0)R_{eff}}{jL\omega_0}$$


$$i_L(\omega_0) = -j [i(\omega_0) \times Q_{eff}]$$

(Possible adverse effect: Electromigration!)

b) The series resonance circuit:

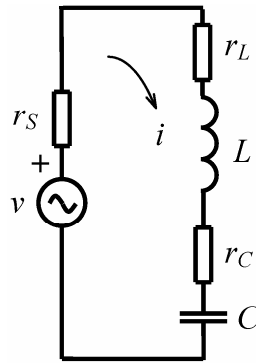

(a)

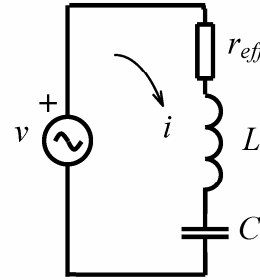

(b)


$$Z = (r_{eff} + sL + \frac{1}{sC}) \rightarrow Z = L \frac{(s - s_{01})(s - s_{02})}{s}$$

$$s_{01,02} = \sigma \mp j\sqrt{\omega_0^2 - \sigma^2}$$


$$\text{where } \omega_0^2 = \frac{1}{LC}, \quad \sigma = -\frac{r_{eff}}{2L} = -\frac{\omega_0}{2Q_{eff}}, \quad Q_{eff} = \frac{\omega_0}{2\sigma} = \frac{L\omega_0}{r_{eff}}$$

$$Z(\omega) = Z(\omega_0)(1 + j\beta Q_{eff}) , \quad \beta = 2\Delta\omega / \omega_0$$

$$|Z(\omega)| = Z(\omega_0)\sqrt{1 + (\beta Q_{eff})^2} \quad \Phi(\omega) = \arctan(\beta Q_{eff})$$

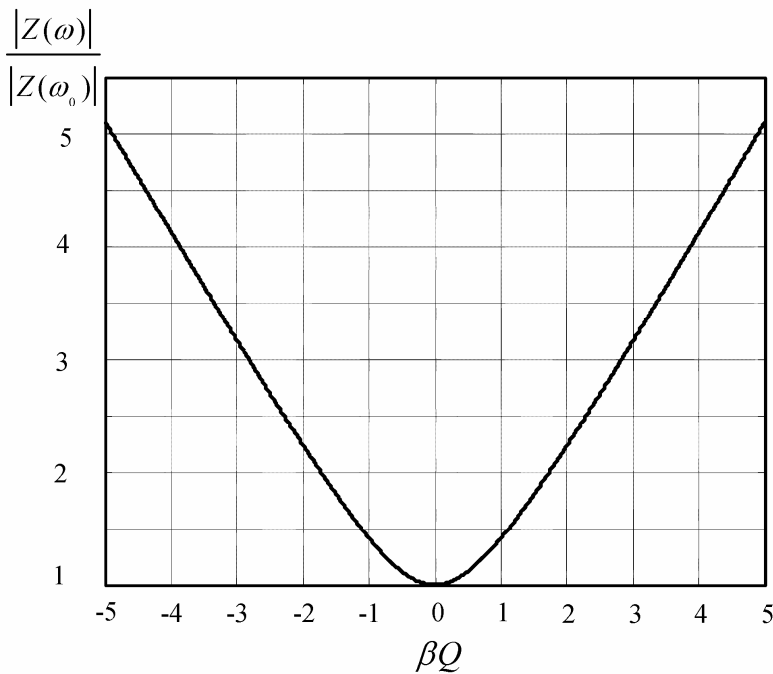

(a)

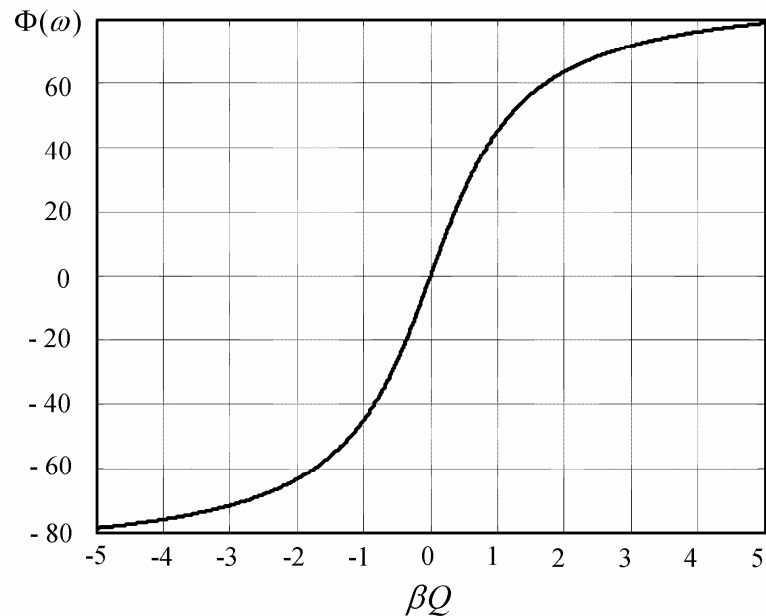

(b)

- At resonance; $Z(\omega_0) = r_{eff}$

- For $\beta Q_{eff} = \mp 1$ $|Z| = \sqrt{2} \times Z(\omega_0)$

- $f(+3 \text{ dB}) = f_0 \mp \frac{f_0}{2Q_{eff}}$, $B = \frac{f_0}{Q_{eff}}$


- At resonance; $\Phi = 0$

- Impedance is

- Capacitive below the resonance frequency,
- Inductive above the resonance frequency.

- $\Phi = \mp \frac{\pi}{4}$ at $+3 \text{ dB}$ frequencies.

Voltages at resonance:

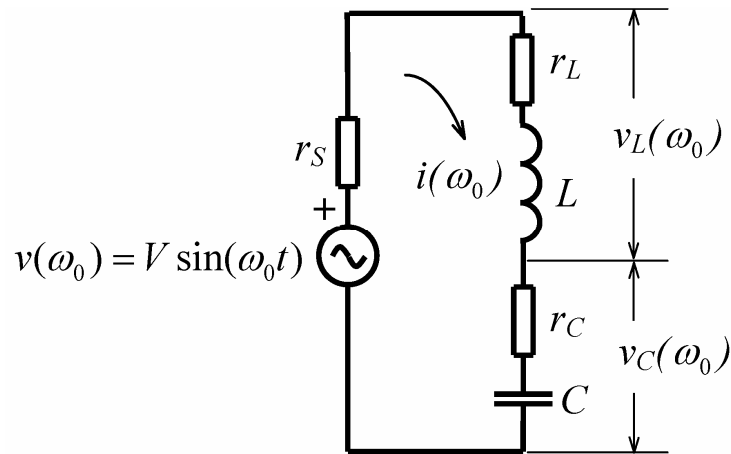

$$v_L(\omega_0) = i(\omega_0)(r_L + jL\omega_0) = v(\omega_0) \frac{r_L + jL\omega_0}{r_{eff}}$$

$$= v(\omega_0) \left(\frac{r_L}{r_{eff}} + jQ_{eff} \right) \cong j v(\omega_0) \times Q_{eff}$$

$$v_C(\omega_0) \cong -j v(\omega_0) \times Q_{eff}$$

(Possible adverse effect: Breakdown of the capacitor dielectric!)