 


8. Broadband LNA/TIA Design

Outline

- Broadband LNAs
 - Applications of TIAs
 - TIA design methodology
 - TIA circuit examples

Typical problem in broadband systems



Applications of broadband LNAs in HF systems

- Low-noise broadband amplifiers in **optical receivers**: signal source photodiode
 - **Goal**: Minimize the noise of the TIA-Photodiode ensemble while maximizing bandwidth and minimizing power


$$FoM = \frac{Z_T \cdot I_{\max} \cdot BW_{3dB}}{i_{\text{neq}}^{\text{rms}} P}$$

- Low noise broadband input comparators in **backplane communications, UltraWideBand (UWB) radio** and **high speed ADCs**: 50Ω signal source

$$FoM = \frac{A_V \cdot V_{\text{imax}} BW_{3dB}}{V_{\text{neq}}^{\text{rms}} P}$$

- **Goal**: Minimize noise in 50-Ohm system e.g. minimum input amplitude of broadband data: 10 mVpp at 40 Gb/s

Typical short-reach fiberoptic receiver

 

General observations

Problem

Either the real part of the input impedance or the real part of the noise impedance, or both, are frequency dependent.

Consequence


Cannot match both simultaneously over broad bandwidth without compromising F_{MIN} !

Solution

Use lossy feedback to accomplish both with minimal damage.

Shunt feedback is best because it minimizes power dissipation

Low-noise broadband amplifiers

 


TIA signal path analysis: infinite bandwidth amp

$$Z_T(s) = \frac{-R_T}{1 + s/\omega_p}$$

$$R_T = \frac{A}{A+1} R_F \quad \omega_p = \frac{A+1}{R_F C_T}$$

$$C_T = C_1 + C_D$$

 

Single-pole, finite bandwidth amplifier


If amplifier has a finite bandwidth f_A , then the two-pole transfer function stability condition ($Q=0.707$) gives:

$$f_A > \frac{1}{2\pi} \frac{2A}{R_F C_T}$$

$$BW_{3dB} = \frac{1}{2\pi} \frac{\sqrt{2A(A+1)}}{R_F C_T}$$

$$R_T \leq \frac{A f_A}{2\pi C_T BW_{3dB}^2}$$
 
$$Z_T(s) = \frac{-R_F \left(\frac{A}{1+A} \right)}{\frac{s^2}{\omega_p \omega_A (1+A)} + s \left(\frac{\omega_p + \omega_A}{\omega_p \omega_A (1+A)} \right) + 1}$$



TIA noise matching in 50-Ohm system

$$F_{Z_0} = 1 + R_{NA} Z_0 \left| Y_{CORA} + \frac{1}{Z_0} + \frac{1}{R_F} \frac{1 - j\omega_0}{1 + \omega_0^2} \right|^2 + Z_0 G_{NA} + \frac{Z_0}{R_F} \frac{1}{1 + \omega_0^2}$$


$$I_E(W_{OPT}) = \frac{1}{\omega} \sqrt{\left(\frac{1}{Z_0} + \frac{1}{R_F} \frac{1}{1 + \omega_0^2} \right)^2 + \left(\frac{1}{R_F} \frac{\omega_0}{1 + \omega_0^2} \right)^2} \sqrt{\frac{1}{\frac{G}{R} + G_C^2 + B^2}} \quad Z_{IN} = \frac{R_F}{1 + \frac{R_C I_T}{V_T}}$$

$$\omega_0 = \frac{R_F}{L_F}$$

Finding $I_E(W)_{OPT}$ is equivalent to matching the TIA(HBT) noise impedance to 50Ω at ω .



Algorithmic design methodology for broadband low-noise TIAs

 1. Bias HBT(MOSFET) at optimal noise current density J_{OPT} (0.15 mA/ μm) at amplifier's BW_{3dB}
2. Choose the DC voltage drop across R_C for linearity requirements. This fixes the loop gain $A = g_m R_C (=g_m r_o)$
3. Set the feedback resistance R_F for 50 Ω input match.
4. Size the emitter length (gate width) of Q1 for low-noise, using the equation from the previous slide.
5. Add inductors to extend bandwidth and filter high-frequency noise.




50 Ω , 43-Gb/s SiGe HBT TIA

(T.Dickson et al., JSSC, Aug.-06)

  


 - J_{opt} at GHz = 1.5 mA/μm²
- $I_T = 8$ mA, $I(Q_{1,2}) = 2$ × $I(Q_{3,4}) = 4$ mA
- $Q_{1,2,3,4} = 2 \times 0.17 \mu\text{m} \times 8 \mu\text{m}$
- $R_1 = R_2 = 27 \Omega$, $R_F = 260 \Omega$
- $A = g_m (R_1 + R_2) / 2 = 4.2$



 Example: 90-nm n-MOS TIA

- Bias at min. noise current density $0.15 \text{ mA}/\mu\text{m}$.
- p-MOS active load to increase gain at low V_{DD} .
- Feedback inductor L_F resonates out the capacitance at the TIA node and helps improve BW
- $L_F = 500 \text{ pH}$ designed for high SRF.







$$Z_{IN} = \frac{R_F}{1 + A} = \frac{180}{2.92} = 60.8 \Omega$$

$$A = \frac{g_{m1}}{g_{o1} + g_{o2} + \frac{1}{R_F}} = \frac{80 \text{ mS}}{12 \text{ mS} + 24 \text{ mS} + 5.55 \text{ mS}} = 1.92$$


$$C_{IN} = C_{gs1} + (1 + A)C_{gd1} = (2.5 \text{ fF}/\mu\text{m}) \times 80 \mu\text{m} = 200 \text{ fF}$$

$$C_{out} = C_{db1} + C_{gd1} + C_{gd2} + C_{db2} + C_{gs3} + 2C_{gd3} = 120 + 40 + 80 + 320 + 40 + 40 = 640 \text{ fF}$$

    90-nm CMOS TIA (T. Dickson et al. JSSC-Aug.06)






Noise Figure comparison of TIAs

 

MOSFET TIAs
exhibit lower
noise than SiGe
HBT TIAs


Broadband CMOS LNA topology scaling

   - f_T of 65-nm CMOS inv = n-MOS cascode f_T
- MOSFETs biased at 0.15 mA/ μm
- Size and current of MOS TIA do not change with technology nodes
- Noise and bandwidth improve as technology scales



65-nm LP CMOS vs. n-MOS TIAs

(T. Chalvatzis et al. JSSC Aug. 2007)

 


$$A = \frac{g_{m1} + g_{m2}}{g_{o1} + g_{o2} + \frac{1}{R_F}} = \frac{40\text{mS}}{3\text{mS} + 6\text{mS} + 5\text{mS}} = 2.85$$

$$Z_{IN} = \frac{R_F}{1 + A} = \frac{200}{3.85} = 52\Omega$$

$$C_{IN} = C_{gs1} + C_{gs2} + (1 + A)(C_{gd1} + C_{gd2}) = 20\text{fF} + 40\text{fF} + 3.85 \times 30\text{fF} = 175.5\text{fF}$$

$$C_{out} = C_{db1} + C_{gd1} + C_{gd2} + C_{db2} + C_{gs3} + 2C_{gd3} = 30 + 10 + 20 + 60 + 40 + 40 = 200\text{fF}$$

65-nm LP CMOS vs. n-MOS TIAs


 


- CMOS
- 3.9 mW
- 28 GHz


vs. n-MOS

14.4 mW


21 GHz

  

65-nm LP n-MOS vs CMOS TIAs (cont'd)



 


n-MOS: 37 Gb/s

 


CMOS: 40 Gb/s

   
81-Gb/s retimer (S. Shahramian, CSICS 2008)



65-nm bulk p-MOSFETs at 80 Gbs/GHz


 


Data Path

 


Clock path

Cascode and diff. CMOS TIA topologies

  


UWB LNA: Marc Tibout (Infineon), CSICS-06 Short Course

 [Ref. Salerno et Al., ESSCIRC, Sep. 2005]




 Diff. mode half-ckt. for feedback and amplifier networks



$$[Y] = \begin{bmatrix} \frac{1}{R_F} & \frac{1}{R_F} \\ \frac{1}{R_F} & \frac{1}{R_F} \end{bmatrix}$$
 
$$[C_Y] = 4kT \Delta f \Re[Y] = 4kT \Delta f \begin{bmatrix} \frac{1}{R_F} & \frac{1}{R_F} \\ \frac{1}{R_F} & \frac{1}{R_F} \end{bmatrix}$$



$$\langle i_{n1}, i_{n1}^* \rangle = 4kT \Delta f R g_m \frac{f^2}{f_T^2}$$


$$\langle i_{n2}, i_{n2}^* \rangle = 4kT \Delta f P g_m$$

$$\langle i_{n1}, i_{n2}^* \rangle = 4kT \Delta f j C \sqrt{PR} g_m \frac{f}{f_T}$$

$$[C_Y] = [C_{Ya}] + [C_{Yf}] = 4kT \Delta f \begin{bmatrix} R g_{m1} \frac{f^2}{f_{T1}^2} + \frac{1}{R_F} & \frac{1}{R_F} + j C \sqrt{PR} g_{m1} \frac{f}{f_{T1}} \\ \frac{1}{R_F} - j C \sqrt{PR} g_{m1} \frac{f}{f_{T1}} & P g_{m1} + \frac{1}{R_F} \end{bmatrix}$$



$$[Y] = [Y_a] + [Y_f] \approx \begin{bmatrix} j\omega [C_{gs1} + C_{gd1}(1 + g_{m1} R_{D1})] + \frac{1}{R_F} & \frac{1}{R_F} \\ \frac{g_{m1} g_{m2}}{g_{o1}} + \frac{1}{R_F} & \frac{1}{R_F} + g_{o2} + j\omega (C_{gd2} + C_{db2}) \end{bmatrix}$$

Low-gain mode

 


[Paparisto, ESSCIRC, Sep. 2002]


Transimpedance Limiting Amplifier

  

Example

 

Variable-Gain TIA

 

Summary

- TIAs feature the broadest bandwidth with the lowest noise and lowest power dissipation amongst lumped broadband amplifier topologies.
- TIAs offer optimal solution for fiberoptics, backplane and UWB applications
- An optimal transistor size exists for a given photodiode capacitance and/or 3dB bandwidth
- Transistors must be biased at J_{opt}
- Both SiGe HBT and CMOS TIAs are now viable at 10 to 80+ Gb/s