

# Digital Logic Design: a rigorous approach ©

## Chapter 14: Shifters

Guy Even   Moti Medina

School of Electrical Engineering Tel-Aviv Univ.


April 10, 2012

Book Homepage:

<http://www.eng.tau.ac.il/~guy/Even-Medina>
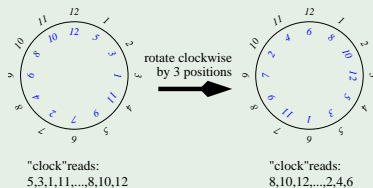
## Example

- assume that we place the bits of  $a[1 : 12]$  on a wheel.
- $a[1]$  is at one o'clock,  $a[2]$  is at two o'clock, etc.
- rotate the wheel, and read the bits in clockwise order starting from one o'clock and ending at twelve o'clock.
- the resulting string is a cyclic shift of  $a[1 : 12]$ .



# Definition of a Cyclic Shifter

We denote  $(a \bmod b)$  by  $\text{mod}(a, b)$ .

## Definition

The string  $b[n - 1 : 0]$  is a **cyclic left shift by  $i$  positions** of the string  $a[n - 1 : 0]$  if

$$\forall j : \quad b[j] = a[\text{mod}(j - i, n)].$$

## Example

Let  $a[3 : 0] = 0010$ . A cyclic left shift by one position of  $\vec{a}$  is the string 0100. A cyclic left shift by 3 positions of  $\vec{a}$  is the string 0001.

# Definition of BARREL-SHIFTER( $n$ )

## Definition

A BARREL-SHIFTER( $n$ ) is a combinational circuit defined as follows:

**Input:**  $x[n-1:0] \in \{0,1\}^n$  and  $sa[k-1:0] \in \{0,1\}^k$   
where  $k = \lceil \log_2 n \rceil$ .

**Output:**  $y[n-1:0] \in \{0,1\}^n$ .

**Functionality:**  $\vec{y}$  is a cyclic left shift of  $\vec{x}$  by  $\langle \vec{sa} \rangle$  positions.  
Formally,

$$\forall j \in [n-1:0] : y[j] = x[\text{mod}(j - \langle \vec{sa} \rangle, n)].$$

We often refer to the input  $\vec{x}$  as the **data input** and to the input  $\vec{sa}$  as the **shift amount input**. **To simplify the discussion, we assume that  $n$  is a power of 2, namely,  $n = 2^k$ .**

# BARREL-SHIFTER( $n$ ) Implementation

We break the task of designing a barrel shifter into smaller sub-tasks of shifting by powers of two. We define this sub-task formally as follows.

A  $\text{CLS}(n, 2^i)$  is a combinational circuit that implements a cyclic left shift by zero or  $2^i$  positions depending on the value of its select input.

## Definition

A  $\text{CLS}(n, i)$  is a combinational circuit defined as follows:

**Input:**  $x[n-1:0]$  and  $s \in \{0, 1\}$ .

**Output:**  $y[n-1:0]$ .

**Functionality:**

$$\forall j \in [n-1:0] : y[j] = x[\text{mod}(j - s \cdot i, n)].$$

## Subtask: $\text{CLS}(n, i)$ Implementation

A  $\text{CLS}(n, i)$  is quite simple to implement since:

- $y[j]$  is either  $x[j]$  or  $x[\text{mod}(j - i, n)]$ .
- So all one needs is a MUX-gate to select between  $x[j]$  or  $x[\text{mod}(j - i, n)]$ .
- The selection is based on the value of  $s$ .
- It follows that the delay of  $\text{CLS}(n, i)$  is the delay of a MUX, and the cost is  $n$  times the cost of a MUX.


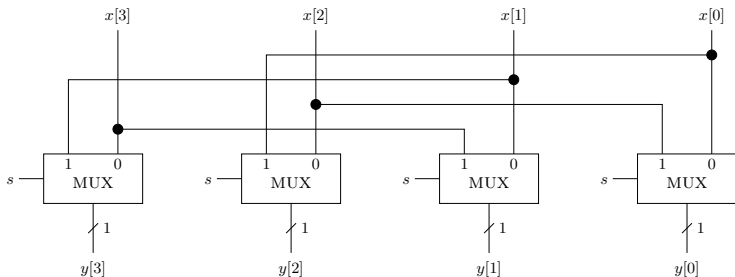


Figure: A row of multiplexers implement a  $\text{CLS}(4, 2)$ .

# Back to BARREL-SHIFTER( $n$ )

- The design of a BARREL-SHIFTER( $n$ ) is based on CLS( $n, 2^i$ ) shifters.
- The implementation is based on  $k$  levels of CLS( $n, 2^i$ ), for  $i \in [k - 1 : 0]$ .
- The  $i$ th level is controlled by  $sa[i]$ .

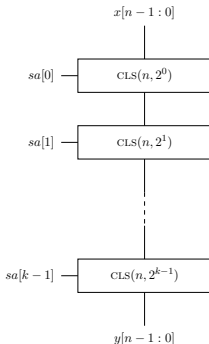

**Figure:** A BARREL-SHIFTER( $n$ ) built of  $k$  levels of CLS( $n, 2^i$ ) ( $n = 2^k$ ).

## Observation

*For every  $x, q \in \mathbb{Z}$ ,*

$$\text{mod}(x, n) = \text{mod}(x + qn, n).$$

## Observation

*If  $\alpha = \text{mod}(a, n)$  and  $\beta = \text{mod}(b, n)$ , then*

$$\text{mod}(a - b, n) = \text{mod}(\alpha - \beta, n).$$

## Claim

*The barrel shifter design depicted in the previous slide is correct.*

## Proof.

Prove by induction on  $i$ , that output of  $\text{CLS}(n, 2^i)$  equals the cyclic left shift of  $x$  by  $\langle sa[i : 0] \rangle$ . □



## Claim

*The cost and delay of BARREL-SHIFTER( $n$ ) satisfy:*

$$c(\text{BARREL-SHIFTER}(n)) = n \log_2 n \cdot c(\text{MUX})$$

$$d(\text{BARREL-SHIFTER}(n)) = \log_2 n \cdot d(\text{MUX}).$$

## Proof.

Follows from the fact that the design consists of  $\log_2 n$  levels of  $\text{CLS}(n, 2^i)$  shifters. □

# The cone of the Barrel Shifter

Consider the output  $y[0]$  of  $\text{BARREL-SHIFTER}(n)$  .

## Claim

*The cone of the Boolean function implemented by the output  $y[0]$  contains at least  $n$  elements.*

## Corollary

*The delay of  $\text{BARREL-SHIFTER}(n)$  is asymptotically optimal.*

# Logical Shift

## Definition

The binary string  $y[n-1:0]$  is a **logical left shift** by  $\ell$  positions of the binary string  $x[n-1:0]$  if

$$y[i] \triangleq \begin{cases} 0 & \text{if } i < \ell \\ x[i - \ell] & \text{if } \ell \leq i < n. \end{cases}$$

## Example

$y[3:0] = 0100$  is a logical left shift of  $x[3:0] = 1001$  by  $\ell = 2$  positions. When we apply a logical left shift to  $x[n-1:0]$  by  $\ell$  positions, we obtain the string  $x[n-1-\ell:0] \circ 0^\ell$ .

## Fast multiplication

In binary representation, logical shifting to the left by  $s$  positions corresponds to multiplying by  $2^s$  followed by modulo  $2^n$ .

# Logical Shifters (cont.)

## Definition

The binary string  $y[n-1:0]$  is a **logical right shift** by  $\ell$  positions of the binary string  $x[n-1:0]$  if

$$y[i] \triangleq \begin{cases} 0 & \text{if } i \geq n - \ell \\ x[i + \ell] & \text{if } 0 \leq i < n - \ell. \end{cases}$$

## Example

$y[3:0] = 0010$  is a logical right shift of  $x[3:0] = 1001$  by  $\ell = 2$  positions. When we apply a logical right shift to  $x[n-1:0]$  by  $\ell$  positions, we obtain the string  $0^\ell \circ x[n-1:\ell]$ .

## Fast division

In binary representation, logical shifting to the right by  $s$  positions corresponds to the integer part of the quotient after division by  $2^s$ .

# Notation.

- Let  $LLS(\vec{x}, i)$  denote the logical left shift of  $\vec{x}$  by  $i$  positions.
- Let  $LRS(\vec{x}, i)$  denote the logical right shift of  $\vec{x}$  by  $i$  positions.

# A bi-directional logical shifter

A bi-directional logical shifter is defined as follows.

## Definition

A  $L\text{-SHIFT}(n)$  is a combinational circuit defined as follows:

Input:

- $x[n-1:0] \in \{0,1\}^n$ ,
- $sa[k-1:0] \in \{0,1\}^k$ , where  $k = \lceil \log_2 n \rceil$ , and
- $\ell \in \{0,1\}$ .

Output:  $y[n-1:0] \in \{0,1\}^n$ .

Functionality: The output  $\vec{y}$  satisfies

$$\vec{y} \triangleq \begin{cases} \text{LLS}(\vec{x}, \langle \vec{s}\vec{a} \rangle) & \text{if } \ell = 1, \\ \text{LRS}(\vec{x}, \langle \vec{s}\vec{a} \rangle) & \text{if } \ell = 0. \end{cases}$$

# A bi-directional logical shifter (cont.)

## Example

- let  $x[3 : 0] = 0010$ .
- If  $sa[1 : 0] = 10$  and  $\ell = 1$ , then  $\text{L-SHIFT}(4)$  outputs  $y[3 : 0] = 1000$ .
- If  $\ell = 0$ , then the output equals  $y[3 : 0] = 0000$ .

# Implementation

As in the case of cyclic shifters, we break the task of designing a logical shifter into sub-tasks of logical shifts by powers of two.

## Definition

An  $\text{LBS}(n, i)$  is a combinational circuit defined as follows:

**Input:**  $x[n-1:0]$  and  $s, \ell \in \{0, 1\}$ .


**Output:**  $y[n-1:0]$ .

**Functionality:** The output  $\vec{y}$  satisfies

$$\vec{y} \triangleq \begin{cases} \vec{x} & \text{if } s = 0, \\ \text{LLS}(\vec{x}, i) & \text{if } s = 1 \text{ and } \ell = 1, \\ \text{LRS}(\vec{x}, i) & \text{if } s = 1 \text{ and } \ell = 0. \end{cases}$$

The role of the input  $s$  is to determine if a shift (in either direction) takes place at all. If  $s = 0$ , then  $y[j] = x[j]$ , and no shift takes place. If  $s = 1$ , then the direction of the shift is determined by  $\ell$ .



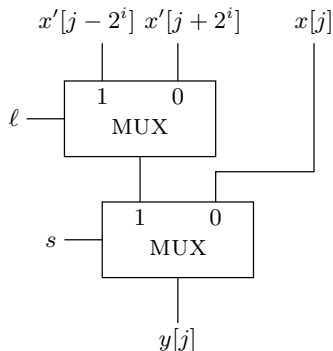

**Figure:** A bit-slice of an implementation of  $\text{LBS}(n, 2^i)$ .

question

Design a bi-directional logical shifter  $\text{L-SHIFT}(n)$ .

Arithmetic shifters are used for shifting binary strings that represent signed integers in two's complement representation.

**Since left shifting is the same in logical shifting and in arithmetic shifting, we discuss only right shifting** (i.e., division by a power of 2).

## Definition

The binary string  $y[n-1:0]$  is an **arithmetic right shift** by  $\ell$  positions of the binary string  $x[n-1:0]$  if the following holds:

$$y[i] \triangleq \begin{cases} x[n-1] & \text{if } i \geq n - \ell \\ x[i + \ell] & \text{if } 0 \leq i < n - \ell. \end{cases}$$

## Example

- $y[3 : 0] = 0010$  is an arithmetic shift of  $x[3 : 0] = 0101$  by  $\ell = -1$  positions.
- On the other hand,  $y[3 : 0] = 1110$  is an arithmetic shift of  $x[3 : 0] = 1001$  by  $\ell = -2$  positions.
- When we apply an arithmetic shift by  $\ell < 0$  positions to  $x[n - 1 : 0]$ , we obtain the string  $x[n - 1]^\ell \circ x[n - 1 : \ell]$ .

## Notation.

Let  $\text{ARS}(\vec{x}, i)$  denote the arithmetic right shift of  $\vec{x}$  by  $i$  positions.

# An arithmetic right shifter

## Definition

An ARITH-SHIFT( $n$ ) is a combinational circuit defined as follows:

**Input:**  $x[n-1:0] \in \{0,1\}^n$  and  $sa[k-1:0] \in \{0,1\}^k$ ,  
where  $k = \lceil \log_2 n \rceil$ .

**Output:**  $y[n-1:0] \in \{0,1\}^n$ .

**Functionality:** The output  $\vec{y}$  is a (sign-extended) arithmetic right shift of  $\vec{x}$  by  $\langle \vec{sa} \rangle$  positions. Formally,

$$y[n-1:0] \triangleq \text{ARS}(x[n-1:0], \langle \vec{sa} \rangle).$$

## Example

Let  $x[3:0] = 1001$ . If  $sa[1:0] = 10$ , then ARITH-SHIFT(4) outputs  $y[3:0] = 1110$ .

## question

Design an arithmetic right shifter ARITH-SHIFT( $n$ )