 


Chapter 6: Tuned Power Amplifiers

Outline

- Tuned PA Fundamentals
- Classes of Tuned PAs and Voltage Waveforms
- Linear Modulation of PAs
- Class A PA Design Methodology
- Examples of CMOS and SiGe HBT mm-wave PAs
- Efficiency and power combining techniques

Characteristics of PAs (L. Larson 2007)



Power : 0.1 mW - 2 W

Linearity Requirement: Moderate-Severe

Cost: Very Low (<\$3)

Efficiency Requirement: PAE > 30%

Worldwide Market: > 800M/yr(!).

Power : 50W - 200W

Linearity Requirement: Severe(!)

Cost: High (>\$100)

Efficiency Requirement: PAE > 10%


Worldwide Market > 1000K/yr.

Tuned PA Fundamentals


- G is the power gain of the PA
- P_{out} is the output power of the PA
- f is the centre frequency of the PA
- $PAE = (P_{OUT} - P_{IN}) / P_{DC}$
- Fourier series analysis required

$$FoM_{PA} = P_{OUT} \times G \times PAE \times f^2$$
 
$$P_{OUT} = \frac{1}{T} \int_0^T V_{DD} \cos(\omega t) \frac{V_{DD} \cos(\omega t)}{R_L} dt = \frac{V_{DD}^2}{2TR_L} \int_0^T [1 + \cos(2\omega t)] dt = \frac{V_{DD}^2}{2R_L}$$



Classes of tuned PAs

 


- Controlled current source: A (100% conduction), B (50% conduction), AB ($50\% < \text{conduction angle} < 100\%$), C (<50% conduction)
- Switching PAs (high efficiency > 50%): Class D, E, F, F⁻¹

PA Design Fundamentals: R_{LOPT}


$$P_{OUT} \sim (V_{MAX} - V_{MIN}) * I_{MAX}$$

$$PAE \sim (1 - V_{MIN}/V_{MAX})$$

 
$$R_{LOPT} = \frac{V_{opp}}{I_{opp}} \approx \frac{V_{MAX}}{I_{MAX}} = \frac{V_{MAX}}{2 \cdot I_{DC}}$$



Z_{out} as a function of P_{in}

 

Load pull contours

 

Courtesy of Stephen Long
UCSB

Output matching network design

- Performs several functions:
 - transforms the load impedance Z_0 to R_{LOPT}
 - provides a short-circuit at all harmonics so that only the power of the fundamental is transferred to the load, and
 - maintains the impedance transformation over the entire transmit bandwidth.

$$Q = \sqrt{\frac{Z_0}{R_{LOPT}} - 1} = \sqrt{\frac{50}{2} - 1} = 4.9 \approx 5$$


Use one (or two cascaded) lossless matching L networks

Class A voltage and current waveforms

$$Z_L(f_0) = R_L; Z_L(nf_0) = 0$$

For $n > 1$
 
$$n_{drain} = \frac{P_L}{P_{DC}} = \frac{\frac{(V_{DS} - V_{MIN})(I_{DS} - I_{MIN})}{\sqrt{2}}}{V_{DS} \cdot I_{DS}}$$



Class B voltage and current waveforms

I_{MAX} , P_{OUT} and R_{LOPT} similar to class A, but conducts only for %50 of T :

- g_m and G lower than class A.
- Highly nonlinear to increases PAE
- Maximum PAE= 78%.


$$I_{DC} = \frac{-I_{MAX}}{2\pi} \int_{\pi}^{2\pi} \sin \theta d\theta = \frac{I_{MAX}}{\pi} = \frac{2 \cdot V_{DD}}{\pi \cdot R_L}$$

$$R_{LOPT} = \frac{V_1}{I_1} = \frac{V_{DD}}{\frac{I_{MAX}}{2}} = \frac{2V_{DD}}{I_{MAX}} = \frac{V_{MAX}}{I_{MAX}}$$





$$\eta_{drain} = \frac{P_L}{P_{DC}} = \frac{V_1 \cdot I_1}{2 \cdot I_{DC} \cdot V_{DD}} = \frac{V_{DD} \cdot \frac{I_{MAX}}{2}}{2 \cdot V_{DD} \cdot I_{MAX}} = \frac{\pi}{4}$$

$$Z_L(f_0) = R_L; Z_L(nf_0) = 0$$

$$n > 1$$

 

    Push-pull class B voltage and current waveforms



Class AB PA

- Workhorse (still) of the PA industry
- Reaches a compromise between the linearity of the class A and the efficiency of the class B power amplifiers.
- Current waveforms are a train of “chopped” sinusoids

$$i_D(t) = I_{DC} + I_p \sin(\omega t) \text{ for } \omega t \leq \frac{3\pi}{2} - \frac{\theta_{off}}{2}$$

$$i_D(t) = 0 \text{ for } \frac{3\pi}{2} - \frac{\theta_{off}}{2} \leq \omega t \leq \frac{3\pi}{2} + \frac{\theta_{off}}{2}$$

$$i_D(t) = I_{DC} + I_p \sin(\omega t) \text{ for } \omega t \geq \frac{3\pi}{2} + \frac{\theta_{off}}{2}$$

Class AB equations

- I_{DC} = drain bias current when $P_{in} = 0$,

$$I_{DC} + I_p \sin\left(\pi + \frac{\pi - \theta_{off}}{2}\right) = 0$$

- I_p is amplitude of sinusoid

Angle of cutoff conduction θ_{off}

$$\theta_{off} = 2 \cos^{-1} \left(\frac{I_{DC}}{I_p} \right)$$

- DC component of current $I_{DC} = I_p \left\{ \cos\left(\frac{\theta_{off}}{2}\right) + \frac{1}{\pi} \left[\sin\left(\frac{\theta_{off}}{2}\right) - \left(\frac{\theta_{off}}{2} \right) \cos\left(\frac{\theta_{off}}{2}\right) \right] \right\}$

- Fundamental component of current $I_1 = I_p \left\{ 1 - \frac{1}{2\pi} [\theta_{off} - \sin(\theta_{off})] \right\}$

$$R_{LOPT} = \frac{V_{DS} - V_{MIN}}{I_1}$$


$$\eta_{drain} = \frac{1}{2} \frac{1 - \frac{1}{2\pi} [\theta_{off} - \sin(\theta_{off})]}{\cos\left(\frac{\theta_{off}}{2}\right) + \frac{1}{\pi} \left[\sin\left(\frac{\theta_{off}}{2}\right) - \frac{\theta_{off}}{2} \cos\left(\frac{\theta_{off}}{2}\right) \right]} \left(\frac{V_{DD} - V_{MIN}}{V_{DD}} \right)$$

Switching-mode PAs

Switching mode PAs minimize power in the transistor by avoiding overlap between current and voltage waveforms

 Examples: Class D, E, F, F⁻¹

But require special linearization techniques





Courtesy of Stephen Long

Class D concept (T-P Hung et al. MTT Dec 2007)

Switches provide square wave voltage source

Nominally open circuit at all harmonics

  (In reality, need to optimize for given transistor)



Problem:

Energy wasted in switch

$$E = \frac{1}{2} (C_{out} V^2)$$

Power loss is high: Ex f

But gaining popularity.

Asbeck 2004

41

Class D CMOS INV implementation




$$Z_L(f_0) = R_L; Z_L(nf_0) = \infty$$

$$V_1 = \frac{1}{\pi} \int_{-\pi/2}^{\pi/2} V_{DD} \cdot \cos(\theta) d\theta = \frac{2V_{DD}}{\pi} = \frac{2V_{MAX}}{\pi}$$


$$R_{LOPT} = \frac{V_1}{I_1} = \frac{2V_{MAX}}{\pi I_{MAX}} = \frac{2}{\pi} \frac{V_{DD}}{I_{MAX}}$$

$$P_L = \frac{V_1 I_1}{2} = \frac{2V_{DD} I_{MAX}}{2\pi} = \frac{V_{DD} I_{MAX}}{\pi}$$

   
$$\eta = \frac{P_L}{P_{DC}} = \frac{V_{DD} \cdot I_{MAX}}{\frac{\pi \cdot V_{DD} \cdot I_{MAX}}{\pi}} = 1$$





Class E concept

 

 - $V_{DS} = 0$ and $dV_{DS}/dt = 0$ when switch closes, avoids $\frac{1}{2} (CV^2f)$ loss
- $dV_{DS}/dt = 0$ when switch closes makes operation insensitive to rise time of input signal
- $V_{MAX} = 3.6V_{DD}$, $I_{MAX} = 1.7V_{DD}/R_L$



Class F voltage and current waveforms

  


$$Z_L(f_0) = R_L; Z_L(2k \times f_0) = 0; Z_L[(2k+1) \times f_0] = \infty$$

$$I_{DC} = \frac{I_{MAX}}{\pi} \quad I_1 = \frac{I_{MAX}}{2} \quad V_1 = \frac{4V_{DD}}{\pi} = \frac{2V_{MAX}}{\pi}$$


$$R_{LOPT} = \frac{V_1}{I_1} = \frac{4V_{MAX}}{\pi I_{MAX}} = \frac{8V_{DD}}{\pi^2 I_{DC}}$$

 - Suffers from $\frac{1}{2} (CV^2f)$ loss





Inverse class F (F^{-1}) stage
 
$$Z_L(f_0) = R_L; Z_L(2k f_0) = \infty; Z_L[(2k+1)f_0] = 0$$



$$P_L = \frac{V_1 I_1}{2} = \frac{V_{MAX} I_{MAX}}{2\pi}$$
  
$$R_{LOPT} = \frac{V_1}{I_1} = \frac{\pi V_{MAX}}{4 I_{MAX}} = \frac{\pi^2 V_{DC}}{8 I_{DC}}$$




$$I_{DC} = \frac{I_{MAX}}{2}$$

Comparison of PA classes

param/class	A	B	D	E (one case)	F	F^{-1}
V_{DD}	$V_{MAX}/2$	$V_{MAX}/2$	V_{MAX}	$V_{MAX}/3.6$	$V_{MAX}/2$	V_{MAX}/π
I_{DC}	$I_{MAX}/2$	I_{MAX}/π	I_{MAX}/π	$I_{MAX}/2.06$	I_{MAX}/π	$I_{MAX}/2$
$P_L/V_{MAX}I_{MAX}$	0.13	0.13	0.16	0.16	0.16	0.16
R_{LOPT}	V_{MAX}/I_M \propto	V_{MAX}/I_{MAX}	$2V_{MAX}/\pi I_{MAX}$	$1.075V_{MAX}/I_{MAX}$	$4V_{MAX}/\pi I_{MAX}$	$\pi V_{MAX}/4I_{MAX}$
η_d	50%	78%	100%	100%	100%	100%

Linear modulation of PAs



 
- Class A, B, AB: directly in the input signal
- Class C,D, E, F: separately from the carrier, typically through the supply node



Class A FET PA Design Fundamentals

- Linear voltage swing at input/output decreases in each new node
- OP_{1dB} current swing $J_{swing,pp}$ is constant across nodes at about $0.4 \text{ mA}/\mu\text{m}$
   
$$OP_{1dB} = W \cdot J_{swing,pp} \frac{(V_D - V_{dsat})}{4} = W \cdot J_{swing,pp} \frac{(V_{MAX} - V_{dsat})}{8}$$



Class A PA Design Fundamentals (ii)

- P_{sat} current swing $J_{sat,pp}$ is about $0.6 \text{ mA}_{\mu\text{m}}$ for n-FETs and $2J_{pfT}$ for HBTs
- P_{sat} voltage swing V_{satpp} is $2V_{DD} \leq V_{MAX}$

$$P_{sat} = \frac{W \cdot J_{sat,pp} V_{DD}}{4} = \frac{W \cdot J_{sat,pp} V_{MAX}}{8}$$

Typical Class A PA Power Densities and R_{Lopt}

- 90/65nm CMOS

◆ $V_{MAX} = 1.5V$, $J_{sat,p} = 0.6mA/\mu m$; $P_{sat} = 0.11mW/\mu m$; $R_{Lopt} = 2.5k\Omega \times \mu m$,

- 0.15 μm GaN FET

◆ $V_{MAX} = 40 V$, $J_{satpp} = 1 mA/\mu m$; $P_{sat} = 5 mW/\mu m$; $R_{Lopt} = 40 k\Omega \times \mu m$

- 50 GHz GaAs HBT

◆ $V_{MAX} = 6 V$, $J_{satpp} = 0.5 mA/\mu m$; $P_{sat} = 0.375 mW/\mu m$; $R_{Lopt} = 12 k\Omega \times \mu m$

- 230 GHz SiGe HBT

◆ $V_{MAX} = 3 V$, $J_{at,pp} = 3.9 mA/\mu m$; $P_{sat} = 1.5 mW/\mu m$; $R_{Lopt} = 770 \Omega \times \mu m$

Example of 1W PA design (through 40 GHz)

- 90/65nm n-MOS: $W = 9.09\text{mm}$; $R_{\text{Lopt}} = 0.27 \Omega$ (impossible to match from 50Ω)
- 150nm GaN FET: $W = 0.2\text{mm}$; $R_{\text{Lopt}} = 200 \Omega$ (easy to match from 50Ω)
- 50GHz GaAs HBT: $I_E = 2.66\text{mm}$; $R_{\text{Lopt}} = 4.5 \Omega$ (possible to match from 50Ω)
- 230GHz SiGe HBT: $I_E = 0.67\text{mm}$; $R_{\text{Lopt}} = 1.16 \Omega$ (possible but difficult to match from 50Ω)

Conclusion: Need high voltage device for $>1\text{W}$

mm-Wave Class-A PA Design Methodology

Start with output stage

- Voltage Swing: $V_{\text{swing}} = V_{\text{MAX}} - V_{\text{dsat}}$,

$$V_{\text{DD}} = V_{\text{dsat}}/2 + V_{\text{MAX}}/2$$

- Bias Current Density: set $J_p = 0.3 \text{ mA}/\mu\text{m}$ for linearity


- Device Size: find W from $\text{OP}_{1\text{dB}}$, V_{swing} , $I_{\text{swing}} = 0.4 \text{ mA}/\mu\text{m}$

- L_s : If $V_{\text{swing}}/\text{MAG} > V_{\text{in,swing}}$ add degeneration

- Output matching network (L_D , C_D) from $V_{\text{swing}}/I_{\text{swing}}$ to 50Ω

- Repeat steps for 2nd. last stage and scale W by 0.66 to 0.5

 - Design input stage to match to 50Ω and to maximize gain.



Ex: Output Stage with $P_{1\text{dB}} = 10\text{dBm}$ at 60 GHz

Given: $V_{DD} = 1.2V$, $V_{DS,sat} = 0.3 V$ at $0.3\text{mA}/\mu\text{m}$ $OP_{1\text{dB}} = 10\text{dBm} = 10 \text{mW}$

$$V_o = V_{DD} - V_{DS,sat} = 0.9 V (1.8V_{pp})$$



$$\text{From } OP_{1\text{dB}} = 10 \text{ mW} = V_o \times I_{DC}/2 \Rightarrow, I_o = 22 \text{ mA}$$

$$W = I_{DC}/0.28\text{mA}/\mu\text{m} = 78\mu\text{m}$$



$$R_L = V_o/I_o = 900/22 = 41 \Omega$$

Since MAG @ 60 GHz is only 6 dB (voltage gain of 2), the swing at input of last stage is $1.8V_{pp}/2 = 0.9V_{pp} > 0.45V_{pp}$. We need degeneration, hence L_s .

 
 
2-stage cascode + 1 CS stage PA in 90nm CMOS (M. Khanpour et al, CSICS-2007)



  
Measurements across dies and vs. supply voltage



OP_{1dB}, PAE and P_{SAT} measurements

  


 77GHz SiGe HBT PA (S. Nicolson et al. IMS-2007)




$$P_{sat} \leq \frac{I_{DC} \cdot V_{CC1}}{2} = \frac{44\text{mA} \cdot 1.5\text{V}}{2} = 33\text{mW} = 15.2\text{dBm}$$

PA Layout

 

Other CS mm-wave CMOS PAs (ISSCC-2008)

 


- 77GHz CS PA (Fujitsu)

- G=12dB, $P_{sat} = 7$ dBm

- 50-60GHz CS PA (Berkeley)

- G= 5.5dB, $P_{sat} = 12$ dBm

 


Efficiency Enhancement Techniques

Dynamic biasing techniques (L. Larson, 2007)


Dynamic Current Biasing Amplifier

Strategy: Vary I_{dc}
as signal level changes

 
- Used by most amplifiers for wireless systems (to some extent)
- Significant benefit obtained automatically with Class AB operation



Class AB operation
asymmetric output waveform
has dc component

 


Asbeck 2004

 

In Class B, $I_{dc} \sim K I_{max} \sim \sqrt{P_{out}}$

PA subranging


 
- Optimally biased for efficiency (binary-weighted) PA sections are switched in and out as needed by the transmitter
- But R_{LOPT} changes with number of switched on stages



HBT example: (L. Larson, 2007)

Maintaining Constant Gain Over Wide Range of DC Bias

  *Si/SiGe HBT BiCMOS WCDMA Power Amplifiers
With Dynamic Biasing and Reconfiguration Via MOSFET Switches*




**By selecting number of HBT fingers,
the input and output load capacitance
can be varied with power level, keeping
gain nearly constant**

Deng, 2004


39

 5GHz digitally-controlled class A WLAN PAs (Atheros, ISSCC-2008)




- 4-bit control, digitally-programmable output power level 10mW
- Thick gate oxide common-gate device for reliability
- Replica bias and I_{leak} to avoid overstress of the thin-oxide CS device

 Envelope tracking technique (L.Larson 2007)



 - Maximizes PA efficiency by keeping RF transistor closer to saturation for all envelope amplitudes
- Envelope Amplifier provides dynamic drain voltage



Kimball, 2001

44

In Envelope Tracking, PA is Class AB.
Input signal contains envelope and phase information.

2GHz PA with pulse-width modulation and ER (TI -2005, Univ. of Washington ISSCC-2008)

 


Figure 31.5.1: Generalized PWPM PA.

 




Figure 31.5.2: Schematic of the Class-E PWPM PA.

- Envelope restoration => Amplitude information is coded in the pulse width
- Pure digital signal applied at PA gate => sinusoidal output
- Output power is controlled by 4 bits

Doherty amplifier (L.Larson 2007)

Uses two coupled amplifiers

Peaking amplifier acts as "active load" for main amplifier

  


Asbeck 2004

49

LINC amplifier (L. Larson 2007)

- Linear Amplification with Nonlinear Components

 DSP generates signals with constant envelope to encode complex signals



Problems


Mismatch between parallel branches

Power combining losses

Asbeck 2004

50

Digital predistortion (L. Larson 2007)


 


- Digital predistortion creates an “inverse” PA nonlinearity in the DSP.
- Issues: bandwidth expansion; DSP memory table size and updating.

Power combining techniques


- Critical in nanoscale CMOS where voltage swing is low
 - Two-way: balanced, push-pull, in-phase power combining using Wilkinson couplers
 - multi-way power combining
 - series connection of transistor output voltage
 - half-wavelength paralleling
 - simple
 - Bagley polygon
 - spatial (through the air) $\lambda/2$ power combining

Power combining examples

 
 


(a)

Chip Outline


 


(b)

  

2-GHz Class B, 3W PA (Axiom, ISSCC-08)

  - Two (wide) concentric coils for the primary
- One thin (high voltage) coil for the secondary
- 8 differential stages are serially combined




1.5mm

2.8mm

Series stacking of transistors

- M.Shifrin, et al. 1991 with GaAs MESFET
- S. Prompromlikit et al, 2010, SOI n-MOSFET
- I. Sarkas et al., ISSCC 2012 SOI CMOS
 
$$Z_{source,i} \approx \frac{1}{g_{m,i}} \left(\frac{C_{gs,i}}{C_i} + 1 \right) \frac{1}{1 + j \frac{\omega}{\omega_T}} \approx \frac{1}{g_{m,i}} \left(\frac{C_{gs,i}}{C_i} + 1 \right)$$



Summary

- The most important parameter affecting PAE and P_{sat} is V_{MAX}
- Design of class A, AB PA is scalable through 200 GHz.
- In class A MOSFET PAs, biasing at $0.3\text{-}0.4\text{mA}/\mu\text{m}$ ensures maximum linearity and PAE
- Q of matching network is critical (>10 . i.e. $1\text{dB loss} = 21\%$ power loss)
- Switching PAs (D, E, F) used primarily at GHz frequencies for efficiency but making inroads into mm-waves
- For $>1\text{W}$ PAs, special devices are employed: GaAs HBT, LDMOS, GaN HEMTs or stacked SOI MOSFETs