 


High Speed Digital Blocks

Outline


- Systems using high-speed logic
- High-speed logic families
- Frequency response of basic ECL/CML cells
- Design methodology for high-speed logic gates
- Examples of typical high-speed digital gates
 - Selector, AND
 - Latch, latched XOR, DFF
 - Dividers
 - 4:1 MUX
 - 8:1 Transmitter

Example of a fiberoptics SerDes




[1]

Serializer w/o full-rate retiming

 


(a)


 


(b)



4:1 40-Gb/s Multiplexer

 



2:1 Selector

  


2:1 Static Divider with D-type latches

  


MOS-CML D-type latch

  


Deserializer Block Diagram

 

10-Gb/s 1:16 Demultiplexer

 


Transceiver with re-timed MUX & DMUX

 

High-speed digital logic families

- All high-speed logic families use diff. topologies
- Current-Mode Logic (CML)
 - Bipolar
 - SCFL (using MESFETs)
 - MOS
 - BiCMOS
- ECL or E²CL(Emitter-Coupled Logic)
 - Bipolar
 - III-V FET
 - BiCMOS

CML vs. CMOS


 


$$P_D = I_T V_{DD}$$

$$\Delta V = I_T R_L$$

$$V_{OH} = V_{DD}$$

$$V_{OL} = V_{DD} - \Delta V$$

  


General Characteristics of CML

- Operate in the active region for highest speed
i.e. triode region avoided
- All high-speed logic families use differential amplifier topologies
they typically consist of inverters, cascodes, SF/EF+INV
- Static power only
i.e. for a given gate, power dissipation does not depend on
switching speed

ECL Cells

 - Inverter (emitter/source coupled pair)
- Emitter/source follower
- Cascode
- Ind. peaking
- All of the above




Design goals in high-speed digital blocks

- Maximize speed:
 - topology optimization (inv, cascode, EF..)
 - transistor biasing & sizing (I_T , I_E , W_f , N_f)
- Minimize power dissipation:
 - Lowest tail current for given speed
 - Lowest bias supply (related to topology)
 - Optimal inter-stage scaling (current & size)
- Achieve output swing in matched 50Ω load.

Switching speed analysis

- Digital gates can be treated as small signal amplifiers
- The open circuit time constant technique (Elmore delay) can be used to analyze the small signal frequency response

 Analysis of fanout-of-k MOS-CML inverter stages



For full switching: $|A_V| > \sqrt{2}$



$$\tau_1 = R_L (C_{gd} + C_{db})$$

$$\tau_2 = \left(R_L + \frac{R_g}{k} \right) [k C_{gs} + (1 + g_m R_L) k C_{gd}]$$

$$\tau = \tau_1 + \tau_2 = R_L (C_{gd} + C_{db}) + R_L \left(k + \frac{R_g}{R_L} \right) [C_{gs} + (1 + g_m R_L) C_{gd}]$$

$$A_V = -R_L g_m; \quad g_m = \frac{I_T}{V_{eff}}; \quad R_L = \frac{\Delta V}{I_T}; \quad \text{hence } A_V = \frac{-\Delta V}{V_{eff}}$$


Cascading MOS-CML inverter stages

  


$$\tau_1 = \Delta V \frac{C_{gd} + C_{db} + C_{int}}{I_T} + \left(k + \frac{R_g}{R_L}\right) \Delta V \frac{C_{gs} + (1 - A_V) C_{gd}}{I_T}$$

Keep $R_g < 0.1 \times R_L$ Not difficult to do!

 Quasi-Large Signal Analysis of Gate Delay



 $J_{peakfT} = 0.3 \text{ mA}/\mu\text{m}$ and remains constant over technology nodes




$$W_G = \frac{I_T}{0.3 \text{ mA}/\mu\text{m}}$$

- There is no improvement in delay beyond

$$I_T = 0.3 \text{ mA}/\mu\text{m}$$

$$\Delta V_{MIN} = 2 \times [V_{GS}(I_{DS} = 0.15 \text{ mA}/\mu\text{m}) - V_T] \text{ scales with } L$$

BiCMOS Current-Mode Logic

 

- ✓ High slew rate
- ✗ High $R_B C_{BC}$
- ✗ Lower yield
- ✗ High V_{CC}

$$\tau_{\text{BiCMOS}} \approx \Delta V \frac{C_{BC} + C_{CS}}{I_T} + \left(k + \frac{R_G}{R_L} \right) \Delta V \frac{C_{GS} + C_{GD}}{I_T}$$

- ✓ MOS low input time constant
- ✓ HBT low output time constant

- ✗ High C_{DB}
- ✓ Low $R_G C_{GD}$
- ✓ High Yield
- ✓ Low V_{DD}

BiCMOS cascode gate delay

$$SL_{\text{HBT}} = \frac{I_{\text{Cpeak}} f_T}{C_{\text{bc}} + C_{\text{cs}}}$$

$$SL_{\text{FET}} = \frac{I_{\text{Dpeak}} f_T}{C_{\text{gd}} + C_{\text{db}}}$$

$$\tau_{\text{HBT}} \approx \Delta V \frac{C_{\text{bc}} + C_{\text{cs}}}{I_T} + \left(k + \frac{R_b}{R_L} \right) \Delta V \frac{C_{\pi} + (1 - A_V) C_{\text{bc}}}{I_T}$$

$$\tau_{\text{FET}} \approx \Delta V \frac{C_{\text{gd}} + C_{\text{db}}}{I_T} + \left(k + \frac{R_g}{R_L} \right) \Delta V \frac{C_{\text{gs}} + (1 - A_V) C_{\text{gd}}}{I_T}$$



$$\tau_{\text{BiCMOS}} \approx \Delta V \frac{C_{\mu} + C_{\text{cs}}}{I_T} + \left(k + \frac{R_g}{R_L} \right) \Delta V \frac{C_{\text{gs}} + C_{\text{gd}}}{I_T}$$

BiCMOS CML Logic

Main ideas:

- Use MOSFETs on clock path only to reduce $R_g \times C_{in}$ time constant
- Use HBT in upper levels to reduce output time constant
- Logic swing remains that of the bipolar CML at 250 mV_{pp} , hence speed
- Only clock path needs to have MOS-CML swing

MOS vs. SiGe BiCMOS CML Delay

  

- Speed improvement as FETs scale is due to ΔV scaling.
- Adding a SiGe HBT to a CMOS process almost doubles the speed

Using Inductive Peaking to Improve Bandwidth or Reduce Power

- ΔV is set when technology choice is made

Design equations without peaking:


$$BW_{3dB} = \frac{1}{2\pi R_L C_L}; \quad R_L = \frac{\Delta V}{I_T}; \quad BW_{3dB} = \frac{I_T}{2\pi \Delta V C_L}$$

- Design equations with peaking and constant group delay


$$L_p = \frac{C_L R_L^2}{3.1} \quad L_p = \frac{C_L}{3.1} \frac{\Delta V^2}{I_T^2} \quad BW_{3dB} = \frac{1.6 \times I_T}{2\pi \Delta V C_L}$$

- For a given speed and technology there is maximum realizable inductor $L_{P_{MAX}}$ and a minimum I_T and **power** that are needed to achieve that speed
 
$$I_{Tmin} = \Delta V \sqrt{\frac{C_L}{3.1 L_{pmax}}}$$



 
Inductive Broadbanding in Latches and Selector





T. Suzuki *et al.*, *IEEE ISSCC Proc.*, pp.192-193, Feb. 2002.

Design Methodology for Max. Speed

- Set $\Delta V = 1.5 \times \Delta V_{\text{MIN}}$ (600 mV in 130 nm, 400 mV in 90 nm, 250mVpp in BiCMOS)
- Set I_T as low as possible for given speed
- Size MOSFETs to be biased at $J_{\text{pT}}/2 = 0.15$ mA/ μm with I_T at 0.3 mA/ μm . HBTs biased at $3J_{\text{pT}}/2$
- Start with inverters, add peaking and broadbanding,
- Add (if needed) EF/SF biased at $1/3 \dots 1/2 J_{\text{pT}}$
- Optimize scaling ratio between stages: a 1.5 .. 2 ratio is a good start.

 


Pseudo-CML

  

- Need $V_{DS} > 0.5$ V to operate at 40+Gb/s => remove I_T
- V_{GS} of data-path FETs determines V_{DS} of clock-path FETs => LVT+HVT

Design Ex.: 1.2-V 90-nm CMOS latch

 

- No current source in clock-path
- High- V_T devices on clock path.
- $I_{BIAS} = I_{pT} / 2 = 0.15 \text{ mA}/\mu\text{m}$.
- To fully switch the 90-nm MOS diff pair at $0.15 \text{ mA}/\mu\text{m}$: $\Delta V > 300 \text{ mV}$
- For $I_{BIAS} = 4.5 \text{ mA}$ and $R_L = 40 \Omega$:

$$\Delta V = (I_{M1} + I_{M2}) R_L = 9 \text{ mA} \times 40 \Omega = 360 \text{ mV}$$

- Total capacitance at the drain of M3 ($A_V = -1.2$):


$$C_T = C_{db3} + C_{gd3} + C_{gd5} + C_{db5} + C_{gs6} + (1 - A_V) C_{gd6} + k(C_{gs6} + (1 - A_V) C_{gd6}) = 197 \text{ fF}$$

- $L = 100 \text{ pH}$ extends the BW to:

$$BW_{3dB} = \frac{1.6}{2 \pi R_L C_T} = 32.3 \text{ GHz}$$



- Power consumption: 10.8 mW/latch .

Retiming DFF – Die Photo

 

- TIA
- DFF
- Output driver
- Clock tree
- $P = 130 \text{ mW @ } V_{DD} = 1.2 \text{ V}$
- Area = $600 \times 800 \mu\text{m}^2$

Measurements at 40 Gb/s and 1.5 V

  


- Error-free 508-bit pattern.
- Input (top), output (bottom).
- BER not measured due to limitations of test setup.


An 81Gb/s, 1.2V TIALA-Retimer in Standard 65-nm CMOS

**Shahriar Shahramian et
al.
IEEE CSICS-2008**

Block Diagram

 


TIALA schematics

 


- Simulated small-signal gain is 20.5dB with a 3dB bandwidth of 44GHz .

Single-ended to differential conversion

 


- Differential pairs with active current sources provide single-ended to differential conversion.

Clock distribution network

 

- Simulated differential, small-signal gain of 6dB between 50GHz and 85GHz.


81-Gb/s flip-flop schematic

 


- Combination of HVT and LVT transistors allows for operation from 1.2V.

Simulated 80Gb/s eye-diagrams


Transient Response

 

 
A: (14.1316p 611.892m) delta: (572.702f -74.811u)
B: (14.7043p 611.817m) slope: -130.628M



 A: (6.625p 1.04235) delta: (45.5638f -469.765m)
B: (6.67056p 572.586m) slope: -10.31T



 
A: (9.16012p 1.08469) delta: (24.6454f -450.777m)
B: (9.18477p 633.91m) slope: -18.2906T



A: (6.6876p 179.405m) delta: (1.45422p 132.347u)
B: (8.14182p 179.537m) slope: 91.0094M


Die photograph

DC and Biasing

 


- 0.57mm x 1.2mm
- $V_{dd} = 1.2V$, Total Power = 200mW



Measurement result: 78Gb/s

 

 
Measurements: 81Gb/s with 80 mV_{pp} input




MOS-HBT (pseudo) CML

  

 
- HBT ECL to BiCMOS CML
- 3.3 V to 2.5 V and reduced number of tails
- 1.8 V (lower power) at same speed
- Inductive peaking to increase speed



 12-GHz Latch Design (E Laskin, CSICS-2005)



43-Gb/s BiCMOS CML Latch Design Example

 

- $J_{\text{pT}} = 8\text{mA}/\mu\text{m}$, $C_{\text{be}} = 23.2\text{pF} \times I_{\text{C}}$, $C'_{\text{cs}} = 1.1\text{fF}/\mu\text{m}$, $C_{\text{bc}} = 11\text{fF}/\mu\text{m}^2$, $A_{\text{V}} = 2.85$
- $W(\text{M1}, \text{M2}) = I_{\text{T}} / 0.3\text{mA}/\mu\text{m} = 4\text{mA} / 0.3 = 13\mu\text{m}$
- $I_{\text{E}}(\text{Q1-Q4}) = 4\text{mA} / (0.17\mu\text{m} \times 12\text{mA}/\mu\text{m}) = 2\mu\text{m}$
- $I_{\text{E}}(\text{Q5-Q6}) = 2\text{mA} / (0.17\mu\text{m} \times 4\text{mA}/\mu\text{m}) = 3\mu\text{m}$
- $R_{\text{L}} = \Delta V / I_{\text{T}} = 300\text{mV} / 4\text{mA} = 75\Omega$
- $L = 130\text{pH}$ for $k=1$ & 184pH for $k=2$


$$C_{\text{T}} = C_{\text{cs1}} + C_{\text{bc1}} + C_{\text{bc4}} + C_{\text{cs4}} + C_{\text{be3}} + (1 - A_{\text{V}})C_{\text{bc3}} + k(C_{\text{be}} + (1 - A_{\text{V}})C_{\text{bc}}) = 72\text{fF}$$

$$\text{BW}_{3\text{dB}} = 1.6 \times \frac{1}{2\pi R_{\text{L}} C_{\text{T}}} = 47\text{GHz} (33.8\text{GHz for } k=2)$$

Examples of Logic Gates


Example of Logic Gate

Selector: BiCMOS CML

 

- n-MOS current tails for voltage headroom
- Inductive peaking may be needed

Selector: CMOS CML (60 Gb/s in 90-nm)

 


- Inductive peaking
- n-MOS only
- source follower for clock level
- reduced swing for headroom

Broadcom patent US 2002/0017921 A1:


“Current-controlled CMOS circuits with inductive ***broadbanding***”

Selector: BiCMOS 80-Gb/s


(T. Dickson et al, ISSCC-2005)

 

 
- EF^2 & series-shunt peaking for highest speed
- 3-D stacked inductor



 BiCMOS CML XOR Schematic (E. Laskin CSICS-2005)







AND: BiCMOS CML

 


- n-MOS current tails for voltage headroom
- Cascode for good isolation and symmetry

   
 
Divide-by-2 block diagram and latch schematics



Divider layout (20 x 16 μm^2)

 


PVT performance of 65-nm GP CMOS divider

  


- Operates up to 78.5 GHz at 100 °C from 1.1V supply and at 80 GHz at 125 °C from 1.4 V
- Does not divide below 57GHz

 
65-nm GP/LP CMOS vs. SiGe HBT and BiCMOS dividers



2.5-V, 1.4-W, 90-Gb/s Transmitter

 


2.5-V, 90-Gb/s BiCMOS Selector

 


90-Gb/s selector consumes 60mW

2.5-V, 90-Gb/s BiCMOS Output Driver


 


- MOS g_m and input capacitance relatively constant as bias current changes.
- Excellent for output stages with adjustable amplitude control.

 
2.5V, 40-GHz PLL with Resettable BiCMOS latch



- 38-42 GHz lock range

  


Measured Results: 80 Gb/s

 

- Running for more than 1 hour continuously in the lab.
- Jitter: 560 fs (rms) , Rise/fall time: 4-5 ps, Amplitude: 300 mV_{pp} per side


90 Gb/s: amplitude control

 


Little degradation in eye quality as amplitude varies from 150 mV to 300 mV per side

80 Gb/s at 100 °C

Agilent 07:04:24 Sep 3, 2007

 

 Freq/Channel
Center Freq 41.0500000 GHz
Start Freq 40.0500000 GHz
Stop Freq 42.0500000 GHz
CF Step 200.000000 MHz



Summary


- Minimum delay of MOS/BiCMOS CML gates occurs at $0.3\text{mA}/\mu\text{m}$
- Minimum MOS-CML voltage swing and delay decreases with every new node: 600mV_{pp} in 180nm, 450mV_{pp} in 130-nm, 350mV_{pp} in 90-nm and 65-nm CMOS
- In the $0.15 - 0.4\text{mA}/\mu\text{m}$ range, CML delay is robust V_T , I_{DS} , and V_{GS} variation.
- Algorithmic design methodology for MOS, HBT and BiCMOS CML gates

Back-up slides

Device model parameters


<i>Device Parameter</i>	<i>90nm CMOS</i>	<i>130nm SiGe HBT</i>	<i>GaAs p-HEMT</i>	<i>InP HEMT</i>
$g_m/\mu m$	1.2 mS	38*IC	0.5 mS	0.65 mS
$C_{gd}(C_{bc})/\mu m$	0.4 fF	2.5 fF	75 aF	175 aF
$C_{gs}(C_{be})/\mu m$	1 fF	3fF + 0.3p*gm	750 aF	584 aF
$C_{db}(C_{cs})/\mu m$	1.5fF	1.1 fF	170 aF	220 aF
$J_{pft} (mA/\mu m)$	0.3	2	0.3	0.3
$SL (V/ps)$	0.16	0.56	0.81	0.56
$BV_{CEO}/GDO (V)$	1.5	1.6	6	2
$V_{BE}/V_T (V)$	0.3 (0.75)	0.9	-0.9	-0.6
$V_{supply} (V)$	1.2	1.8-3.3	5	3

CE/CS Stage

 

$$A_V = \frac{-g_m R_L}{1 + s[R_{\pi 0}(C_{\pi} + C_{\mu}(1 + g_m R_L)) + R_L(C_{\mu} + C_{cs} + C_L)]}$$
 
$$\tau_1 = R_{\pi 0} C_{\pi} + R_{\mu 0} C_{\mu} + R_L(C_{\mu} + C_{cs} + C_L)$$



$$R_{\pi 0} = r_{\pi} \parallel R_b$$

$$R_{\mu 0} = R_{\pi 0}(1 + g_m R_L) + R_L$$

$$\frac{1}{\tau_2} = \frac{1}{R_{\pi 0} C_{\pi}} + \frac{1}{R_L C_{\pi}} + \frac{1}{R_L C_{\mu}} + \frac{1}{R_L C_{cs}} + \frac{1}{R_L C_L} + \frac{g_m}{C_{\pi}}$$

CE/CS stage: input impedance

$$Z_{\text{input}} \approx R_b + \frac{1}{[C_{\pi} + (1 + g_m R_L) C_{\mu}] s}$$

$$Z_{\text{input}} = R_b + \frac{1}{s C_{\pi}} \parallel \frac{1 + R_L (C_{\mu} + C_{cs} + C_L) s}{s C_{\mu} (1 + g_m R_L + R_L s C_{cs})}$$

$$\tau_{\text{delay}} = \frac{\ln(2)}{\omega_{3\text{dB}}} = \frac{0.69}{6.28 \times 20 \text{ GHz}} = 5.5 \text{ ps}$$

CE/CS stage: numerical example

$$A_v = -g_m R_L = \frac{-I_C R_L}{V_T} \quad R_b = 0; R_L \times 2I_C = \Delta V = 250 \text{ mV}; A_v = -5$$

$$\tau_1 = R_L (C_\mu + C_{cs} + C_L) = \Delta V \frac{(C'_\mu + C'_{cs}) A_E}{I_T} + \Delta V \frac{C_L}{I_T}$$

$$\tau_1 = \Delta V \left(\frac{C'_\mu + C'_{cs}}{\frac{I_T}{I_{CpT}} J_{CpfT}} + \frac{C_L}{I_T} \right) = \Delta V \left(\frac{1}{SL_I} + \frac{C_L}{I_T} \right) \quad \tau_1 (\text{ps}) = 0.25 \left(2 + \frac{C_L (\text{fF})}{I_T (\text{mA})} \right)$$

- It takes 1 mA of tail current for each 2 fF of load capacitance to maintain 50% of intrinsic slew rate!
- The base resistance term cannot be neglected in HBT implementations.
- The gate resistance term can be minimized in MOSFET inverters by reducing finger width W_f

130nm CMOS example ($R_g=0$)

$$A_v = -R_L g_m = -2; g_m = \frac{I_T}{V_{eff}};$$


$$V_{eff} = 0.3V; \Delta V = 0.6V; A_v = -2; C_{int} = 0; k = 2, C'_{gd} = 0.5fF/\mu m, \\ C'_{db} = 1.7fF/\mu m$$

$$SL_I = \frac{0.3mA/\mu m}{0.5fF/\mu m + 1.7fF/\mu m} = 0.136V/ps$$

$$\tau_1(ps) = \Delta V(7.35 + 9.166 \times k) + \Delta V \frac{C_{int}}{I_T} = 4.41ps + 2 \times 5.5ps = 15.4ps$$

What happens if FET is biased beyond peak f_T in the linear I_D -
 V_{GS} region?

 CMOS inverter chain delay ($V_{A_n} = V_{A_p}$, $W_p = 2W_n$)



$$\tau_1 = (r_{on} \parallel r_{op}) [C_{gd}(p) + C_{db}(p) + C_{gd}(n) + C_{db}(n)] = \frac{3}{2} r_o (C_{gd} + C_{db})$$

$$\tau_2 = \left(\frac{r_o}{2} + \frac{R_g}{2k} \right) [3k C_{gs} + (1 + g_m r_o) 3k C_{gd}]$$

$$\tau_2 = \frac{3}{2} r_o \left(k + \frac{R_g}{r_o} \right) [C_{gs} + (1 + g_m r_o) C_{gd}]$$

$$\tau = \frac{3}{2} r_o (C_{gd} + C_{db}) + \frac{3}{2} r_o \left(1 + \frac{R_g}{k r_o} \right) [C_{gs} + (1 + g_m r_o) C_{gd}]$$

- Delay expression is similar to MOS-CML delay if $R_L = r_o$ and $A_v = -g_m r_o$
- In real implementations, for the same g_m , $R_L \ll r_o$ and CMOS inverter $|A_v| = 6 \dots 10 > 2$
- MOS-CML delay >3 times smaller than CMOS delay

Bipolar and MOS cascode stages

$$A_V \approx \frac{-g_{m1} R_L}{1 + s[R_b(C_{\pi 1} + 2C_{\mu 1}) + R_L(C_{\mu 2} + C_{cs2} + C_L)]} \quad Z_{\text{input}} = R_b + \frac{1}{[C_{\pi} + 2C_{\mu}]s}$$

$$\tau_1 = R_b(C_{\pi 1} + 2C_{\mu 1}) + R_L(C_{\mu 2} + C_{cs2} + C_L) \quad \tau_2 \approx \frac{C_{\pi 2} + C_{cs1} + 2C_{\mu 1}}{g_{m2}} \approx \frac{1}{\omega_{T2}}$$

$$A_V = \frac{-g_{m1} R_L}{1 + s[R_g(C_{gs} + 2C_{gd}) + R_L(C_{gd} + C_{db} + C_L)]}$$

$$\tau_2 \approx \frac{C_{gs2} + C_{bd1} + C_{sb2} + 2C_{gd1}}{g_{m2}} > \frac{2}{\omega_{T2}}$$

Cascading bipolar cascode inverters


$$\tau_1 = \Delta V \frac{C_\mu + C_{cs} + C_w}{I_T} + \left(k + \frac{R_b}{R_L} \right) \Delta V \frac{C_\pi + (1 - A_V) C_\mu}{I_T} \approx \frac{\Delta V}{S L_I} + \frac{\Delta V}{2 V_T} \frac{k + \frac{\text{tech}}{\Delta V}}{\omega_T}$$

$$A_V = -1; \quad \Delta V = I_T R_L; \quad g_m = \frac{I_T}{2 V_T}$$

$$R_b = (100 \dots 300) \Omega \mu m \times I_E (\mu m); \quad \frac{R_b}{R_L} = \frac{R_{bl} w_E J_{CpfT}}{\Delta V} = \frac{0.12 \dots 0.36 V}{\Delta V}$$

Cannot be reduced by
optimizing layout!


EF/SF stage with capacitive load

 

$$A_V(s) = \frac{g_m + sC_\pi}{R_S(C_\pi C_L + C_\pi C_\mu + C_\mu C_L)s^2 + (g_m R_S C_\mu + C_L + C_\pi)s + g_m}$$

$$\tau_1 \approx R_S C_\mu + \frac{C_\pi + C_L}{g_m}$$

 - Two poles -> potentially unstable -> ringing
- R_S includes R_b
- If C_L is small, bandwidth is limited by f_T .
- Slows down with C_L (loading ...) or by reducing f_T (bias current density)




EF/SF stage: input/output impedance

$$Z_{\text{input}} = R_b + Z_{\mu} \parallel [Z_{\pi} + (1 + g_m Z_{\pi}) Z_L]$$

$$Z_{\text{input}} = R_b + \frac{1}{j\omega C_{\mu}} \parallel \left[\frac{1}{j\omega C_{\pi}} + \frac{1}{j\omega C_L} - \frac{g_m}{C_{\pi} C_L \omega^2} \right] \text{ Negative resistance}$$

$$Z_{\text{out}} \approx \frac{R_S C_{\pi} s + 1}{g_m + C_{\pi} s} \quad \text{looks inductive up to } f_T \dots$$

 Cascading ECL stages ($R_b=0$, from EF τ_p)




$$Z_{L1} \approx \frac{1}{skC_\mu} \parallel \left[\frac{1}{skC_\pi} + \frac{1}{sC_{L2}} \right] \quad Z_{L2} = \frac{1}{[pkC_\pi + pk(1+g_m R_L)C_\mu]s}$$

$$\tau_{p1} \approx R_L (C_{cs} + C_\mu + kC_\mu) + \frac{(p+1)C_\pi + p(1+g_m R_L)C_\mu}{g_m}$$

$$\tau_{p1} \approx \frac{\Delta V}{SL_1} + \frac{p+1}{\omega_T} + \Delta V \frac{(p+k-1)C_\mu}{I_T} = 1.5p + 0.5k + 1 \text{ ps}$$


Cascading SCFL stages: from SF τ_p

 

$$\tau_{p1} \approx R_L (C_{db} + C_{gd} + k C_{gd}) + \frac{(p+1)C_{gs} + C_{sb} + p(1+g_m R_L)C_{gd}}{g_m}$$

$$\tau_{p1} \approx \frac{\Delta V}{SL_I} + \frac{p+1}{\omega_T} + \Delta V \frac{(p+k-1)C_{gd} + C_{sb}}{I_T} \approx 4ps + 2p + 0.375k (\text{GaAs pHEMT})$$


Cascading SCFL Stages

 

$$\tau_1 = \Delta V \frac{C_{gd} + C_{db} + C_{int}}{I_T} + k \Delta V \frac{C_{gd} + \frac{C_{int}}{k} + C_{gs} \parallel [C_{sb} + p(C_{gs} + (1 + A_V)C_{gd})]}{I_T} + \tau_{SF}$$


$$\frac{\Delta V}{SL_I} + \frac{\Delta V}{V_{eff}} \frac{1.1k}{\omega_T} > \tau_1 > \frac{\Delta V}{SL_I} + \frac{\Delta V}{V_{eff}} \frac{(0.66 \dots 0.8)k}{\omega_T}$$

AND - unbalanced: BiCMOS CML

 



- n-MOS current tails for voltage headroom
- Cascode for good isolation and symmetry + extra tail

D-Latch: Bipolar CML (slow)

 

- n-MOS current tails for voltage headroom
- Inductive peaking
- No EF in latch

D-Latch: Bipolar ECL (fast: 60 GHz)


 
 


n-MOS current tails
for voltage
headroom

Inductive peaking

Fast - EF in latch




D-Flip-Flop: bipolar CML

   


CLK

D-Latch: BiCMOS CML (12 GHz)

(E. Laskin CSICS 2005)

   


BiCMOS XOR Latch

 

Further Power Reduction

 
- Same technology
- Removed current source
- $V_{DD} = 1.8\text{ V}$, $I_{total} = 1\text{ mA}$
- Power reduced:
 $2.5\text{ mW} \rightarrow 1.8\text{ mW}$
- Same speed: 12 GHz
- Simulated with
extracted layout parasitics



 V. Kozlov et al, IEEE CSICS 2012

Scaling to Next Tech. Node

- 90 nm SiGe BiCMOS [3]
- HBT f_T : 160 $\rightarrow$ 230 GHz
- MOS f_T : 80 $\rightarrow$ 120 GHz
- Same power: 1.8 mW
- f_T improvement: x1.42
- Inductive peaking: x1.5
- ΔV reduced: x1.3
- Speed increased : 12 GHz $\rightarrow$ 30 GHz
- Simulated with extracted layout parasitics



4:1 MUX

